

- **BJT Implementation:**

- *Needs additional circuitry*

(I_Q - Q_3 - Q_4)

- Q_3 - Q_4 *diode-connected*

transistors and both


are *biased by the same*

current I_Q

- This produces a *DC bias*

V_{BIAS} between the *bases*

of Q_1 - Q_2

 

Circuit Schematic

- Consider *idling condition* with R_L *open-circuited* ($I_0 = 0$)
- *Neglecting base currents* of Q_1 - Q_2 , I_Q *flows through Q_3 - Q_4* and *develops a voltage drop*:

$$V_{BIAS} = V_{BE3} + V_{BE4} = V_T \ln \left(\frac{I_Q^2}{I_{S3} I_{S4}} \right)$$

- I_Q , I_{S3} , and I_{S4} *chosen such that $V_{BIAS} \approx 2V_\gamma$*
- *Note*: V_{BIAS} *is also equal to* ($V_{BE1} + V_{EB2}$)
 \Rightarrow Q_1 - Q_2 *remain at the verge of conduction,*
carrying a standby (or idling) current $I_{Standby}$

- This *extra current* of $(I_Q + I_{\text{standby}})$ causes *standby* (or *idling*) power dissipation
- Noting that:

$$V_{\text{BIAS}} = V_{\text{BE1}} + V_{\text{EB2}} = V_T \ln \left(\frac{I_{\text{Standby}}^2}{I_{S1} I_{S2}} \right)$$

$$\Rightarrow I_{\text{Standby}} = I_Q \sqrt{\frac{I_{S1} I_{S2}}{I_{S3} I_{S4}}}$$

- Now, *Q_1 - Q_2 has to supply/sink large amount of current to/from load* \Rightarrow *Their BE junction areas are made large* \Rightarrow *Large I_{S1} - I_{S2}*


➤ $I_{S1}-I_{S2}$ typically 10 times or more than $I_{S3}-I_{S4}$


⇒ $I_{standby} \geq 10I_Q$

⇒ Adds to the power overhead of the circuit

➤ Another option of prebias circuit:

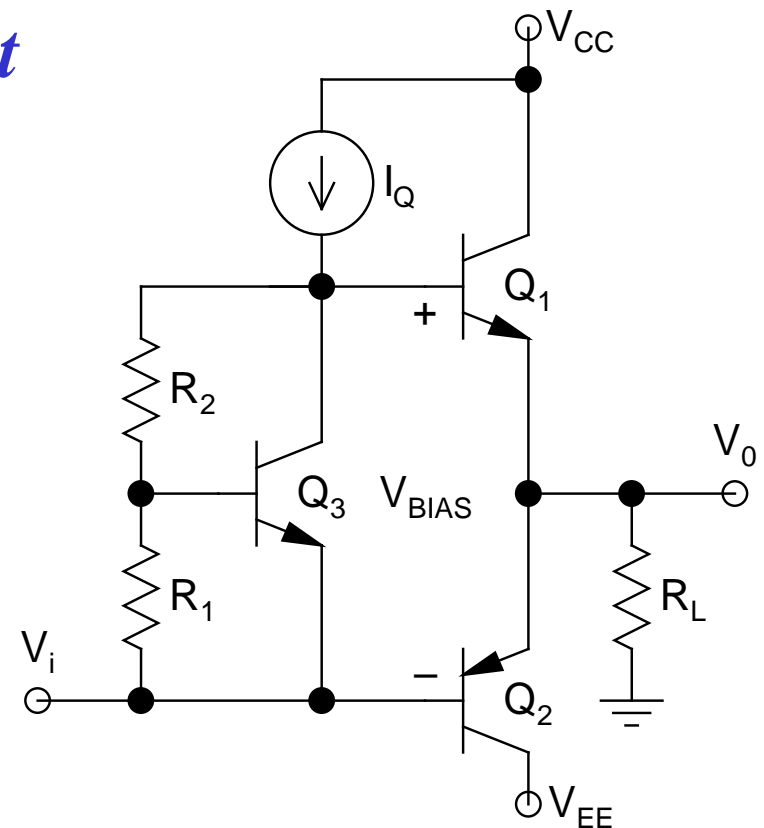- V_{BE} -Multiplier
- $V_{BIAS} = V_{BE3} (1 + R_2/R_1)$
- Values of R_1 and R_2 chosen to give $V_{BIAS} = 2V_\gamma$



 

The Voltage Transfer Characteristic (VTC)

- *The VTC does not pass through origin*
- *Intercepts* (known as *input-output offset*):
 - $V_i = 0, V_o = +V_{EB2}$
 - $V_o = 0, V_i = -V_{EB2}$
- *For $V_i > -V_{EB2}$, $V_{be1} \uparrow$ and $V_{eb2} \downarrow$, with their sum remaining constant at V_{BIAS}*
 - ⇒ *Q_1 starts to conduct and supply current to the load (R_L), while Q_2 starts to go deeper into cutoff*
 - ⇒ *V_o starts to follow V_i with a slope ~ 1 (CC stage)*

- *V_o can rise all the way up to $[V_{CC} - V_{CE1}(HS)]$, provided that V_i can drive it that far*
- Similarly, *for $V_i < -V_{EB2}$, $V_{eb2} \uparrow$ and $V_{be1} \downarrow$, with their sum again remaining constant at V_{BIAS}*
 - \Rightarrow *Q_2 starts to conduct and pull current away from the load (R_L), while Q_1 starts to go deeper into cutoff*
 - \Rightarrow *V_o again starts to follow V_i with a slope ~ 1 , and can go down all the way to $[V_{EE} + V_{EC2}(HS)]$*