


Sinusoidal Frequency Response

- Behavior of circuits under sinusoidal excitation having *varying frequency*
- Since inductive and capacitive reactances change with frequency, hence, the circuit response would also change with frequency
- Need to have the concept of *Transfer Function* and *Bode Plot*
- Also, to understand various types of *filter* topologies: *Low-Pass, High-Pass, Band-Pass*

Transfer Function:

* Expressed as:
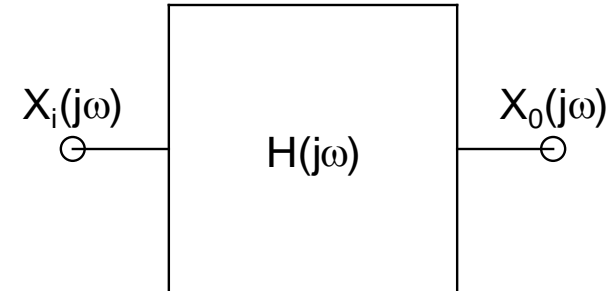
$$H(j\omega) = \frac{X_o(j\omega)}{X_i(j\omega)}$$



X: either voltage (V) or current (I)

* **Four** different topologies possible:

- **Voltage Gain** = V_o/V_i (dimensionless)
- **Current Gain** = I_o/I_i (dimensionless)
- **Transresistance Gain** = V_o/I_i (Ω)
- **Transconductance Gain** = I_o/V_i (\mathcal{U})

* In ***polar*** form:

$$H(j\omega) = |H| \angle \theta$$

$|H|$: ***Magnitude*** and θ : ***Phase*** of the transfer function

* ***Note***: $H(j\omega)$ is ***not*** a phasor

It simply is a ***complex number***

* ***Example***: Consider a ***voltage amplifier*** ($X = V$)

Let V_i and V_o be expressed in phasor form as:

$$\bar{V}_i(j\omega) = |V_i| \angle \phi_i \quad \text{and} \quad \bar{V}_o(j\omega) = |V_o| \angle \phi_o$$

$$\Rightarrow \bar{V}_o(j\omega) = H(j\omega) \bar{V}_i(j\omega)$$

$$\Rightarrow |V_o| = |H| |V_i| \quad \text{and} \quad \phi_o = \theta + \phi_i$$

Sinusoidal Frequency Response:


$$Z_{eq} = \left(\frac{1}{R_L} + j\omega C \right)^{-1} = \frac{R_L}{1 + j\omega R_L C}$$

$$H(j\omega) = \frac{V_0}{V_i} = \frac{Z_{eq}}{Z_{eq} + R_1}$$

$$= \frac{R_L}{(R_L + R_1) + j\omega R_L R_1 C} = \frac{K}{1 + j\omega/\omega_c}$$

$$(K = R_L/(R_L + R_1) = 10/11, \omega_c = 1/[(R_1 \parallel R_L)C] = 110 \text{ rad/sec})$$

$$|H| = \frac{K}{\sqrt{1 + (\omega/\omega_c)^2}}, \angle\theta = -\tan^{-1}(\omega/\omega_c)$$

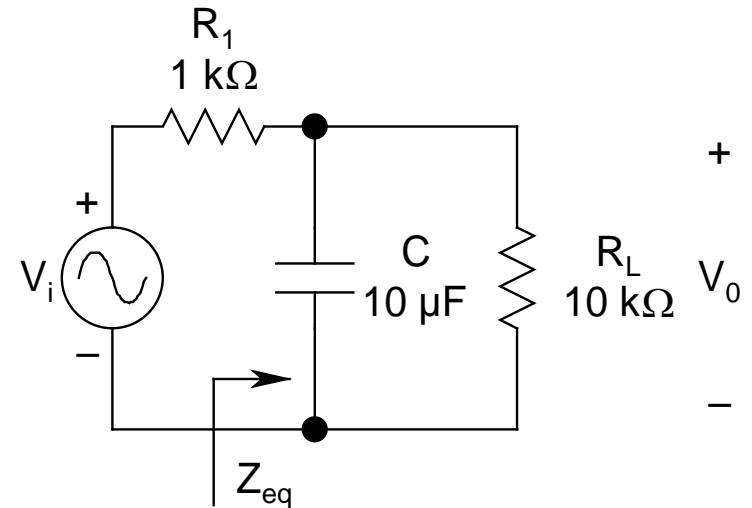

- ***Filters:***
 - Pass signals of desired frequency and block all others
 - Immensely useful module in all kinds of circuit design
 - Four Types:
 - ***Low-Pass Filter (LPF)***
 - ***High-Pass Filter (HPF)***
 - ***Band-Pass Filter (BPF)***
 - ***Band-Reject (or Notch) Filter (BRF)***

Low-Pass Filter (LPF):

* As $\omega \rightarrow 0$, $X_C = 1/(j\omega C) \rightarrow \infty$

\Rightarrow C behaves like an *open-circuit*


$\Rightarrow V_0$ *follows* V_i

* As $\omega \rightarrow \infty$, $X_C \rightarrow 0$

\Rightarrow C behaves like a *short-circuit*

$\Rightarrow V_0 = 0$

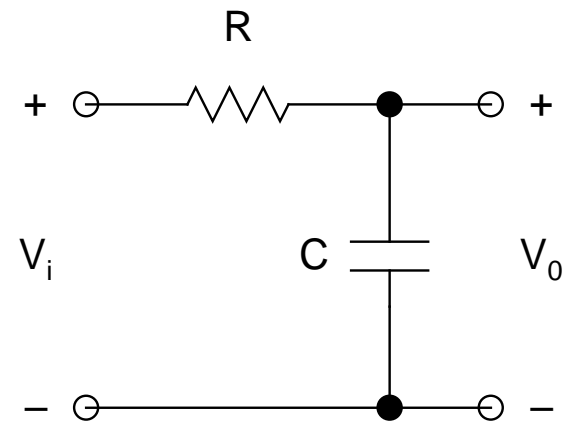* Thus, low frequency signals are *passed* (known as *pass-band*) while high frequency signals are *blocked* (known as *stop-band*) \Rightarrow **LPF**



* Transfer function:


$$H(j\omega) = \frac{V_o}{V_i} = \frac{1/(j\omega C)}{R + 1/(j\omega C)} = \frac{1}{1 + j\omega/\omega_c}$$

$\omega_c = 1/(RC)$ is known as the ***upper cutoff frequency***

* ***Note:*** As $\omega \rightarrow 0$, $|H| \rightarrow 1$; as $\omega \rightarrow \infty$, $|H| \rightarrow 0$.

and at $\omega = \omega_c$, $|H| = |H|_{\max} / \sqrt{2} = 0.707 |H|_{\max}$

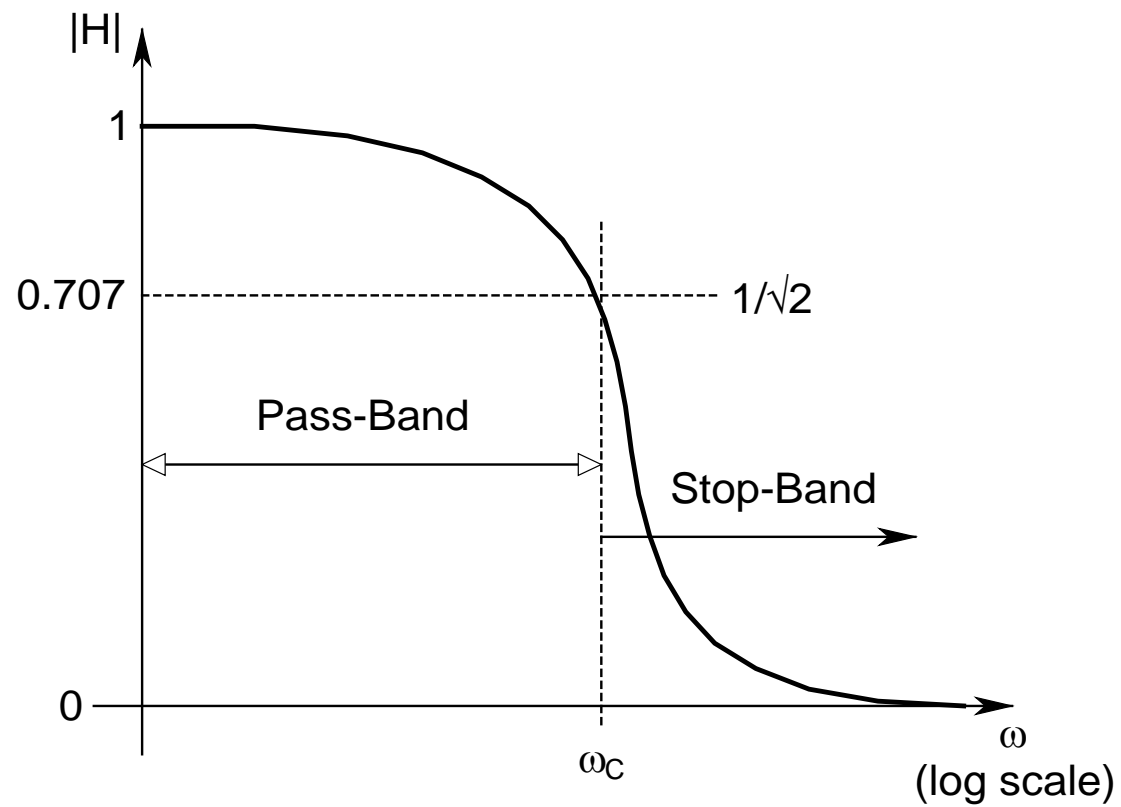
\Rightarrow This is the definition of ***cutoff frequency***



For LPFs, pass-band extends from 0 to ω_c
and stop-band extends from ω_c to ∞

High-Pass Filter (HPF):

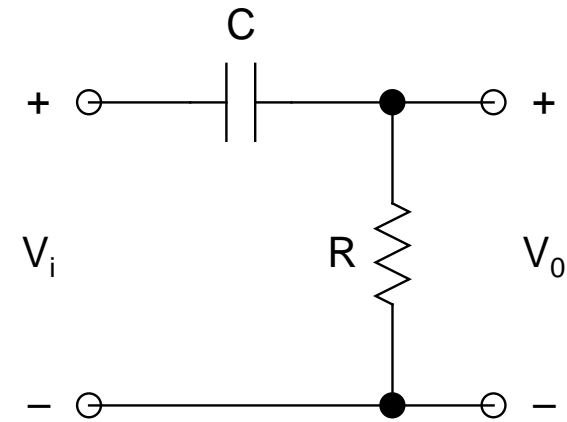- * Just *interchanging* R and C *converts* an *LPF* to an *HPF*
- * As $\omega \rightarrow 0$, $X_C = 1/(j\omega C) \rightarrow \infty$
 \Rightarrow The capacitor behaves like an *open-circuit*, and V_i is *blocked*
 $\Rightarrow V_0 = 0$
- * As $\omega \rightarrow \infty$, $X_C \rightarrow 0$ (*short-circuit*)
 $\Rightarrow V_0$ *follows* V_i




* Thus, low frequency signals are *blocked (stop-band)* while high frequency signals are *passed (pass-band)*
 \Rightarrow **HPF**

* Transfer function:

$$H(j\omega) = \frac{V_0}{V_i} = \frac{R}{R + 1/(j\omega C)} = \frac{j\omega/\omega_c}{1 + j\omega/\omega_c}$$

$\omega_c = 1/(RC)$ is known as the *lower cutoff frequency*

* **Note:** As $\omega \rightarrow 0$, $|H| \rightarrow 0$; as $\omega \rightarrow \infty$, $|H| \rightarrow 1$; and
at $\omega = \omega_c$, $|H| = 1/\sqrt{2}$

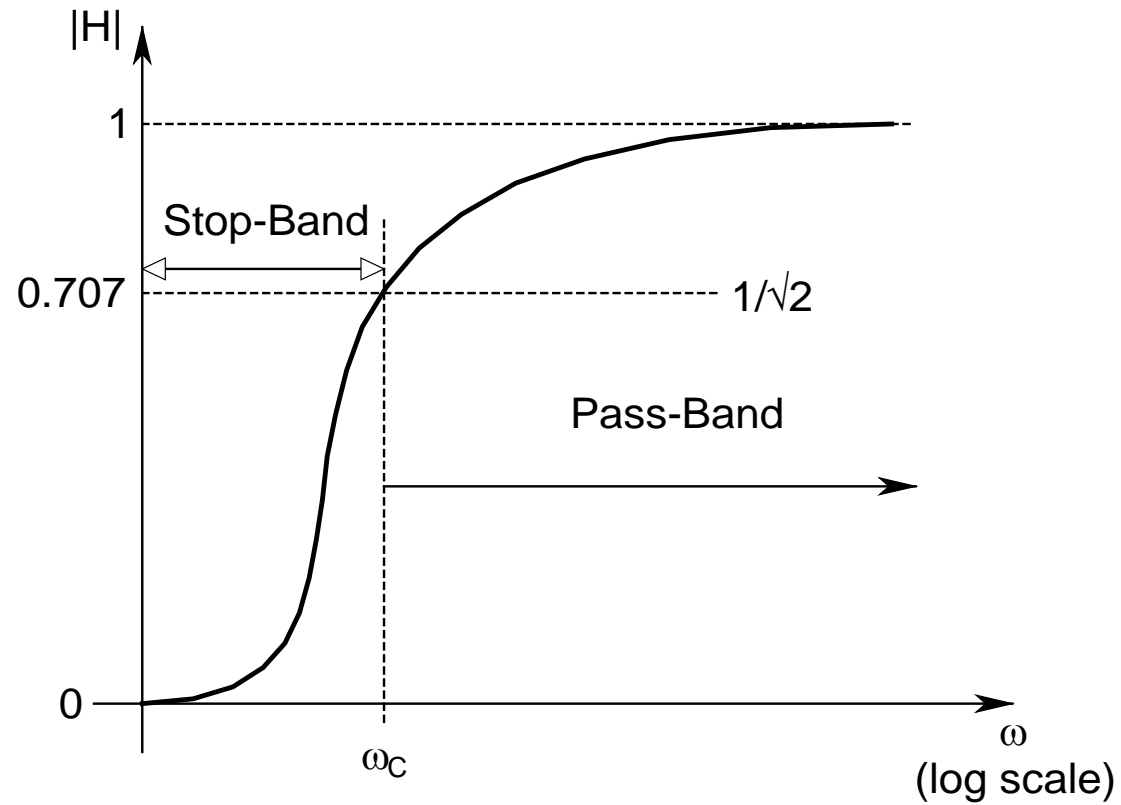


For HPFs, pass-band extends from ω_c to ∞
and stop-band extends from 0 to ω_c

Band-Pass Filter (BPF):


- * Extremely useful circuit to pass signals within a certain range of frequencies bounded between two ***cutoff frequencies*** ω_1 and ω_2 , with $\omega_2 > \omega_1$
 ω_1 : ***Lower Cutoff Frequency*** (0 to ω_1 : ***stop-band***)
 ω_2 : ***Upper Cutoff Frequency*** (ω_2 to ∞ : ***stop-band***)
 ω_1 to ω_2 : ***pass-band***
- * Can be constructed simply by putting an ***LPF*** and an ***HPF*** in ***series***!

Simplest Construction of a BPF:

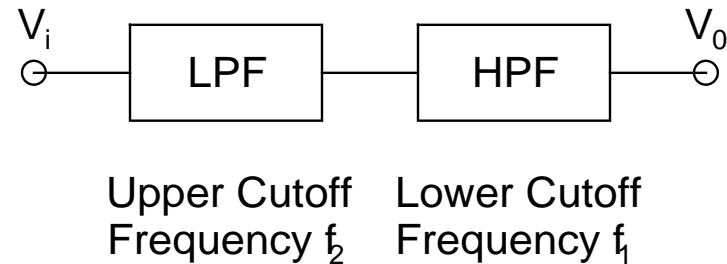- * Connect an *LPF* (with *upper cutoff frequency f_2*) in *series* with an *HPF* (with *lower cutoff frequency f_1*)



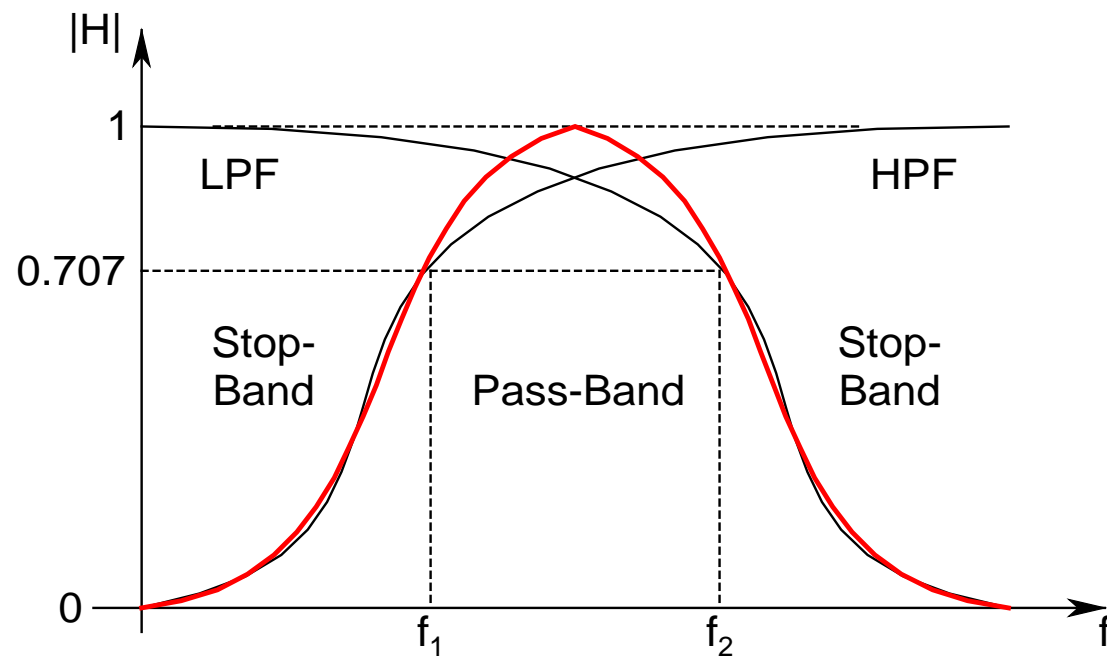- * Make sure that $f_2 > f_1$
- * The *LPF* would *pass* all signals *till f_2*
- * The *HPF* would *block* all signals *below f_1*
- * Thus, all signals *below f_1* and *above f_2* will be *blocked* (*stop-bands*), while *passing* signals *within a range between f_1 and f_2* (*pass-band*) \Rightarrow *BPF*



Band-Pass Filter Response

Implementation of a BPF Using RLC 2nd-Order Circuit:


* For *very low frequency*, C behaves like *open-circuit*, and V_i gets blocked

$$\Rightarrow V_0 = 0$$

* For *very high frequency*, L behaves like *open-circuit*, and again V_i gets blocked

$$\Rightarrow V_0 = 0$$

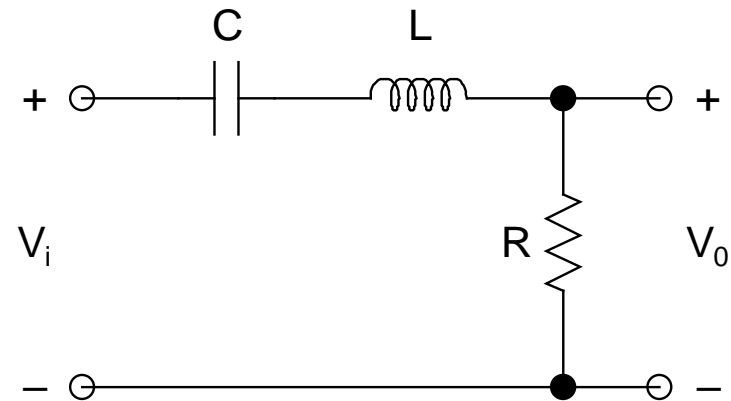* In between, V_0 *increases* with ω initially, reaches a *peak*, and then starts to *drop* again



RLC Circuit Implementation
for a Band-Pass Filter

Series Resonance:

* **Transfer function:** $H(j\omega) = \frac{V_0}{V_i} = \frac{R}{R + j(X_L - X_C)}$

with $X_L = \omega L$ and $X_C = 1/(\omega C)$


$$\Rightarrow |H(j\omega)| = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$\text{and } \angle\theta = -\tan^{-1}\left(\frac{X_L - X_C}{R}\right)$$

* If $X_L > X_C$, the circuit is ***inductive*** and $\angle\theta$ is ***negative***

* If $X_C > X_L$, the circuit is ***capacitive*** and $\angle\theta$ is ***positive***

- * **Note:** At a certain frequency ω_0 , X_L would become *equal* to X_C
 $\Rightarrow |H(j\omega)| = 1$ and $\angle\theta = 0^\circ$
- * Thus, the circuit becomes *purely resistive*
 \Rightarrow Known as *series resonance*
- * Under this condition, V_0 attains its *maximum* value and occurs at $\omega_0 =$ *resonance frequency*
 $= 1/\sqrt{LC}$
- * For $\omega < \omega_0$, the circuit response is *capacitive*
- * For $\omega > \omega_0$, the circuit response is *inductive*

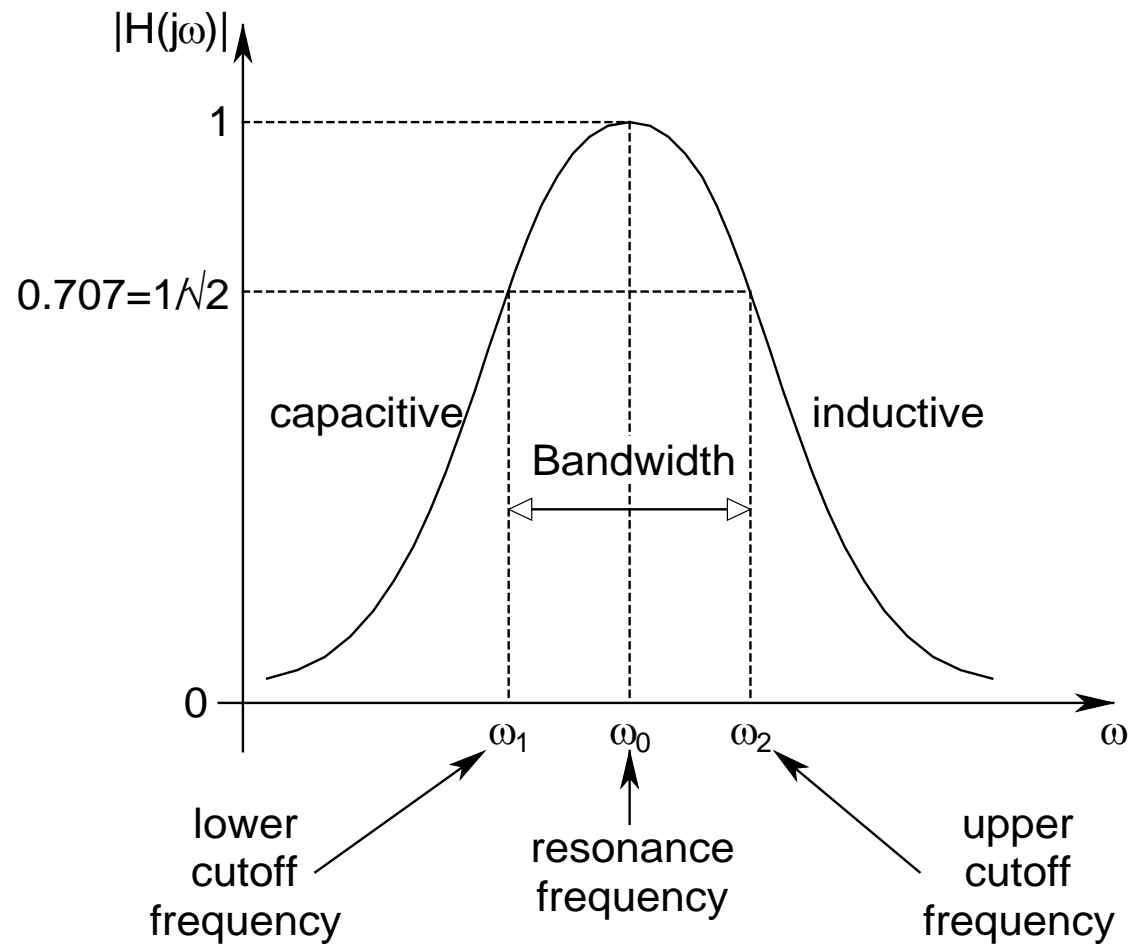

* ***Second-order circuit*** with ***two roots*** (ω_1 and ω_2)

* To find them, put $|H(j\omega)| = 1/\sqrt{2}$

$$\Rightarrow \omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\text{and } \omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

* ***Note:*** ω_1 and ω_2 are ***perfectly symmetric*** around ω_0

\Rightarrow The response is a ***mirror image*** around ω_0

* Actually, ω_0 is a ***geometric mean*** of ω_1 and ω_2

$$\Rightarrow \omega_0 = \sqrt{\omega_1 \omega_2}$$

* **Bandwidth** $BW = \omega_2 - \omega_1 = R/L$

* The **sharpness** of the peak is defined by the **Quality Factor** (QF):

$$QF = \frac{\omega_0}{BW} = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

* A **high** QF implies a **very narrow** and **sharp** response


* **Note:** For given values of L and C, QF is an **inverse** function of R

\Rightarrow **Small** R gives **sharp** response, and vice versa

* **Application:** Selectively picking up a **narrow band** of signal \Rightarrow **tuning circuits**

Parallel RLC Circuit (Parallel Resonance):

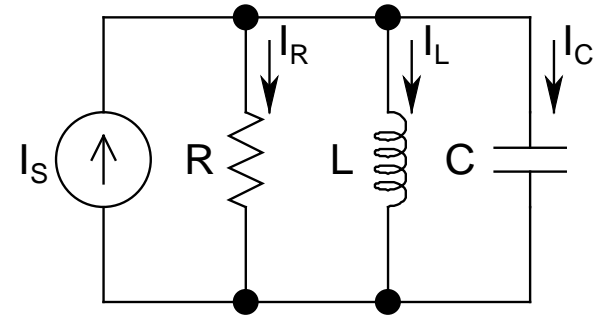- * **Tank Circuit:** L and C in parallel
- * **Admittance method** works best for this circuit



- * **Note:** All currents are *sinusoids*
- * Net admittance $Y = G + j(B_C - |B_L|)$

$$G = 1/R, \quad |B_L| = 1/(\omega L), \quad B_C = \omega C$$

$$\Rightarrow Y = G + j\left(\omega C - \frac{1}{\omega L}\right)$$

- * **Note:** For $\omega C = 1/(\omega L)$, imaginary part of Y *vanishes*

* Known as *parallel resonance*, with the *parallel resonance frequency* $\omega_0 = 1/\sqrt{LC}$ (same as *series resonance*)


* *Transfer function:*

$$H(j\omega) = \frac{I_R}{I_S} = \frac{1/R}{1/R + 1/(j\omega L) + j\omega C} = \frac{j\omega L}{R(1 - \omega^2 LC) + j\omega L}$$

$$\Rightarrow |H(j\omega)| = \frac{\omega L}{\sqrt{R^2(1 - \omega^2 LC)^2 + (\omega L)^2}}$$

* *Note:* At resonance, $|H(j\omega)| = 1$

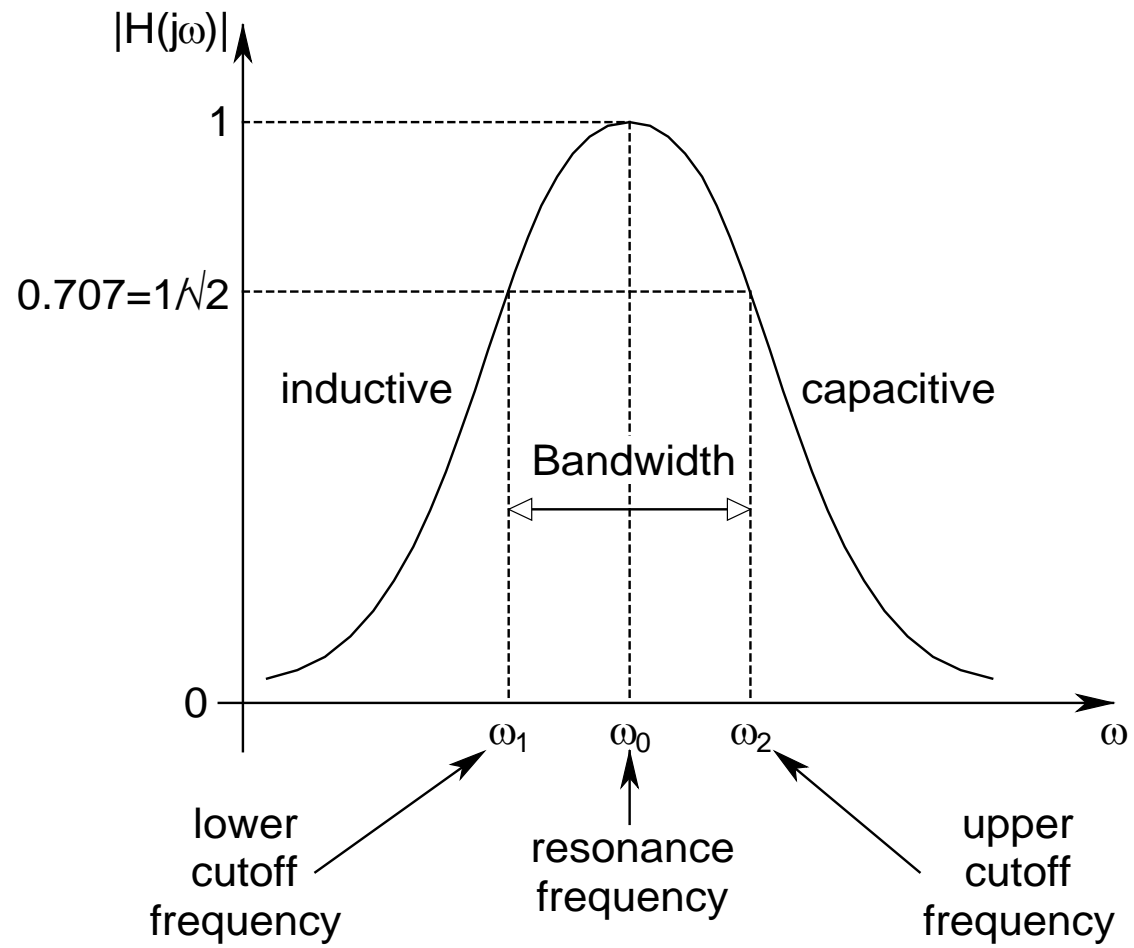\Rightarrow Current through R is *maximum* under this condition



* Again a *second-order circuit* with two roots (ω_1 and ω_2)

* To find them, put $|H(j\omega)| = 1/\sqrt{2}$

$$\Rightarrow \omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\text{and } \omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

* Again note that ω_1 and ω_2 are perfectly *symmetric* around ω_0

$$* BW = \omega_2 - \omega_1 = 1/(RC)$$

$$* QF = \omega_0/BW = \omega_0 RC = R\sqrt{\frac{C}{L}}$$

Observations:

* In *series* RLC circuit at *resonance*:

- Net *impedance* is *minimum*
 - ⇒ *Current* drawn from the voltage source is *maximum*
 - ⇒ *Voltage* drop across R is *maximum*
- Voltage drops across L and C are *equal in magnitude* but *opposite in phase*
 - ⇒ They *cancel out*, making the entire source voltage *drop across R*
- As R *decreases*, the response becomes *sharper*

* In *parallel* RLC circuit at *resonance*:

- Net *admittance* is *minimum*

⇒ Net *impedance* is *maximum*

⇒ *Current* drawn from the voltage source is *minimum*

⇒ *Current* through R is *maximum*

- Currents flowing through L and C are *equal in magnitude* but *opposite in phase*


⇒ known as *circulating current*

⇒ Entire current supplied by source *flows through R*


- As R *increases*, the response becomes *sharper*

Band-Reject (or Notch) Filter:

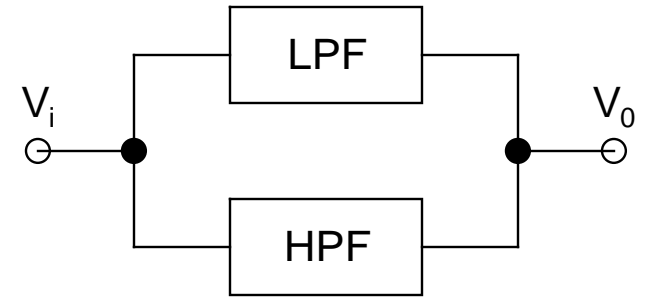
- * ***Simplest implementation:*** put an ***LPF*** having upper cutoff frequency f_1 and an ***HPF*** having lower cutoff frequency f_2 (with $f_2 > f_1$) in ***parallel***



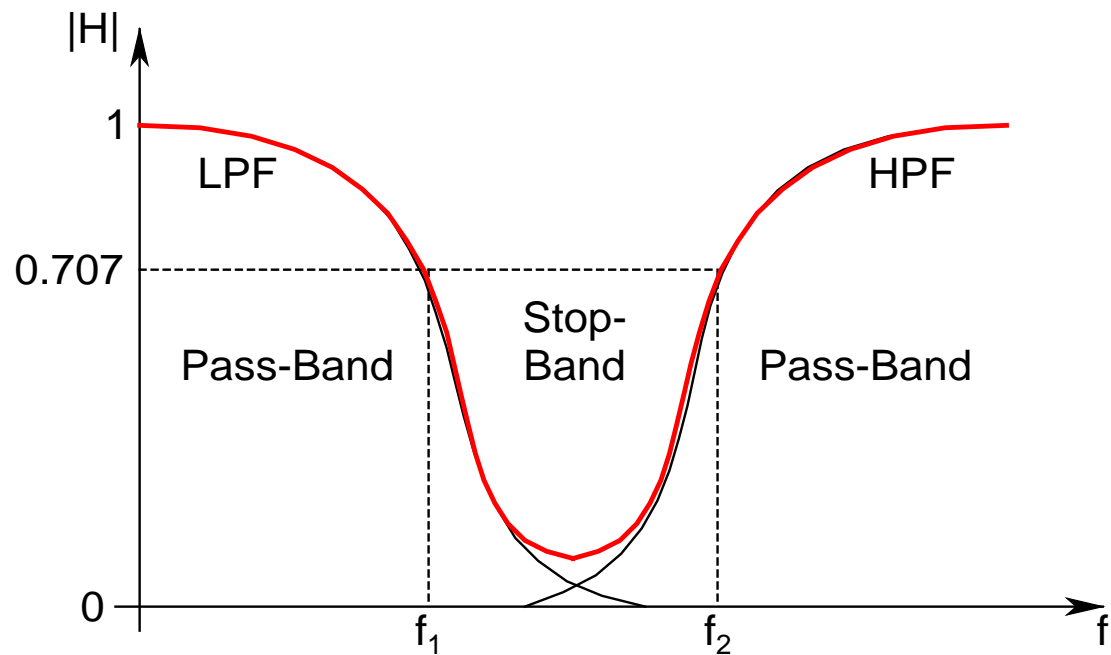- * It will ***pass*** frequencies below f_1 and above f_2 (***pass-bands***), while ***blocking*** frequencies within the band $(f_2 - f_1)$ (***stop-band***)
 \Rightarrow ***Band-reject filter***
- * If $(f_2 - f_1)$ is made extremely ***narrow***, then we arrive at the ***notch filter***



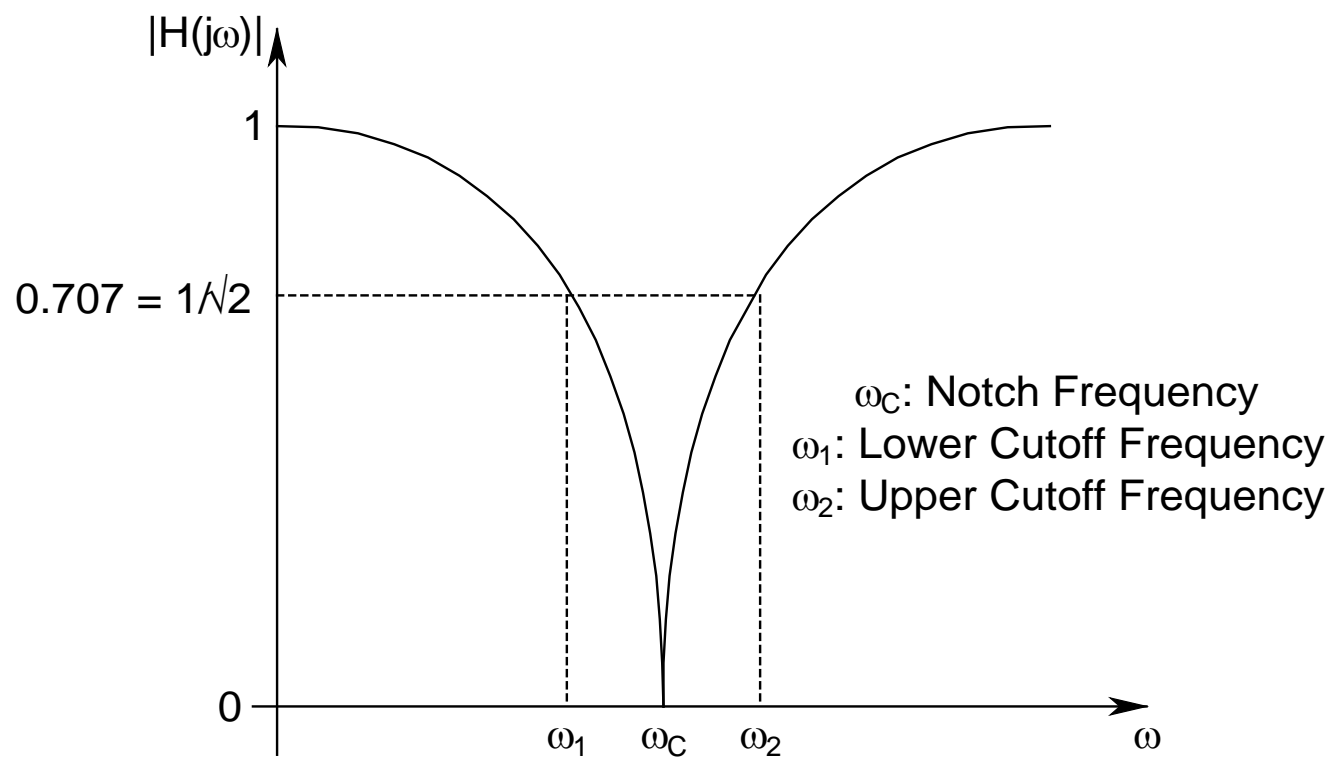Band-Reject Filter Response
 Note: Upper cutoff frequency of LPF =
 Lower cutoff frequency of BRF
 Lower cutoff frequency of HPF =
 Upper cutoff frequency of BRF



Notch Filter Response

Simplest RLC Implementation of a Notch Filter:

- * Z = Impedance of parallel combination of L and C


$$= \frac{j\omega L}{1 - \omega^2 LC}$$

- * **Note:** For $\omega^2 LC = 1$, $Z \rightarrow \infty$

$$\Rightarrow V_i \text{ gets } \textit{blocked} \text{ and } V_o = 0$$

- * This frequency is known as the *notch frequency*
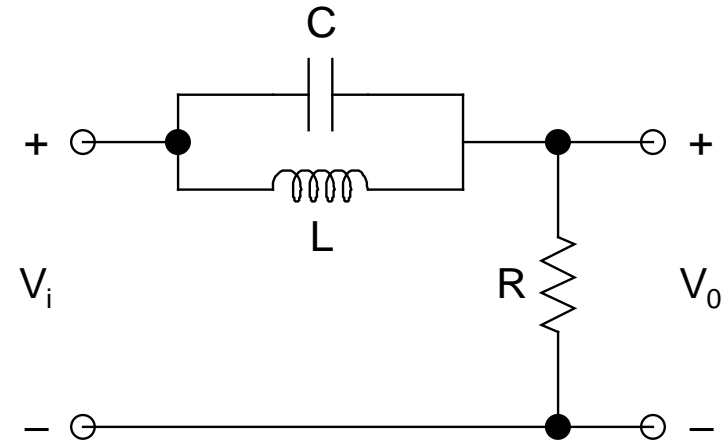
$$\omega_c, \text{ and is given by } \omega_c = \frac{1}{\sqrt{LC}}$$



* ***Transfer function:***

$$H(j\omega) = \frac{V_0}{V_i} = \frac{R}{R + Z} = \frac{R}{R + \frac{j\omega L}{1 - \omega^2 LC}}$$

* ***Ex.:*** Find ω_1 and ω_2 by substituting $|H(j\omega)| = \frac{1}{\sqrt{2}}$

and show that $\omega_c = \sqrt{\omega_1 \omega_2}$

* ***BW*** = $\omega_2 - \omega_1$

* ***QF*** = $\frac{\omega_c}{BW}$

Bode Plot:

- * The most convenient way to plot a ***transfer function***
- * Conceived by ***Hendrik W. Bode*** of the ***Bell Telephone Laboratories***
- * Provides a very easy and convenient method of extracting information regarding variation of ***magnitude*** and ***phase*** of any transfer function as a function of ***frequency***
- * Can be made even simpler by a technique known as the ***Asymptotic Bode Plot***

* $|H|$ is plotted in *decibels* (dB), while $\angle\theta$ is plotted in *degrees* ($^\circ$), both in *linear scale*, while the *frequency* is plotted in *log scale*, in a *semilog graph*

* $|H|(dB) = 20 \log_{10} |H(j\omega)|$

* *Inverse operation:*

$$|H(j\omega)| = 10^{|H|(dB)/20}$$

* *Note:* In Bode plot, the *frequency* ω is always plotted in *log scale*

$ H(j\omega) $	$ H (\text{dB})$	$ H(j\omega) $	$ H (\text{dB})$
0.001	-60	0.01	-40
0.1	-20	$1/\sqrt{2}$	-3
1	0	$\sqrt{2}$	3
5	14	10	20
100	40	1000	60

Bode Magnitude Plot:

* Consider the transfer function:

$$H(j\omega) = 1 + j\frac{\omega}{a}$$

$$\Rightarrow |H(j\omega)| = \sqrt{1 + \frac{\omega^2}{a^2}} \quad \text{and}$$

$$|H|(\text{dB}) = 20 \log_{10} \left(\sqrt{1 + \frac{\omega^2}{a^2}} \right)$$


Observations:

* For $\omega \ll a$, $|H(j\omega)| \simeq 1$, and $|H|(\text{dB}) = 0$

- * For $\omega \gg a$, $|H(j\omega)| \simeq \omega / a$, and $|H|(\text{dB}) = 20\log_{10}(\omega / a)$, which is *linear* with respect to ω ($\because \omega$ is plotted in *log scale*), and increases at the rate of + 20 dB / decade
- * At $\omega = a$, $|H(j\omega)| = \sqrt{2}$, and $|H|(\text{dB}) = 3$
- * The angular frequency a has several names: *corner frequency, cutoff frequency, break-point frequency, +3-dB frequency*, etc.
- * It is also known as the *zero* of the transfer function

Concept of Asymptotes:

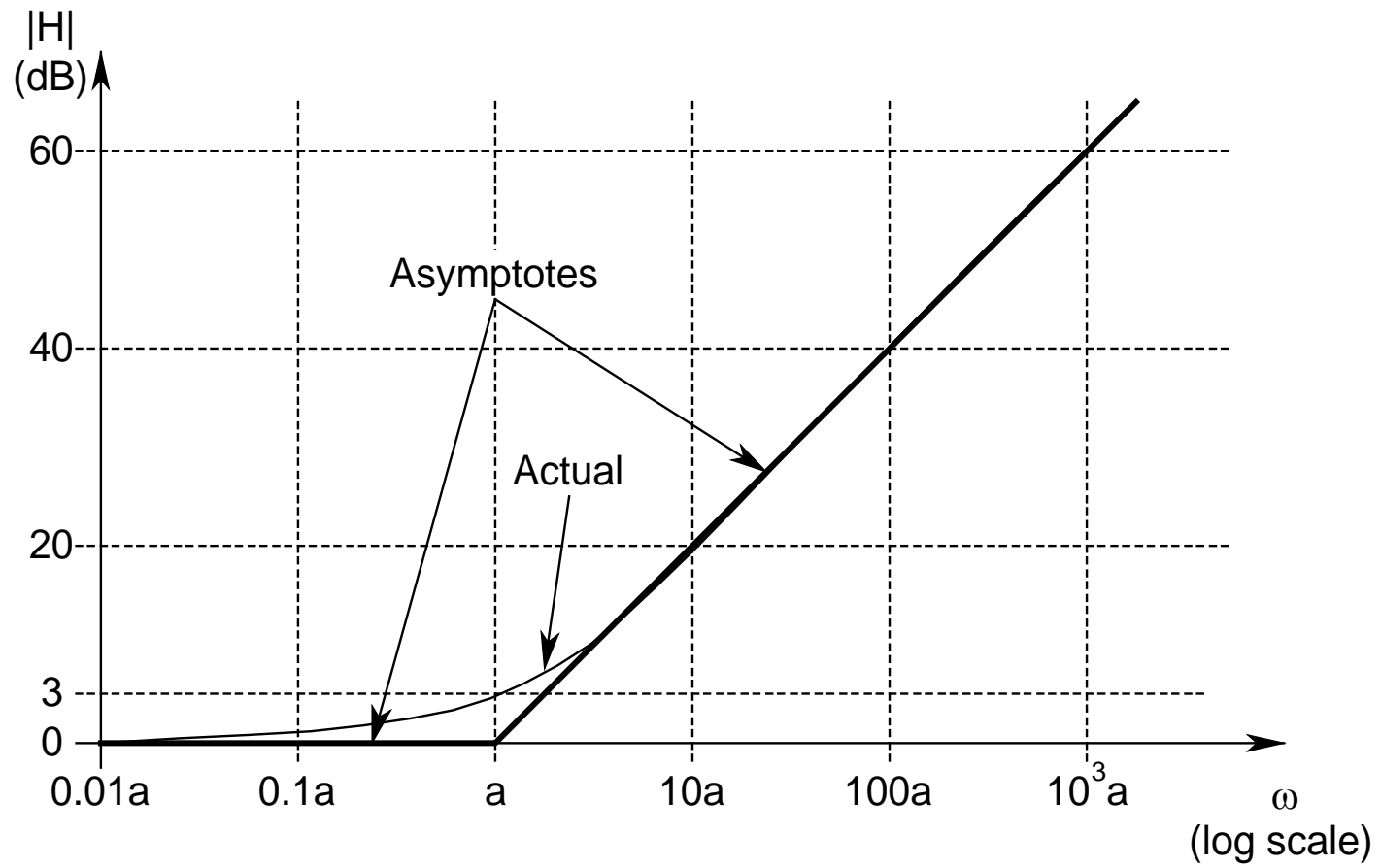- * ***Simplification*** of the actual Bode plot
- * For $\omega \leq a$, it is taken to be equal to ***zero***
- * For $\omega > a$, it is assumed to be a ***straight line***, starting from a , with a slope of ***+ 20 dB/decade***
- * ***Note:*** Maximum error occurs at $\omega = a$, which is equal to 3 dB
 $\Rightarrow a$ is known as the ***3-dB frequency***




Bode Phase Plot:

* **Phase** ϕ of the transfer function:

$$\phi = \tan^{-1} \left(\frac{\omega}{a} \right)$$

Observations:

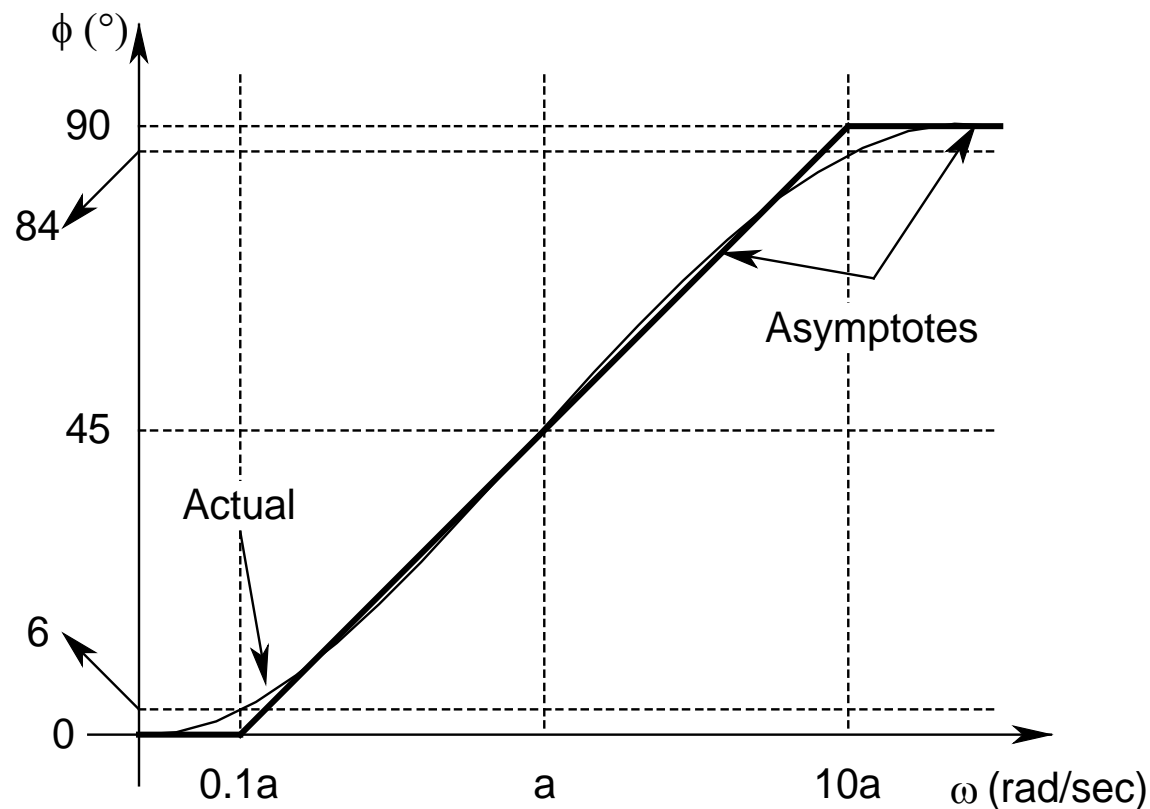- * At $\omega = a$, $\phi = 45^\circ$; $\omega = 0.1a$, $\phi = 6^\circ$; $\omega = 10a$, $\phi = 84^\circ$;
and as $\omega \rightarrow \infty$, $\phi = 90^\circ$
- * Can be adequately described by **three asymptotes**:
 1. 0° for $\omega \leq 0.1a$
 2. 90° for $\omega \geq 10a$
 3. Between $0.1a$ and $10a$, changing **linearly** with a slope of **$+45^\circ/\text{decade}$**



Note: Actual phase at $0.1a$ and $10a$ is equal to 6° and 84° respectively, hence, these two frequencies are known as *lower and upper 6° frequencies*

* Consider another transfer function:

$$H(j\omega) = \frac{1}{1 + j\omega/b}$$

$$\Rightarrow |H(j\omega)| = 1/\sqrt{1 + \omega^2/b^2} \text{ and}$$


$$|H|(\text{dB}) = -20 \log_{10} \left(\sqrt{1 + \omega^2/b^2} \right)$$

Observations:

* For $\omega \ll b$, $|H(j\omega)| \simeq 1$, and $|H|(\text{dB}) = 0$

* For $\omega \gg b$, $|H(j\omega)| \simeq b/\omega$, and $|H|(\text{dB}) = 20 \log_{10}(b/\omega)$, which is ***linear*** with respect to ω , and changes at the rate of ***-20 dB/decade***

- * Also, at $\omega = b$, $|H(j\omega)| = 1/\sqrt{2}$, and $|H|(\text{dB}) = -3$
- * Similar to a, the angular frequency b also has several names : *corner frequency, cutoff frequency, break-point frequency, -3-dB frequency*, etc.
- * It is also known as the *pole* of the transfer function
- * *Asymptotes*:
 - For $\omega \leq b$, it is taken to be equal to *zero*
 - For $\omega > b$, it is assumed to be a *straight line*, starting at b , with a slope of *-20 dB/decade*

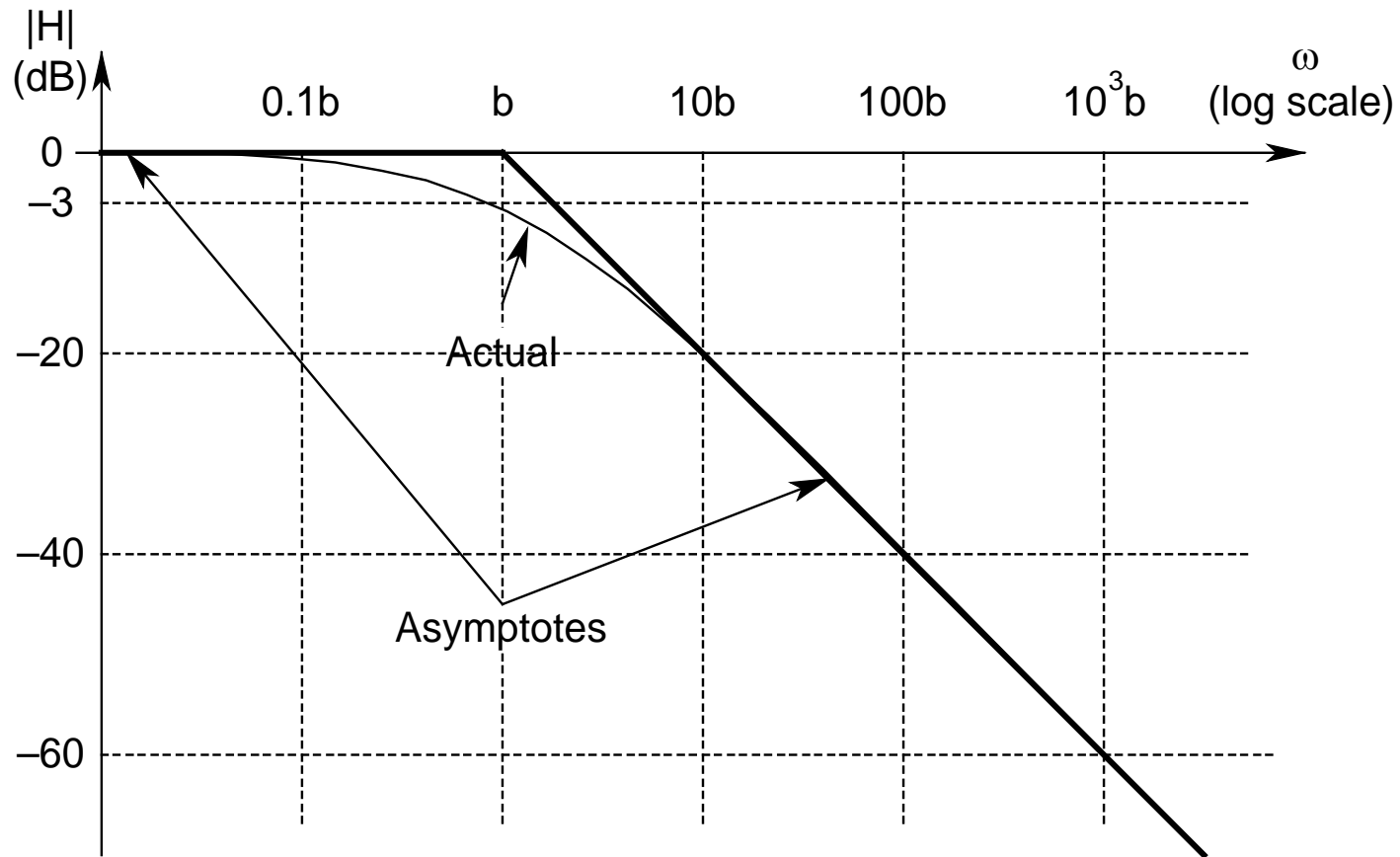

Note: Maximum error occurs at $\omega = b$, which is equal to -3 dB


Hence, b is known as the ***-3-dB frequency***

* **Phase** ϕ of the transfer function:

$$\phi = -\tan^{-1}\left(\frac{\omega}{b}\right)$$

Observations:

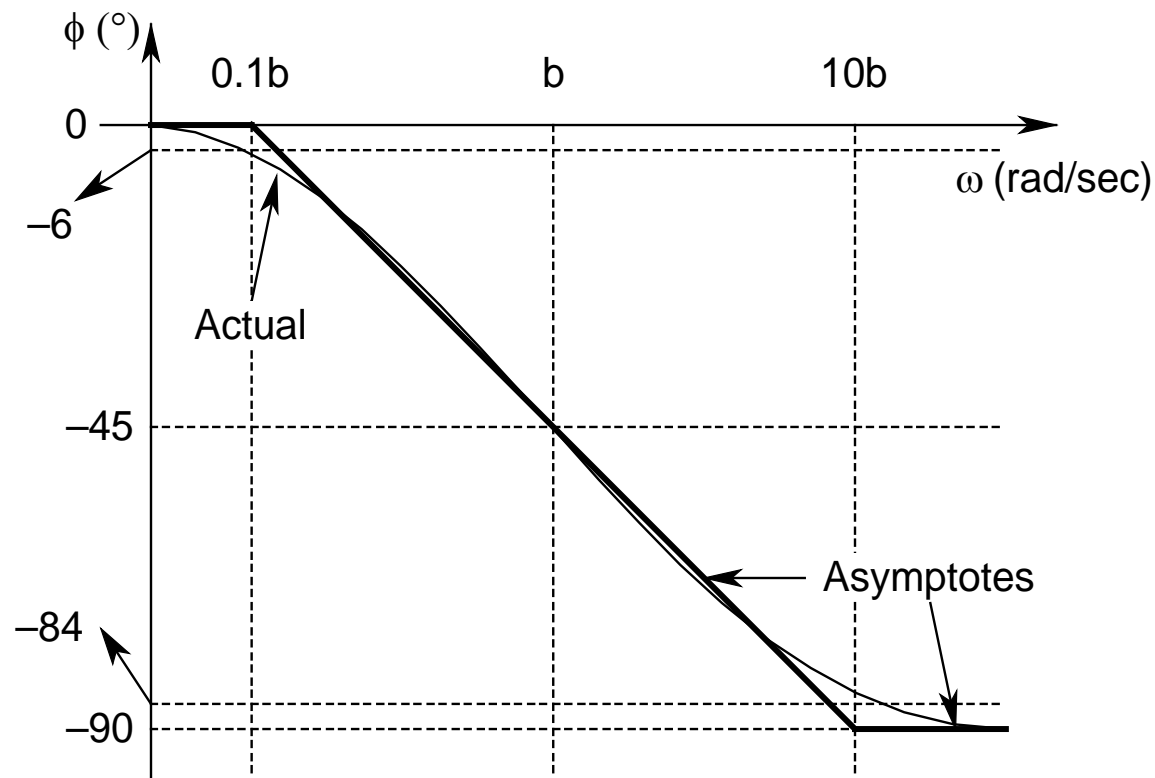- * At $\omega = b$, $\phi = -45^\circ$; $\omega = 0.1b$, $\phi = -6^\circ$;
 $\omega = 10b$, $\phi = -84^\circ$; and as $\omega \rightarrow \infty$, $\phi = -90^\circ$
- * Can be adequately described by **three asymptotes**:
 1. 0° for $\omega \leq 0.1b$
 2. -90° for $\omega \geq 10b$
 3. Between $0.1b$ and $10b$, changing **linearly** with a slope of **$-45^\circ/\text{decade}$**



Note: Actual phase at $0.1b$ and $10b$ is equal to -6° and -84° respectively, hence, these two frequencies are known as *lower and upper 6° frequencies*

- * Consider another simple transfer function: $H(j\omega) = j\omega$
 - $\Rightarrow |H| = \omega$, and $|H|(\text{dB}) = 20 \log(\omega)$, and a constant phase of **90°**
 - $\Rightarrow |H|(\text{dB})$ versus ω is a ***straight line*** in the asymptotic Bode plot, having a positive slope of ***20 dB/decade***, and crossing the 0 dB line at $\omega = 1$ rad/sec
- * Similarly, the asymptotic Bode plot of the function $H(j\omega) = (j\omega)^{-1}$ is another ***straight line*** having a slope of ***-20 dB/decade***, crossing the 0 dB line at $\omega = 1$ rad/sec, and having a constant phase of ***-90^\circ***

Ex: Asymptotic magnitude and phase Bode plots for the

function:
$$H(j\omega) = \frac{j\omega(1 + j\omega/100)}{(1 + j\omega/10)(1 + j\omega/1000)}$$

Magnitude Plot:

$j\omega$: straight line with a slope of +20 dB/decade, crossing
0 dB at $\omega = 1$ rad/sec (***plot a***)


$(1 + j\omega/100)$: 0 for $\omega \leq 100$ rad/sec, then increasing
@+20 dB/decade (***plot b***)

$(1 + j\omega/10)$: 0 for $\omega \leq 10$ rad/sec, then decreasing
@−20 dB/decade (***plot c***)

$(1 + j\omega/1000)$: 0 for $\omega \leq 1000$ rad/sec, then

decreasing @ -20 dB/decade (*plot d*)

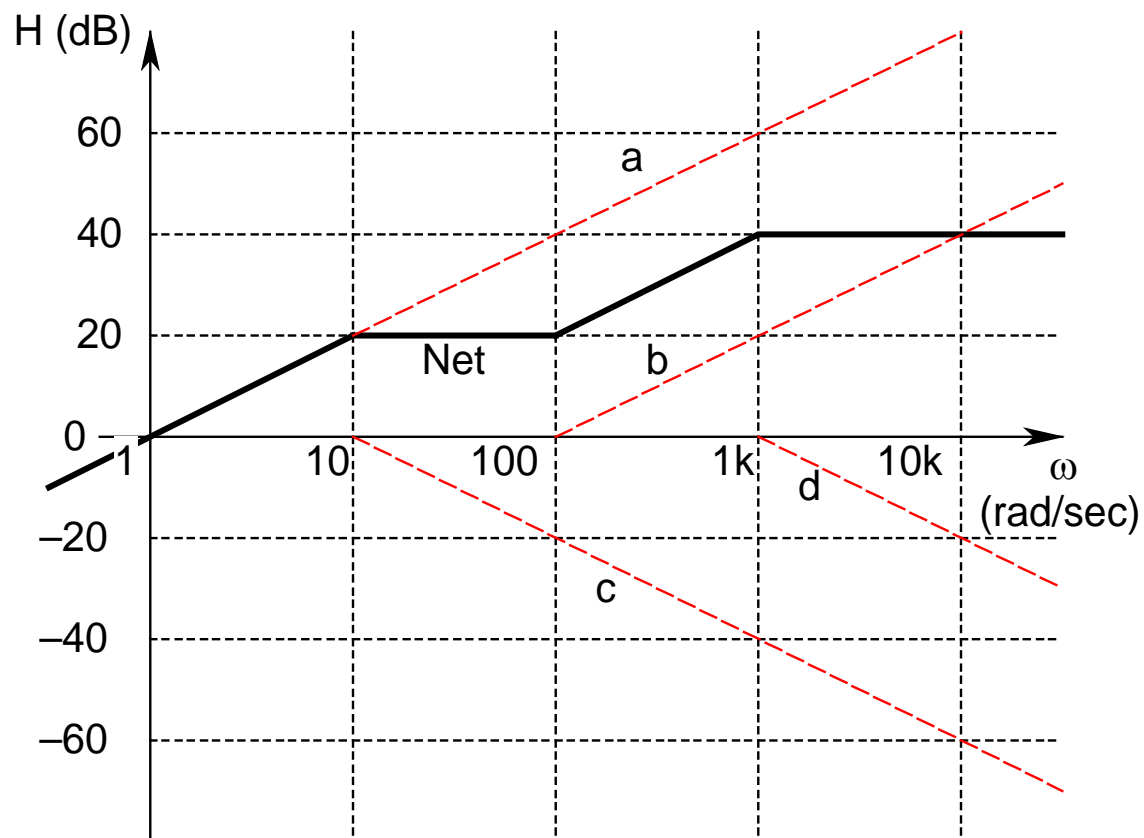The net plot is an *algebraic sum* of all the individual plots



Phase Plot:


$j\omega$: constant phase of 90° (***a***)

$(1 + j\omega/100)$: 0° for $\omega \leq 10$ rad/sec, 45° at $\omega = 100$ rad/sec, and 90° for $\omega \geq 1000$ rad/sec (***b***)

$(1 + j\omega/10)$: 0° for $\omega \leq 1$ rad/sec, -45° at $\omega = 10$ rad/sec, and -90° for $\omega \geq 100$ rad/sec (***c***)

$(1 + j\omega/1000)$: 0° for $\omega \leq 100$ rad/sec, -45° at $\omega = 1000$ rad/sec, and -90° for $\omega \geq 10^4$ rad/sec (***d***)

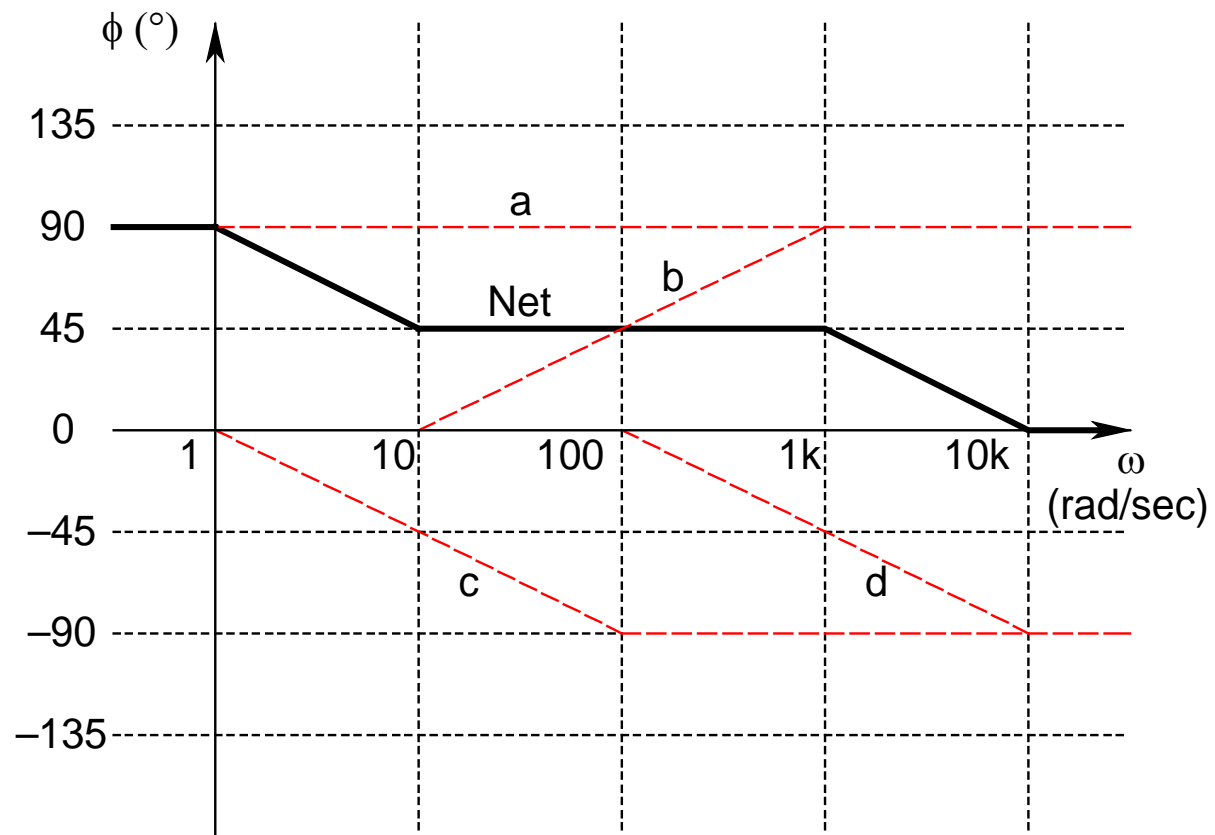The net plot is an ***algebraic sum*** of all the individual plots



Note: If the transfer function contains any ***constant*** K, then it will add a ***constant offset*** of $20\log_{10}K$ to the ***magnitude plot***, while the ***phase plot*** will remain ***unaffected***