

➤ *Differential Current:*

$$\partial I_d = I_{d1} - I_{d2} = 2\xi$$

➤ *Differential-Mode Output Voltage:*

$$\begin{aligned} V_{od} &= V_{o1} - V_{o2} = (V_{DD} - I_{d1}R_D) - (V_{DD} - I_{d2}R_D) \\ &= -(\partial I_d)R_D = -2\xi R_D \end{aligned}$$

➤ *Note:*

- When  $V_{id} = 0$ ,  $\xi = 0$ ,  $\partial I_d = 0$ , and  $V_{od} = 0$
- *This is the perfect DC bias point*
- *No need for interstage coupling capacitor*
- $I_{D1} = I_{D2} = I_{SS}/2$
- $V_{Id} = 0 \Rightarrow$  *Tie both gates to ground* and *use a negative power supply*

➤ *ac Analysis:*

- *The procedure adopted for npn DA can be lifted verbatim*

➤ *Differential-Mode Half-Circuit: Calculation of  $A_{dm}$ :*

- *The common-source node is at ac ground (from symmetry)*


- *Body is also at ac ground*

$$\Rightarrow v_{bs} = 0 \Rightarrow g_{mb} v_{bs} = 0$$

- *Simple CS stage:*

$$\Rightarrow A_{dm} = v_{od}/v_{id} = -g_m R_D$$

$$g_m = k_N \Delta V$$

 

**Differential-Mode  
Half-Circuit**

➤ **Common-Mode Half-Circuit: Calculation of  $A_{cm}$ :**

- **CS(D) stage**, but now **with body effect present**

$$\begin{aligned}\Rightarrow A_{cm} &= v_{oc}/v_{ic} \\ &= -g_m R_D / [1 + (g_m + g_{mb})2R_{SS}]\end{aligned}$$


➤ Thus:

$$\begin{aligned}CMRR &= 20\log_{10}(|A_{dm}/A_{cm}|) \\ &\approx 20\log_{10}[2(g_m + g_{mb})R_{SS}]\end{aligned}$$

➤ Again,  **$R_{SS}$  plays no role in**

**$A_{dm}$** , but **determines  $A_{cm}$  and CMRR**

 **$\Rightarrow$  A high value of  $R_{SS}$  highly desirable**



**Common-Mode  
Half-Circuit**

- *Actual situation is not so rosy and hunky-dory*
- *The DA can become unbalanced if there is a mismatch between the devices and/or the resistors, and our analysis would fail!*
- Gives rise to *offset voltage* (*for both npn and NMOS DA*) and *offset current* (*only for npn DA*)
- *This mismatch is caused by technology and is totally random*
- *Fortunately, the effect is not that severe, since there are technological innovations to match devices and/or resistors*


# Actively Loaded Amplifier Stages

- *Main Goal: To reduce usage of resistors as much as possible and use transistors instead as active load*
- Interesting to note that *transistors offer much higher resistance than physical resistors*, while *occupying much smaller chip area*

- *npn CE Stage With pnp Active Load:*

- $Q_1$ : *Driver*,  $Q_2$ : *Load*
- Identify  $Q_2$ - $Q_3$  as a *pnp current mirror*
- $Q_2$ - $Q_3$  constitute a *matched pair*
- *Neglecting base currents:*  
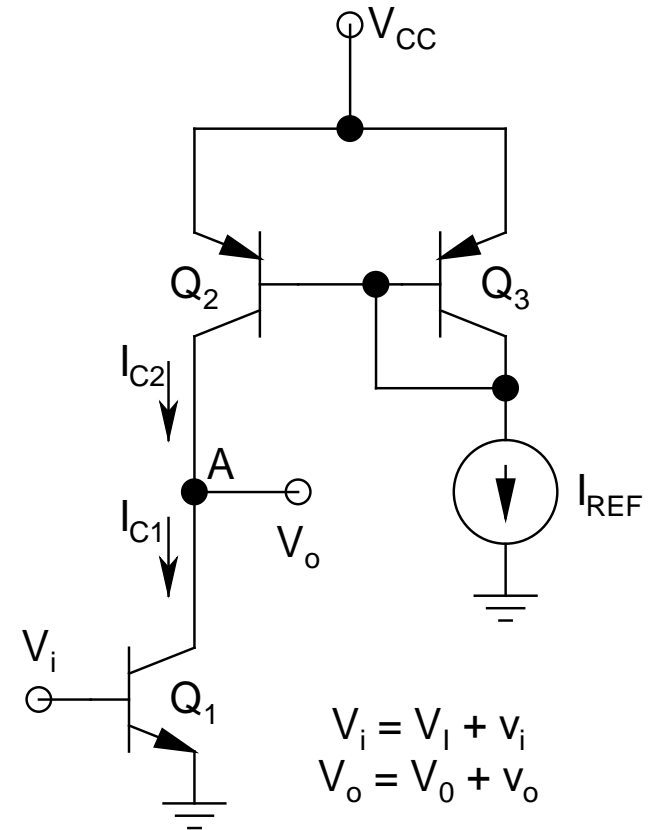
$$I_{C2} = I_{REF}$$
- *Biasing of the circuit is tricky*



**Circuit Diagram**