

- **Simple npn CM:**

- Q_1 has its **B and C shorted**

- **Can never saturate** ($V_{BC} = 0$)
- Known as **diode-connected BJT**


- Q_1 and Q_2 have **same V_{BE}**

- $I_{REF} = \text{Reference Current}$
 $= (V_{CC} - V_{BE})/R$

- $I_0 = \text{Output Current} = I_{C2}$


- $V_0 = \text{Output Voltage}$

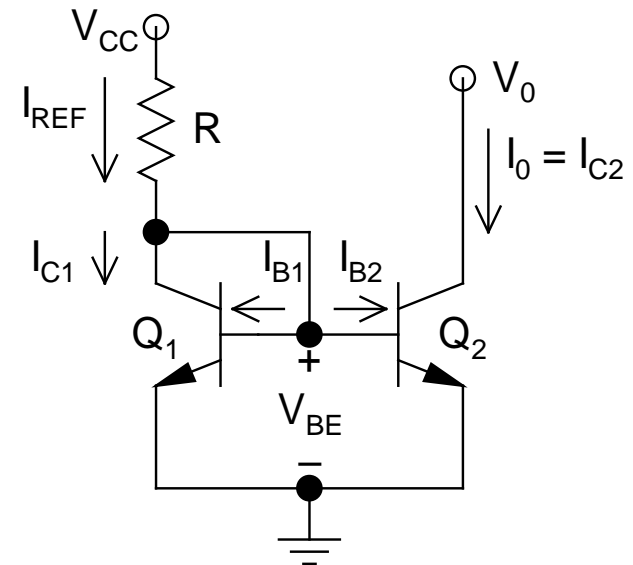- **Variable, depends on the load connected to it**



- **Output Resistance R_o :**

➤ First, *investigate Q_1*

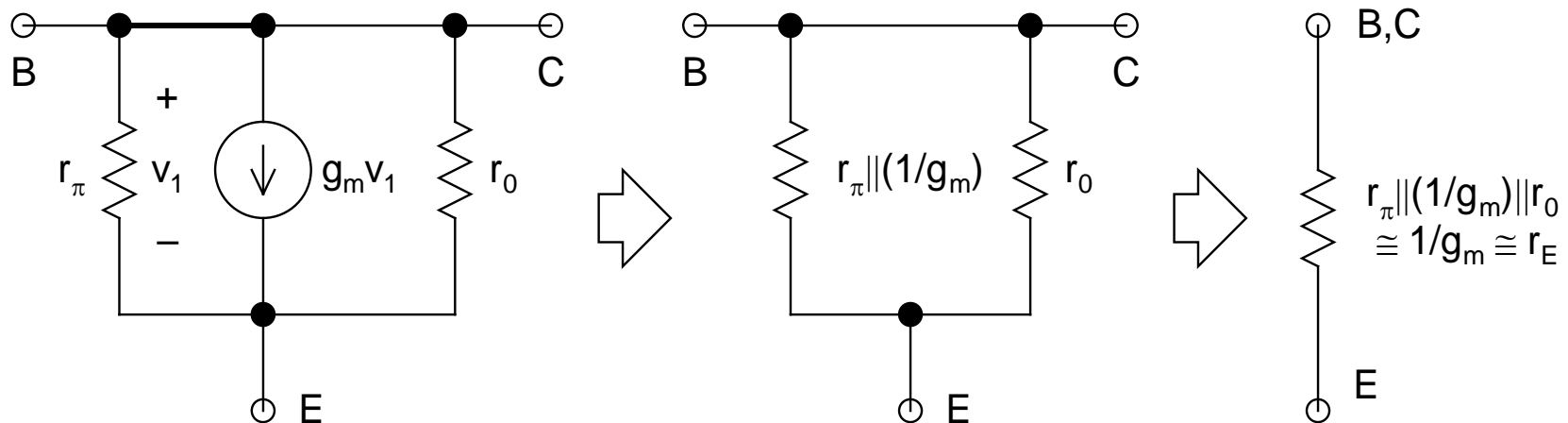

- The *small-signal equivalent* consists simply of r_E , which is the same as that for a **diode**
- Hence the name *diode-connected BJT*

- *Algorithm to find R_0 :*
 - *Short all independent DC/ac voltage sources*
 - *Open all independent DC/ac current sources*
 - *Replace the active device by its low-frequency hybrid- π model*
 - *Excite the output terminal by a test voltage source (ac) v_t*
 - *Find the current (ac) i_t drawn from v_t*
 - *Then, $R_0 = v_t/i_t$*

- *For the complete circuit:*

- *Left part of the circuit has no source*

$$\Rightarrow v_2 = 0$$

$$\Rightarrow g_{m2}v_2 = 0$$

- Thus, $R_0 = v_t/i_t = r_{o2} = V_{A2}/I_0$

- For a *good current source*, R_0 should be as large as possible (ideally infinite)

$$\Rightarrow V_{A2} \text{ should be as large as possible and/or } I_0 \text{ should be as small as possible}$$
