

# THE OPERATIONAL AMPLIFIER (OP-AMP)

- ***The Ultimate***: A *phenomenal application* of everything that we have learnt so far in this course
- *Op-Amp*: *Operational Amplifier*
- *Hugely powerful block*
- *Capable of performing various circuit functions*
- *Original inventor*: *George Philbrick* of *Bell Labs* in *1952* using *vacuum tube technology*

- *Remarkable innovations* in *design* in the form of an *IC* by *Bob Widlar* of *Fairchild Semiconductors* in *1963*
- After that, *several improvements* took place, and the *most versatile design*, widely came to be known as the *741 op-amp*, originated
- Basically a *three-stage architecture*:
  - *The Input Stage*
  - *The Gain Stage*
  - *The Output Stage*


- *The Input Stage:*
  - *Should be capable of double-ended to single-ended conversion*
  - *Should have moderate to high gain*
  - *Must definitely have extremely large CMRR (this is the main requirement)*
  - *Almost invariably a Differential Amplifier (DA)*

- *The Gain Stage:*


- *Can be any one of the many that we have studied in the chapter on Amplifiers*
- *CC-CE Darlington configuration preferred*
- *Should have moderate to large gain*

- *The Output Stage:*

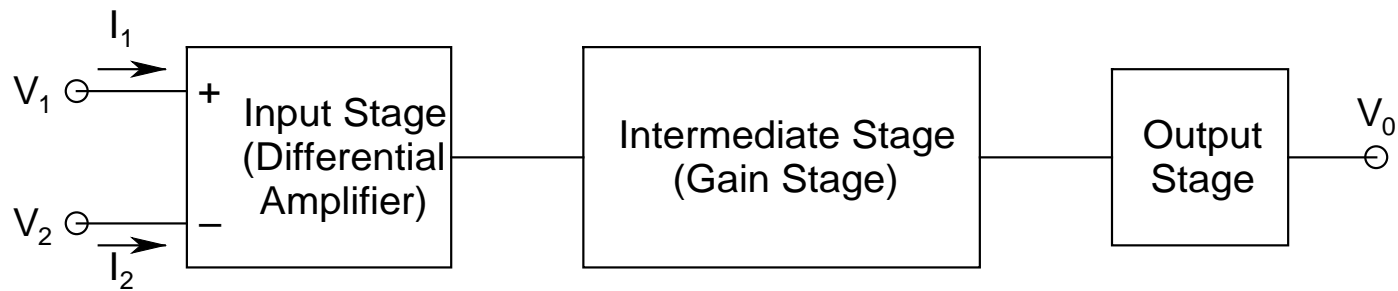- *Needed when the op-amp is expected to either source or sink large amount of current to or from the load*


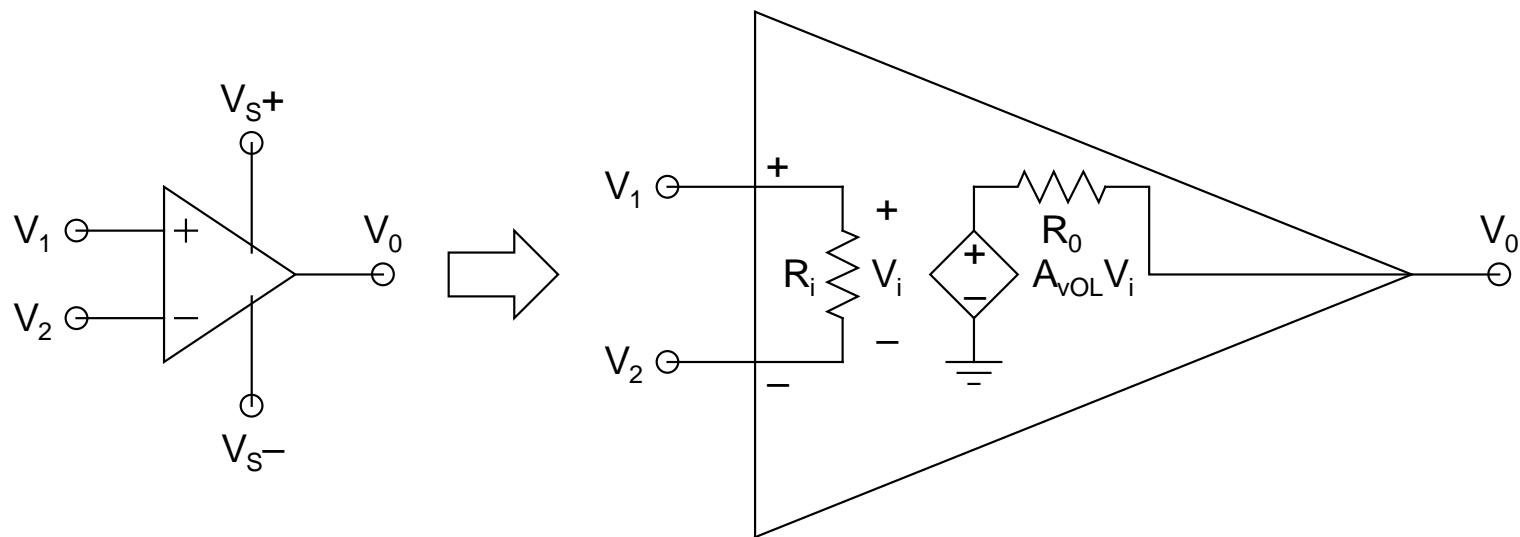
## Basic Three-Stage Architecture of an Op-Amp



Symbol

MacroModel

- **2 Input Terminals:**
  - $V_1$  (*non-inverting* [+])
  - $V_2$  (*inverting* [-])
- **1 Output Terminal:**  $V_0$
- $V_1$ ,  $V_2$ , and  $V_0$  can be *simply DC*, or *simply ac*, or a *combination of both*
- $I_1$ ,  $I_2$ : *Input currents flowing into the + and – terminals respectively*
- **Dual symmetric power supplies** ( $V_{S+}$  and  $V_{S-}$ )

- Refer to the *MacroModel*:

- $R_i$ : *Input Resistance*

- *Very high (ideally infinite)*

- $R_o$ : *Output Resistance*

- *Very small (ideally zero)*

- $A_{vOL}$ : *Open-Loop Gain*

- *Very large (ideally infinite)*

- *Input-Output Relation*:

$$V_o = A_{vOL}(V_1 - V_2)$$



- $V_1$ ,  $V_2$ , and  $V_0$  are measured *w.r.t. ground*, but  $V_i$  is a *floating signal* (*difference* between  $V_1$  and  $V_2$ )
- The *controlled source* in the *MacroModel* is *VCVS*
- For  $V_1 > (<) V_2$ ,  $V_0$  is *positive* (*negative*)
- *Typical values for 741 op-amp*:
  - $A_{VOL} \sim 10^5$  (*100 dB*),  $R_i > 1\text{ M}\Omega$ ,  $R_o < 100\ \Omega$ ,  
CMRR  $\sim 80\text{-}100\text{ dB}$ ,  $V_{S+}$  and  $V_{S-}$ :  $\pm 3\text{ V to } \pm 15\text{ V}$