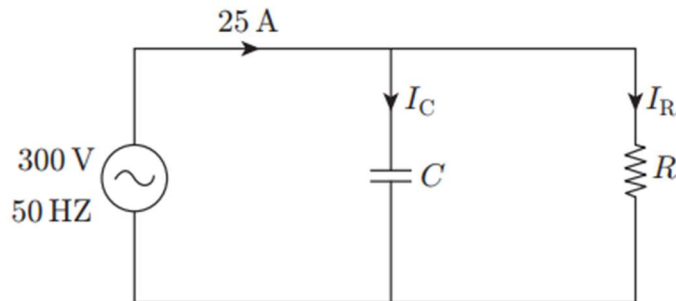


## Tutorial 7

1. A circuit, having  $159.23 \mu\text{F}$  capacitor in parallel with a resistance  $R$ , draws current of  $25 \text{ A}$  from a  $300 \text{ V}$ ,  $50 \text{ Hz}$  mains. Using phasor relations, find the frequency ( $f$ ) at which circuit draws the same current from a  $360 \text{ Volts}$  mains.



Solution-

from the ckt, we have


$$I_C = \frac{V}{Z_C}$$

$$|I_C| = \omega C V = 300 \times 2\pi \times 50 \times 159.23 \times 10^{-6} = 15 \text{ A}$$

$$I_R = \sqrt{I^2 - I_C^2} = \sqrt{(25)^2 - (15)^2} = 20 \text{ A}$$

$$R = \frac{V_R}{I_R} = \frac{300}{20} = \underline{\underline{15 \Omega}}$$

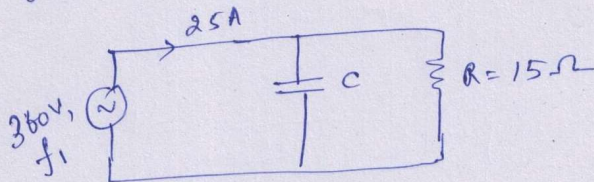With  $360 \text{ V}$  mains, the circuit is



$$I_R = \frac{360}{15} = 24 \text{ A}$$

$$|I_C| = \sqrt{25^2 - 24^2} = 7 \text{ A}$$


$$|I_C| = V \omega C$$

$$7 = 360 \times 2\pi \times f_1 \times 159.23 \times 10^{-6}$$

$$\boxed{f_1 = 19.4 \text{ Hz}}$$

2. A balanced delta connected load of  $(8 + j6)\Omega$  per phase is connected to a 400 V, 50 Hz, 3-phase supply lines. If the input power factor is to be improved to 0.9 by connecting a bank of star connected capacitors, Find required kVAR of the capacitor bank.

Solution-

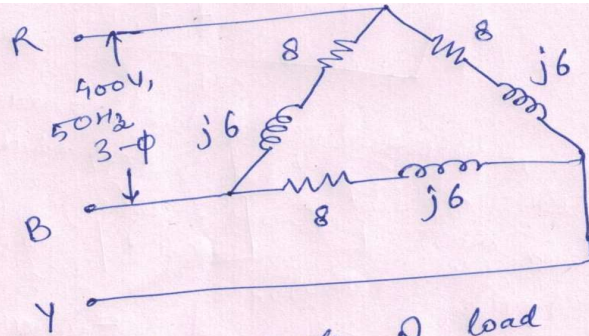

Power factor angle of load

$$\phi = \tan^{-1}\left(\frac{6}{8}\right) = 36.86^\circ$$

Active power consumed by the delta connected balanced load is -

$$P = 3 V_{ph} I_{ph} \cos \phi$$

$$= 3 \times 400 \times \frac{400}{\sqrt{8^2 + 6^2}} \times \cos 36.86 = 38400 \text{ W}$$

Reactive power consumed by  $\Delta$ -connected balanced load is -

$$Q_1 = 3 \times V_{ph} \times I_{ph} \times \sin \phi$$

$$= 3 \times 400 \times \frac{400}{\sqrt{8^2 + 6^2}} \times \sin 36.86$$

$$= 28793.36 \text{ VAR}$$

Active power remains same even after capacitor bank is connected. Reactive power consumed by  $\Delta$ -connected load at a p.f of 0.9 will be -

$$Q_2 = \frac{P}{0.9} \sin(\cos^{-1} 0.9)$$

$$= \frac{38400}{0.9} \times \sin(25.84)$$

$$= 18597.96 \text{ VAR}$$


$$Q_2 = 18597.96 \text{ VAR.}$$

Reactive power supplied by Y-connected capacitor bank =  $Q_1 - Q_2 = 28793.36 - 18597.96$

$$= 10195.4 \approx 10.2 \text{ kVAR}$$



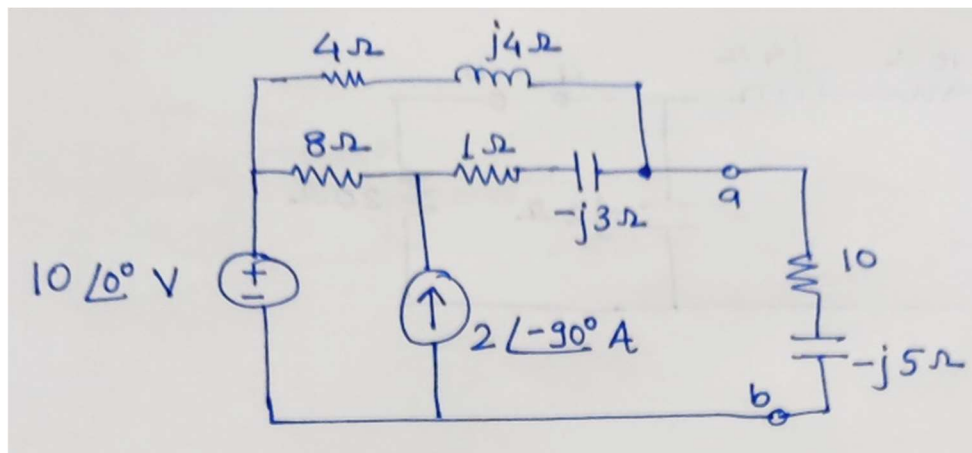3. For the circuit shown, find the Norton's Equivalent between points a & b.




Solution –

$$Z_n = (4 + j4) \parallel (8 + 1 - j3) = \frac{(4 + j4)(9 - j3)}{4 + 4j + 9 - j3}$$


$$Z_n = \frac{48 + j24}{13 + j}$$

Now,

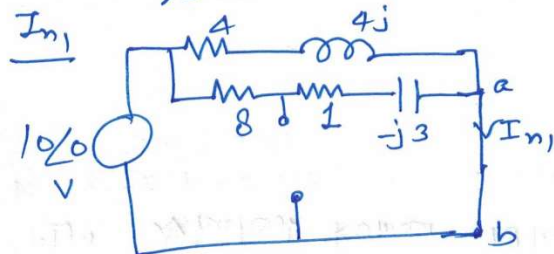$I_n$  can be calculated by taking one source at a time.


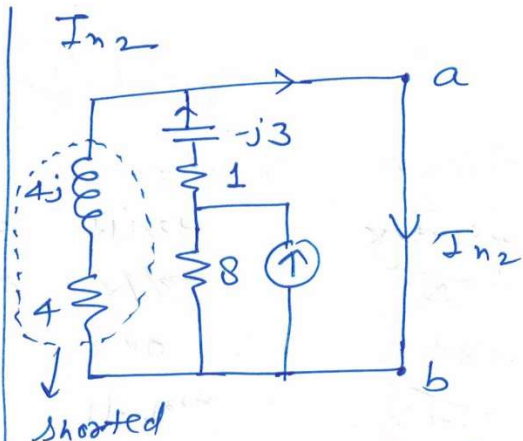
$$I_{n1} = \frac{10 \angle 0^\circ}{(4 + j4) \parallel (9 - j3)} = (2.25 - 0.916j) \text{ A}$$



$$\therefore I_{n2} = \frac{2 \angle -90^\circ \times 8}{8 + 1 - j3} \text{ (current division)}$$


$$I_n = (0.533 - 1.6j) \text{ A}$$

$$I_n = I_{n1} + I_{n2} = 2.783 - j2.516 \text{ A} = 3.701 \angle -42.11^\circ \text{ A}$$

4.

Q) A three-phase balanced Y-connected source supplies a balanced delta connected load. The impedance per phase of the delta load is  $Z = 12 + j9 \Omega$ . If the line impedance is zero and the line current in 'a' phase is  $I_a = 24 \angle 16.27^\circ \text{ A}$ , load voltage  $V_{AB}$  is

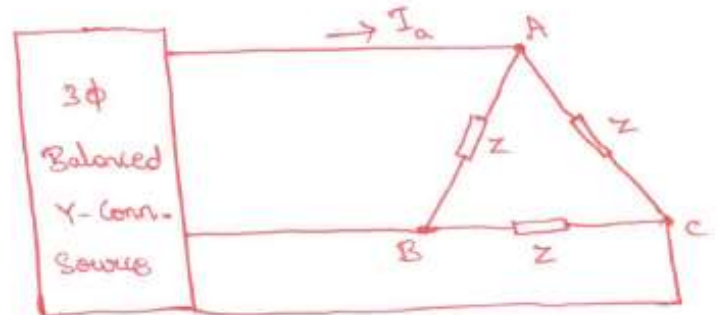
- a)  $208 \angle 83.13^\circ \text{ V}$
- b)  $120 \angle 83.13^\circ \text{ V}$
- c)  $150 \angle 53.13^\circ \text{ V}$
- d)  $208 \angle 53.13^\circ \text{ V}$



Converting delta connected load into eq. Y-configuration,

$$Z_Y = \frac{Z_\Delta}{3} = \frac{12 + j9}{3} = 4 + j3 \Omega = 5 \angle 36.86^\circ$$

Per phase Y-Y eq. circuit,

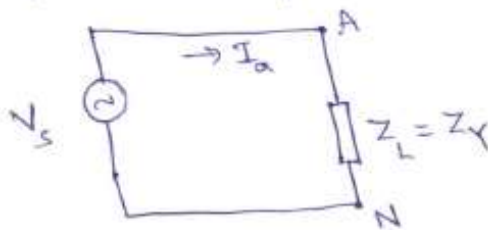


Per phase load voltage,  $V_{AN} = I_a \cdot Z_L = 24 \angle 16.27^\circ \times 5 \angle 36.86^\circ$   
 $= 120 \angle 53.13^\circ \text{ V}$

Line voltage,  $V_{AB} = \sqrt{3} V_{AN} \angle 30^\circ$   
 $= \sqrt{3} \times 120 \angle 83.13^\circ$   
 $= 208 \angle 83.13^\circ \text{ V}$


5.

Q) what impedance  $Z_L$  should be connected between 'a' and 'b' so that a maximum average power will be absorbed by it?

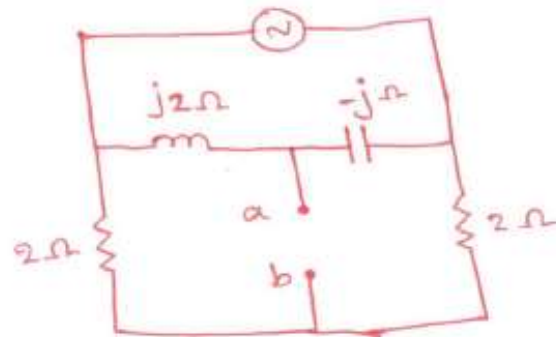
- a)  $1 + j0 \Omega$
- b)  $4 + j2 \Omega$
- c)  $4 - j2 \Omega$
- d)  $1 + j2 \Omega$



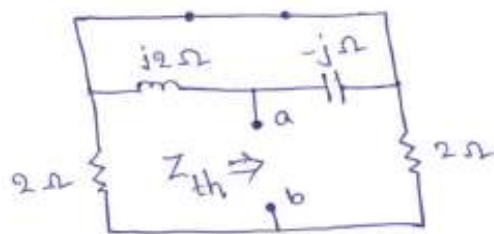Obtain thevenin impedance from terminal a, b



Redrawing the circuit in a simpler way

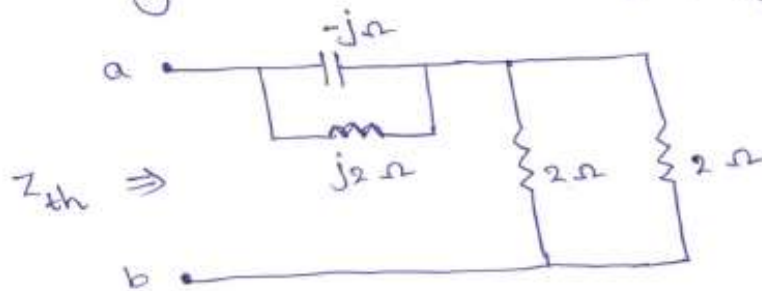

$$Z_{th} = (-j1 \parallel j2) + (2 \parallel 2)$$

$$= 1 - j2 \Omega$$

For maximum power transfer,  $Z_L = Z_{th}^*$

$$Z_L = 1 + j2 \Omega$$

6. Three star-connected impedances  $Z_1 = 20 + j37.7 \Omega$  per phase are connected in parallel with three delta-connected impedances  $Z_2 = 30 - j159.3 \Omega$  per phase. The line voltage is 398 V. Find the active power taken by the combination.

$$Z_Y = Z_1 = 20 + j37.7 \Omega$$

$$Z_\Delta = Z_2 = 30 - j159.3 \Omega$$

We have to convert the whole arrangement into its equivalent star config.

$$Z_{\text{equiv.}} = \left( Z_1^{-1} + \left( \frac{Z_2}{3} \right)^{-1} \right)^{-1}$$

$\xrightarrow{\text{[delta to star conversion]}}$

$$= \left( \frac{1}{20 + j37.7} + \frac{1}{10 - j53.1} \right)^{-1} \Omega = 68.37 \angle 9.92^\circ \Omega$$

$$I_{\text{ph}} = \frac{V_{\text{ph}}}{Z_{\text{ph}}} = \frac{398/\sqrt{3}}{68.37 \angle 9.92} = 3.36 \angle -9.92^\circ \text{ A} = I_{\text{line}}$$

$$P = \sqrt{3} V_{\text{line}} I_{\text{line}} \cos \phi = (\sqrt{3} \times 398 \times 3.36 \times \cos 9.92) \text{ W}$$

$$= \underline{2281.6 \text{ W}} \quad (\bar{A})$$