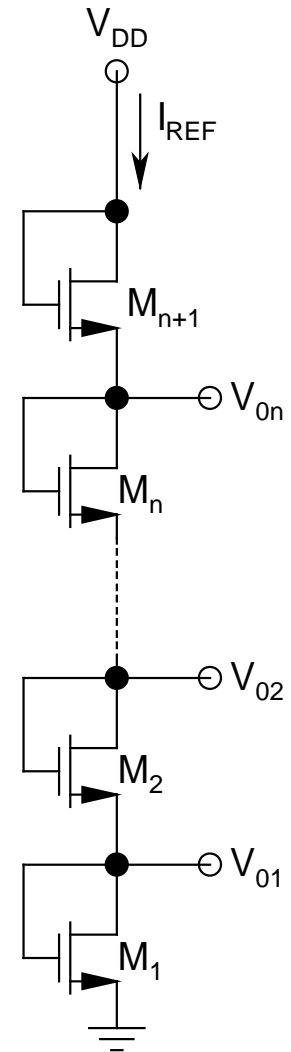


- ***NMOS Voltage Reference:***
  - *Highly popular due to its simplicity and effectiveness*
  - *Can generate  $n$  voltage references from  $(n + 1)$  MOSFETs*
  - *All MOSFETs diode-connected*  
⇒ *Always saturated*
  - *No resistors needed*
  - *All bodies connected to ground*



- *Only for  $M_1$* ,  $V_{TN1} = V_{TN0}$
- *All other MOSFETs will have body effect*,  
e.g.,  $V_{TN2} = V_{TN0} + \gamma \left( \sqrt{2\phi_F + V_{01}} - \sqrt{2\phi_F} \right)$
- Generally, *all  $\lambda$ s also same*, but *aspect ratios are different*
- $V_{01}, V_{02}, \dots, V_{0n}$  are the *needed reference taps*
- $V_{GS1} = V_{DS1} = V_{01}$ ,  $V_{GS2} = V_{DS2} = V_{02} - V_{01}$ ,  
 $V_{GS3} = V_{DS3} = V_{03} - V_{02}, \dots$
- $V_{SB1} = 0$ ,  $V_{SB2} = V_{01}$ ,  $V_{SB3} = V_{02}, \dots$
- *Same DC current  $I_{REF}$  flows through all MOSFETs*

- Assuming that *all MOSFETs* have *same*  $\lambda$  and *same*  $k'_N$ :

$$\begin{aligned} I_{REF} &= \frac{k'_N}{2} \left( \frac{W}{L} \right)_1 (V_{01} - V_{TN1})^2 (1 + \lambda V_{01}) \\ &= \frac{k'_N}{2} \left( \frac{W}{L} \right)_2 (V_{02} - V_{01} - V_{TN2})^2 [1 + \lambda (V_{02} - V_{01})] \end{aligned}$$

...

- *First  $I_{REF}$  needs to be found by ensuring that the circuit dissipates least DC power*
- *Then, all  $(W/L)$ s can be calculated*

- *Choice depends on several design paradigms*
- $P_D = V_{DD} \times I_{REF}$   
 $\Rightarrow$  *For minimum  $P_D$ ,  $I_{REF}$  should be minimum*
- *Need to pick up a reference MOSFET to start the design process*
- *Area of a MOSFET*  $= W \times L$
- *For minimum area,  $W = L = MFS$* 
  - ***MFS**: Minimum Feature Size (that is allowed by the technology)*
- Pick the *reference MOSFET* by choosing its  $(W/L) = 1$ , and having the *least*  $V_{GT}^2 (1 + \lambda V_{DS})$

- *This will yield minimum  $P_D$*
- *Once the reference MOSFET is chosen,  $I_{REF}$  becomes known, and  $(W/L)$ s of all other MOSFETs can be calculated*
- *Total area taken up by the circuit:*

$$\sum_n (W \times L)_n$$
- *Care: No dimension can be  $< MFS$*
- *Then what to do if  $(W/L) < 1$ ?*