

Plug $dP_1/dI_{c1} = 0$ to get $I_{c1} = V_{CC}/(2R_L)$

This is the *mid-point of the load line*, with *coordinates* $[V_{CC}/2, V_{CC}/(2R_L)]$

$$\Rightarrow P_{\max} = \frac{V_{CC}^2}{2R_L} \text{ (using a Safety Factor of 2)}$$


❖ There is also *standby power*:

$$P_{\text{Standby}} = V_{CC} \times I_{\text{Standby}}$$

❖ In general, $P_{\max} \gg P_{\text{Standby}}$

❖ Refer to the figure in the next slide

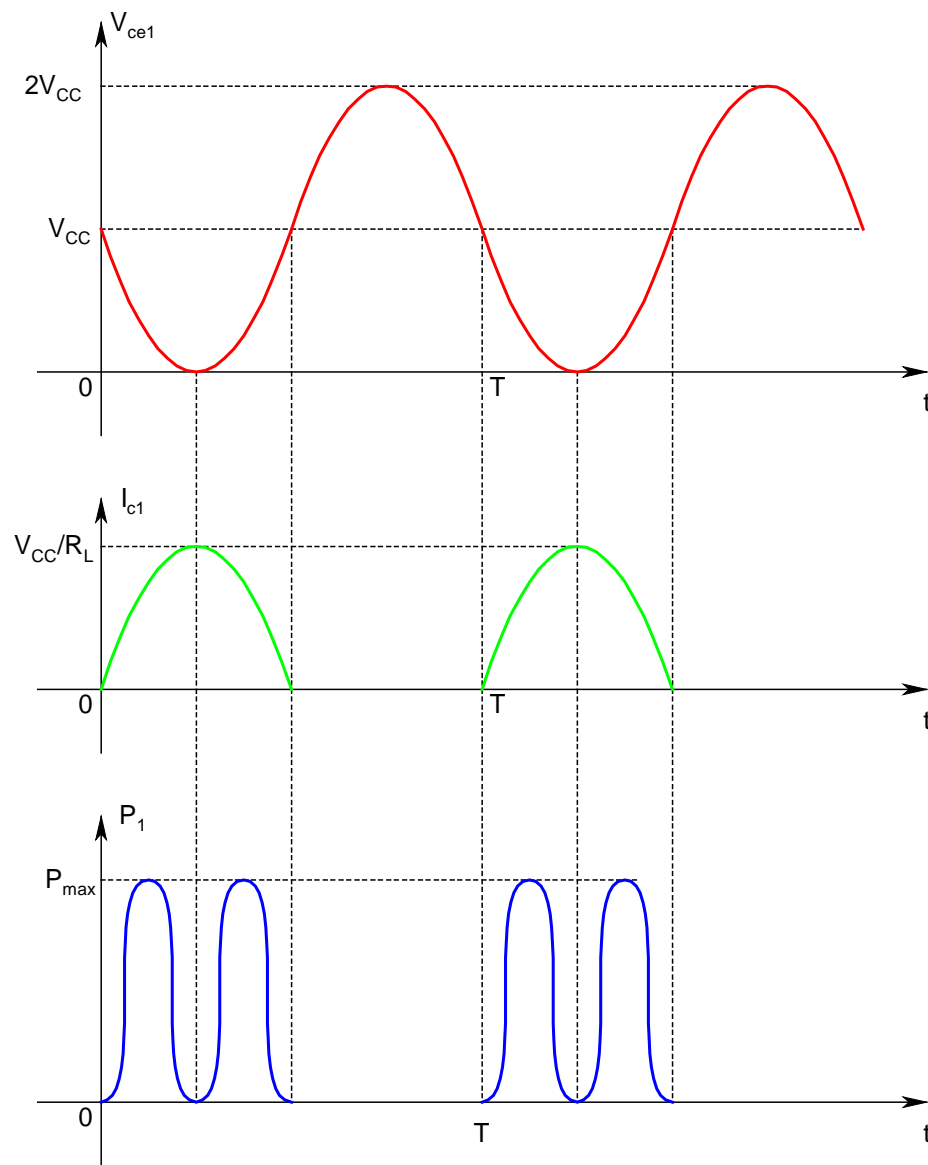- o V_{ce1} *oscillates between 0 and $2V_{CC}$*
- o I_{c1} *appears only during the positive half cycle, with peak value of V_{CC}/R_L (when $V_{ce1} = 0$)*
- o $P_1 (= V_{ce1} \times I_{c1})$ *oscillates* between 0 and $V_{CC}^2/(4R_L)$ at *twice the frequency* only during the *positive half cycle*



❖ *Two Special Cases:*

- o $R_L \rightarrow \infty$ (*open-circuit*):

Load line becomes horizontal with $I_{c1} = 0$

$\Rightarrow P_1 = 0 \Rightarrow$ *no issue*

- o $R_L = 0$ (*short-circuit*):

Load line becomes vertical with $I_{c1} \rightarrow \infty$

Potentially dangerous situation

Resulting power dissipation and consequent heat generation can completely damage the device

❖ *In actual situation, I_{c1} won't reach infinite value due to:*

- o *Limited current driving capability of the driver stage*
- o *Fall of β at high current levels due to High-Level Injection or Kirk Effect*

❖ These two are *in-built self-protection mechanisms*

❖ Nevertheless, *practical output stages need short-circuit protection*

➤ **Linearity and Output Resistance:**

- *While supplying/sinking current to/from load, Q_1/Q_2 operate in CC mode*

$$\Rightarrow A_v = R_L / (R_L + r_{Ei}) \quad (i = 1, 2) \quad (r_{Ei} = V_T / I_{ci})$$

- Thus, if $R_L \gg r_{Ei}$, then $A_v \rightarrow 1$, and *very high linearity in the VTC can be achieved*
- However, r_{Ei} *is not constant* - rather *it changes with the load current*
- Thus, A_v *can depart significantly from unity*, when the *load current is very small* (*large r_{Ei}*)
- Referring to the *VTC*, the *slope of the characteristic near $\pm V_\gamma$* will be *significantly less than unity* (*Class B*)

- However, *as $V_o \uparrow$, load current \uparrow , $r_{Ei} \downarrow$* , and the *VTC starts to attain its maximum slope of unity*
- Thus, *for major part*, the *VTC is highly linear* and *produces an almost distortionless output*
- *Output Resistance:*
 - *Open R_L and look back from the output*
 - $R_o = r_{Ei}$ (*by inspection*), since *bases of Q_1 - Q_2* can be considered to be at *ac ground*
 - R_o *is variable*, but *for major part, extremely small*
- Generally, the *linearity and output resistance* are *calculated* at the *region of maximum slope* of the *VTC*