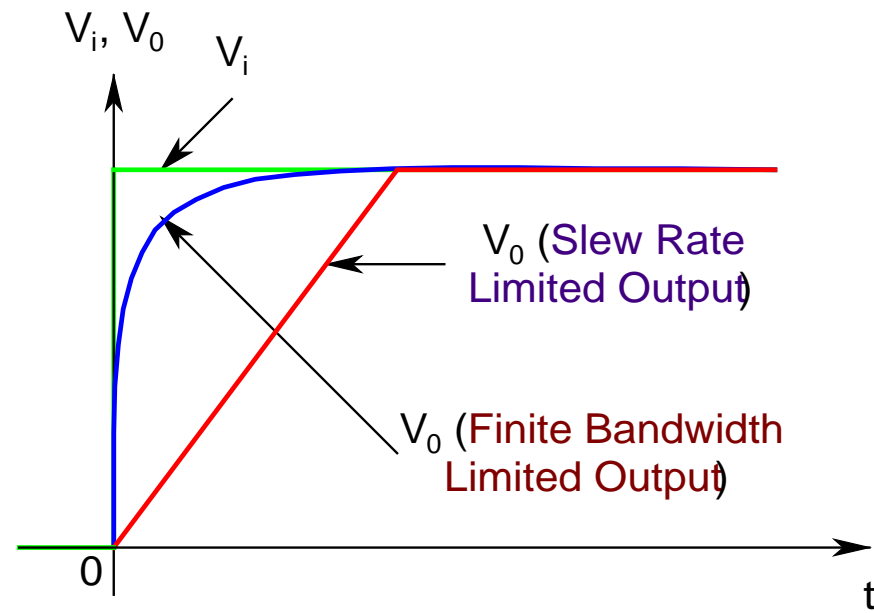


- Similarly, when a *large positive signal* is applied at the *base* of Q_1 (w.r.t. the base of Q_2), Q_2 - Q_4 branch would *instantly turn off*
 - \Rightarrow *Entire bias current* I_{C8} would *flow* through the Q_1 - Q_3 *branch*, *pushing the same current* through Q_5
 - \Rightarrow Q_6 would *carry the same current* (*mirror* with Q_5)
- This *current* would *flow* from the *output node* through C_C to Q_6
 - \Rightarrow C_C would *start to discharge*, and V_0 would *start to fall*, going into its *negative swing*
- Since the *same current* (I_{C8}) is used to *discharge* the *output node*:


$$SR^+ = SR^- = 1.52 \text{ V}/\mu\text{sec}$$




Slew Rate Limitation of Op-Amps

- Situation becomes *more dramatic* if a *sinusoidal signal* is applied at the *non-inverting input* of the op-amp, connected in a *voltage-follower* configuration
- Let *input signal* $V_i = V_M \sin(\omega t)$, with *large* V_M
 \Rightarrow *Transistors* in the *differential input stage* act as *switches*
- Under *unity feedback*, V_o would *follow* V_i
 $\Rightarrow dV_o/dt = dV_i/dt = V_M \omega \cos(\omega t)$
- The *maximum value* of this *derivative* occurs when $\omega t = n\pi$ ($n = 0, 1, 2, \dots$)
 \Rightarrow It occurs when the *signal crosses zero*
- So long as *this rate* remains *smaller* than SR, V_o would *follow* V_i with *fidelity*


- However, as soon as dV_0/dt becomes $\geq SR$, V_0 won't be able to follow V_i anymore – rather, it would start to become triangular
- **Note:** $dV_0/dt \uparrow$ with an increase of either V_M or ω or both
 - \Rightarrow What essentially matters is the product $V_M \omega$
- If this product keeps on increasing beyond the SR, then V_0 remains triangular, however, two major observations become apparent:
 - ❖ The zero crossings of V_0 do not quite coincide with those of V_i
 - ❖ The peak-to-peak swing of V_0 starts to become smaller than that of V_i due to V_0 not getting enough time to reach its maximum possible value

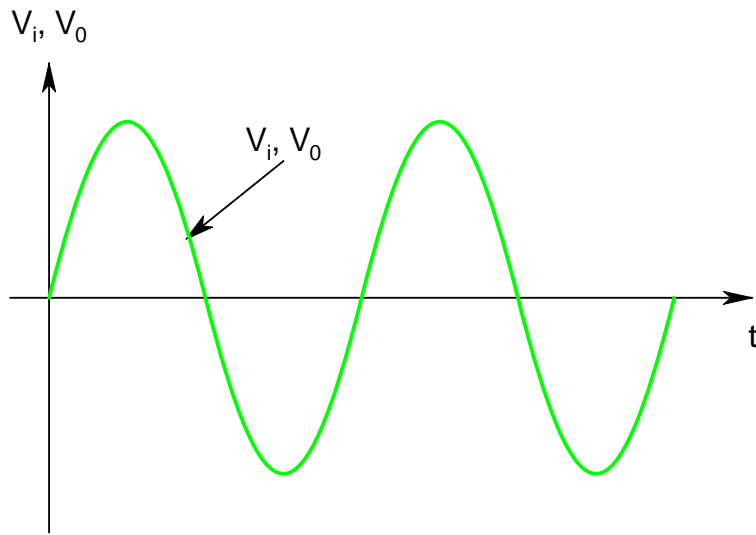

Normal Behavior

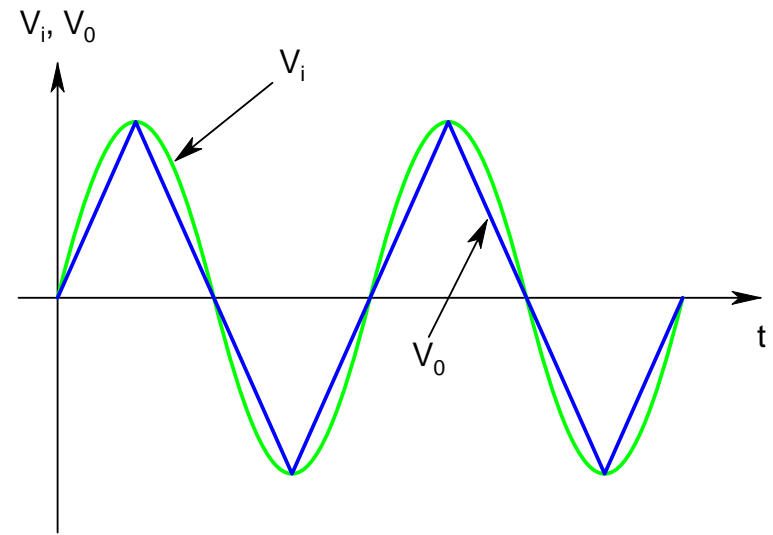

Onset of Slew Rate Limitation

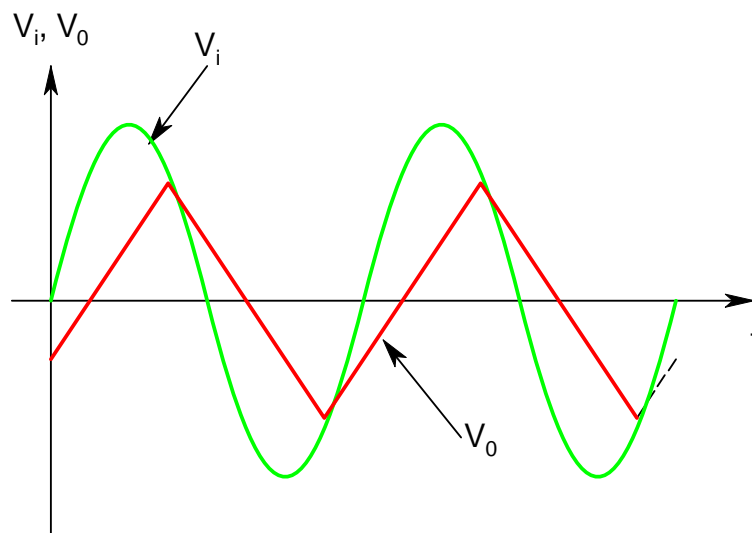

Severely Slew Rate Limited

- If $V_M\omega$ becomes *very large*, then there *may not be any output at all*
 - $\Rightarrow V_0$ would *become zero*, implying that the op-amp is *not able to keep up with the variation* of V_i at all!
- *Mathematical Description:*
 - ❖ Let the *gain* of the op-amp = A
 - $\Rightarrow (dV_0/dt)_{\max} = AV_M\omega$
 - ❖ This must be *less* than the SR of the op-amp to get a *distortion-free output*
 - ❖ *Maximum possible value* of $AV_M = V_{SAT}$
 - \Rightarrow The *maximum allowed value* of ω ($= \omega_M$) of V_i for V_0 to be *without any distortion* due to *slew rate limitation*:

$$\omega_M = SR/V_{SAT}$$

- This is an *extremely important relation*, and ω_M is referred to as the *full-power bandwidth*
- It is a *constant* for a given op-amp
- This *derivation* is for V_0 *swinging* between $\pm V_{SAT}$
- If the *swing* of V_0 is *less* than this, then ω can be *increased* beyond ω_M , following the *relation*:

$$SR = \omega_M V_{SAT} = \omega_0 V_0 = \omega_0 A V_i$$

ω_0 : *Frequency till which V_0 won't have any slew rate limited distortion*

\Rightarrow *Maximum amplitude* of V_i (of *frequency* ω_0), beyond which *slew rate limited distortion* would *set in at the output*:

$$V_{i,max} = \omega_M V_{SAT} / (\omega_0 A)$$

