

# ESC201T : Introduction to Electronics

MQ5 (20/11/2020)

Q. Design an opamp based circuit that would generate the following output ( $V_{out}$ ) given two input voltages  $v_{s1}$  and  $v_{s2}$

$$V_{out} = 2.5v_{s1} - 4v_{s2}.$$

You may assume ideal opamp characteristics. Choose resistor values as small as possible but with the **constraint that they must be larger than or equal to  $1k\Omega$ .**

As usual, show all steps of your work to receive full credit for the answer.