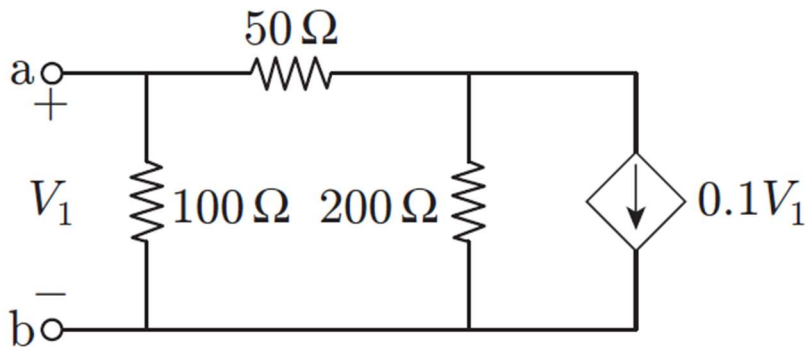



1. Determine the Thevenin equivalent resistance R_{TH} between terminals a and b, shown in the figure below.




Solⁿ: The problem can be solved using source transformation.

The n/w contains only dependent source, therefore its $V_{TH} = 0$

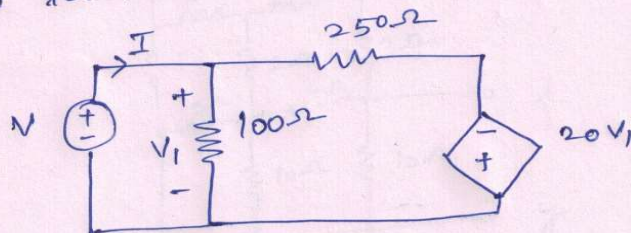For finding, R_{TH} , one test voltage 'V' is applied b/w terminals a and b.



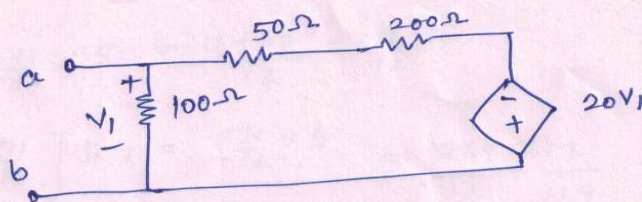
$$-I + \frac{V}{100} + \frac{V + 20V_1}{250} = 0$$





Here, $V = V_1$, therefore

$$I = \frac{V}{100} + \frac{21V}{250}$$
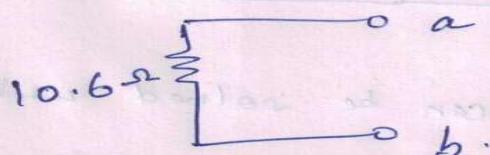
$$\frac{V}{I} = R_{TH} = \frac{500}{47} = 10.6 \Omega$$



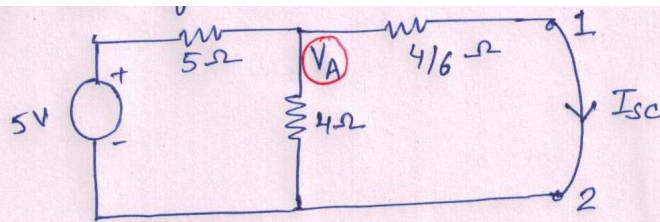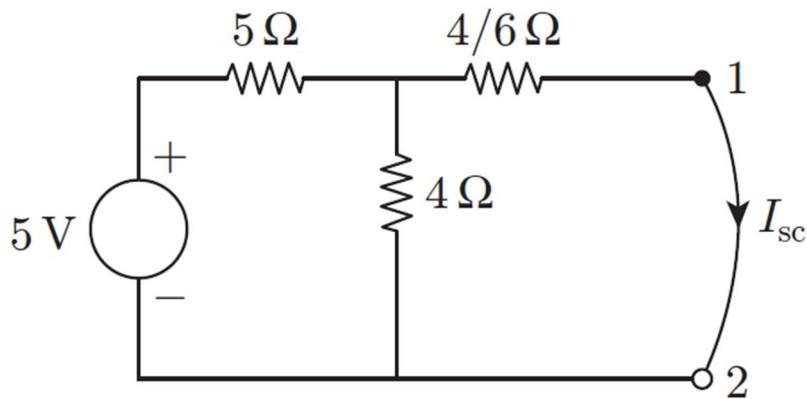2. In the Norton's equivalent of the given network, the values of current, I_{sc} , and Thevenin equivalent resistance, R_{Th} , are, respectively:




Solⁿ: Consider the given circuit, the nodal analysis of node 1 gives:-

$$\frac{V_A - 5}{5} + \frac{V_A}{4} + \frac{V_A \times 6}{4} = 0$$

$$\frac{4V_A - 20 + 5V_A + 30V_A}{20} = 0$$


$$\text{or } 39V_A = 20 \Rightarrow V_A = \frac{20}{39} = 0.512V$$
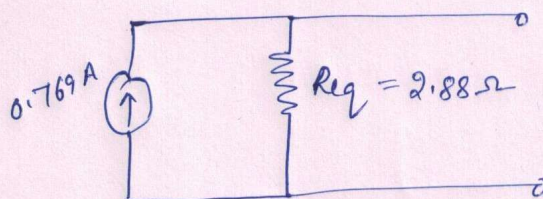
$$I_{sc} = \frac{0.512 \times 6}{4} = \underline{\underline{0.769A}}$$



$$R_{eq} = \frac{4}{6} + \frac{20}{9} = \underline{\underline{2.88\Omega}}$$

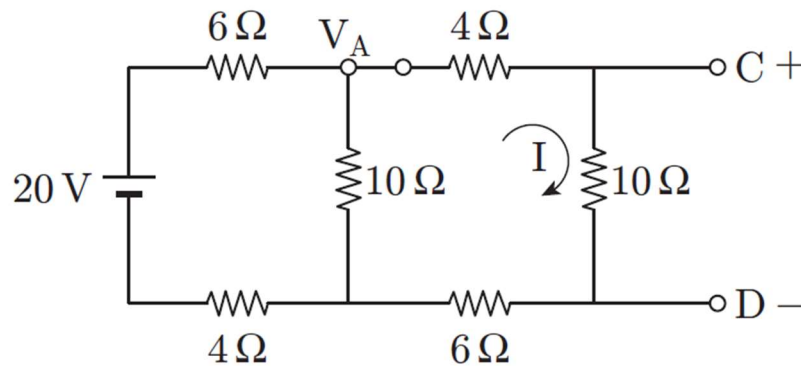3. Find the parameters of Thevenin equivalent circuit for the following circuit.



Solⁿ: From the circuit,

$$\frac{V_A - 20}{6} + \frac{V_A}{10} + \frac{V_A}{20} = 0$$


$$2V_A - 40 + 2V_A + V_A = 0$$

$$5V_A = 40 \Rightarrow \underline{V_A = 8V}$$

$$I = \frac{8}{20} = 0.4A$$

$$V_{CD} = 10 \times 0.4 = \underline{4V}$$

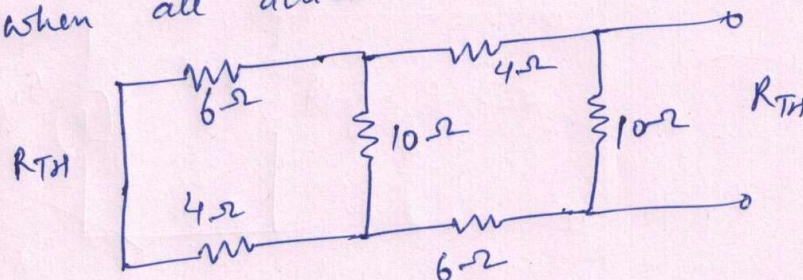The equivalent resistance across the terminals, when all active sources are zero is -




$$\Rightarrow \left(\frac{10 \times 10}{20} + 10 \right) \parallel 10 = \frac{15 \times 10}{25} = \underline{6\Omega}$$

$$\boxed{R_{TH} = 6\Omega}$$

$$\boxed{V_{TH} = 4V}$$

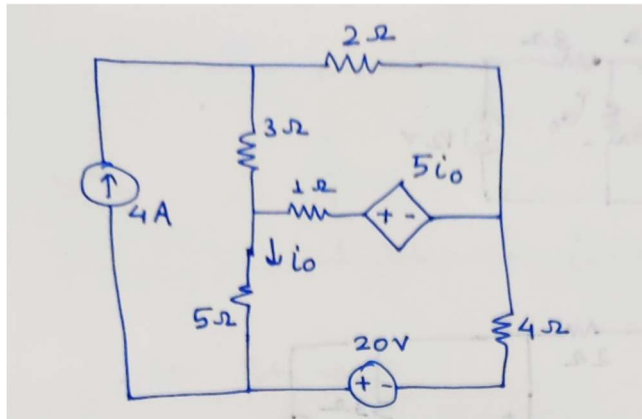4. Find the current i_o in the following circuit using superposition theorem.



Solution -

For 4A Source

For loop 1, $i_1 = 4A$

For loop 2,

$$-3i_1 - 6i_2 - i_3 - 5i_o = 0$$

For loop 3

$$-5i_1 - i_2 + 10i_3 + 5i_o = 0$$

At ground node,

$$i_3 = 4 - i_o$$

$$\therefore 3i_2 - 2i_o = 8$$

$$i_2 + 5i_o = 20$$

$$\therefore i_o = \frac{52}{17} A$$

For 20V source

For loop-4

$$6i_4 - i_5 - 5i_o = 0$$

for loop-5

$$-i_4 + 10i_5 - 20 + 5i_o = 0$$

also $i_5 = -i_o$

$$\therefore 6i_4 - 4i_o = 0$$



$$i_4 + 5i_o = -20$$

$$\therefore i_o = -\frac{60}{17} A$$

Resultant

$$i_o = -\frac{8}{17} \text{ Amp}$$

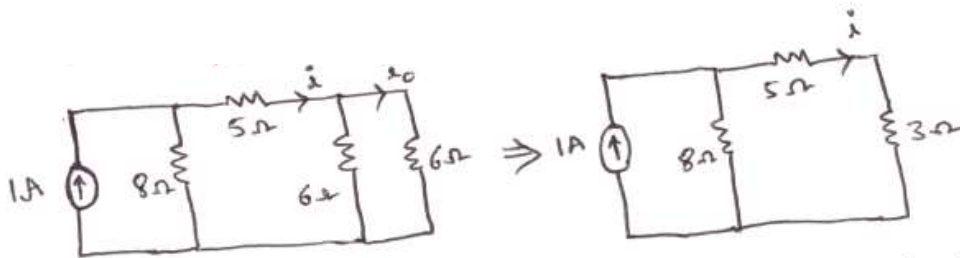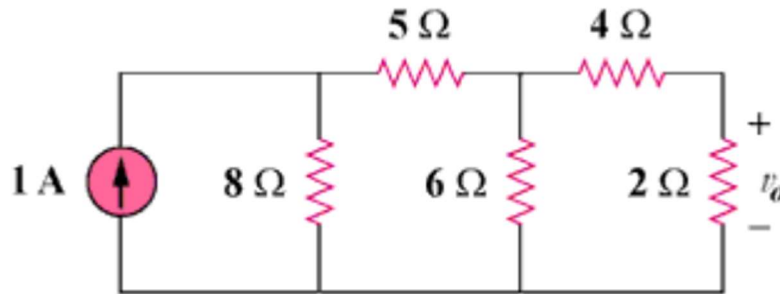5. Find V_0 in the circuit below where the source is 1 Ampere current source. Let this V_0 be $V_{0,old}$. Now, if the current source is reduced to 1 mA and the V_0 be $V_{0,new}$, the values of $V_{0,old}$ and $V_{0,new}$ respectively are,



⇒ Since we have two parallel 6Ω resistors, current gets divided equally. So, $i = 0.5\text{ A}$.

⇒ From this circuit, we can see that 'i' gets divided equally among two parallel 6Ω resistors. So, $i_0 = 0.25\text{ A}$



⇒ So, current through 2Ω resistor in the original circuit is $i_0 = 0.25\text{ A}$. So, $V_0 = 2 \times 0.25 = 0.5\text{ V}$. $V_{0,old} = 0.5\text{ V}$

⇒ If current source is reduced to 1 mA, by linearity principle, V_0 also gets reduced by same proportion.

Source		V_0
1 A	→	0.5 V
1 mA	→	0.5 mV

→ $V_{0,new} = 0.5\text{ mV}$

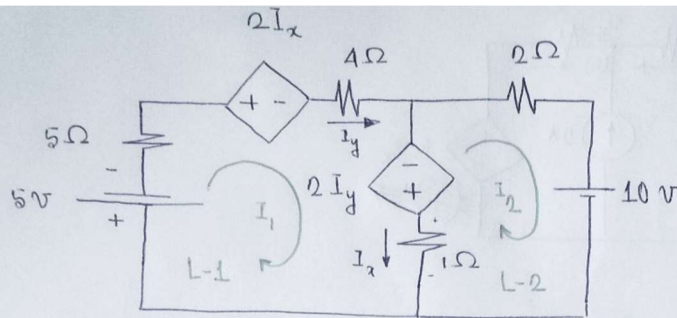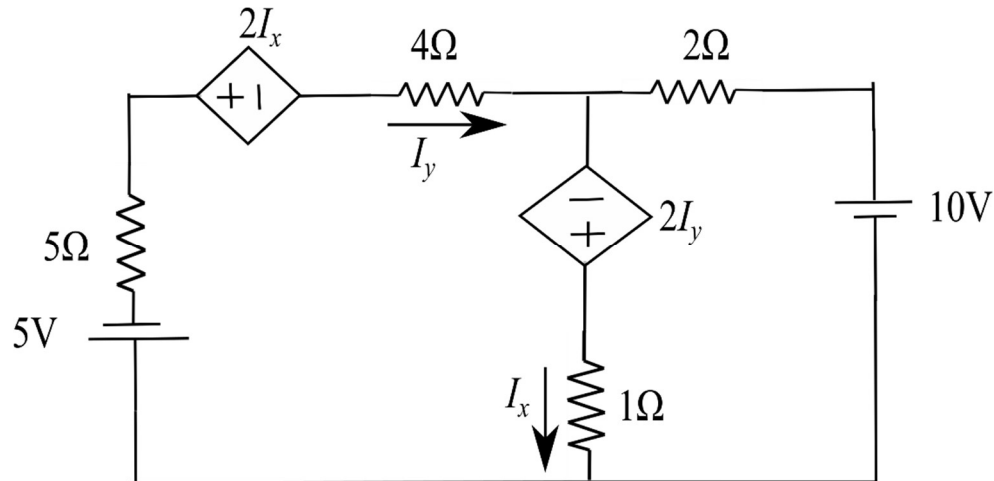6. Find the value of I_x in the circuit shown in figure below -



$$\begin{aligned} I_y &= I_1 \\ I_x &= I_1 - I_2 \end{aligned}$$

Loop eqⁿ for L-1 is:-

$$5 + 5I_1 + 2I_x + 4I_1 - 2I_y + I_x = 0$$

$$\text{or, } 5 + 9I_1 + 3I_x - 2I_y = 0$$

$$\text{or, } 5 + 9I_1 + 3(I_1 - I_2) - 2I_1 = 0$$

$$\text{or, } 5 + 10I_1 - 3I_2 = 0 \quad \text{--- (1)}$$

Loop eqⁿ for L-2 is:-

$$I_x - 2I_y - 2I_2 - 10 = 0$$

$$\text{or, } I_1 - I_2 - 2I_1 - 2I_2 - 10 = 0$$

$$\text{or, } -I_1 - 3I_2 - 10 = 0$$

$$\text{or, } I_1 + 3I_2 + 10 = 0 \quad \text{--- (2)}$$

Solving (1) & (2) we get,

$$I_1 = -1.3636 \text{ A}$$

$$I_2 = -2.8787 \text{ A}$$

$$I_x = I_1 - I_2 = 1.5152 \text{ A (A)}$$

