

Digital Logic Circuits

- ***Combinatorial:***
 - Output depends on **combination of inputs**
- ***Sequential:***
 - Output depends on **inputs** as well as a **clock signal** (*sequenced operation*)
- ***Digital Signals:***
 - ***Discrete***, having values of only 0 and 1 (**binary**)
 - **Hi** (*Logic 1*) and **Lo** (*Logic 0*)
 - There is a region in between which is ***indeterminate (non-discernible)***

Binary Number System:

* ***Based on powers of 2:*** contrast with ***decimal number system***, which is based on ***powers of 10***

* **Uses only two digits: 0 and 1**

* ***Representation and Place Value:***

• ***Integer Part:***

... 2^4 (16) 2^3 (8) 2^2 (4) 2^1 (2) 2^0 (1) .

• ***Fractional Part:***

. 2^{-1} (0.5) 2^{-2} (0.25) 2^{-3} (0.125) 2^{-4} (0.0625) ...

* ***Example:*** $101.101 = 5.625$

* ***Example: Binary to Decimal Conversion:***

$$1 \ 1 \ 0 \ 0 \ 1 = (1 \times 2^4 + 1 \times 2^3 + 1 \times 2^0) = 25$$

* ***Example: Decimal to Binary Conversion:***

$$15 = (1 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0) = 1111$$

* ***Fractional Numbers: Binary to Decimal:***

$$11.101 = (1 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 1 \times 2^{-3}) = 3.625$$

* ***Fractional Numbers: Decimal to Binary:***

$$0.4475 = (1 \times 2^{-2} + 1 \times 2^{-3} + 1 \times 2^{-4}) = 0.0111$$

* **Note:** The decimal equivalent of 0.0111 is 0.4375, but we started with 0.4475 \Rightarrow Known as **Conversion** (or **Quantization**) **Error (QE)**: *The number of bits is not sufficient, we need to increase it to reduce the error*

* **Note:**

- **1 bit numbers:** 0 and 1 (*Decimal equivalent:* 0 and 1)
- **2 bit numbers:** 00 01 10 and 11 (*Decimal equivalent:* 0 to 3)
- **3 bit numbers:** 000 ... 111 (*Decimal equivalent:* 0 to 7)
- **4 bit numbers:** 0000 ... 1111 (*Decimal equivalent:* 0 to 15)

- * ***Inference:*** With N number of bits, we can represent decimal numbers ranging from 0 to $(2^N - 1)$
- * The ***leftmost bit*** is known as the **Most Significant Bit (*MSB*)**, while the ***rightmost bit*** is known as the **Least Significant Bit (*LSB*)**
- * ***Definitions:***
 - 4 Bits \rightarrow 1 Nibble
 - 8 Bits or 2 Nibbles \rightarrow 1 Byte
 - 16 Bits or 2 Bytes or 4 Nibbles \rightarrow 1 Word

* *Addition of Binary Numbers:*

$0 + 0 = 0$, $0 + 1 = 1$, $1 + 0 = 1$, $1 + 1 = 0$ (with a carry of 1)

* *Subtraction of Binary Numbers:*

$0 - 0 = 0$, $1 - 0 = 1$, $1 - 1 = 0$, $0 - 1 = 1$ (with a borrow of 1)

* *Example:* $5 + 6 \Rightarrow 101 + 110 = 1011 \Rightarrow 11$

$9 - 5 \Rightarrow 1001 - 101 = 0100 \Rightarrow 4$

* *Multiplication of Binary Numbers:*

$0 \times 0 = 0$, $0 \times 1 = 0$, $1 \times 0 = 0$, $1 \times 1 = 1$ (no carry)

* *Division of Binary Numbers:*

$0 \div 1 = 0$, $1 \div 1 = 1$, **Division by zero not allowed**
(*overflow*)

* *Some more examples:*

- **Convert decimal 35 to binary (*by division*):**

$35 \div 2 = 17 + \mathbf{1}$ (LSB), $17 \div 2 = 8 + \mathbf{1}$ (next bit),
 $8 \div 2 = 4 + \mathbf{0}$, $4 \div 2 = 2 + \mathbf{0}$, $2 \div 2 = 1 + \mathbf{0}$, $1 \div 2 =$
 $0 + \mathbf{1}$ (MSB)

\Rightarrow **Final binary representation:** 100011

- **Express 0.9×2 in binary:**

$1.8 = \mathbf{1}$ (the lone digit in the integer part) + 0.8
 $0.8 \times 2 = \mathbf{1}$ (the first digit in the fractional part) +
0.6, $0.6 \times 2 = \mathbf{1} + 0.2$, $0.2 \times 2 = \mathbf{0} + 0.4$, ...

\Rightarrow **Final binary representation:** 1.1100...

- * Note that with 4 digits after the decimal point, the converted number is 1.75, which gives ***QE*** of 0.05, which is the same even if we had only 2 digits after the decimal point
 - ⇒ Concept of ***Bit Optimization*** depending on the **maximum allowed QE**
 - ⇒ ***Generally, increase in number of bits leads to lower QE, but not always, as this example clearly illustrates***

Complements and Negative Numbers:

- * *Note:* $X - Y$ is same as $X + (-Y)$
- * Thus, before subtraction, if we *negate* the number that is to be subtracted, then we just need to do an *addition* operation \Rightarrow **simplifies circuitry**
- * *Two methods of negation:*
 - **One's Complement**
 - **Two's Complement**
- * *One's Complement:*
 - Just *invert* all the bits of the binary number
 - *Example:* +5 (0101) becomes -5 (1010)

- To get the original number back, apply *reverse process*, i.e., *invert* all the bits
- Not much used, since it returns both *positive and negative zero* (+0 and -0) (to be discussed)

* *Two's Complement:*

- **One's complement plus 1**, i.e., *invert all the bits, and add 1 to the LSB*
- *Example*: +5 (0101) becomes -5 (1011)
- **Avoids the problem of positive and negative zeros**
- Apply *reverse process* to get the original number back
- *Widely used by modern computer systems*

Sign-Magnitude Convention:

- * In this convention, the ***MSB is reserved for the sign bit*** (0 for positive, and 1 for negative)
- * Thus, for an ***N bit number***, with 1 bit reserved for sign, we can express **0 to $\pm(2^{N-1} - 1)$**
- * ***Example:*** An ***8 bit number*** can represent ***0 to ± 127***
- * ***One's Complement Notation:***
 - ***Example:*** $+15 \rightarrow 01111$, $-15 \rightarrow 10000$
 - ***Note:*** $0000 \rightarrow +0$, $1111 \rightarrow -0$
 - This is why one's complement notation is ***avoided***

* ***Two's Complement Notation:***

- ***Example:*** $3 - 7 = 3 + (-7) = -4$

- ***Note:*** To express -7 in two's complement notation, we need ***4 bits***

- ***Add sign bit:*** $3 \rightarrow 0011$

$$-7 \rightarrow \underline{1001}$$

$$\text{Add} \rightarrow 1100 \rightarrow -4$$

- ***Note:*** In two's complement notation, $+4 \rightarrow 0100$, while $-4 \rightarrow 1100 \Rightarrow$ ***Unique situation***

- ***Example:*** $2 - 7 = 2 + (-7) = -5$

$$\Rightarrow 0010 + 1001 = 1011, \text{ which is } -5$$

The Hexadecimal Number System:

- * Abbreviated as **HEX** (H): *base 16*, and *grouped in 4 bits each*
- * Extremely convenient and all computer systems use HEX number system
- * 0000 to 1001: 0_D to 9_D : 0_H to 9_H , 1010: 10_D : A_H ,
1011: 11_D : B_H , 1100: 12_D : C_H , 1101: 13_D : D_H ,
1110: 14_D : E_H , and 1111: 15_D : F_H (***D : Decimal***)
- * Thus, $(1010\ 1111)_B \leftrightarrow (AF)_H$ (***B : Binary***)

The Octal Number System:

- * *Base 8, and grouped in 3 bits each*
- * **Can count only from 0 to 7 (000 to 111)**
- * $542_8 = 5 \times 8^2 + 4 \times 8^1 + 2 \times 8^0 = 320 + 32 + 2 = 354_{10}$
- * 542_8 *grouped in 3 bits each:* 101 100 010₂
- * $101100010_2 = 2^8 + 2^6 + 2^5 + 2^1 = 256 + 64 + 32 + 2$
 $= 354_{10}$
- * 101100010_2 *grouped in 4 bits* would result in HEX
- * $0001\ 0110\ 0010_2 = 162_{16} = 1 \times 16^2 + 6 \times 16^1 + 2 \times 16^0$
 $= 256 + 96 + 2 = 354_{10}$ (**Note: Added 3 zeros to left**)
- * Neat, isn't it?

Boolean Algebra:



- * Developed by ***George Boole***
- * **Uses only two variables: *0 and 1*: Binary**
- * Mathematics associated with binary number system is ***Boolean Algebra***
- * **Positive Logic: 1 (*True - Hi*) and 0 (*False - Lo*)**
- * **Negative Logic: 1 (*False - Hi*) and 0 (*True - Lo*)**
- * **Logical Addition: *OR (+) Operation*:**
 - $0 + 0 = 0, 0 + 1 = 1, 1 + 0 = 1, 1 + 1 = 1$
- * **Logical Multiplication: *AND (·) Operation*:**
 - $0 \cdot 0 = 0, 0 \cdot 1 = 0, 1 \cdot 0 = 0, 1 \cdot 1 = 1$

* **Truth Table:** *Listing of all possible input combinations and corresponding outputs*

OR Gate:

* *Switches in parallel:*

  ⇒ If *either* one of them is *on*, the light will *glow*




* **Truth Table:**

A	B	F	
0	0	0	
0	1	1	$F = A + B$
1	0	1	
1	1	1	

AND Gate:

* *Switches in series:*

 ⇒ Light will *glow*
only if *both*
switches are *on*



* *Truth Table:*

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \cdot B$$

* **Note that the number of entries in the truth table is 2^N , where N = number of input variables**

NOT Gate:

* *Simply an inverter*


* *Truth Table:*

A	F
---	---

0	1
---	---

$$F = A' \text{ (or } \overline{A}\text{)}$$

1	0
---	---

 

Some Useful Rules:

$$0 + X = X, \quad 1 + X = 1, \quad X + X = X, \quad X + \overline{X} = 1,$$

$$0 \cdot X = 0, \quad 1 \cdot X = X, \quad X \cdot X = X, \quad X \cdot \overline{X} = 0, \quad \overline{\overline{X}} = X,$$

$$X + Y = Y + X, \quad X \cdot Y = Y \cdot X, \quad X + (Y \cdot Z)$$

$$= (X + Y) + Z, \quad X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$$

Some Useful Rules (Contd.):

$$\begin{aligned} X \cdot (Y + Z) &= X \cdot Y + X \cdot Z, & X + X \cdot Z &= X, & X \cdot (X + Y) &= X, \\ (X + Y) \cdot (X + Z) &= X + Y \cdot Z, & X + \overline{X} \cdot Y &= X + Y, \\ X \cdot Y + Y \cdot Z + \overline{X} \cdot Z &= X \cdot Y + \overline{X} \cdot Z \end{aligned}$$

De Morgan's Theorem:

*** Two extremely important theorems:**

$$\bullet \overline{X + Y} = \overline{X} \cdot \overline{Y} \quad \text{and} \quad \overline{X \cdot Y} = \overline{X} + \overline{Y}$$

*** *Thus, any logic function can be implemented by using either only OR and NOT gates, or only AND and NOT gates***

- * *AND and OR operations are DUAL of each other*
- * **Any function can be realized by just one of these basic two operations, along with the complement operation**
- * *Two families of logic functions:*
 - **Sum of Products (*SOP*)** $\rightarrow (X \cdot Y) + (W \cdot Z)$
 - **Product of Sums (*POS*)** $\rightarrow (A + B) \cdot (C + D)$
- * **Any logical expression can be reduced to one of these two forms, which are actually equivalent**

Logic Minimization by Simplification:

* Consider $f(A,B,C,D) = A'B'D + A'BD + BCD + ACD$

$$= A'D(B' + B) + BCD + ACD = A'D + BCD + ACD$$

$$= (A' + AC)D + BCD = (A' + C)D + BCD$$

$$= A'D + CD + BCD = A'D + CD(1 + B)$$

$$= A'D + CD \text{ (SOP)} = (A' + C)D \text{ (POS)}$$

* Note that in the final expression, B is not even there!

* *Applied prudently, logic minimization is immensely powerful, and saves a lot of hardware in implementing logic functions*

Realization of Logic Function from Truth Table:

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

* Need to form *SOP*

* **Pick rows for which $Y = 1$, and write A, B, and C in AND form, to produce $Y = 1$**

* For example, 2nd row would be:

$$Y = A'B'C$$

* Thus, $Y = A'B'C + A'BC + AB'C' + AB'C + ABC' + ABC$

* Now, start *minimizing*:

$$\begin{aligned} Y &= A'B'C + A'BC + AB'C' + AB'C + ABC' + ABC \\ &= A'C(B' + B) + AB'(C' + C) + AB(C' + C) \\ &= A'C + AB' + AB = A'C + A(B' + B) \\ &= A'C + A = A + C \end{aligned}$$

* Implementation is a simple **OR** gate with two inputs A and C (note that B doesn't even appear in the final expression)

* *Though both SOP and POS are valid representations, generally, SOP representation yields a lower gate count as compared to POS representation*

Example:

* $Y = A + BC$ (**SOP**) \Rightarrow

* Let's convert it to **POS**



representation:

$$\overline{Y} = \overline{A + BC} = \overline{A} \cdot \overline{BC}$$

$$= \overline{A} \cdot (\overline{B} + \overline{C})$$

$$\overline{\overline{Y}} = Y = \overline{\overline{A} \cdot (\overline{B} + \overline{C})}$$

\Rightarrow **POS Representation**

  

* **Note:** While SOP representation needed only **2 gates**,

POS representation needed **6 gates**


\Rightarrow **SOP representation preferred**

NAND and NOR Gates:

- * **Complements of AND and OR Gates**, respectively
- * Called ***Universal Gates***, since any logic function can be implemented using these two gates
- * ***Gate Array*** based designs have only ***NAND*** and ***NOR***
Gate Arrays – only ***interconnections*** need to be changed to implement any logic function
⇒ Extremely powerful and versatile
- * Special class of VLSI circuits known as **Field Programmable Gate Array (*FPGA*)**
⇒ The interconnections can be done ***in-situ***


* **NAND: *NOT AND***: Performs *logical addition* of the complements of the inputs
 
$$Y = \overline{AB} = \overline{A} + \overline{B}$$



* **NOR: *NOT OR***: Performs *logical multiplication* of the complements of the inputs
 
$$Y = \overline{A + B} = \overline{A} \cdot \overline{B}$$



Truth Tables of NAND and NOR Gates:


NAND: A B AND NAND

0	0	0	1
0	1	0	1
1	0	0	1


Odd one: 1 1 1 0

NOR: A B OR NOR

0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 

NOT Gate

 


NOT Gate

Exclusive-OR (XOR) and Exclusive-NOR (XNOR):


XOR: Basically OR gate, *with one exclusion*, i.e., when both inputs are 1, output is 0

Truth Table:	A	B	Y	$Y = A \oplus B = AB' + A'B$
	0	0	0	Either A high or B <i>high</i> ,
	0	1	1	<i>but not both</i> , would produce
	1	0	1	a <i>high</i> output
	1	1	0	Known as <i>odd parity detector</i>

 

XNOR: Basically **NOR** gate, *with one exclusion*, i.e.,
when both inputs are 1, output is 1

<i>Truth Table:</i>	A	B	Y	$Y = \overline{A \oplus B} = A'B' + AB$
	0	0	1	For output to be <i>high</i> ,
	0	1	0	<i>both</i> A and B should
	1	0	0	<i>either be high or low</i>
	1	1	1	Known as <i>even parity detector</i>

 

Karnaugh Map (K-Map) and Logic Design:

- * Named after its inventor *Maurice Karnaugh* (1953)
- * Extremely simple yet highly efficient
- * Used extensively for *logic minimization* to arrive at the **most optimal logic design**

		B	
		0	1
A	0		
	1		

2-Variable
Karnaugh Grid

		BC			
		00	01	11	10
A	0				
	1				

3-Variable
Karnaugh Grid

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

4-Variable
Karnaugh Grid

- * For N *variables*, total number of grid boxes = 2^N
- * Rows and columns are assigned such that the adjacent terms *change by only 1 bit*, e.g.,
00, 01, 11 (**note that it is not 10**), and 10
- * Each cell content is known as a **minterm**
 - *Example*: 3-variable minterms: $A'B'C'$, $A'B'C$, $A'BC'$, $A'BC$, $AB'C'$, $AB'C$, ABC' , and ABC
- * Grid boxes are filled by putting *either 0 or 1*, corresponding to the *input-output combination*

Example:

X	Y	Z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

		YZ			
		00	01	11	10
X	0	⁰ 0	¹ 1	³ 1	² 0
	1	⁴ 0	⁵ 1	⁷ 1	⁶ 0

X: MSB
Z: LSB

- * K-map is **foldable** (*left/right* and *up/down*) \Rightarrow what is put in the **first row/column** is immaterial
- * **Each cell is numbered** (left top corner), corresponding to the decimal equivalent of the **binary bits**

Steps of Minimization:

- * Define a **supercube** (some books say *subcube*) as a set of 2^m adjacent cells, all of which have *logical value 1*, for $m = 1, 2, 3, \dots, N$
- * Thus, a subcube can consist of **1, 2, 4, 8, 16, 32, ...**, number of individual cubes
- * Identify the *largest possible* such supercubes (**there may be more than one such supercube in a K-map**)
- * *How does it do the minimization?*
 - Since $(XY + X'Y)$ is always equal to Y
 \Rightarrow **X becomes immaterial (*redundant*)**

* For the example considered, first note that we have formed a *supercube* by combining adjacent 1s in the cubes

		YZ			
		00	01	11	10
X	0	⁰ 0	¹ 1	³ 1	² 0
	1	⁴ 0	⁵ 1	⁷ 1	⁶ 0

* Thus, $f = 1$ when either $X'Y'Z$ or $X'YZ$ or $XY'Z$ or XYZ is 1

$$\begin{aligned}
 \Rightarrow f &= X'Y'Z + X'YZ + XY'Z + XYZ \\
 &= (Y' + Y)X'Z + (Y' + Y)XZ \\
 &= X'Z + XZ = (X' + X)Z = Z
 \end{aligned}$$

* From the K-map, we see that $f = 1$ only when $Z = 1$, and X and Y both are either 0 or 1

$$\Rightarrow \mathbf{X \text{ and } Y \text{ are redundant and } f = Z}$$

Some More Examples:

		YZ			
		00	01	11	10
X	0	⁰ 1	¹ 1	³ 0	² 0
	1	⁴ 0	⁵ 0	⁷ 1	⁶ 1

$$f = X'Y' + XY$$

		YZ			
		00	01	11	10
X	0	⁰ 1	¹ 1	³ 1	² 0
	1	⁴ 0	⁵ 0	⁷ 1	⁶ 1

$$f = X'Y' + XY + YZ$$

YZ WX	00	01	11	10
00	⁰ 1	¹ 0	³ 0	² 0
01	⁴ 1	⁵ 1	⁷ 0	⁶ 1
11	¹² 0	¹³ 0	¹⁵ 1	¹⁴ 0
10	⁸ 0	⁹ 1	¹¹ 0	¹⁰ 1

W: MSB, Z: LSB

$$f = W'Y'Z' + W'XY' + W'XZ' + WXYZ + WX'Y'Z + WX'YZ'$$

Tips:

- * Make sure that all 1s are accounted for
- * Pay special attention to the corner 1s and foldability
- * No supercube should have odd number of cubes
(*except 1 – monocube*)
- * Supercubes can be intersecting

YZ WX	00	01	11	10
00	⁰ 1	¹ 0	³ 0	² 0
01	⁴ 1	⁵ 0	⁷ 1	⁶ 1
11	¹² 1	¹³ 0	¹⁵ 1	¹⁴ 1
10	⁸ 1	⁹ 0	¹¹ 0	¹⁰ 0

$$f = Y'Z' + XY$$

YZ WX	00	01	11	10
00	⁰ 1	¹ 1	³ 1	² 1
01	⁴ 0	⁵ 0	⁷ 0	⁶ 0
11	¹² 0	¹³ 0	¹⁵ 0	¹⁴ 0
10	⁸ 1	⁹ 1	¹¹ 1	¹⁰ 1

$$f = X'$$

More Complicated Example:

		CD			
		00	01	11	10
AB	00	⁰ 1	¹ 1	³ 0	² 1
	01	⁴ 0	⁵ 1	⁷ 0	⁶ 0
	11	¹² 0	¹³ 1	¹⁵ 1	¹⁴ 0
	10	⁸ 1	⁹ 1	¹¹ 1	¹⁰ 0

A: MSB, D: LSB

$$f = A'B'D' + C'D + AD + B'C'$$

- * ***K-map*** is an excellent tool for ***logic minimization***
- * Consider $f = XY + X'Z + YZ$
 - Can't be minimized any more using ***Boolean algebra***


	YZ				
X		00	01	11	10
0		⁰ 0	¹ 1	³ 1	² 0
1		⁴ 0	⁵ 0	⁷ 1	⁶ 1

$$f = X'Z + XY$$

(A simpler form)


- * Note that the YZ term is ***redundant*** (the dotted supercube), since all 1s have already been accounted for using the two other supercubes

* Consider another case:

 

* This minimization is ok, however, *inefficient*, since it can be further reduced

- Look for the *largest supercube*:

 

Product of Sums (POS) Realization & Minimization:

- * Resulting expression in the form $(A + B) \cdot (C + D)$
- * SOP and POS representations are completely *equivalent*, however, in general, *SOP representation is more efficient*

Algorithm for POS Representation:

- * Instead of 1, bunch *0*s in supercubes
- * Variables causing this *0* is written in **OR** form
- * After identifying all such terms, **AND** them
- * Thus, the output will be *0* only if all the results of the functions are *0*

Example:

X \ YZ	00	01	11	10
0	0 ⁰	1 ¹	1 ³	1 ²
1	1 ⁴	1 ⁵	0 ⁷	0 ⁶

** Term A will be zero if X or Y or Z or all are zero*

\Rightarrow It is equivalent to $(X + Y + Z)$

** Term B will be zero if $X = 1$ ($X' = 0$) and/or $Y = 1$ ($Y' = 0$), with Z immaterial*

\Rightarrow It is equivalent to $(X' + Y')$

** Thus, POS Representation:*

$$f = (X + Y + Z) \cdot (X' + Y')$$

Formal Definitions:

- * **Minterm:** Boolean expression resulting in output **1**
for a single cell or a group of cells
(arranged in 2^N supercube)
- * **Maxterm:** Boolean expression resulting in output **0**
for a single cell or a group of cells
(arranged in 2^N supercube)

Σ and π Notations:

- * Σ_m : **SOP** (m - *minterms*)
- * π_M : **POS** (M - *maxterms*)
- * Very compact means of describing ***Truth Tables***

Example: $f(A,B,C,D) = \Sigma_m (0,1,3,4,5,7,12,13,15)$

		CD			
AB \		00	01	11	10
00	0	1	1	1	0
01	4	1	1	1	0
11	12	1	1	1	0
10	8	0	0	0	0

$$f = A'C' + A'D + BC' + BD$$

Example: $f(A,B,C,D) = \pi_M(2, 6, 8, 9, 10, 11, 14)$

		CD			
		00	01	11	10
AB	00	⁰ 1	¹ 1	³ 1	² 0
	01	⁴ 1	⁵ 1	⁷ 1	⁶ 0
	11	¹² 1	¹³ 1	¹⁵ 1	¹⁴ 0
	10	⁸ 0	⁹ 0	¹¹ 0	¹⁰ 0

$$f = (A' + B) \bullet (C' + D)$$

- * Note: Both representations yielded the *same final result*, which obviously, is expected!
- * Care: In *POS* minimization, make sure that **all 0s are accounted for**

DON'T CARE (X) Condition:

- * In digital logic design, there may be *some states* which may *never occur* in real situations or may be *completely redundant*
 - ⇒ These states are referred to as **DON'T CARE (X)** states, and can be assigned *either 0 or 1*, as per our convenience ⇒ *tremendous flexibility*
- * In **SOP** representation, it would be prudent to assign *1* to these states
- * In **POS** representation, it would be prudent to assign *0* to these states

Example:

		BC			
		00	01	11	10
A	0	⁰ 0	¹ 0	³ 0	² 0
	1	⁴ 0	⁵ 1	⁷ X	⁶ X

Assigning $X = 1$ (SOP)
 $f = AC$

		BC			
		00	01	11	10
A	0	⁰ 0	¹ 0	³ 0	² 0
	1	⁴ 0	⁵ 1	⁷ X	⁶ X

Assigning $X = 0$ (POS)
 $f = A \bullet C$

Note: Both representations yielded the *same final result*, which obviously, is expected!

More Complicated Example (POS):

		CD			
AB		00	01	11	10
		00	01	11	10
00		⁰ 1	¹ 0	³ 1	² 0
01		⁴ 0	⁵ 0	⁷ 0	⁶ 1
11		¹² 0	¹³ X	¹⁵ X	¹⁴ X
10		⁸ 0	⁹ 1	¹¹ X	¹⁰ X

$$f = (A + C + D') \cdot (A + B' + C) \cdot (B + C' + D) \cdot (A' + D) \cdot (B' + D')$$

Exercise: Using this expression for f , show that for $A = B = C = D = 0$, $f = 1$.