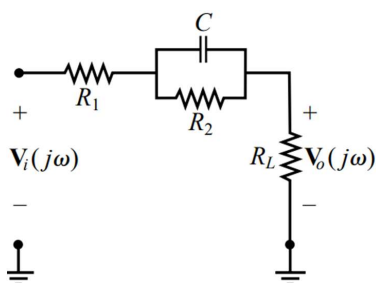


Q. 7 Determine the nature of filter for each one of the two circuits shown below. Give brief justification -----2 Marks




Filter-A

$$\begin{aligned} (\omega \rightarrow 0) \rightarrow V_o &\rightarrow \frac{R_L}{R_1 + R_2 + R_L} \\ (\omega \rightarrow \infty) \rightarrow V_o &\rightarrow \frac{R_L}{R_1 + R_L} \end{aligned} \quad \left. \begin{array}{l} 0.5 \\ 0.5 \end{array} \right\}$$

$V(\omega \rightarrow 0) < V(\omega \rightarrow \infty) \Rightarrow \text{High Pass Filter}$

Or All pass filter

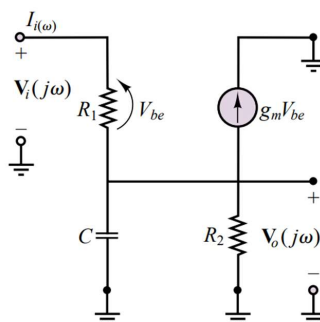

Filter-B

$$\begin{aligned} (\omega \rightarrow 0) \rightarrow V_o &\rightarrow \text{non zero} \\ (\omega \rightarrow \infty) \rightarrow V_o &\rightarrow 0 \end{aligned} \quad \left. \begin{array}{l} 0.5 \\ 0.5 \end{array} \right\}$$

$\Rightarrow \text{Low Pass Filter}$

### The most common mistakes and the related grading scheme

**Filter A:** A student shows that the circuit passes both low and high frequencies. ✓ 0.5

However concludes that the circuit is bandstop (or bandpass for some student) ✗ 0

**Note:** In order for a circuit to be band stop or band pass filter it has to stop some other band of frequencies. A circuit passes low and high frequencies does not imply that it stops some other frequency band.

**Filter B:** A student claims that the output voltage is negative at low frequency and zero at high frequency, hence the circuit must be a high pass filter. ✗ 0

**Note:** (1)  $V_o/V_i$  could be negative only under certain condition

(2) Most importantly, whether a filter is low pass or high pass depends on its **magnitude** response. Sign is irrelevant here.