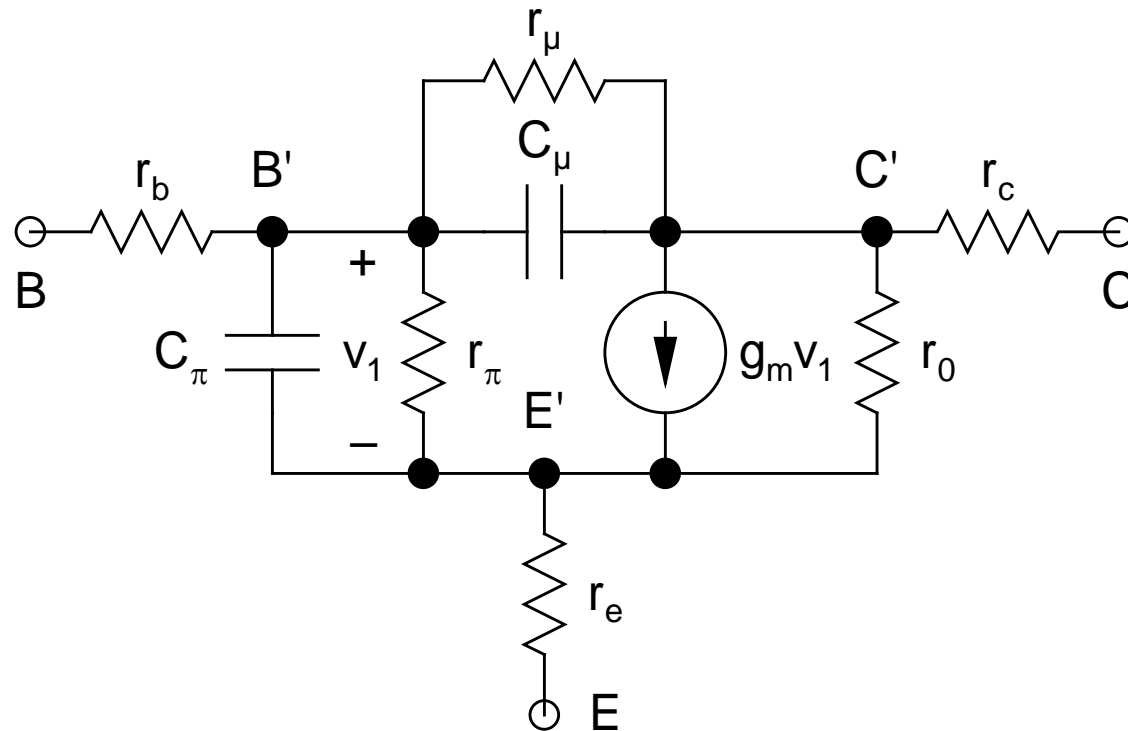



The Hybrid- π Model



E,B,C: Extrinsic Terminals
E',B',C': Intrinsic Terminals

- ***Simplifications:***

- r_e, r_b, r_c can be *safely neglected* under *low to moderate frequencies* of operation
- r_μ can be *neglected*, since it's *extremely large*
- At *low to moderate frequencies*, the *capacitive reactances* of C_π and C_μ will be *extremely large* \Rightarrow can be *neglected*
- Leads to the ***Low-Frequency T-Model***, having only *three components*: $r_\pi, g_m v_1$, and r_o
- *Simplest possible equivalent results if r_o is also neglected!*

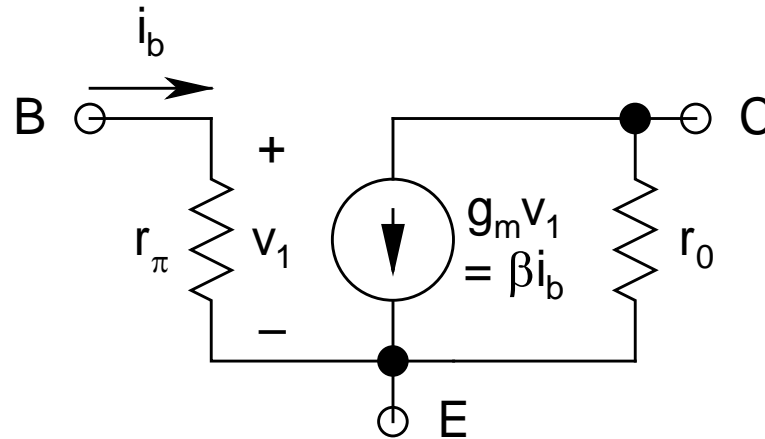

Low-Frequency T-Model

- **Note:** The *output circuit* resembles a **non-ideal current source** of *magnitude* $g_m v_1$ (or equivalently, βi_b) with *output resistance* r_o

- *This model is appropriate when the ac input is applied to base*
- *When the ac input is applied to the emitter, then need to draw this circuit in a slightly different way*

