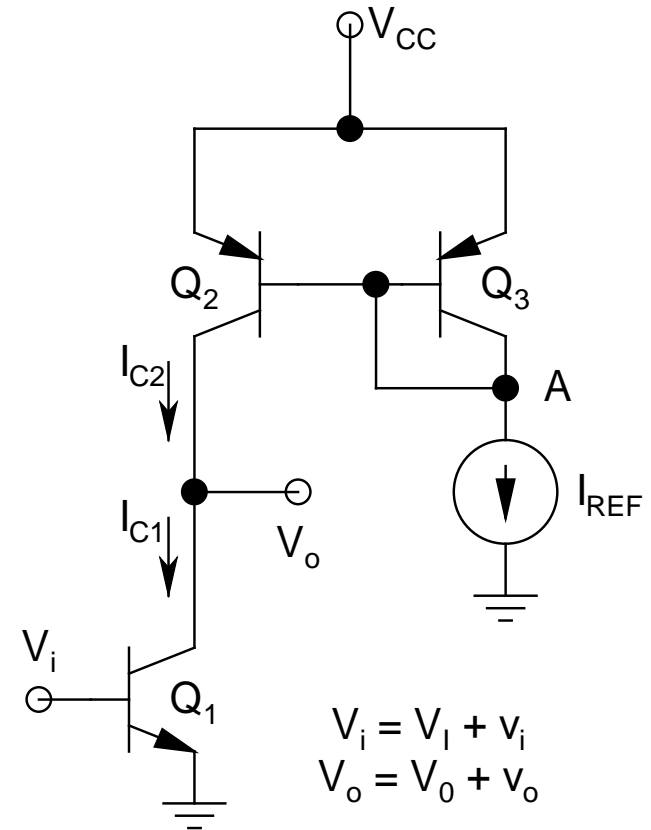


- *npn CE Stage With pnp Active Load:*

- $Q_1$ : *Driver*,  $Q_2$ : *Load*
- Identify  $Q_2$ - $Q_3$  as a  
*pnp current mirror*
- $Q_2$ - $Q_3$  constitute a  
*matched pair*
- *Neglecting base currents:*  
 $I_{C2} = I_{REF}$
- *Biasing of the circuit is tricky*




**Circuit Diagram**

- There is a *trivial solution* of  $I_{C1} = I_{C2} = 0$ , and the *circuit collapses*
- For *proper biasing*,  $I_{C1}$  must equal  $I_{C2}$  ( $= I_{REF}$ )
- Thus,  $V_I$  should be properly adjusted, such that:


$$V_I = V_T \ln(I_{REF}/I_{S1})$$

- *Such a high precision in  $V_I$  may not be practically achievable*
- ⇒ *Use a resistor in series with  $V_I$  and self-consistently solve for the bias point*

➤ *ac Analysis:*

 

ac Midband Equivalent

 

Simplified Equivalent

- First, note that  $Q_3$  is *diode-connected* (*BC short*)  
 $\Rightarrow$  The *equivalent* of  $Q_3$  is simply a *resistor*  $r_{E3}$
- *Node A* is a peculiar one, and can be considered *open or short both*!
  - ❖ *Open because the current source  $I_{REF}$  is ideal*
  - ❖ *Short because the base of  $Q_2$ - $Q_3$  is at a fixed DC potential, and thus ac ground*
- In either case,  $v_2 = 0 \Rightarrow g_{m2}v_2$  *disappears*!  
 $\Rightarrow$  Leads to the *simplified equivalent*
- *By inspection*:  $R_i = r_{\pi1}$  and  $R_o = r_{o1} || r_{o2}$
- $A_v = v_o/v_i = -g_{m1}R_o = -1/(\eta_n + \eta_p)$   
 $\eta_n = V_T/V_{AN}$  and  $\eta_p = V_T/V_{AP}$
- *Enormously large gain possible!*

# p-channel MOSFET (PMOS)

- Before moving to *NMOS stages with active load*, it will be prudent to visit some details regarding *PMOS*
- *Substrate: n-type* ( $N_D$ )
  - *Bulk Potential:*
$$\phi_F = V_T \ln(N_D/n_i)$$
- *Source/Drain: p<sup>+</sup>*
- *Channel Carriers: Holes*

