 


- **The Input Offset Current ( $I_{OS}$ ):**
  - ❖ **Difference** between the **base currents** (known as **Input Bias Currents**  $I_1$  and  $I_2$ ) of  $Q_1$  and  $Q_2$
  - ❖ **Extremely small** ( $\sim$  **tens to hundreds of nA**)
- $I_{OS}$  and  $V_{OS}$  are actually **interrelated**, since both of them are created due to **device mismatch**, and have almost **identical manifestations**



Both  $V_{OS}$  and  $I_{OS}$  are not used  
 $V_{OS}$  ( $I_{OS}$ ) is used when the  
 input is voltage (current)

**Modeling of the Anomalies  
 With Regard to  $V_{OS}$  and  $I_{OS}$**

## ➤ *Saturation Voltages:*

- An *ideal op-amp* should have *rail-to-rail swing* at the *output*
- The *actual output swing* of a *real op-amp* is *never between rail-to-rail*
- Refer to the *op-amp schematic*, in conjunction with the *schematics* of the *gain stage* and the *output stage*
- As  $V_{i2}$  of the *gain stage* becomes *positive*,  $V_{o2}$  ( $= V_{i3}$ ) goes *negative* with a *large gain*  
 $\Rightarrow V_2$  and  $V_0$  *follow*  $V_{i3}$  due to *emitter follower* (CC) action
- With  $V_0$  *negative*,  $Q_{14}$  *turns off*, and  $Q_{20}$  *draws current from the load*

- Assuming that  $Q_{17}$  can *soft saturate*, and neglecting the *voltage drop* across  $R_8$ , the *minimum possible value* of  $V_0$ :

$$V_0^- = -V_{CC} + V_{CE17}(SS) + V_{EB23A} + V_{EB20} = -13.4 \text{ V}$$

- Note that it is about *two diode drops above*  $-V_{CC}$
- Now, for *negative*  $V_{i2}$ ,  $V_{02}$  *swings* to a *large positive value, followed by*  $V_2$  and  $V_0$
- With  $V_0$  *positive*,  $Q_{20}$  *turns off*, and  $Q_{14}$  *supplies current to load*
- Maximum positive limit* of  $V_0$  is *reached* when  $Q_{13A}$  *soft saturates*:

$$V_0^+ = V_{CC} - V_{EC13A}(SS) - V_{BE14} = 14.1 \text{ V}$$

- Note again that it is *lower* than  $V_{CC}$  by *little more than one diode drop*
- Also, interesting to note is that the *positive* and *negative* peaks of  $V_0$  are *not same*  
 $\Rightarrow$  *Maximum possible output swing is asymmetric*
- These *two limits* of  $V_0$  are known as *positive and negative saturation voltages* ( $V_{SAT}^+$  and  $V_{SAT}^-$  respectively)
- If the *input drive* to the *op-amp* and the *gain* are such that the *magnitude* of  $V_0$  becomes *greater* than either  $V_{SAT}^+$  or  $|V_{SAT}^-|$ , then  $V_0$  would get *clipped* at either of these *two values*

➤ *Minimum Allowed Supply Voltage:*

- Circuit for 741 is *extremely robust*, and can be *operated* with a *very wide range* of *supply voltage*
- However, there is a *lower limit* of the *supply voltage*, below which it *can't be ensured* that *all transistors* operate in the *FA region*
- To find this, look for the *branch* containing the *most number of transistors*, since *that branch* would obviously *need the largest voltage* across it to *ensure* that all its *constituent transistors operate in the FA region*
- From the *circuit schematic* of 741, *this branch* can be very easily identified to be *either of the two sections of the input stage*

- Considering the *left branch*, neglecting the *potential dropped* across  $R_1$ , and not letting *CE voltage* of any of the *transistors* to *drop below* 0.7 V (*onset of saturation*), there would *four diode drops* ( $\sim 2.8$  V) *along this branch*
  - $\Rightarrow$  *741 should work satisfactorily for power supply all the way down to about  $\pm 3$  V*
  - $\Rightarrow$  *Under this power supply,  $V_o^+$  and  $V_o^-$  will be 2.1 V and  $-1.4$  V respectively*
- Thus, there is a *wide range* of *power supply*, *starting from  $\pm 3$  V*, for which *741 should work satisfactorily*
  - $\Rightarrow$  *Shows the robustness of the circuit*

➤ *Slew Rate and Full-Power Bandwidth:*

- This *limitation* is *observed* under *large-signal operation*, when the *input signal swing* is *greater* than the *linear range* of the *input differential pair*
- *Recall*: The *linear range* of a *bipolar differential pair* is  $\sim \pm 4V_T$
- *Beyond this*, it basically *acts like a switch*, *transferring the bias current between the two branches*, *depending on the sign of the input voltage*
- Under such cases, the *compensation capacitor*  $C_C$  *limits* the *maximum possible rate of change* of  $V_0$
- This is known as the *Slew Rate* (SR) of the op-amp:  
$$SR = (dV_0/dt)_{\max}$$

- **Two** SRs are defined:  $SR^+$  (*positive SR*) and  $SR^-$  (*negative SR*) for *positive* and *negative* excursions of  $V_0$  respectively, generally expressed in  $V/\mu sec$
- A *rough estimate* of these quantities can be obtained by referring to the *schematic* of the op-amp
- Assume that a *large negative signal* is applied at the *base* of  $Q_1$  (w.r.t. the base of  $Q_2$ )
- This will instantly turn the  $Q_1$ - $Q_3$  branch *off*  
 $\Rightarrow Q_5$ , and thus,  $Q_6$ , *turn off*  
 $\Rightarrow$  *Entire bias current*  $I_{C8}$  would *flow through* the  $Q_2$ - $Q_4$  branch, and *start to charge*  $C_C$



- Note that the *rate of this charging* would be *constant* (*constant current charging*)  
 $\Rightarrow$  *Collector potential* of  $Q_{17}$  would *increase linearly with time*
- Due to *emitter follower* action of  $Q_{23A}$  and  $Q_{14}$ ,  $V_0$  would also start to *increase linearly with time*
  - ❖  $Q_{20}$  *remains off*, since  $V_0$  is in its *positive excursion*
- Thus:  

$$SR^+ = I_{C8}/C_C = (19 \mu A)/12.5 \text{ pF} = 1.52 \text{ V}/\mu\text{sec}$$
- If the *frequency* of the *input signal* is such that the *required time rate of change* of  $V_0$  is *more* than this, then  $V_0$  *won't be able to follow* the input – rather, it will be *dictated* by the  $SR^+$ , and will *change linearly with time*