

Complete Circuit

ac Midband Schematic

 C_B : Base Blocking Capacitor , C_C : Collector Coupling Capacitor C_E : Emitter Bypass Capacitor , R_S : Source Resistance , R_L : Load Resistance

 V_0