
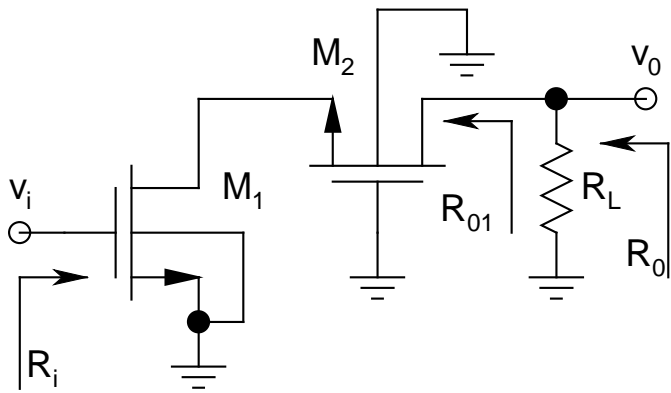


- ***NMOS Cascode:***

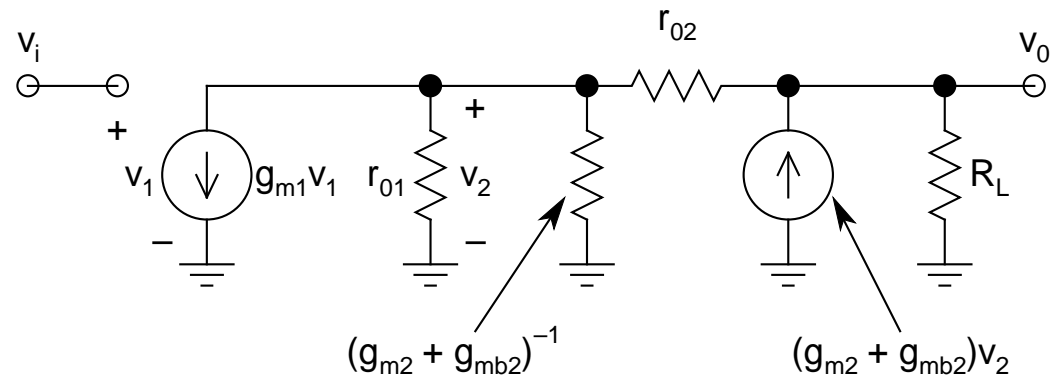

ac Schematic



ac Midband Equivalent

- ***CS***, followed by ***CG***
- ***Generally, both M_1 and M_2 are biased with the same I_D***
- ***M_1 does not have body effect, but M_2 has***

- *A_v gets affected a little if r_{01} and r_{02} were included*
- *Since r_{01} comes in parallel with $(g_{m2} + g_{mb2})^{-1}$, its effect on A_v is less pronounced than that of r_{02}*
- *By inspection:*

$$R_{01} \approx (g_{m2} + g_{mb2})r_{01}r_{02} \text{ (Show!)}$$
- *Note that if either of r_{01} or $r_{02} \rightarrow \infty$, $R_{01} \rightarrow \infty$ (Why?)*


- ***Differential Amplifier (DA)/Differential Pair (DP):***

- ***Most versatile analog building block***

- ***Immensely useful and widely used*** (particularly for ***sensing/telemetry/instrumentation*** applications)

- ***Two inputs*** (V_{i1} , V_{i2})/***Two outputs*** (V_{o1} , V_{o2})

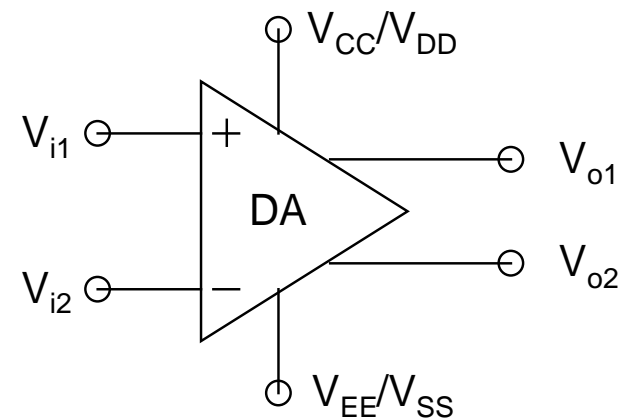- ***Dual Supply*** (V_{CC}/V_{DD} , V_{EE}/V_{SS})




Symbol for DA

- ***Unique Property:***
 - *Amplifies the difference between V_{i1} and V_{i2} , while rejecting/suppressing signals common to both V_{i1} and V_{i2}*
 - *Very efficient noise suppressor*
- ***The stage can be direct coupled to the next stage without the need for any coupling capacitor***
- In ***BJT technology***, known as ***Emitter-Coupled Pair (ECP)***
- In ***MOS technology***, known as ***Source-Coupled Pair (SCP)***

- ***npn DA (ECP):***

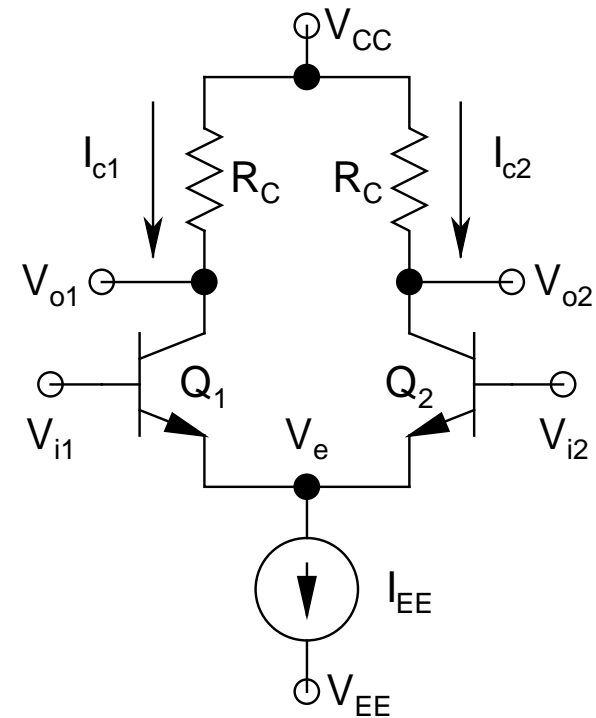- Q_1 - Q_2 constitute a ***matched pair***, and have their ***emitters connected together***, hence, the name
- I_{EE} : ***DC bias current source***
- ***All voltages and currents*** (*apart from those used for biasing*) are ***instantaneous*** (***DC + ac***)



npn DA Topology

➤ $V_{be1} = V_{i1} - V_e$, and $V_{be2} = V_{i2} - V_e$

➤ ***KVL around Q_1 - Q_2 BE loop:***

$$V_{i1} - V_{be1} + V_{be2} - V_{i2} = 0$$

$$\Rightarrow V_{be1} - V_{be2} = V_{i1} - V_{i2} = V_{id}$$

V_{id} : ***Differential-Mode Input Voltage***

➤ ***Neglecting Early effect:***

$$V_{id} = V_T \ln(I_{c1}/I_{c2})$$

$$\Rightarrow I_{c1}/I_{c2} = \exp(V_{id}/V_T) \quad (1)$$

➤ ***Neglecting base currents:***

$$I_{c1} + I_{c2} = I_{EE} \text{ (*always!*)} \quad (2)$$

This is because I_{EE} is an ideal current source

➤ *Solving Eqs.(1) and (2):*

$$I_{c1} = I_{EE}/[1 + \exp(-V_{id}/V_T)]$$

$$I_{c2} = I_{EE}/[1 + \exp(V_{id}/V_T)]$$

➤ *Extremely interesting results:*

- *For $V_{id} = 0$, $I_{c1} = I_{c2} = I_{EE}/2$*

I_{EE} shared equally between Q_1 and Q_2

- *For positive V_{id} , $I_{c1} \uparrow$ and $I_{c2} \downarrow$*

For negative V_{id} , $I_{c1} \downarrow$ and $I_{c2} \uparrow$

But for both cases, their sum is constant and equal to I_{EE}

- *For $V_{id} > 4V_T$, $I_{c1} \rightarrow I_{EE}$*

For negative V_{id} , with $|V_{id}| > 4V_T$, $I_{c2} \rightarrow I_{EE}$