

# Bipolar Junction Transistors (BJTs)

- Basically two *back-to-back diodes*
- Immensely important device
- Name originates from *Transfer of Resistor*
- *Three-Layer/Terminal* [*Emitter* (E), *Base* (B), *Collector* (C)] *Two-Junction* [*Base-Emitter* (BE), *Base-Collector* (BC)] device
- Current through two terminals (E and C) can be *controlled* by the current through the third terminal (B)

- *Active device*  $\Rightarrow$  capable of producing *voltage/current/power gain*
- *Two basic usage:*
  - Amplification (*Analog Circuits*)
  - Switching (*Digital Circuits*)
- *Two types: npn and pnp*
- We will be discussing only npn BJTs
- *Bipolar*: both *electrons* and *holes* contribute to *current transport* through the device
- *Current controlled device*


## Symbol and Current/Voltage Convention:

- \* For an *npn* transistor, the *collector and base currents* ( $I_C$  and  $I_B$  respectively) *flow in* and the *emitter current* ( $I_E$ ) *flows out* of the transistor

⇒ Applying KCL, treating the whole of the transistor as a *big node*:


$$I_E = I_C + I_B$$

 - \* E and C are *n-type*, while B is *p-type*
- \* Note the *notational convention* of the applied voltages ( $V_{BE}$  and  $V_{BC}$ ) – *p-side first*



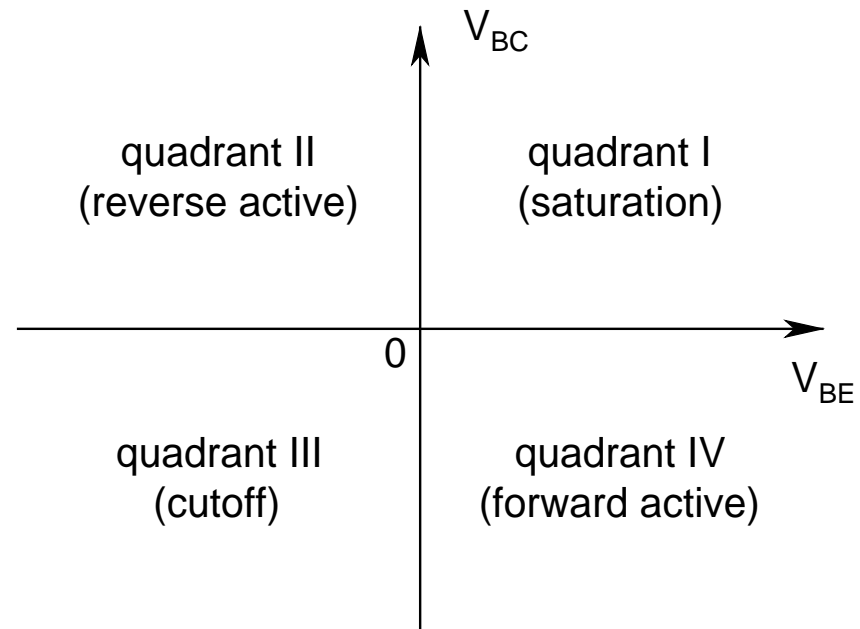
## *Modes of Operation:*

- \* *BE* and *BC* junctions can either be *forward* or *reverse* biased  $\Rightarrow$  *4 possible modes of operation*
  - **Forward Active:** *BE junction forward biased*  
*BC junction reverse biased*
  - **Reverse Active:** *BE junction reverse biased*  
*BC junction forward biased*
  - **Saturation:** *Both junctions forward biased*
  - **Cutoff:** *Both junctions reverse biased*



Quadrants III and IV: Analog Domain  
Quadrants I and II: Digital Domain  
Quadrant II: Finds use only in TTL circuits
 
## Operation in the Forward Active (FA) Mode:



- ① Injection Component
- ② Recombination Component
- ③ Collection Component

- \* **BE junction forward biased:** *electrons injected from E to B*, thus *emitter current ( $I_E$ ) flows out of the emitter terminal*
- \* In B, electrons *diffuse* towards the *BC junction* due to the presence of *diffusion gradient*  
*Note: electrons are minority carriers in p-base*
- \* In this process, some electrons will *recombine* with the *majority carriers (holes)* present in B
- \* The holes *lost* due to this *recombination process* will be *supplied* by the *external circuit*, thus, *base current ( $I_B$ ) flows into the base terminal*

- \* Electrons, which did not recombine, will reach the edge of the BC depletion region, and will get swept to C by the *junction electric field*
- \* Thus, *collector current ( $I_C$ ) flows into the C terminal*
- \* *A small change in  $I_B$  can cause a large change in  $I_C$  to  $I_E$  ratio*, due to a phenomenon known as **base control**
- \* For a *good* transistor,  $I_B$  *should be as small as possible  $\Rightarrow$  the base region should be as thin as possible*



## **Current Gain:**

- \* Note that the *sum of the collection component and the recombination component must always equal the injection component* (charge conservation)

$$\Rightarrow I_E = I_C + I_B$$

- \* **Common-Emitter Current Gain** ( $\beta$ ) =  $I_C / I_B$

- \* **Common-Base Current Gain** ( $\alpha$ ) =  $I_C / I_E$

- \* Thus,  $\beta = \alpha / (1 - \alpha)$  and  $\alpha = \beta / (\beta + 1)$

- \* For a *good* transistor,  $I_B$  *should be as small as possible*  $\Rightarrow \alpha \rightarrow 1$ , and  $\beta$  is quite large ( $\sim 100-500$ )

- \* *Closer is the value of  $\alpha$  to 1, better is the BJT!*

## **Current-Voltage Characteristic:**

\* Note that ***BE junction basically is a diode***

$$\Rightarrow I_E = I_{ES} \left[ \exp(V_{BE}/V_T) - 1 \right] \simeq I_{ES} \exp(V_{BE}/V_T)$$

***$\therefore$  BE junction is sufficiently forward biased***

***$\therefore$  The  $-1$  term can be neglected***


- $I_{ES}$ : Reverse saturation current of the BE junction
- $V_T$ : ***Thermal Voltage*** ( $= kT/q$ ) = ***26 mV at room temperature*** ( $T = 300 \text{ K}$ )

\* Thus,  $I_C = \alpha I_E = I_S \exp(V_{BE}/V_T)$

- $I_S = \alpha I_{ES}$  = ***saturation current of the BJT***
- $I_B = I_E - I_C$
 
## Output Characteristic:

- \* **Note:**  $V_C = V_{CE}$  (variable), also  $I_B$  is variable
- \* When BJT is in the *forward active* mode,  $V_{BE}$  is assumed to get clamped at  $0.7\text{ V}$  (about  $100\text{ mV}$  above  $V_\gamma$ )  $\Rightarrow$  **Thumb rule**
- \* Now,  $V_{CE} = V_{BE} - V_{BC}$
- \* Thus, for all values of  $V_{CE} > 0.7\text{ V}$ ,  $V_{BC}$  is *negative*, implying the *BC junction remains reverse biased*, and *forward active operation is maintained*



**\* For  $V_{CE} = 0.7 V, V_{BC} = 0$**

**$\Rightarrow$  BC junction is neither forward nor reverse biased – it is actually under zero bias**


**\* As soon as  $V_{CE}$  drops below  $0.7 V$ ,  $V_{BC}$  changes sign and becomes positive**

**$\Rightarrow$  BC junction is now forward biased, and forward active mode of operation is lost**

**$\Rightarrow$  BJT enters saturation mode of operation, with both junctions forward biased**

 **$\Rightarrow V_{CE} = 0.7 V$  is known as onset of saturation**

- \* *Once  $V_{CE}$  drops below 0.7 V, the BJT enters the saturation mode of operation*
- \* *With further reduction in  $V_{CE}$ , the BJT moves deeper into saturation*
  - ⇒ *This is the mode of operation of BJTs for digital circuits, however, BJTs used in analog circuits should never ever enter this mode of operation*
  - ⇒ *∴ A quick check is needed to ensure that  $V_{CE}$  is greater than 0.7 V in analog circuits*



npn BJT Output Characteristic

**Why  $V_{BE} = 0.7\text{ V}$ ?:**

**\* *Note:*  $I_E$  (and thus  $I_C$ ) varies exponentially with respect to  $V_{BE}$**

***$\Rightarrow$  A small change in  $V_{BE}$  can cause a very large change in  $I_C$***

**\* *As a rule of thumb,  $V_{BE}$  under the forward active mode is assumed to get pinned at  $0.7\text{ V}$***

***$\Rightarrow$  This is a heuristic used for quick estimate***

***$\Rightarrow$  The answer may not be accurate, however, good enough!***

### **Degree of Saturation (DoS):**

- \* In saturation, BC junction also becomes forward biased and collector starts injecting electrons to base*
- \* The base gets flooded with minority carriers (electrons), with a corresponding increase in recombination, and thus, the base current ( $I_{B,sat}$ )*
- \* Note that at the same time, the collector current ( $I_{C,sat}$ ) starts to drop due to this reverse injection process*
- \* The net effect is a drop in  $\beta \Rightarrow$  in the saturation region,  $\beta$  is denoted by  $\beta_{sat}$  ( $= I_{C,sat} / I_{B,sat}$ ), and has a value smaller than that in the FA region*



- \*  $DoS \triangleq \frac{\beta}{\beta_{sat}}$ , and *has a value  $\geq 1$*
- \* ***Note:*** At onset of saturation,  $DoS = 1$ , and as the BJT is driven deeper and deeper into saturation, the value of  $DoS$  keeps on increasing
- \* *The value of  $DoS$  is a tell-tale sign of judging how deeply the transistor is driven into saturation*
- \* ***Commonly used values:***  $V_{BE(FA)} = 0.7 \text{ V}$ ,  $V_{CE(FA)} > 0.7 \text{ V}$ ,  
 $V_{CE(OS)} = 0.7 \text{ V}$ ,  $V_{CE(HS)} = 0.1 \text{ V}$ ,  $V_{BE(HS)} = 0.8 \text{ V}$   
***OS : Onset of Saturation, HS : Hard Saturation***

## Load Line Analysis:


- \*  $I_B = \frac{V_B - V_{BE}}{R_B}$ , with  $V_{BE} = 0.7 \text{ V}$  (**FA mode**)

- \* Also,  $I_C = \beta I_B$  (**Note: Independent of  $R_C$** )

- \* Thus, for different values of  $V_B$ , we would get different values of  $I_B$ , and correspondingly different values of  $I_C$

$\Rightarrow$  A series of **output characteristics** (i.e.,  $I_C$  versus  $V_{CE}$ ) can be drawn

 - \* The **DC operating point** or the **Q-point** can lie **anywhere** on any of these curves



- \* Also, by varying  $V_B$  *smoothly*, almost a *continuous* variation of  $I_B$  can be obtained, which would yield almost *continuous* values of  $I_C$
- \* *Thus, the output characteristics, in effect, completely fill up quadrant I*
- \* Now, to fix a *unique bias point*, we need to draw the *load line*, and the *intersection point* of this load line with the particular characteristic for a given  $V_B$  and  $I_B$  would give us the information about the *Q-point*
- \* *Load line equation:* 
$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

\* ***2 boundary points:***

- $I_C = 0, V_{CE} = V_{CC}$
- $V_{CE} = 0, I_C = V_{CC} / R_C$

\* Joining these two points by a ***straight line*** gives the ***load line***

\* This line will ***intersect*** with the output characteristics at ***infinite*** number of points

\* **Each of these points is a possible operating point**


\* **The best choice for the operating point (or Q-point) is right at the center of the load line:**

$$\Rightarrow V_{CEQ(\text{best})} = V_{CC}/2 \text{ and } I_{CQ(\text{best})} = V_{CC}/(2R_C)$$

\* *Justification:*

- When this circuit is to be used as an *amplifier*, then an *ac small-signal*  $v_i$  will be *superimposed* on the *DC bias voltage*  $V_B$
- This would cause the *dynamic operating point* to *move along the load line in either direction*
- As it shifts towards the  $V_{CE}$  axis, Q moves towards cutoff (since  $I_C$  decreases), and as it moves towards the  $I_C$  axis, Q moves towards saturation (since  $V_{CE}$  decreases)

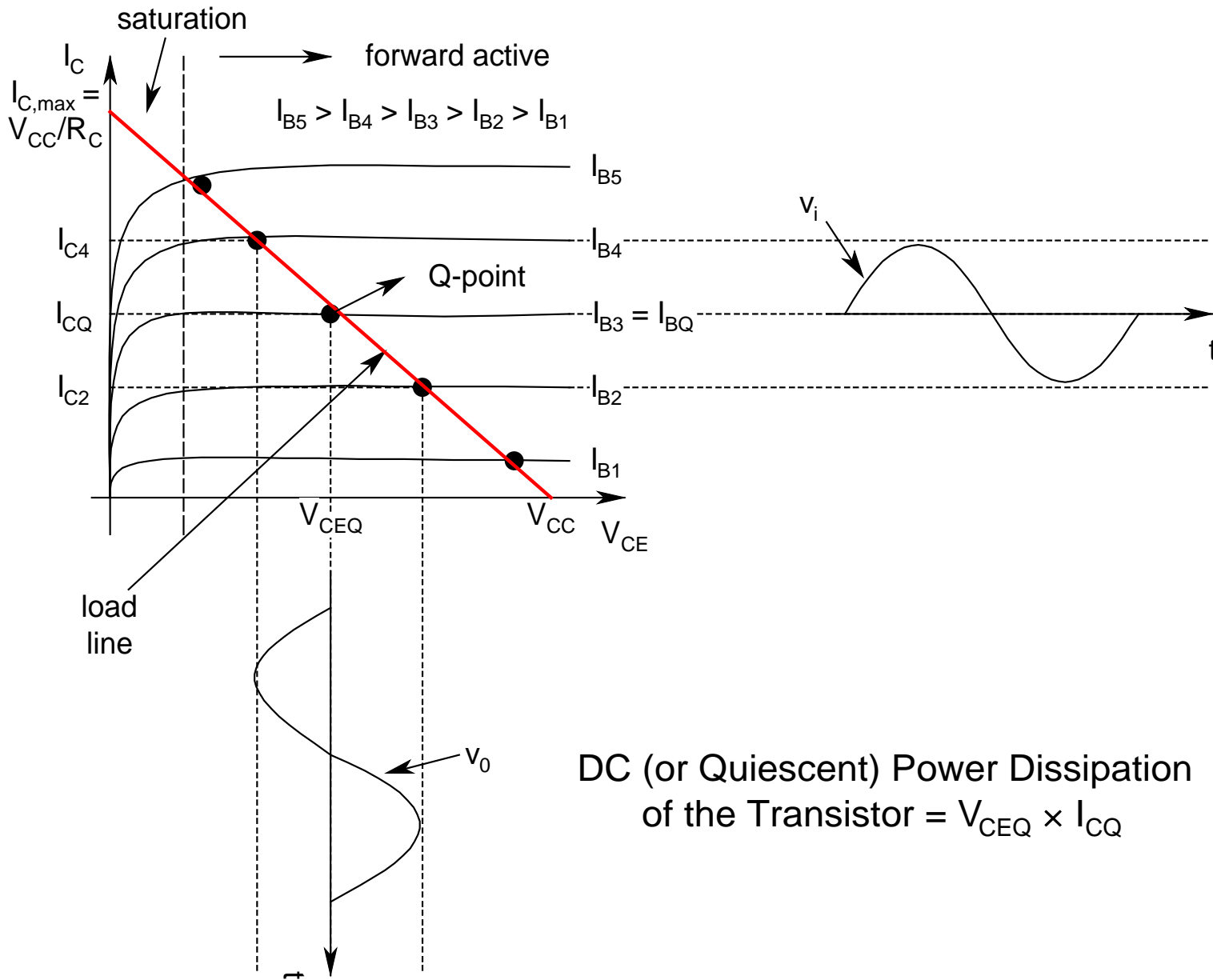- **If  $Q$  enters either cutoff or saturation region, then it would produce clipping (or distortion) in the output voltage  $v_o$**
- $\Rightarrow$  If the  $Q$ -point is located exactly at the center of the load line, then the maximum possible undistorted peak-to-peak swing of the output voltage  $v_o$  will be achieved***
- $\Rightarrow$  Golden Rule of Thumb for BJT biasing**



DC (or Quiescent) Power Dissipation  
of the Transistor =  $V_{CEQ} \times I_{CQ}$

## *What is the Role of $R_C$ ?:*

\* For fixed  $V_B$  (and thus,  $I_B$ ):

- As  $R_C$  decreases,  $I_{C,\max}$  will increase  
 $\Rightarrow Q$  moves towards *cutoff*  
 $\Rightarrow v_0$  will get *clipped* during *positive half cycle*
- As  $R_C$  increases,  $I_{C,\max}$  will decrease  
 $\Rightarrow Q$  moves towards *saturation*  
 $\Rightarrow v_0$  will get *clipped* during *negative half cycle*
- In either of these two cases, the range of the *maximum undistorted peak-to-peak output voltage swing* will be correspondingly reduced



### Observations:

- \* If  $R_C$  is *very high*, then the load line may not have any intersection point at all with the output characteristics under the FA region, and the Q-point will move to the *saturation region*  
 $\Rightarrow$  *Disastrous way to bias a transistor for analog circuit applications*
- \* A transistor biased in the *FA region* behaves like an *ideal current source* with *infinite output resistance*
- \* However, if a transistor is biased in the saturation region, it ceases to behave like a constant current source

- \* In the saturation region,  $I_C$  becomes a strong function of  $V_{CE}$ , showing *very small output resistance*
- \* Transistors used in analog circuit applications like *amplifiers*, should always be biased in the *FA region*, where  $I_C$  does not show any dependence on  $V_{CE}$   
 $\Rightarrow I_{CQ}$  *would not change with any variation of  $V_{CE}$*
- \* This is important to maintain *constant* values of all the *ac small-signal model parameters* (to be discussed)
- \* If  $I_{CQ}$  varied with  $V_{CE}$ , then the behavior of the circuit would become *erratic*

## AC Small-Signal Model:

- \* Representation of the transistor as a ***linear network***
- \* Actual model is quite tedious and complicated
- \* Here, we will present the ***simplest one***, known as the **low-frequency T-model**


- \* It consists of ***only 2 parameters***:

- $\beta$  (or  $\alpha$ ): ***Common-Emitter*** (or ***Common-Base***)

 ***Current Gain***

- $r_E$ : ***Incremental Emitter Resistance***

$$\triangleq dV_{BE}/dI_E = V_T/I_{EQ} \simeq V_T/I_{CQ} (\because \alpha \rightarrow 1)$$



\* **Note:**  $r_E$  is expressed in terms of  $I_{CQ}$  (or  $I_{EQ}$ )

$\Rightarrow$  ***The linearization is done around the DC bias point (Q-point)***

$\Rightarrow \therefore$  ***DC analysis must precede ac analysis***  
in order to obtain the ***bias point information***,  
and thus, ***the value of  $r_E$***

\* Also, note the  $v_{be} = i_e r_E$ , which can also be written

as:  $v_{be} = (\beta+1)i_b r_E \simeq \beta i_b r_E = i_b r_\pi$ , with  $r_\pi = \beta r_E$

$\Rightarrow r_\pi$  is another ***small-signal parameter***, defined  
as ***incremental base-emitter resistance***

$\Rightarrow$  ***Note that this resistance appears in the base lead***

## *Analysis of Amplifiers Using Transistors:*

\* The analysis proceeds as follows:

- First, *DC biasing analysis* is done, which yields the *DC bias point (Q-point)*  
 $\Rightarrow$  Gives  $I_{CQ}$  and  $V_{CEQ}$
- $I_{CQ}$  is needed to obtain the values of the *small-signal parameters*
- $V_{CEQ}$  is needed to ensure that the transistor is biased in the *FA region* ( $V_{CEQ} > 0.7 \text{ V}$ , and ideally  $V_{CC}/2$ , known as the **best bias point**)

- \* Then, the transistor is replaced by its *ac small-signal model*
- \* Subsequently, *usual network analysis* is done to obtain:
  - *Voltage Gain* ( $A_v$ )
  - *Current Gain* ( $A_i$ )
  - *Power Gain* ( $A_p = |A_v \times A_i|$ )
  - *Input Resistance* ( $R_i$ )
  - *Output Resistance* ( $R_o$ )

## ***Biasing:***

- \* Fixing the ***DC operating point*** (known as the ***Q-point*** or ***Quiescent Operating Point***)
- \* Defined by two parameters:  $I_{CQ}$  and  $V_{CEQ}$ , with the subscript Q denoting the ***Q-point values***
- \* If the transistor is to be used as an ***amplifier*** (**analog application**), then it must be biased in the ***FA region***
- \* On the other hand, if the transistor is to be used as a ***switch*** (**digital application**), then it must ***toggle between cutoff and saturation modes of operation***

### Example: Fixed Resistor Bias:

To start the DC bias analysis, assume that Q is in the FA region, with  $V_{BE} = 0.7 \text{ V}$ , and  $V_{CE} > 0.7 \text{ V}$


$$\Rightarrow I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{5 - 0.7}{100 \text{ k}} = 43 \text{ } \mu\text{A}$$

Now, to find  $I_{CQ}$ , we need the value of  $\beta$

Let 's assume  $\beta = 100 \Rightarrow I_{CQ} = \beta I_{BQ} = 4.3 \text{ mA}$

Note that to find  $I_{CQ}$ , we did not need the value of  $R_C$

 ***This is true only if Q is in the FA region, where  $I_C$  is independent of  $R_C \Rightarrow$  Extremely important observation***





Now,  $V_{CEQ} = V_{CC} - I_{CQ}R_C$

Thus,  $R_C$  *controls the value of  $V_{CE}$*

Recall that  $V_{CEQ(\text{best})} = V_{CC}/2 = 2.5 \text{ V}$

$\Rightarrow$  Best value of  $R_C = (2.5 \text{ V}) / (4.3 \text{ mA}) = 581.4 \Omega$

**Note:** For  $R_C < 581.4 \Omega$ ,  $V_{CEQ}$  would *increase* and Q would move towards *cutoff*

On the other hand, if  $R_C > 581.4 \Omega$ ,  $V_{CEQ}$  would *decrease* and Q would move towards *saturation*

The value of  $R_C$  to operate Q at *onset of saturation*  
 $= (5 - 0.7) / (4.3 \text{ mA}) = 1 \text{ k}\Omega$

If the value of  $R_C$  is more than  $1\text{ k}\Omega$ , then Q will be driven into *saturation*

As  $R_C$  increases, Q will go into *deep* (or *hard*) *saturation* with  $V_{CE(HS)} = 0.1\text{ V}$  and  $V_{BE(HS)} = 0.8\text{ V}$

The value of  $\beta$  will change to  $\beta_{sat}$ , with ***DoS***  $> 1$

***Example:*** Let's visit the scene for  $R_C = 10\text{ k}\Omega$

Obviously, Q will be under *hard saturation*

$$\Rightarrow I_{B,sat} = (V_{CC} - V_{BE(HS)}) / R_B = (5 - 0.8) / (100\text{ k}) = 42\text{ }\mu\text{A}$$

$$I_{C,sat} = (V_{CC} - V_{CE(HS)}) / R_C = (5 - 0.1) / (10\text{ k}) = 490\text{ }\mu\text{A}$$

$$\Rightarrow \beta_{sat} = I_{C,sat} / I_{B,sat} = 11.7 \text{ and } \mathbf{DoS} = \beta / \beta_{sat} = 8.6$$

### *How to Check the Mode of Operation?:*

- \* Let's consider the same circuit with  $R_C = 10\text{ k}\Omega$ , but now we assume that Q is in the FA region  
 $\Rightarrow I_B$  and  $I_C$  remain at  $43\text{ }\mu\text{A}$  and  $4.3\text{ mA}$  respectively
- \* But,  $V_{CEQ} = V_{CC} - I_{CQ}R_C = 5 - (4.3\text{ mA}) \times (10\text{ k}\Omega)$   
 $= -38\text{ V!}$
- \* Now, in a circuit with bias voltages ranging from ground (0 V) to  $V_{CC}$  (5 V), it is impossible to have a ***negative voltage*** at any node of the circuit
- \* Thus, the analysis is ***wrong***, and Q is ***NOT*** in the FA region, it's actually in ***hard saturation!***

## *Useful Information for Transistor Circuit Analysis:*

- \* All *pure* ac voltages (i.e., without any DC offset) are *DC short*, since their average value is zero
- \* All *pure* DC voltages are *ac short*, since they don't have any time variation
- \* *In DC analysis, open up all capacitors*
- \* *In ac analysis, short all capacitors*
- \* *In ac analysis, null all independent sources, but don't touch dependent sources*

## *Amplifier Topologies:*

### \* 4 basic topologies:

- CE (*Common-Emitter*)
- CB (*Common-Base*)
- CC (*Common-Collector*)
- CE(D) [*Common-Emitter (Degeneration)*]

### \* CE:

- *Input at B, output from C, E grounded*
- *$A_i$  large ( $= \beta$ ),  $|A_v|$  moderate to large,  $A_p$  huge*
- *$180^\circ$  phase shift between input and output*

**\* CB:**

- *Input at E, output from C, B grounded with or without a resistor*
- $A_i \leq 1$  ( $= \alpha$ ),  $|A_v|$  *moderate*,  $A_p$  *moderate*
- *Input and output in phase*

**\* CC:**


- *Input at B, output from E, C connected either to ground (for negative supply circuits) or to the positive power supply with or without a resistor*
- $A_i$  *large* ( $= \beta + 1$ ),  $|A_v| \leq 1$ ,  $A_p$  *moderate*
- *Input and output in phase*

\* **CE(D):**

- *Input at B, output from C, E grounded through a resistor*
  - *$A_i$  large ( $= \beta$ ),  $|A_v|$  small,  $A_p$  moderate*
  - *$180^\circ$  phase shift between input and output*
  - This topology has an advantage in that it provides for an *excellent frequency response*
- \* As an example, we will discuss a very important circuit block, known as *RC-Coupled Amplifier*, which provides both current as well as voltage gain, and thus, *large power gain*
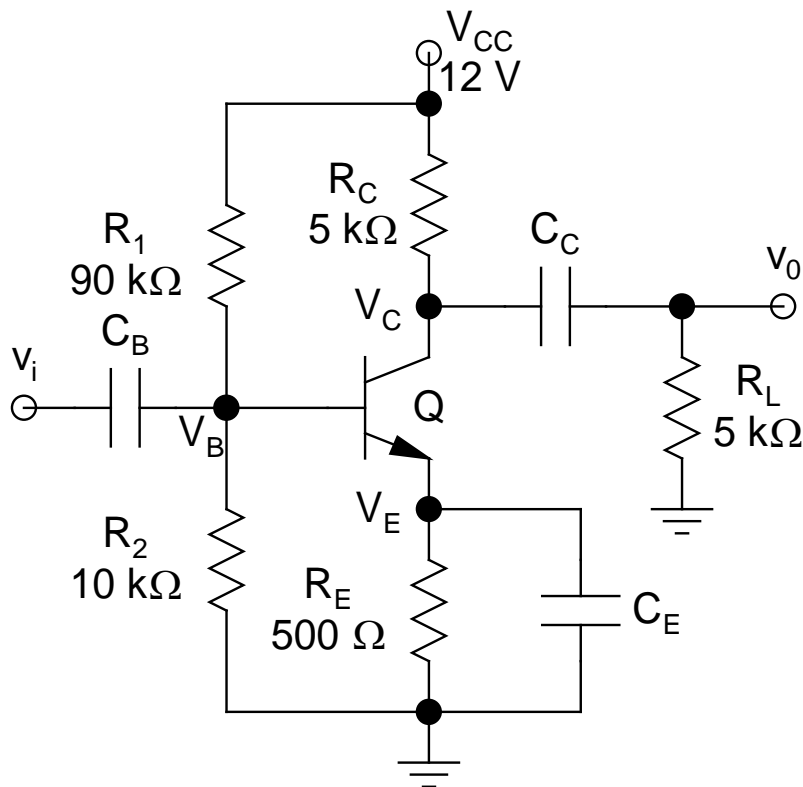
## *RC-Coupled Amplifier:*

- \* Extremely powerful analog circuit amplifier module
- \* Core circuit for *audio amplifiers*



$C_B$ : Base Blocking Capacitor  
 $C_E$ : Emitter Bypass Capacitor  
 $C_C$ : Collector Coupling Capacitor  
All are high-value capacitors ( $> \mu\text{F}$ )  
For DC Analysis: Treated as Open  
For ac Analysis: Treated as Short



## *Purpose of the Capacitors:*

### \* $C_B$ : *Base Blocking Capacitor*

- Isolates the ac signal source from the circuit core
- The DC level of the ac signal (i.e., the *offset*) cannot affect the DC bias point of the circuit

### \* $C_E$ : *Emitter Bypass Capacitor*

- Plays no role in DC analysis, since it opens up
- For ac analysis, it shorts out  $R_E$ , putting the emitter of Q to ac ground

### \* $C_C$ : *Collector Coupling Capacitor*

- Isolates the load resistance  $R_L$  from the circuit core such that it cannot alter the DC bias point

## DC Analysis:

\* *All capacitors open up*

\* Note that typical value of  $\beta$  is  $\geq 100$ ,  
thus,  $I_B$  is a miniscule fraction of  $I_C$

$$\Rightarrow I_E \simeq I_C$$


\* Also,  $I_2 = I_1 - I_{BQ}$

\*  $R_1$  and  $R_2$  are chosen in such a way  
that  $I_1 \gg I_{BQ} \Rightarrow I_2 \simeq I_1$

\* Thus,  $V_B = R_2 V_{CC} / (R_1 + R_2) = 1.2 \text{ V}$

$$\Rightarrow V_E = V_B - V_{BE} = 0.5 \text{ V and } I_{EQ} \simeq I_{CQ} = V_E / R_E = 1 \text{ mA}$$
 
$$\text{and } V_{CEQ} = V_{CC} - I_{CQ} (R_C + R_E) = 6.5 \text{ V (close to } V_{CC}/2)$$




### ac Analysis:

\* *All capacitors shorted*

$\Rightarrow R_E$  gets bypassed

 \*  *$V_{CC}$  nulled*  $\Rightarrow R_1$  comes in parallel to  $R_2$  ( $R'$ ), and  $R_C$  comes in parallel with  $R_L$  ( $R''$ )



\* *Replace  $Q$  by its low-frequency  $T$ -model*

• *Note:*  $i_o = i_c \approx i_e$ ,  $\because$  base current neglected

\* Voltage gain:  $A_v = \frac{v_o}{v_i} = \frac{-i_o R''}{i_e r_E} = -\frac{2.5 \text{ k}\Omega}{26 \Omega} = -96.2$

• *Note:*  $r_E = V_T / I_{CQ} = (26 \text{ mV}) / (1 \text{ mA}) = 26 \Omega$

- \* The *negative* sign for  $A_v$  implies that  $v_o$  is *exactly out-of-phase* with  $v_i$  (i.e., they are *180° apart*)
- \* Note that the input  $v_i$  appears at the *base*, while the output  $v_o$  is taken from *collector*, with emitter grounded  
 $\Rightarrow$  *Common-Emitter (CE) Amplifier*
- \* For a *CE amplifier*, there is a *phase shift of 180°* between the input and output
- \* To *increase*  $A_v$ , either *decrease*  $r_E$ , *increase*  $R''$ , or *both*
- \*  $r_E$  *can be decreased by increasing*  $I_C$  (by a change in bias)
- \*  $R''$  *can be increased by making*  $R_L \gg R_C$  (max.  $R'' = R_C$ )
- \* **Note: Power gain** =  $|A_v \times A_i| > 9620$  (for  $\beta > 100$ )

### What Happens if $C_E$ is not there?:

- \* **DC bias point unchanged**

- \* **Due to the absence of  $C_E$ ,  $R_E$  unbypassed**


- \* Input is still at **base**, and output is still from the **collector**, but

now **emitter is grounded through a resistor**

 **$\Rightarrow$  Common-Emitter (Degeneration) [CE(D)]**


- \* Voltage gain:  $A_v = \frac{V_o}{V_i} = \frac{-i_o R''}{i_e (r_E + R_E)} = -\frac{2.5 \text{ k}\Omega}{526 \Omega} = -4.75$

- \* **Note the drastic reduction in  $A_v$  (gain degeneration!)**



 
## Simple BJT Inverter:

- \* Basic digital building block
- \* Known as *Inverter* (or *NOT Gate*)
- \* Digital circuits have *two levels*:
  - *High* (or *Hi*) – close or equal to  $V_{CC}$
  - *Low* (or *Lo*) – close or equal to 0



 - \* *Operation:*
    - $V_i = 0$  (*Lo*), Q is *off*,  $V_o = V_{CC}$  (*Hi*)
    - $V_i = V_{CC}$  (*Hi*), Q is driven to *hard saturation*,  
 $V_o = V_{CE(HS)} = 0.1 \text{ V}$  (*Lo*)
- $\Rightarrow$  *Inverter*



Voltage Transfer Characteristic (VTC)

$V_{OH}$ : Output Hi

$V_{OL}$ : Output Lo

$V_{IL}$ : Input Lo

$V_{IH}$ : Input Hi

$NM_H$ : Noise Margin (High) =  $V_{OH} - V_{IH}$

$NM_L$ : Noise Margin (Low) =  $V_{IL} - V_{OL}$

$TW$ : Transistion Width =  $V_{IH} - V_{IL}$

$LS$ : Logic Swing =  $V_{OH} - V_{OL}$

### **Design Example:**

Choose  $V_{CC} = 5 \text{ V}$ ,  $R_C = 2 \text{ k}\Omega$ , and  $R_B = 20 \text{ k}\Omega$

$V_i = 0 \text{ V}$ , *Q off*  $\Rightarrow V_{OH} = V_{CC} = 5 \text{ V}$

$V_i = 5 \text{ V}$ , *Q in hard saturation*  $\Rightarrow V_{OL} = V_{CE(HS)} = 0.1 \text{ V}$

$V_{IL}$ : **Maximum value of the input that would still ensure that  $V_o$  remains at  $V_{OH}$**

Taken to be equal to  $V_{BE} = V_\gamma = 0.6 \text{ V}$

Note that Q just starts to conduct at this point

$V_{IH}$ : **Minimum value of the input that would still ensure that  $V_o$  remains at  $V_{OL}$**

Actual computation is quite tedious



### Analysis of $V_{IH}$ :

*It is assumed that when  $V_i = V_{IH}$ ,  $Q$  is at the onset of saturation with  $V_{BE} = 0.7\text{ V}$ , but with  $V_{CE} = 0.1\text{ V}$*

This is a **clear contradiction**, however, it gives a sufficiently close estimate of  $V_{IH}$

$$\Rightarrow I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{5 - 0.1}{2\text{ k}} = 2.45\text{ mA}$$

BJTs used in inverters typically have  $\beta \sim 50-100$

Also,  $\beta$  is assumed to have its *nominal value* (i.e., *the value in the FA region*) at this point

$$\text{Choosing } \beta = 80 \Rightarrow I_B = I_C / \beta = 30.6\text{ }\mu\text{A}$$

$$\Rightarrow V_{IH} = V_{BE} + I_B R_B = 0.7 + (30.6 \mu A) \times (20 \text{ k}\Omega) \\ = 1.3 \text{ V}$$

$$\text{Thus, } \mathbf{LS} = V_{OH} - V_{OL} = \mathbf{4.9 \text{ V}}$$

$$\mathbf{TW} = V_{IH} - V_{IL} = \mathbf{0.7 \text{ V}}$$

$$\mathbf{NM_H} = V_{OH} - V_{IH} = \mathbf{3.7 \text{ V}}$$

$$\mathbf{NM_L} = V_{IL} - V_{OL} = \mathbf{0.5 \text{ V}}$$


$$\mathbf{Transition \text{ Region Gain}} \triangleq \frac{dV_o}{dV_i} = \frac{V_{OH} - V_{OL}}{V_{IL} - V_{IH}} \\ = -\frac{LS}{TW} = \mathbf{-7}$$

- \* **Note:** Higher the magnitude of the gain, sharper is the response
- \* The inverter is the heart of digital circuits, and can be configured in various topologies to produce a variety of digital gates, e.g., **AND**, **OR**, **NAND**, **NOR**, etc.
- \* One of the simplest digital blocks to design, and works very well  $\Rightarrow$  pretty robust circuit
- \* **Note:** Q acts as a **switch**  $\Rightarrow$  either *cutoff* (with output in the **Hi** state) or in *hard saturation* (with output in the **Lo** state)  $\Rightarrow$  that's why it's a **Gate**!
 
## Simple BJT Series Voltage Regulator:

- \* Extremely simple and powerful circuit
- \* Operates under the principle of *negative feedback*
- \*  $V_0 = V_Z - V_{BE} = I_E R_L$
- \* **Recall:**  $I_E$  depends on  $V_{BE}$  exponentially

$\Rightarrow$  Large change in  $I_E$  can be accommodated by a very small change in  $V_{BE}$ , which can be assumed to be clamped at  $\sim 0.7$  V



- \* If for any reason,  $V_0$  tends to *increase*, then  $V_{BE}$  *drops*, which *reduces*  $I_E$ , and thus,  $V_0$  *reduces*
- \* Similarly, if for any reason,  $V_0$  tends to *decrease*, then  $V_{BE}$  *increases*, which *increases*  $I_E$ , and thus,  $V_0$  *increases*
- \* *Note that the cause and effect are opposite*  
 $\Rightarrow$  **Negative Feedback**
- \* Extremely robust circuit, with the output having almost *no ripple*
- \* *Note that  $Q$  should never saturate*  $\Rightarrow V_{CE,\min} = 0.7 \text{ V}$

## ***Design Issues & Constraints:***

\*  $\because V_Z$  has a constant value, let's say 5 V

$\therefore V_0$  will have a fixed and constant value of 4.3 V

***Note:*** This is independent of the value of  $R_L$

\* ***Minimum value of  $V_i$  should be  $\geq V_0 + V_{CE(min)}$***

\* Q is known as ***series pass transistor***, since it passes  $V_i$  to output with a drop of  $V_{CE}$

\* ***Current Relations:***  $I_1 = I_C + I_2$ ,  $I_2 = I_Z + I_B$ ,  $I_C = \beta I_B$ ,  
and  $I_E = (\beta + 1) I_B$

\* ***The role of  $R$  is very critical: it should be chosen extremely carefully***

- \* The output should never be *short-circuited*, i.e.,  $R_L$  should never be made *zero*, since in that case, *huge current* will flow at the output, which will completely *destroy* the regulator due to *over-heating*  
 $\Rightarrow$  Actual regulators have *short-circuit protection*
- \* If the minimum allowed value of  $R_L$  is  $R_{L,min}$ , which leads to the maximum value of  $I_E$  ( $I_{E,max} = V_0 / R_{L,min}$ ) and  $V_i$  is at its minimum value  $V_{i,min}$ , then the current supplied by  $V_i$  should not only supply  $I_{B,max}$   $\left[ = I_{E,max} / (\beta + 1) \right]$ , but also the minimum required Zener current  $I_{Z,min}$  to sustain breakdown

$$\Rightarrow \text{This gives } R_{max} = \frac{V_{i,min} - V_Z}{I_{B,max} + I_{Z,min}}$$

\* With load removed, i.e.,  $R_L$  open-circuited,

$$I_E = I_C = I_B = 0$$

\* Under this situation, with  $V_i$  at its maximum value  $V_{i,max}$ , the Zener current should not exceed its maximum limit of  $I_{Z,max}$

$$\Rightarrow \text{This gives } R_{min} = \frac{V_{i,max} - V_Z}{I_{Z,max}}$$

\* **Exercise:** Verify that any value of  $R$  falling outside this range will be detrimental for the circuit