

■ C_{gd1} :

$$R_{gd1}^0 = R_S + R_{L1} + g_{m1} R_S R_{L1} = 320 \text{ k}\Omega$$

$$\Rightarrow \tau_2 = R_{gd1}^0 C_{gd1} = 320 \text{ ns}$$

■ C_{db1} and C_{gs2} in parallel

$$\Rightarrow \text{Club them to a single capacitor } C_3 = C_{db1} + C_{gs2} \\ = 12 \text{ pF}$$

$$R_3^0 = R_{L1} = 10 \text{ k}\Omega$$

$$\Rightarrow \tau_3 = R_3^0 C_3 = 120 \text{ ns}$$

- C_{gd2} :

$$R_{gd2}^0 = R_{L1} + R_{L2} + g_{m2} R_{L1} R_{L2} = 315 \text{ k}\Omega$$

$$\Rightarrow \tau_4 = R_{gd2}^0 C_{gd2} = 315 \text{ ns}$$

- C_{db2} :

$$R_{db2}^0 = R_{L2} = 5 \text{ k}\Omega$$

$$\Rightarrow \tau_5 = R_{db2}^0 C_{db2} = 10 \text{ ns}$$

- Thus:

$$\tau_{\text{net}} = 815 \text{ ns and } f_H = 195.3 \text{ kHz}$$

- Such a *low value* of f_H is the *result* of the *presence* of a *large number of capacitors* in the circuit

- *Limitations of the ZVTC Technique:*
 - *One obvious limitation is the suppression of information of all other poles and zeros of the system except the DP*
 - *This limitation is not that acute since we are actually interested in only the DP, which gives the information about f_H*
 - *The other limitation is the error, which can reach as high as 22%*
 - However, *this error is negative*, i.e., *underestimation* (far better than *overestimation*)

- The *maximum error* of 22% occurs if the *actual circuit* has *two overlapping poles*
- In *real situations*, this is *highly unlikely*, due to the effect of *pole splitting* caused by *compensation* (*to be discussed in the next chapter*)
- *The resulting circuit after compensation would have a single DP*

➤ *Proof that the maximum error is 22%*

- Consider a circuit having *2 negative real poles* at the *same angular frequency* ω_x

- The *Transfer Function*:

$$A(j\omega) = A_0/(1 + j\omega/\omega_x)^2$$

A_0 : *Midband gain*

$$\Rightarrow |A(j\omega)| = A_0/[1 + (\omega/\omega_x)^2]$$

- At the *upper cutoff frequency* ω_H , the *gain would drop to $1/\sqrt{2}$ of its maximum value*

$$\Rightarrow 1 + (\omega_H/\omega_x)^2 = \sqrt{2}$$

$$\Rightarrow \omega_H = [\sqrt{(\sqrt{2} - 1)}]\omega_x = 0.64\omega_x$$

- Now, using the *ZVTC technique*, the *net time constant*

$$\tau_{\text{net}} = \sum_{i=1}^n (-1/p_i)$$

i = *number of poles*

p_i = *individual poles*

- For the *given problem*, $i = 2$ and $p_i = -\omega_x$ (*for both*)

- Thus:

$$\tau_{\text{net}} = 2/\omega_x \text{ and } \omega_H = 1/\tau_{\text{net}} = 0.5\omega_x$$

- Therefore, the *maximum error is about -22%*
- This being an *underestimation*, is *not that dangerous* :)

- ***Rise/Fall Time:***

- ***Recall:*** f_L caused tilt/sag in the output for square-wave input
- ***On the other side of the frequency spectrum,*** f_H causes rise/fall time of the output for square-wave input
- ***These two phenomena can be thought of as an interlinking between the analog and digital domains***
- Assume that a circuit has some ω_H , with the ***corresponding pole*** at $p_1 (= -\omega_H)$

- The **Transfer Function** is **single-pole**:

$$v_0(s)/v_i(s) = A_0/(1 - s/p_1)$$

A_0 : **Midband gain**

- Now, consider v_i to be **step input** of **amplitude**

$$V_A \quad (\Rightarrow v_i = V_A/s)$$

$$\begin{aligned}\Rightarrow v_0(s) &= (A_0 V_A/s)/(1 - s/p_1) \\ &= A_0 V_A [1/s - 1/(s - p_1)]\end{aligned}$$

- Taking **inverse Laplace Transform**:

$$v_0(t) = A_0 V_A [1 - \exp(p_1 t)]$$

\Rightarrow **Output approaches its maximum value of $A_0 V_A$ with a time constant $1/|p_1|$ (p_1 negative)**

➤ ***Calculation of Rise/Fall Time:***

- *Time taken for the output to rise (fall) from 10% (90%) to 90% (10%)*
- *Can be calculated from the figure*

