
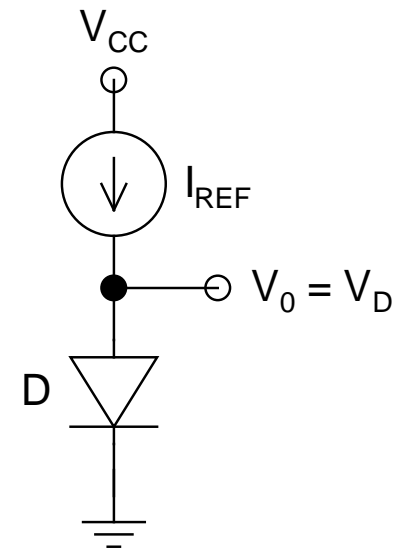


- ***Single Diode Reference:***

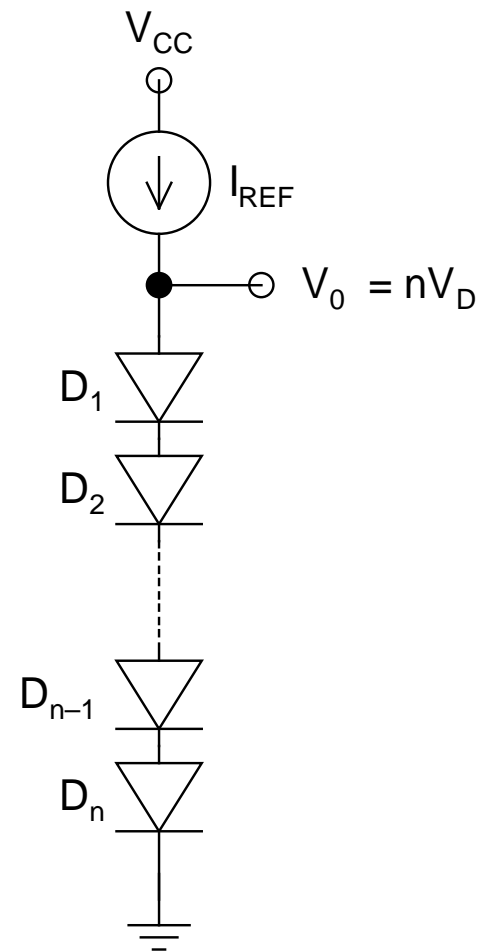- I_{REF} : ***DC Bias Current***
- ***Creates a voltage drop of V_D (or V_{BE}) across the diode of $\sim 0.7\text{ V}$***
- ***Known as V_{BE} (or V_D) Reference***
- ***Precision quite poor***
- ***Thermal tracking poor***




- **Multiple Diode Reference:**
 - **Putting multiple diodes in series**
 - **DC bias current I_{REF} pushed through them**
 - **Each diode creates a drop of V_D across it**
 - **Has same problems as Single Diode Reference**
 - **Note: n can only be an integer**



- **V_{BE} (or V_D) Multiplier Circuit:**

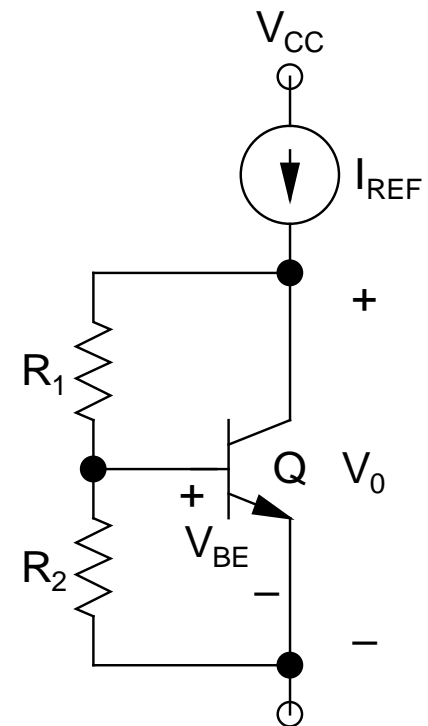- *Previous two circuits provide $V_0 = nV_D$, with n being an integer ≥ 1*
- *For any arbitrary value of n (≥ 1), this circuit becomes useful*
- *Immensely popular because of its simplicity and effectiveness*
- *Biased by a DC current source I_{REF}*



➤ *Neglecting base current:*

$$V_{BE} = \frac{R_2}{R_1 + R_2} V_0$$

$$\Rightarrow V_0 = \left(1 + \frac{R_1}{R_2}\right) V_{BE}$$

$\Rightarrow V_{BE}$ *Multiplier* with *multiplication factor* $(1 + R_1/R_2)$

➤ *Any arbitrary ratio of R_1 and R_2 can be used, but the multiplication factor is always ≥ 1*

- *Least possible $V_0 = V_{BE}$ [$R_1 = 0$ (short-circuit) and $R_2 \rightarrow \infty$ (open-circuit)]*
 \Rightarrow *Diode-Connected BJT*
- *Has excellent thermal tracking, since TC_F of R_1 and R_2 cancel each other, but the TC_F of V_{BE} remains*
- *So far, we have got voltage references having $V_0 \geq V_{BE}$*
- *How to have a voltage reference having $V_0 < V_{BE}$?*

- ***Saturated Transistor:***

- ***Neglecting base current:***

$$V_0 = V_{BE} - I_{REF}R$$

- ***Note: V_0 is actually V_{CE} ,***

which is $< V_{BE}$

$\Rightarrow Q$ saturated

***\Rightarrow Analysis highly approximate,
since base current can't be
neglected in saturation***

- ***Typical range of $V_0 \sim 0.2-0.7 V$***

