

THE OPERATIONAL AMPLIFIER (OP-AMP)

- ***The Ultimate***: A *phenomenal application* of everything that we have learnt so far in this course
- *Op-Amp*: *Operational Amplifier*
- *Hugely powerful block*
- *Capable of performing various circuit functions*
- *Original inventor*: *George Philbrick* of *Bell Labs* in *1952* using *vacuum tube technology*

- *Remarkable innovations* in *design* in the form of an *IC* by *Bob Widlar* of *Fairchild Semiconductors* in *1963*
- After that, *several improvements* took place, and the *most versatile design*, widely came to be known as the *741 op-amp*, originated
- Basically a *three-stage architecture*:
 - *The Input Stage*
 - *The Gain Stage*
 - *The Output Stage*


- *The Input Stage:*
 - *Should be capable of double-ended to single-ended conversion*
 - *Should have moderate to high gain*
 - *Must definitely have extremely large CMRR (this is the main requirement)*
 - *Almost invariably a Differential Amplifier (DA)*

- *The Gain Stage:*


- *Can be any one of the many that we have studied in the chapter on Amplifiers*
- *CC-CE Darlington configuration preferred*
- *Should have moderate to large gain*

- *The Output Stage:*

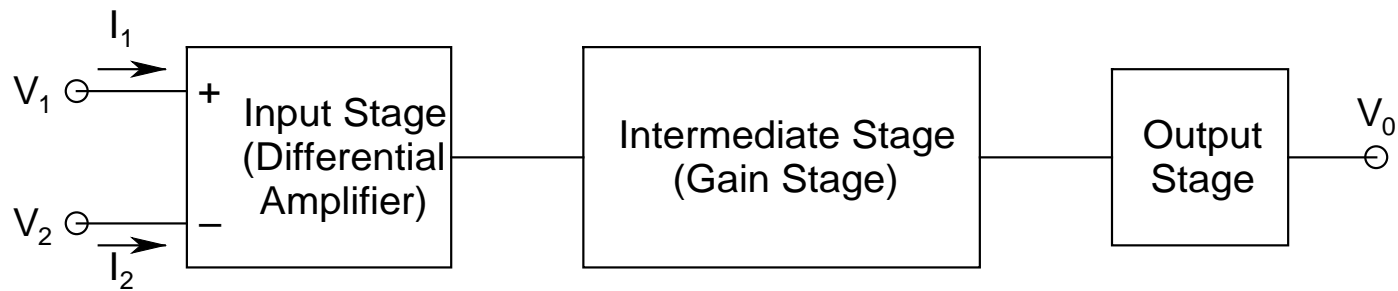- *Needed when the op-amp is expected to either source or sink large amount of current to or from the load*



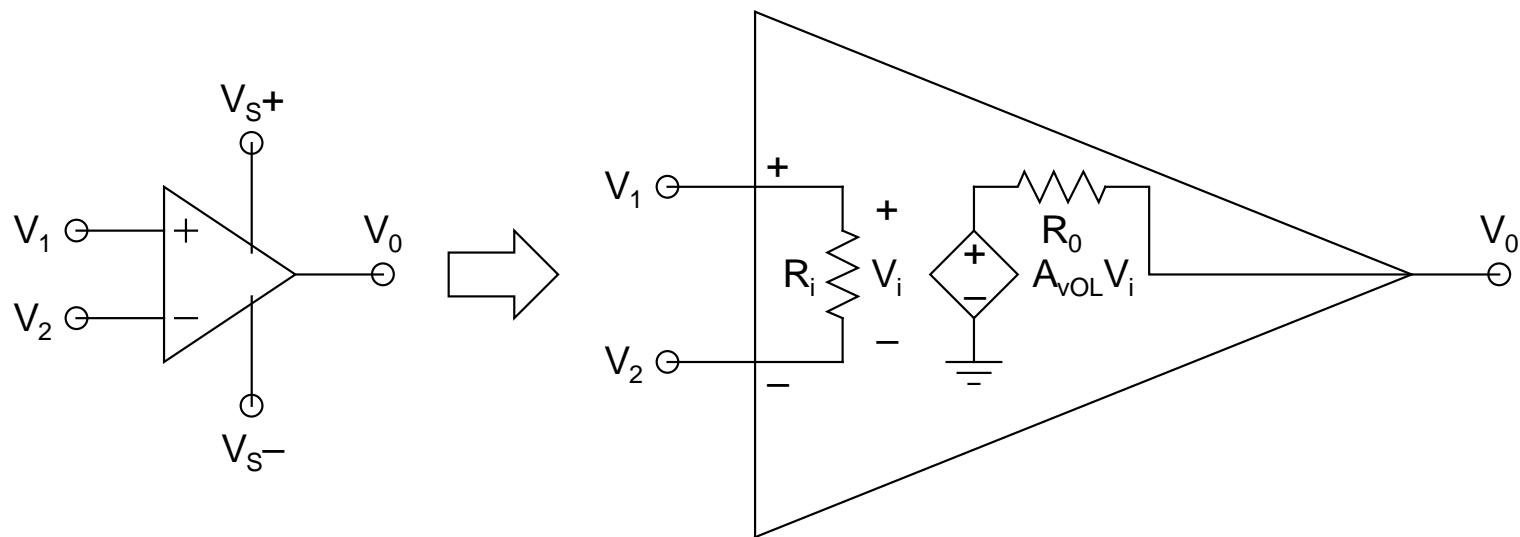Basic Three-Stage Architecture of an Op-Amp



Symbol

MacroModel

- **2 Input Terminals:**
 - V_1 (*non-inverting* [+])
 - V_2 (*inverting* [-])
- **1 Output Terminal:** V_0
- V_1 , V_2 , and V_0 can be *simply DC*, or *simply ac*, or a *combination of both*
- I_1 , I_2 : *Input currents flowing into the + and – terminals respectively*
- **Dual symmetric power supplies** (V_{S+} and V_{S-})

- Refer to the *MacroModel*:

- R_i : *Input Resistance*

- *Very high (ideally infinite)*

- R_o : *Output Resistance*

- *Very small (ideally zero)*

- A_{vOL} : *Open-Loop Gain*

- *Very large (ideally infinite)*

- *Input-Output Relation*:

$$V_o = A_{vOL}(V_1 - V_2)$$


- V_1 , V_2 , and V_0 are measured *w.r.t. ground*, but V_i is a *floating signal* (*difference* between V_1 and V_2)
- The *controlled source* in the *MacroModel* is *VCVS*
- For $V_1 > (<) V_2$, V_0 is *positive* (*negative*)
- *Typical values for 741 op-amp*:
 - $A_{VOL} \sim 10^5$ (*100 dB*), $R_i > 1\text{ M}\Omega$, $R_o < 100\ \Omega$,
CMRR $\sim 80\text{-}100\text{ dB}$, V_{S+} and V_{S-} : $\pm 3\text{ V to } \pm 15\text{ V}$

- V_1 , V_2 , and V_0 are measured *w.r.t. ground*, but V_i is a *floating signal* (*difference* between V_1 and V_2)
- The *controlled source* in the *MacroModel* is *VCVS*
- For $V_1 > (<) V_2$, V_0 is *positive* (*negative*)
- *Typical values for 741 op-amp*:
 - $A_{vOL} \sim 10^5$ (*100 dB*), $R_i > 1\text{ M}\Omega$, $R_o < 100\ \Omega$,
CMRR $\sim 80\text{-}100\text{ dB}$, V_{S+} and V_{S-} : $\pm 3\text{ V to } \pm 15\text{ V}$

- *Uncompensated bandwidth* typically *larger than 1 MHz*
- Such a *large gain* and *high bandwidth* system will be prone to *oscillations* (*instability*)
- Need adequate *compensation*
 - *Compensated bandwidth* drops to about *5-10 Hz*
- *History of 741 Op-Amp:*
 - In *1965*, *Bob Widlar* (remember *Widlar current source*?) of *Fairchild Semiconductors* (now defunct) first came up with the design of a *monolithic* (*single substrate IC*) *op-amp*

- Named it μA 709 (μA was the *trademark* of *Fairchild Semiconductors*)
- Almost immediately thereafter, *a number of improvements* were made on the *original architecture*, and μA 741 evolved
- It became so *popular* that *the term 741* became a *legend*
- *All subsequent op-amp designs continued to be called 741!*
- *Initial design* of course was based on *bipolar technology*, since at that time, *MOSFETs were not even there!*

- In *late 70s*, *JFET version* of op-amps came into existence, followed by the *MOSFET version* in the *80s*
- The *design pedagogy* of the *original version* is a *real beauty*
- So many *brilliant innovations* were *incorporated* in the *design*, that it is a *learner's paradise*!
- In this chapter, we will do a *detailed analysis* of the *bipolar version* of the *741 op-amp*
- So, sit tight and enjoy! :)

 

The schematic of the 741 bipolar op-amp (the pin numbers of the 741 chip is shown in parantheses).

- *Steps of the Analysis:*

- First, we need to do the *DC analysis*
- For this, we need to find the *reference branch*
- This branch should be from *rail-to-rail* (i.e., *between the two power supplies*)
- It should encounter only *base-emitter junctions* and *resistors*
 - ⇒ The branch Q_{11} - Q_{12} - R_5 is our *reference branch*
- *The DC current flowing through this branch fixes the DC bias current of all other branches*

- Next is *identification of modules*
- Q_{10} - Q_{11} - R_4 can be identified as the *Widlar current source*
- Current through Q_{10} is *same* as that of Q_9 , which forms a *mirror configuration* with Q_8
- Current through Q_8 *biases the DA*, which is the *combination* of Q_1 - Q_4
- Q_5 - Q_6 - R_1 - R_2 *combination* can be identified as a *ratioed mirror* with the *keep-alive resistor* R_3 and the *base current boost* provided by Q_7

- *Output of the DA* is fed to Q_{16} - Q_{17} - R_8 - R_9 combination, which is a *CC-CE Darlington*, and acts as the *gain stage*
- The *output of the gain stage* is fed to the *Class-AB output stage*, consisting of:
 - Q_{14} and Q_{20} : *Complementary output transistors*
 - Q_{18} - Q_{19} - R_{10} : *Prebias circuit for the output stage*
 - Q_{15} - Q_{21} - R_6 - R_7 : *Short-circuit protection circuit*
- Q_{13} , Q_{22} - Q_{24} , and the unnumbered $50\text{ k}\Omega$ resistor have *special roles*, which we will discuss about later


- **DC Analysis:**

- **Assumptions:**


- *Neglect base current and Early effect*
- *Both + and –input terminals grounded*
 - ❖ *Recall that is is the most preferred DC biasing arrangement for DAs*
- Q_1 - Q_2 , Q_3 - Q_4 , Q_8 - Q_9 , and Q_{10} - Q_{11} *perfectly matched*
- *± 15 V power supply*

- **Reference branch (Q_{11} - Q_{12} - R_5) current:**
 
$$I_{\text{REF}} = I_{C11} = I_{C12} = [V_{CC} - V_{EB12} - V_{BE11} - (-V_{CC})]/R_5 = 733.3 \mu\text{A}$$



DC Biasing of the Main Branches

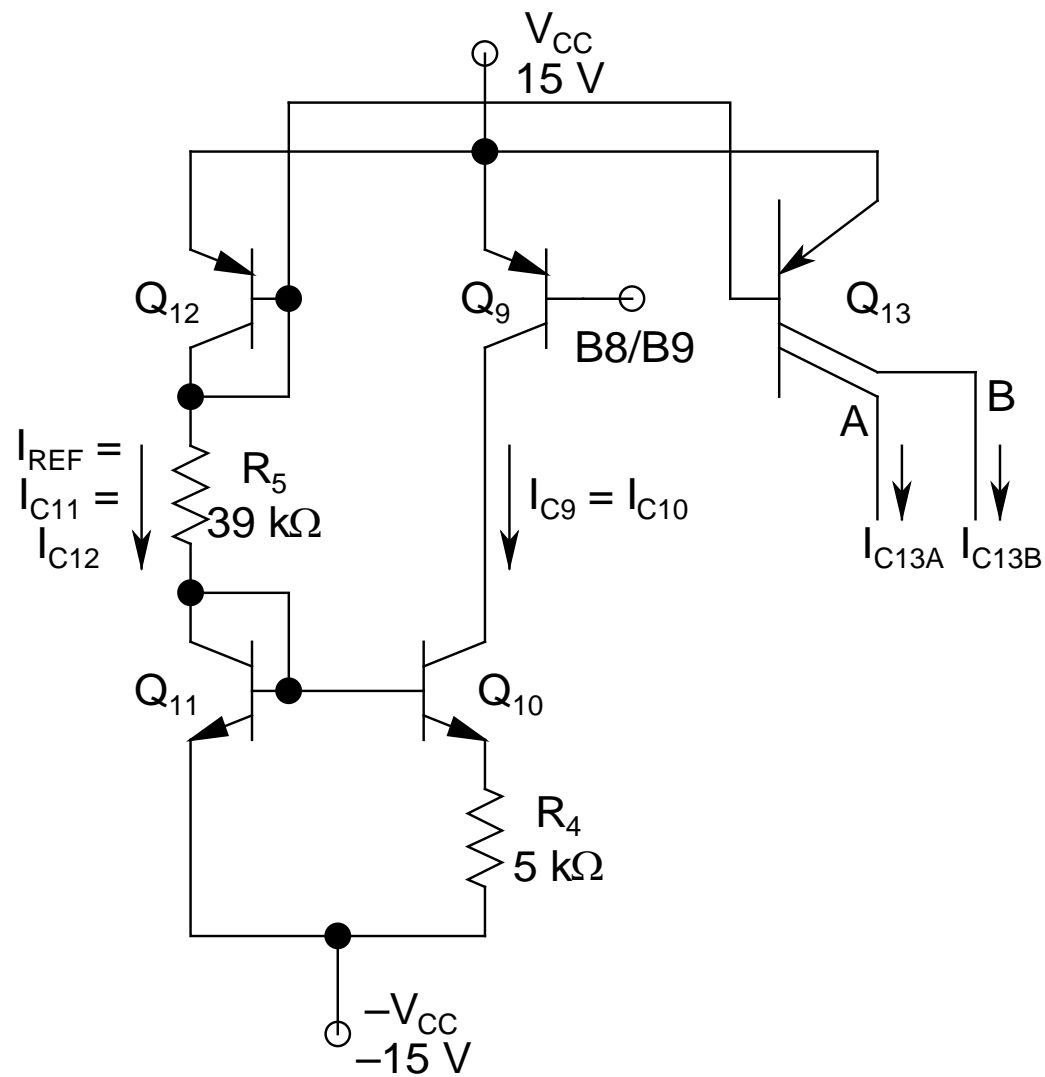

DC Biasing of the Main Branches

- Q_{10} - Q_{11} - R_4 *combination* is a *Widlar current source*:

$$\Rightarrow V_T \ln(I_{REF}/I_{C10}) = I_{C10} R_4$$

$$\Rightarrow I_{C10} = (V_T/R_4) \ln(I_{REF}/I_{C10})$$

Solution of this *transcendental equation*:

$$I_{C10} = 19 \mu A = I_{C9}$$

- Q_{12} - Q_{13} another *mirror*:


$$\Rightarrow I_{C13} = I_{C12} = I_{REF} = 733.3 \mu A$$

- Q_{13} is a *special transistor*, having *split collectors* (A and B), with their *area ratios* 1:3

$$\Rightarrow I_{C13A} = 183.3 \mu A \text{ and } I_{C13B} = 550 \mu A$$

➤ *DC Biasing of the Input Stage:*

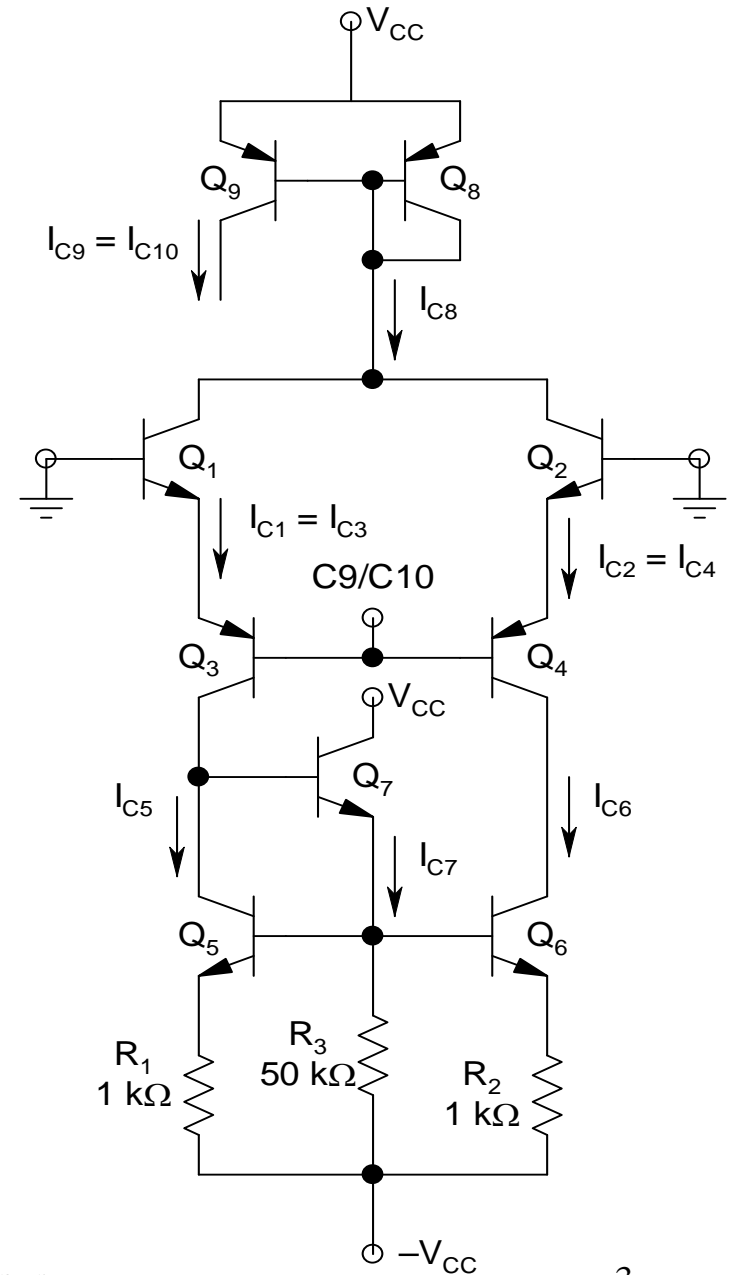- Q_8 - Q_9 form a *current mirror*:
 $\Rightarrow I_{C8} = I_{C9} = I_{C10} = 19 \mu\text{A}$
- This is the *bias current* for the *DA*:
 $\Rightarrow I_{C1} = I_{C2} = I_{C3} = I_{C4}$
 $= I_{C5} = I_{C6} = I_{C8}/2$
 $= 9.5 \mu\text{A}$
 $I_{C5} = I_{C6}$ (*since $R_1 = R_2$*)



- *Calculation* of I_{C7} little more *involved*
 - ❖ *Neglecting base currents*, $I_{C7} \approx I_{R3}$
 - ❖ Assuming $I_{S5} = 1 \text{ fA}$:

$$V_{BE5} = V_T \ln(I_{C5}/I_{S5}) = 597.3 \text{ mV}$$
 - ❖ The *drop* across R_3 :

$$V_{R3} = V_{BE5} + I_{C5}R_1 = 606.8 \text{ mV}$$

$$\Rightarrow I_{C7} \approx I_{R3} = V_{R3}/R_3 = 12.1 \text{ } \mu\text{A}$$

➤ *DC Biasing of the Gain Stage:*


- $I_{C17} = I_{C13B} = 550 \mu\text{A}$
- This is a *large current* and the *base current may not be negligible*

- Assuming $\beta_{17} = 200$:
 $I_{B17} = I_{C17} / \beta_{17} = 2.75 \mu\text{A}$
- Assuming $I_{S17} = 1 \text{ fA}$, the *base voltage* of Q_{17} , *w.r.t.*

the negative power supply ($-V_{CC}$):

$$V_{B17} \text{ (w.r.t. } -V_{CC}) \approx V_T \ln(I_{C17}/I_{S17}) + I_{C17} R_8$$

$$= 757.9 \text{ mV}$$

 


- Thus:

$$I_{R9} = V_{B17}/R_9 \\ = 15.16 \mu A$$

$$\Rightarrow I_{C16} = I_{R9} + I_{B17} \\ = 17.9 \mu A$$

➤ *Finally, the output stage:*

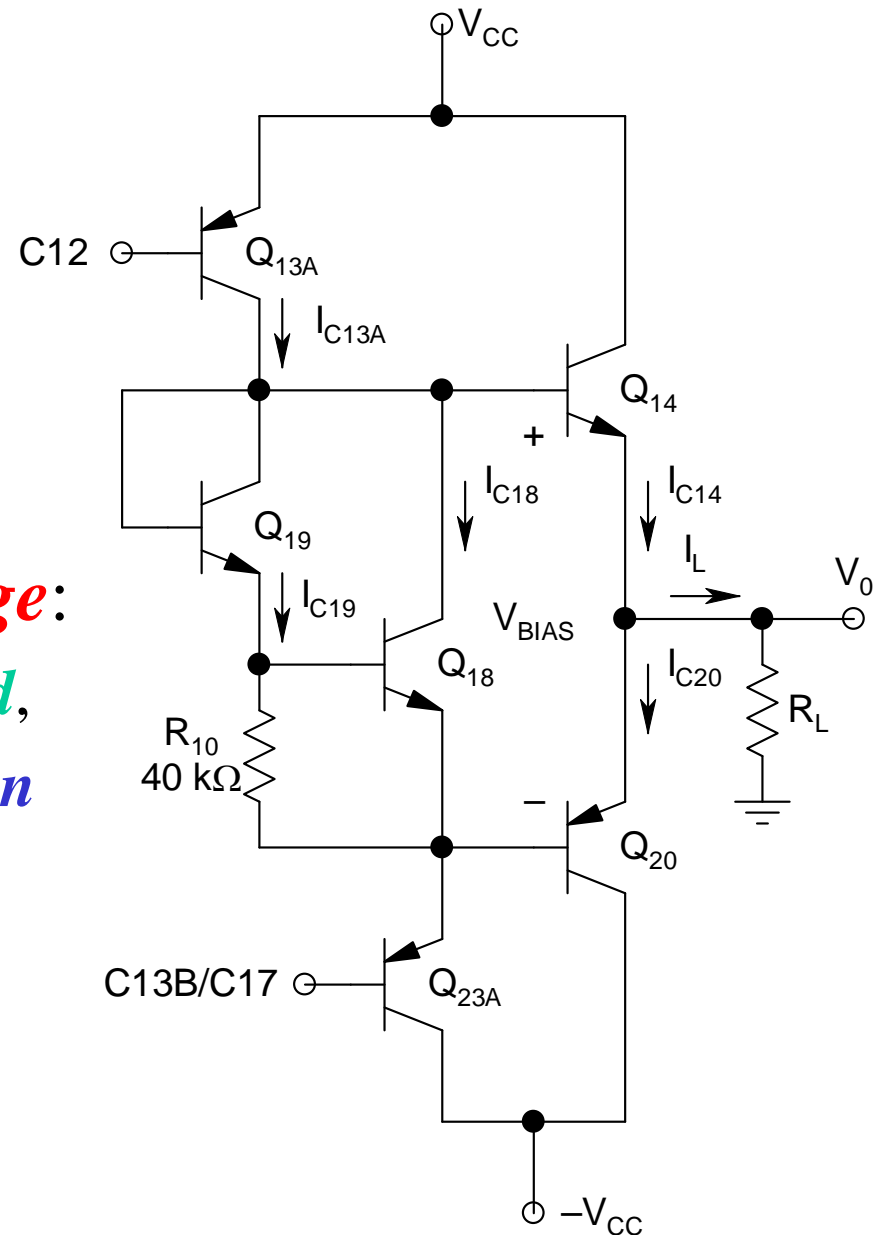- Q_{15} - Q_{21} - R_6 - R_7 *neglected*, since these are *protection devices*, and *come into play* only during *accidental short-circuiting of the output*



- To find the *idling current*, R_L is *removed*, thus making $I_L = 0$
 - \Rightarrow *Standby (Idling) Current* $= I_{C14} = I_{C20}$
- Q_{18} - Q_{19} - R_{10} is an *extremely cleverly and innovatively designed block*
 - ❖ It produces a *prebias voltage* V_{BIAS} (*close to $2V_\gamma$*) *between the bases of Q_{14} and Q_{20}*
 - ❖ At the same time, it *reduces the standby power dissipation of the output branch*
- $I_{C13A} = 183.3 \mu A$, and *splits* into Q_{18} - Q_{19} combination
- Assuming $V_{BE18} = 0.7 V$ and for the time being, *neglecting* I_{B18} :

$$I_{C19} \approx I_{R10} = V_{BE18}/R_{10} = 17.5 \mu A$$

- Thus:

$$I_{C18} = I_{C13A} - I_{C19} = 165.8 \mu A \text{ (*neglecting } I_{B19}*)}$$

- Since I_{C18} is *pretty high*, we need to now *fine tune* our analysis by *including I_{B18}*

- Assuming $I_{S18} = 1 \text{ fA}$ and $\beta = 200$:

$$\begin{aligned} I_{C19} &= I_{B18} + I_{R10} = I_{C18}/\beta_{18} + (V_T/R_{10})\ln(I_{C18}/I_{S18}) \\ &= 17.6 \mu A \end{aligned}$$

- This is *sufficiently close* to our *initial estimate* of $17.5 \mu A$

- Thus:

$$I_{C18} = I_{C13A} - I_{C19} = 165.7 \mu A$$

which is *almost same* as our *original estimate*

- $V_{\text{BIAS}} = V_{\text{BE18}} + V_{\text{BE19}} = V_{\text{BE14}} + V_{\text{EB20}}$
 $\Rightarrow V_T \ln(I_{\text{C18}}/I_{\text{S18}}) + V_T \ln(I_{\text{C19}}/I_{\text{S19}})$
 $= V_T \ln(I_{\text{C14}}/I_{\text{S14}}) + V_T \ln(I_{\text{C20}}/I_{\text{S20}})$

- *Since $I_L = 0$:*

$$\Rightarrow I_{\text{C14}} = I_{\text{C20}} = \sqrt{\frac{I_{\text{S14}} I_{\text{S20}}}{I_{\text{S18}} I_{\text{S19}}}} \sqrt{I_{\text{C18}} I_{\text{C19}}}$$

- The *sizes* of the *output transistors* are typically *much larger* than the other devices, to be able to *supply large current to the load without overheating*
- Assuming $I_{\text{S14}} = I_{\text{S20}} = 4I_{\text{S18}} = 4I_{\text{S19}}$:
 $I_{\text{C14}} = I_{\text{C20}} = 216 \mu\text{A}$
- Thus, the *idling* (*standby*) *power dissipation* of the *output branch* = $(30 \text{ V}) \times (216 \mu\text{A}) = 6.5 \text{ mW}$

- $V_{\text{BIAS}} = V_{\text{BE18}} + V_{\text{BE19}} = V_{\text{BE14}} + V_{\text{EB20}}$
 $\Rightarrow V_T \ln(I_{\text{C18}}/I_{\text{S18}}) + V_T \ln(I_{\text{C19}}/I_{\text{S19}})$
 $= V_T \ln(I_{\text{C14}}/I_{\text{S14}}) + V_T \ln(I_{\text{C20}}/I_{\text{S20}})$
- *Since $I_L = 0$:*

$$\Rightarrow I_{\text{C14}} = I_{\text{C20}} = \sqrt{\frac{I_{\text{S14}} I_{\text{S20}}}{I_{\text{S18}} I_{\text{S19}}}} \sqrt{I_{\text{C18}} I_{\text{C19}}}$$
- The *sizes* of the *output transistors* are typically *much larger* than the other devices, to be able to *supply large current to the load without overheating*
- Assuming $I_{\text{S14}} = I_{\text{S20}} = 4I_{\text{S18}} = 4I_{\text{S19}}$:
 $I_{\text{C14}} = I_{\text{C20}} = 216 \mu\text{A}$
- Thus, the *idling* (*standby*) *power dissipation* of the *output branch* = $(30 \text{ V}) \times (216 \mu\text{A}) = 6.5 \text{ mW}$

- Assuming $I_{S18} = I_{S19} = 1 \text{ fA}$:

$$V_{\text{BIAS}} = V_T \ln[I_{C18} I_{C19} / (I_{S18} I_{S19})] = 1.285 \text{ V}$$
- This produces a *DC bias* of $\sim 643 \text{ mV}$ across the *BE junctions* of Q_{14} and Q_{20} , keeping them at the *verge of conduction*
- Note that instead of the *prebias combination* used, if simply *two diodes* were used in *series*, then the *current* through that *branch* would have been $183.3 \mu\text{A}$, resulting in a current of $733.2 \mu\text{A}$ in the *output branch*, thus creating *standby power dissipation* in the *output branch* of 22 mW (3.4 times)
- Finally, $I_{C23A} = I_{C13A} = 183.3 \mu\text{A}$

| Transistor(s) | Magnitude (μA) |
|--|-----------------------------|
| $I_{C1}, I_{C2}, I_{C3}, I_{C4}, I_{C5}, I_{C6}$ | 9.5 |
| I_{C7} | 12.1 |
| I_{C8}, I_{C9}, I_{C10} | 19 |
| I_{C11}, I_{C12} | 733.3 |
| I_{C13A}, I_{C23A} | 183.3 |
| I_{C13B}, I_{C17} | 550 |
| I_{C14}, I_{C20} | 216 |
| I_{C16} | 17.9 |
| I_{C18} | 165.7 |
| I_{C19} | 17.6 |

The DC Bias Currents of Different Transistors

- The *DC power dissipation* of the circuit:

$$\begin{aligned} P_{DC} &= V_{CC} \times (I_{C12} + I_{C9} + I_{C8} + I_{C13A} + I_{C13B} + \\ &\quad I_{C14} + I_{C7} + I_{C16}) + \\ &\quad | -V_{CC} | \times (I_{C11} + I_{C10} + I_{C5} + I_{C7} + I_{C6} + \\ &\quad I_{R9} + I_{C17} + I_{C23A} + I_{C20}) \\ &= 52.3 \text{ mW} \end{aligned}$$

- Note that the *reference branch* consumes the *highest DC power*, followed by the *Darlington branch*
- On the other hand, the *least DC power* is consumed by the *DA branch*

- *ac Analysis:*
 - *Primary Goal:*
 - *To find R_i , R_o , and A_{vOL}*
 - We will adopt a *modular approach*:
 - *Considering each stage individually*
 - *Finding the 2-port equivalent for each of them*
 - *Eventually joining them together to get the total response*

➤ Assumed:


$$\beta_N = 200, \beta_P = 100, V_{AN} = 130 \text{ V}, V_{AP} = 50 \text{ V}$$

➤ We will also *evaluate* the *required value* of the *compensation capacitor* C_C

➤ The *analysis* will be *simple* and *highly approximate*, however, the *results* will *definitely lie* within $\pm 10\%$ of the *actual*

➤ **Input Stage:**

 - *Differential-mode input*
 v_{id} *split* into $+v_{id}/2$ and $-v_{id}/2$, and *applied* at the *bases* of Q_1 - Q_2
- All *terminals* having *fixed DC potentials* have been tied to *ac ground*
- *Bases* of Q_3 - Q_4 are at *ac ground* due to *perfect symmetry* of the circuit




- $i_{c3} = i_{c5}$ (*neglecting base current of Q_7*)

- $i_{c6} = i_{c5}$ (*ratioed mirror with $R_1 = R_2$*)

- **Output current:**

$$i_0 = i_{c6} - i_{c4} = i_{c5} - i_{c4} = i_{c3} - i_{c4}$$

 - To find the *short-circuit transconductance* of this stage, we *short the output node to ground*



- $v_{id}/2 = v_1 + v_3$

- ***KCL at node A:***

$$v_1/r_{\pi 1} + g_{m1}v_1 = v_3/r_{E3}$$

$$\Rightarrow v_1 = \frac{r_{\pi 1}}{r_{E3}} \frac{1}{1 + g_{m1}r_{\pi 1}} v_3 = \frac{r_{\pi 1}}{r_{E3}} \frac{1}{1 + \beta_1} v_3 \approx \frac{r_{\pi 1}}{\beta_1} \frac{1}{r_{E3}} v_3 \approx \frac{r_{E1}}{r_{E3}} v_3 = v_3$$

$$\Rightarrow v_{id} = 4v_3 \Rightarrow v_3 = v_{id}/4$$

$$\Rightarrow i_{c3} = g_{m3}v_3 = g_{m3}v_{id}/4 \text{ and } i_{c4} = -g_{m3}v_{id}/4$$

$$\Rightarrow i_0 = i_{c3} - i_{c4} = +g_{m3}v_{id}/2$$

- Thus, the ***short-circuit transconductance***:

$$G_{m1} \triangleq \left. \frac{i_0}{v_{id}} \right|_{v_0=0} = \frac{g_{m3}}{2} = \frac{I_{C3}}{2V_T} = 182.7 \mu S$$

- ***Differential-mode input resistance:***

$$R_{id} \triangleq \frac{V_{id}}{i_i} = 2 \times \frac{V_{id}/2}{i_i} = 2(\beta_1 + 1)(r_{E1} + r_{E3}) \simeq 4\beta_1 r_{E1}$$

$$= \frac{4\beta_1 V_T}{I_{C1}} = 2.2 \text{ M}\Omega$$

- This is also the ***input resistance*** R_i of the ***op-amp***
- The ***output resistance*** can be ***calculated*** by following our ***standard procedure*** of ***nulling the independent sources***, ***exciting the output by a test voltage source***, and ***finding the current drawn from it***

- **Base** of Q_6 can be considered to be at a **fixed DC potential**, and thus, **ac ground**

- **By inspection:**

$$R_{04} = r_{04}[1 + g_{m4}(r_{\pi4} || r_{E2})]$$

$$R_{06} = r_{06}[1 + g_{m6}(r_{\pi6} || R_2)]$$


$$r_{04} = V_{AP}/I_{C4} = 5.26 \text{ M}\Omega$$

$$g_{m4} = I_{C4}/V_T = 365 \text{ }\mu\text{A/V}$$

$$r_{\pi4} = \beta_4/g_{m4} = 273.7 \text{ k}\Omega$$

$$r_{E2} = V_T/I_{C2} = 2.74 \text{ k}\Omega$$
 
$$\Rightarrow R_{04} \approx 2r_{04} = 10.5 \text{ M}\Omega$$




$$r_{06} = V_{AN}/I_{C6} = 13.7 \text{ M}\Omega$$

$$g_{m6} = I_{C6}/V_T = 365 \text{ }\mu\text{A/V}$$

$$r_{\pi6} = \beta_6/g_{m6} = 547.9 \text{ k}\Omega$$

$$\Rightarrow R_{06} \approx r_{06}(1 + g_{m6}R_2) = 18.7 \text{ M}\Omega$$
 
$$\Rightarrow R_{0d} = R_{04} \parallel R_{06} = 6.7 \text{ M}\Omega$$



2-Port Equivalent of the Input Stage

➤ **Gain Stage:**


- $r_{E16} = V_T/I_{C16} = 1.45 \text{ k}\Omega$
 $r_{\pi16} = \beta_{16}r_{E16} = 290.5 \text{ k}\Omega$
 $r_{E17} = V_T/I_{C17} = 47.3 \text{ }\Omega$
 $r_{\pi17} = \beta_{17}r_{E17} = 9.45 \text{ k}\Omega$
 $\Rightarrow R_{i17} = r_{\pi17} + (\beta_{17} + 1)R_8$
 $= 29.6 \text{ k}\Omega$

- **Effective load resistance** of Q_{16} :

$$R_{L16} = R_9 \parallel R_{i17} = 18.6 \text{ k}\Omega$$

- Thus, the **input resistance** of the **gain stage**:
 
$$R_{i2} = R_{i16} = r_{\pi16} + (\beta_{16} + 1)R_{L16} = 4.03 \text{ M}\Omega$$



- Next, we have to *calculate* the *short-circuit transconductance* G_{m2} ($= i_0/v_{i2}$), with the *output terminal shorted to ground*
- *Voltage gain* of Q_{16} :

$$v_1/v_{i2} = R_{L16}/(R_{L16} + r_{E16}) = 0.93$$
- *Overall transconductance* of Q_{17} - R_8 combination (*emitter degenerated stage*):

$$G_{m17} = i_0/v_1 = g_{m17}/(1 + g_{m17}R_8) \approx 1/(r_{E17} + R_8) = 6.8 \text{ mA/V}$$


$$\Rightarrow G_{m2} = i_0/v_{i2} = (i_0/v_1) \times (v_1/v_{i2}) = 6.3 \text{ mA/V}$$
- Next is the *output resistance* R_{02}
- *From inspection*: $R_{02} = R_{013B} \parallel R_{017}$

- $R_{013B} = r_{013B} = V_{AP}/I_{C13B} = 90.9 \text{ k}\Omega$
- $r_{017} = V_{AN}/I_{C17} = 236.4 \text{ k}\Omega$
- Since **base** of Q_{17} can be considered to be at **ac ground**, and $r_{\pi 17} \gg R_8$:

$$R_{017} \approx r_{017}(1 + g_{m17}R_8) = r_{017}(1 + R_8/r_{E17}) \\ = 736.2 \text{ k}\Omega$$


- Thus:
 
$$R_{02} = R_{013B} \parallel R_{017} = 80.9 \text{ k}\Omega$$




2-Port Equivalent of the Gain Stage

➤ *Output Stage:*

 

Circuit

 

Schematic

- *Analysis slightly different*, since the *transistors operate with large signal swings, typically from rail-to-rail*, and *small-signal analysis is not quite valid*
- Will attempt an *approximate analysis* under some *specific assumptions*:
 - ❖ v_0 under *positive excursion*, with Q_{14} *supplying current to load* (R_L) and Q_{20} *off*
 - ❖ $R_L = 5 \text{ k}\Omega$ and $i_L = 2 \text{ mA}$
 $\Rightarrow v_0 = 10 \text{ V}$
- *Ex.*: Show that Q_{18} - Q_{19} - R_{10} *combination* effectively appears as a *resistance* $r_{eq} = 168.7 \text{ }\Omega$
- $r_{E14} = V_T/I_{C14} = 13 \text{ }\Omega$
- $r_{013A} = r_{023A} = V_{AP}/I_{C13A} = V_{AP}/I_{C23A} = 272.8 \text{ k}\Omega$

- $r_{E23A} = V_T/I_{C23A} = 141.8 \Omega$
- $r_{\pi23A} = \beta_{23A}r_{E23A} = 14.2 \text{ k}\Omega$
- $R_{i14} = (\beta_{14} + 1)(r_{E14} + R_L) = 1 \text{ M}\Omega$
- $R' = r_{013A} \parallel R_{i14} = 214.3 \text{ k}\Omega$
- ***Effective load*** of Q_{23A} :
 $R_{L23A} = r_{eq} + R' = 214.5 \text{ k}\Omega$
- R_{L23A} appears in ***parallel*** with r_{023A}
 $\Rightarrow R_{eq} = r_{023A} \parallel R_{L23A} = 120.1 \text{ k}\Omega$
 $\Rightarrow R_{i3} = r_{\pi23A} + (\beta_{23A} + 1)R_{eq} = 12.1 \text{ M}\Omega$

- Note the *enormously large input resistance* of the *output stage*, primarily due to *two factors*:
 - ❖ *Buffering action* of Q_{23A} , putting its *entire emitter load to base after multiplying it by β*
 - ❖ *Relatively large value of R_L*
- Thus, the *choice* of putting Q_{23A} in the *signal path* is obvious
 - ❖ It also provides a *DC level shift* of $\sim +0.7$ V
- Note also that R_{i3} appears as the *load of the gain stage*, having an *output resistance* R_{o2} of only 80.9 k Ω
 - \Rightarrow *Negligible loading*

- Since this stage is basically a *cascade of voltage followers*, hence, it would be *more prudent* to find the *overall voltage gain* of this stage, rather than the *short-circuit transconductance*
- Thus:

$$v_1/v_{i3} = R_{eq}/(R_{eq} + r_{E23A}) = 0.9988$$

$$v_2/v_1 = R'/(R' + r_{eq}) = 0.9992$$

$$v_0/v_2 = R_L/(R_L + r_{E14}) = 0.9974$$


$$\Rightarrow A_{v3} = v_0/v_{i3} = (v_0/v_2) \times (v_2/v_1) \times (v_1/v_{i3})$$

$$= 0.9954 \approx 1$$
- Note that in spite of *keeping* so many *significant digits* after the *decimal point* in all the *intermediate results*, the *end result* is still *extremely close to unity*


- The **output resistance** R_{03} can be *evaluated* from a *simple inspection* of the circuit:

$$R'' = r_{013A} \parallel (r_{eq} + r_{E23A}) = 310.1 \, \Omega$$
 
$$\Rightarrow R_{03} = r_{E14} + R''/(\beta_{14} + 1) = 14.5 \, \Omega$$




2-Port Equivalent of the Output Stage

 

➤ Overall Performance:


- Just *cascade* the *2-port equivalents* of the *three stages*

 

Complete 2-Port Representation of 741 Op-Amp

➤ Overall Performance:

- Just *cascade* the *2-port equivalents* of the *three stages*

 

Complete 2-Port Representation of 741 Op-Amp

- ***Voltage gain of the input stage:***

$$A_{v1} = v_{01}/v_{id} = -G_{m1}(R_{01}||R_{i2}) = -459.7$$

- ***Voltage gain of the gain stage:***

$$A_{v2} = v_{02}/v_{01} = -G_{m2}(R_{02}||R_{i3}) = -506.3$$

- ***Voltage gain of the output stage:***

$$A_{v3} \sim 1$$

- Thus, the ***overall voltage gain*** of ***741 op-amp***:

$$\begin{aligned} A_{vOL} &= v_0/v_{id} = (v_0/v_{i3}) \times (v_{i3}/v_{i2}) \times (v_{i2}/v_{id}) \\ &= 2.33 \times 10^5 \text{ (107.3 dB)} \end{aligned}$$

Note: $v_{i3} = v_{02}$, and $v_{i2} = v_{01}$

- This is an ***excellent value***, in spite of the ***significant loading effect*** of the ***gain stage*** on the ***input stage***

➤ *Observations:*


- A_{vOL} is actually the *differential-mode gain* (A_{dm})
- It is *positive*
 - ❖ *Positive* v_{id} produces *positive* v_o
 - ❖ *Bases* of Q_1 and Q_2 are termed as *non-inverting* (+) and *inverting* (−) terminals respectively
- *Input and output resistances* are $2.2\text{ M}\Omega$ and $14.5\text{ }\Omega$ respectively, both of which are *excellent values*
- The *exact value* of A_{cm} is *slightly difficult to evaluate*, however, an *estimate of CMRR can be made*
- Using the *result* of our *simple analysis* of *DA*:
$$CMRR \approx 2g_{m1}r_{o8} = 1923\text{ (66 dB)}$$
- This is not too bad!
 - ❖ *Actual value is much higher than this*

- *Compensation:*

- Actual evaluation of the *frequency response* characteristic of 741 is a *huge task*, even with the *ZVTC technique*
- There will be *numerous poles and zeros*, out of which, some will be *important*, while others will be *inconsequential*
- However, there will of course be a *Dominant Pole* (DP), and rough calculation shows that it is $\sim 1\text{ MHz}$, which is the *bandwidth* of the *uncompensated op-amp*

- Now, ~ *100 dB open-loop gain* with *1 MHz bandwidth* is a *ready recipe for disaster* as far as the *stability of the system* is concerned
- Hence, for *unconditional stability* under *unity negative feedback*, e.g., *voltage follower*, *compensation is imperative*
- In 741, this task is accomplished by the technique of *Dominant Pole Compensation* (DPC) through the use of the *compensation capacitor* C_C , *connected between the input and output of the gain stage*

 - To obtain the *required value* of C_C , we use the cascade of the *2-port networks*, as was done earlier to compute the *overall voltage gain*



- Denote $R' = R_{01} \parallel R_{i2} = 2.5 \text{ M}\Omega$
and $R'' = R_{02} \parallel R_{i3} = 80.4 \text{ k}\Omega$

- The *simplified circuit* can be easily identified as the *three-legged creature*, and using the *ZVTC technique*:

$$R_C^0 = R' + R'' + G_{m2} R' R'' = 1.27 \text{ G}\Omega$$

- Now, to get an estimate of the *DPF* f_d , we assume that the *open-loop gain* is exactly 100 dB, and the *first pole* of the *uncompensated op-amp* is *exactly 1 MHz*

$$\Rightarrow f_d = 10 \text{ Hz}$$

- Also, $f_d = \omega_d / (2\pi)$, with $\omega_d = 1/\tau$, and
- $$\tau = R_C^0 C_C$$

- The *simplified circuit* can be easily identified as the *three-legged creature*, and using the *ZVTC technique*:

$$R_C^0 = R' + R'' + G_{m2} R' R'' = 1.27 \text{ G}\Omega$$

- Now, to get an estimate of the *DPF* f_d , we assume that the *open-loop gain* is exactly 100 dB, and the *first pole* of the *uncompensated op-amp* is *exactly 1 MHz*

$$\Rightarrow f_d = 10 \text{ Hz}$$

- Also, $f_d = \omega_d / (2\pi)$, with $\omega_d = 1/\tau$, and $\tau = R_C^0 C_C$

➤ Thus:


$$C_C = \tau/R_C^0 = 12.5 \text{ pF}$$

➤ Note that with this *compensation scheme*, the *open-loop bandwidth* of the *compensated op-amp* drops all the way down to *10 Hz* from *1 MHz*

➤ However, this is not really a *limitation*, since the *open-loop gain* is *so high*, that even with *negative feedback*, *sufficiently high values of gain can be achieved*

➤ **Unity-Gain Bandwidth (f_T):**

- **Product** of the **dominant pole frequency** and the **open-loop gain**
- This is also the **bandwidth** of the system when the **gain is unity** (hence the name!)
- Also known as the **gain-bandwidth product** (GBP)
- It is **1 MHz** for this case
- Note that under **DPC**, it's also the **first pole** of **uncompensated system**
- With **negative feedback**, the **GBP remains constant**
⇒ **As gain ↓, bandwidth ↑, and vice-versa**

 

A_{v0} : **Midband Gain**, ω_d : **Compensated Bandwidth**, ω_T : **Unity-Gain Bandwidth**
 N_1 and ω_1 , N_2 and ω_2 : **Amount of Feedback and Corresponding Bandwidth**
 A_1 , A_2 : **Gain With Feedback N_1 , N_2**
 $A_{v0}\omega_d = A_1\omega_1 = A_2\omega_2 = \omega_T$

- *Protection Circuits:*

- Q_{15} - R_6 : *Overload protection circuit* for Q_{14}
- Similar to that discussed in the chapter on *Output Stages*
- R_6 *senses* the *current* being *sourced* by Q_{14} to *load*
- When the *drop* across R_6 *approaches* V_γ of Q_{15} , it starts to *bypass* the *base current* of Q_{14}
⇒ *The current does not increase indefinitely*
- *Protection scheme of Q_{20} is slightly different*

- For the *previous case* of Q_{14} , the *load current* was *flowing out* of the circuit
- However, for Q_{20} , the *load current* is *flowing into* the circuit
- Thus, the circuit should be *protected* by *limiting* the amount of this *current*
- Here, R_7 *senses* the *current* being *sunk* by Q_{20}
- As soon as the *drop* across R_7 *approaches* V_γ of Q_{21} , it *turns on* and starts to *bypass* the *current* through Q_{20}

- *Values of R_6 and R_7 are slightly different to account for the difference in V_γ for npn and pnp BJTs*
- Initially, this *shunted current* starts to *flow* through the *unnumbered* 50 k Ω resistor to $-V_{CC}$
- When the *drop* across this 50 k Ω resistor *approaches* V_γ of Q_{24} , it starts to *turn on*, which makes Q_{22} to *turn on* too (note that Q_{22} and Q_{24} form a *mirror*)
- Now, the *collector* of Q_{22} is *connected* to the *base* of Q_{16}

- Thus, Q_{16} starts to *lose* its *base drive*, since a *part of it* is *shunted away* by Q_{22}
- Hence, Q_{16} *conducts less*, and produces a *chain reaction*, which *limits* the *current sinking capability* of the *output stage*
- Thus, the *circuit gets protected*
- Now, about the *role played by Q_{23B}*
- *Note*: $V_{B16} = V_{E23B}$, and $V_{C17} = V_{B23B}$
 $\Rightarrow V_{EB23B} = V_{B16} - V_{C17}$
- Also, $V_{C17} = V_{B17} + V_{CB17}$

- Noting that $V_{B17} = V_{E16}$:

$$V_{EB23B} = V_{B16} - V_{E16} - V_{CB17} = V_{BE16} - V_{CB17}$$
- Under *normal operating condition*, $V_{BE16} \sim 0.7 \text{ V}$
- If Q_{17} also is in the *FA mode*, which is the *desired mode of operation*, then the *CB junction* of Q_{17} will be *reverse biased*
 - $\Rightarrow V_{CB17}$ is *positive*
 - $\Rightarrow V_{EB23B} < V_{BE16}$, and Q_{23B} would *remain off*
- Now, if *for any reason whatsoever*, Q_{17} *moves towards saturation*, then V_{CB17} would *decrease*

- Noting that $V_{B17} = V_{E16}$:

$$V_{EB23B} = V_{B16} - V_{E16} - V_{CB17} = V_{BE16} - V_{CB17}$$
- Under *normal operating condition*, $V_{BE16} \sim 0.7 \text{ V}$
- If Q_{17} also is in the *FA mode*, which is the *desired mode of operation*, then the *CB junction* of Q_{17} will be *reverse biased*
 - $\Rightarrow V_{CB17}$ is *positive*
 - $\Rightarrow V_{EB23B} < V_{BE16}$, and Q_{23B} would *remain off*
- Now, if *for any reason whatsoever*, Q_{17} *moves towards saturation*, then V_{CB17} would *decrease*

- As soon as V_{CB17} *equals zero* (corresponding to *onset of saturation* of Q_{17}):
 - ⇒ Q_{23B} would *turn on* and *rob* the *base drive away from the base* of Q_{16}
 - ⇒ Q_{17} *pushed back* to the *FA mode of operation*
- This *chain of events* is *pretty complicated indeed*
- Thus, Q_{23B} *prevents* Q_{17} from *saturating*, and thus, *ensures optimum performance* of the circuit

- *Anomalies and Limitations:*
 - *Common-Mode Rejection*
 - *Input Offset Voltage/Input Offset Current*
 - *Saturation Voltages*
 - *Minimum Allowed Supply Voltage*
 - *Slew Rate and Full-Power Bandwidth*

➤ *Common-Mode Rejection:*

- An *extremely important parameter* (**CMRR**)
- *Depends on:*
 - ❖ The *output resistance* r_{o8} of Q_8
 - ❖ *Matching of the input transistors* (Q_1 - Q_2 and Q_3 - Q_4)
- *Higher $r_{o8} \Rightarrow$ Better CMRR*
- *More mismatch in the input transistors \Rightarrow Worse CMRR*
- *Exact calculation of A_{cm} is pretty tedious*
- A *rough estimate* of A_{cm} can be *obtained* by noting that:
 - ❖ For *common-mode input*, the *common collector point* of Q_1 - Q_2 is *not at ac ground*, but *connected to the collector* of Q_8
 - ❖ $r_{o8} = V_{AP}/I_{C8} = 2.6 \text{ M}\Omega$

- Now, refer to the *2-port equivalent* of the *differential-input stage*, having the *input resistance* R_{i2} of the *gain stage* as its *load*
- Noting that the stage is basically *CE(D)*:

$$\Rightarrow A_{cm} \simeq \frac{-(R_{o1} \parallel R_{i2})}{1/G_{m1} + 2r_{o8}} = -0.48$$

- Thus:

$$CMRR = |A_{dm}/A_{cm}| = 4.85 \times 10^5 \text{ (113.76 dB)}$$

which is *phenomenal*

- This figure is *much higher* than that *computed earlier*
- Of course, the *analysis* is *highly simplistic*
- Even then, the *actual value* may be *well above 100 dB*

➤ **Input Offset Voltage/Input Offset Current:**


- Created due to a **mismatch** between the **input transistors**
- For an **op-amp** with $A_{vOL} = 10^5$, operated with a **power supply** of ± 10 V, V_{id} **needed** to cause V_0 to **reach either of these two extremes** $= \pm 100 \mu\text{V}$
- The **mismatch** between the **input transistors** typically create a **voltage difference** between the **inputs**, known as the **Input Offset Voltage** (V_{OS})
- **Typical value** of V_{OS} for **741 op-amp** ~ 5 - 10 mV
- This would **cause** V_0 to **saturate** at either $+V_{CC}$ or $-V_{CC}$
- This is known as **saturation** or **latch-up** problem

- In **741**, there is a *provision* to *eliminate* this *problem*, known as *offset nulling*
- Refer to the *circuit* of 741, and note *pin numbers* 1 and 5 *connected* to the *emitters* of Q_5 and Q_6
- Between these *two pins*, a *potentiometer* is connected, with its *wiper* connected to $-V_{CC}$
- This *potentiometer* is known as the *offset null resistor*
- It *eliminates* the *effect* of V_{OS} by *creating* an *unequal division* of *bias currents* in the *two branches* of the *input circuit*, just enough to *balance* the *difference* caused due to *device mismatch*

■ **Procedure:**

- ❖ **Tie both inputs to ground:** V_0 would most likely *saturate* at either $+V_{CC}$ or $-V_{CC}$
- ❖ Next, **move the wiper** of the *potentiometer* in the *direction* that creates a **magnitude reduction** of V_0
- ❖ Towards the *end*, it will become *very sensitive*, and a **perfect nulling**, i.e., V_0 becoming *exactly zero*, *may not be possible*
- ❖ The **typically expected minimum value** of V_0 may be $\sim 5\text{-}10$ mV
- ❖ Leave the *potentiometer setting* at the *best possible* achieved result
- ❖ **Done!**

 - **The Input Offset Current (I_{OS}):**
 - ❖ **Difference** between the **base currents** (known as **Input Bias Currents** I_1 and I_2) of Q_1 and Q_2
 - ❖ **Extremely small** (\sim **tens to hundreds of nA**)
- I_{OS} and V_{OS} are actually **interrelated**, since both of them are created due to **device mismatch**, and have almost **identical manifestations**



Both V_{OS} and I_{OS} are not used
 V_{OS} (I_{OS}) is used when the
 input is voltage (current)

**Modeling of the Anomalies
 With Regard to V_{OS} and I_{OS}**

➤ *Saturation Voltages:*

- An *ideal op-amp* should have *rail-to-rail swing* at the *output*
- The *actual output swing* of a *real op-amp* is *never between rail-to-rail*
- Refer to the *op-amp schematic*, in conjunction with the *schematics* of the *gain stage* and the *output stage*
- As V_{i2} of the *gain stage* becomes *positive*, V_{o2} ($= V_{i3}$) goes *negative* with a *large gain*
 $\Rightarrow V_2$ and V_0 *follow* V_{i3} due to *emitter follower* (CC) action
- With V_0 *negative*, Q_{14} *turns off*, and Q_{20} *draws current from the load*

- Assuming that Q_{17} can *soft saturate*, and neglecting the *voltage drop* across R_8 , the *minimum possible value* of V_0 :

$$V_0^- = -V_{CC} + V_{CE17}(SS) + V_{EB23A} + V_{EB20} = -13.4 \text{ V}$$

- Note that it is about *two diode drops above* $-V_{CC}$
- Now, for *negative* V_{i2} , V_{02} *swings* to a *large positive value, followed by* V_2 and V_0
- With V_0 *positive*, Q_{20} *turns off*, and Q_{14} *supplies current to load*
- Maximum positive limit* of V_0 is *reached* when Q_{13A} *soft saturates*:

$$V_0^+ = V_{CC} - V_{EC13A}(SS) - V_{BE14} = 14.1 \text{ V}$$

- Note again that it is *lower* than V_{CC} by *little more than one diode drop*
- Also, interesting to note is that the *positive* and *negative* peaks of V_o are *not same*
 \Rightarrow *Maximum possible output swing is asymmetric*
- These *two limits* of V_o are known as *positive and negative saturation voltages* (V_{SAT}^+ and V_{SAT}^- respectively)
- If the *input drive* to the *op-amp* and the *gain* are such that the *magnitude* of V_o becomes *greater* than either V_{SAT}^+ or $|V_{SAT}^-|$, then V_o would get *clipped* at either of these *two values*

➤ *Minimum Allowed Supply Voltage:*

- Circuit for 741 is *extremely robust*, and can be *operated* with a *very wide range* of *supply voltage*
- However, there is a *lower limit* of the *supply voltage*, below which it *can't be ensured* that *all transistors* operate in the *FA region*
- To find this, look for the *branch* containing the *most number of transistors*, since *that branch* would obviously *need the largest voltage* across it to *ensure* that all its *constituent transistors operate in the FA region*
- From the *circuit schematic* of 741, *this branch* can be very easily identified to be *either of the two sections of the input stage*

- Considering the *left branch*, neglecting the *potential dropped* across R_1 , and not letting *CE voltage* of any of the *transistors* to *drop below* 0.7 V (*onset of saturation*), there would *four diode drops* (~ 2.8 V) *along this branch*
 - \Rightarrow *741 should work satisfactorily for power supply all the way down to about ± 3 V*
 - \Rightarrow *Under this power supply, V_o^+ and V_o^- will be 2.1 V and -1.4 V respectively*
- Thus, there is a *wide range* of *power supply*, *starting from ± 3 V*, for which *741 should work satisfactorily*
 - \Rightarrow *Shows the robustness of the circuit*

➤ *Slew Rate and Full-Power Bandwidth:*

- This *limitation* is *observed* under *large-signal operation*, when the *input signal swing* is *greater* than the *linear range* of the *input differential pair*
- *Recall*: The *linear range* of a *bipolar differential pair* is $\sim \pm 4V_T$
- *Beyond this*, it basically *acts like a switch*, *transferring the bias current between the two branches*, *depending on the sign of the input voltage*
- Under such cases, the *compensation capacitor* C_C *limits* the *maximum possible rate of change* of V_0
- This is known as the *Slew Rate* (SR) of the op-amp:
$$SR = (dV_0/dt)_{\max}$$


- **Two** SRs are defined: SR^+ (*positive SR*) and SR^- (*negative SR*) for *positive* and *negative* excursions of V_0 respectively, generally expressed in $V/\mu sec$
- A *rough estimate* of these quantities can be obtained by referring to the *schematic* of the op-amp
- Assume that a *large negative signal* is applied at the *base* of Q_1 (w.r.t. the base of Q_2)
- This will instantly turn the Q_1 - Q_3 branch *off*
 $\Rightarrow Q_5$, and thus, Q_6 , *turn off*
 \Rightarrow *Entire bias current* I_{C8} would *flow through* the Q_2 - Q_4 branch, and *start to charge* C_C

- Note that the *rate of this charging* would be *constant* (*constant current charging*)
 \Rightarrow *Collector potential* of Q_{17} would *increase linearly with time*
- Due to *emitter follower* action of Q_{23A} and Q_{14} , V_0 would also start to *increase linearly with time*
 - ❖ Q_{20} *remains off*, since V_0 is in its *positive excursion*
- Thus:

$$SR^+ = I_{C8}/C_C = (19 \mu A)/12.5 \text{ pF} = 1.52 \text{ V}/\mu\text{sec}$$
- If the *frequency* of the *input signal* is such that the *required time rate of change* of V_0 is *more* than this, then V_0 *won't be able to follow* the input – rather, it will be *dictated* by the SR^+ , and will *change linearly with time*

- Similarly, when a *large positive signal* is applied at the *base* of Q_1 (w.r.t. the base of Q_2), Q_2 - Q_4 branch would *instantly turn off*
 - \Rightarrow *Entire bias current* I_{C8} would *flow* through the Q_1 - Q_3 *branch*, *pushing the same current* through Q_5
 - \Rightarrow Q_6 would *carry the same current* (*mirror* with Q_5)
- This *current* would *flow* from the *output node* through C_C to Q_6
 - \Rightarrow C_C would *start to discharge*, and V_0 would *start to fall*, going into its *negative swing*
- Since the *same current* (I_{C8}) is used to *discharge* the *output node*:

 
$$SR^+ = SR^- = 1.52 \text{ V}/\mu\text{sec}$$




Slew Rate Limitation of Op-Amps

- Situation becomes *more dramatic* if a *sinusoidal signal* is applied at the *non-inverting input* of the op-amp, connected in a *voltage-follower* configuration
- Let *input signal* $V_i = V_M \sin(\omega t)$, with *large* V_M
 \Rightarrow *Transistors* in the *differential input stage* act as *switches*
- Under *unity feedback*, V_o would *follow* V_i
 $\Rightarrow dV_o/dt = dV_i/dt = V_M \omega \cos(\omega t)$
- The *maximum value* of this *derivative* occurs when $\omega t = n\pi$ ($n = 0, 1, 2, \dots$)
 \Rightarrow It occurs when the *signal crosses zero*
- So long as *this rate* remains *smaller* than SR, V_o would *follow* V_i with *fidelity*


- However, as soon as dV_0/dt becomes $\geq SR$, V_0 won't be able to follow V_i anymore – rather, it would start to become triangular
- **Note:** $dV_0/dt \uparrow$ with an increase of either V_M or ω or both
 - \Rightarrow What essentially matters is the product $V_M \omega$
- If this product keeps on increasing beyond the SR, then V_0 remains triangular, however, two major observations become apparent:
 - ❖ The zero crossings of V_0 do not quite coincide with those of V_i
 - ❖ The peak-to-peak swing of V_0 starts to become smaller than that of V_i due to V_0 not getting enough time to reach its maximum possible value

 

Normal Behavior

 

Onset of Slew Rate Limitation

 

Severely Slew Rate Limited

- If $V_M\omega$ becomes *very large*, then there *may not be any output at all*
 - $\Rightarrow V_0$ would *become zero*, implying that the op-amp is *not able to keep up with the variation* of V_i at all!
- *Mathematical Description:*
 - ❖ Let the *gain* of the op-amp = A
 - $\Rightarrow (dV_0/dt)_{\max} = AV_M\omega$
 - ❖ This must be *less* than the SR of the op-amp to get a *distortion-free output*
 - ❖ *Maximum possible value* of $AV_M = V_{SAT}$
 - \Rightarrow The *maximum allowed value* of ω ($= \omega_M$) of V_i for V_0 to be *without any distortion* due to *slew rate limitation*:

$$\omega_M = SR/V_{SAT}$$

- This is an *extremely important relation*, and ω_M is referred to as the *full-power bandwidth*
- It is a *constant* for a given op-amp
- This *derivation* is for V_0 *swinging* between $\pm V_{SAT}$
- If the *swing* of V_0 is *less* than this, then ω can be *increased* beyond ω_M , following the *relation*:

$$SR = \omega_M V_{SAT} = \omega_0 V_0 = \omega_0 A V_i$$

ω_0 : *Frequency till which V_0 won't have any slew rate limited distortion*

\Rightarrow *Maximum amplitude* of V_i (of *frequency* ω_0), beyond which *slew rate limited distortion* would *set in at the output*:

$$V_{i,max} = \omega_M V_{SAT} / (\omega_0 A)$$

