

Small-Signal Model Parameters

- **Transconductance** (g_m):

$$g_m \triangleq \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS} \text{ and } V_{SB} \text{ constant}}$$
$$= k_N V_{GT} (1 + \lambda V_{DS}) = \sqrt{2k_N I_D (1 + \lambda V_{DS})}$$

➤ *If $\lambda V_{DS} < 0.1$:*

$$g_m \approx k_N V_{GT} \approx \sqrt{2k_N I_D}$$

- An important *Figure of Merit* is *transconductance to current ratio*
 - For *MOSFETs*: $g_m/I_D = 2/V_{GT}$
 - For *BJTs*: $g_m/I_C = 1/V_T$
 - Thus, *BJTs produce more g_m per unit current*
- As we will see later, a *high value of g_m is highly desirable*, since it *dictates the gain*
- *g_m/I_D can be changed by changing the bias current and/or aspect ratio*
- *g_m/I_C is a function only of temperature*

- **Body Transconductance** (g_{mb}):

$$g_{mb} \triangleq \left. \frac{\partial I_D}{\partial V_{BS}} \right|_{V_{GS} \text{ and } V_{DS} \text{ constant}} = \chi g_m$$

$$\chi = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}} = \textit{Body factor} \quad (\sim 0.1-0.3)$$

- *Note: As $V_{SB} \uparrow$, $V_{TN} \uparrow \Rightarrow I_D \downarrow$*
- *$\partial I_D / \partial V_{SB}$ would have yielded negative g_{mb}*
- *If both B and S are tied to fixed DC potentials (including ground), g_{mb} won't matter!*

- **Output Conductance** (g_0)/

Output Resistance (r_0):

$$g_0 = r_0^{-1} \triangleq \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{GS} \text{ and } V_{SB} \text{ constant}} = \frac{\lambda I_D}{1 + \lambda V_{DS}}$$

➤ *If $\lambda V_{DS} < 0.1$:*

$$g_0 = 1/r_0 \approx \lambda I_D$$

➤ *λ has a very wide range ~ 0.01 - 0.5 V^{-1}*

➤ *When $\lambda \rightarrow 0$, $g_0 \rightarrow 0$, and $r_0 \rightarrow \infty$*

- *Device starts to behave like a constant current source*