

## Tutorial - 9

1. Consider a 20 kVA, 2200/220 V, 50 Hz, single phase transformer. Core loss at rated voltage and copper loss at 80% of the full load of this transformer are 200 W and 500 W, respectively. Calculate the percentage efficiency of the transformer if the output power at the LV side of the transformer is 10 kVA at 0.9 pf lagging.

Solution -

① 20 kVA, 2200/220 V, 50 Hz, 1- $\phi$  Transformer

$P_{\text{core}}$  (at rated voltage) = 200 W

$P_{\text{cu}}$  (at 80% of rated current) = 500 W

Since  $P_{\text{cu}} \propto I^2$

$\therefore P_{\text{cu}} (\text{full load}) = P_{\text{cu}} (80\%) \times \frac{1^2}{0.8^2} = 781.25 \text{ Watts}$


$\therefore$  at 10 kVA at 0.9 lagging,

$x = \left( \frac{10}{20} \right) = 0.5$

$\therefore \eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{core}} + x^2 \times P_{\text{cu}} (\text{full-load})}$

$\% \eta = \frac{10,000 \times 0.9 \times 100}{10,000 \times 0.9 + 200 + 781.25 \times (0.5)^2} = 95.73 \%$

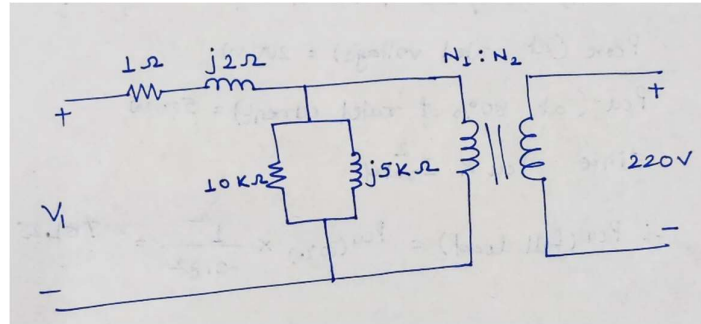2. The equivalent circuit for a 50 kVA, 2200/220 V, 50 Hz single-phase transformer is shown in figure below. Assume that the transformer is operating at rated secondary voltage and rated apparent power with a 0.8 power factor (lagging). Estimate the copper loss in watts.



Solution –

②

50 kVA, 2200/220 V, 50 Hz, 1- $\phi$  transformer

$$\text{Iron Loss} = \frac{E_1^2}{R_c} = \frac{2200^2}{10 \times 10^3} = 484 \text{ Watts}$$

$$\text{Rated Secondary Current, } I_2 = \frac{S_{\text{rated}}}{V_2} = \frac{50 \times 10^3}{220} = 227.27 \text{ Amp}$$

pf is given as 0.8 lagging  $\therefore \bar{I}_2 = 227.27 \angle -36.86^\circ \text{ Amp}$

$$\text{Load current referred to HV side, } \bar{I}_2' = \frac{220}{2200} \times \bar{I}_2 = 22.727 \angle -36.86^\circ \text{ Amp}$$

$$\text{Exciting current, } \bar{I}_e = \frac{2200 \angle 0^\circ}{10 \times 10^3} + \frac{2200 \angle 0^\circ}{j5 \times 10^3} = (0.22 - j0.44) \text{ Amp}$$

$$\text{Primary H.V. current } \Rightarrow \bar{I}_1 = \bar{I}_e + \bar{I}_2' = 23.168 \angle -37.4^\circ \text{ Amp}$$

$$\therefore \text{Cu losses, } P_{cu} = 23.168^2 \times 1 = \underline{\underline{536.756 \text{ Watts}}}$$


3. An 11500/2300 V transformer is rated at 100 kVA as a 2-winding transformer. If the windings are connected in series to form an autotransformer, what will be the maximum output power in kVA?

Solution -

For two winding transformer,

Rated current for 11500 V winding =  $\frac{100 \times 1000}{11500} = 8.696 \text{ Amp}$

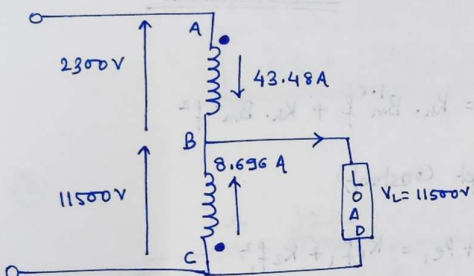Rated current for 2300 V winding =  $\frac{100 \times 1000}{2300} = 43.48 \text{ Amp}$



$V_{AB} = 2300 \text{ V}, V_{BC} = 11500 \text{ V}$


$\therefore V_H = V_{AB} + V_{BC} = 13800 \text{ V}$

$V_L = V_{BC} = 11500 \text{ V}$

Vtg transformation Ratio =  $\frac{V_H}{V_L} = \frac{13800}{11500} = \frac{6}{5}$

Load current =  $43.48 + 8.696 = 52.176 \text{ Amp}$

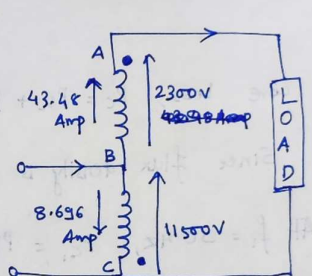power output =  $52.17 \times 11500 = 600 \text{ KVA}$



$V_{BC} = 11500 \text{ V}, V_{AB} = 2300 \text{ V}$

$\therefore V_H = V_{AB} + V_{BC} = 13800 \text{ V}$

$V_L = V_{BC} = 11500 \text{ V}$


$\therefore$  Vtg transformation ratio =  $\frac{13800}{11500} = \frac{6}{5}$

Load current = 43.48 Amp

$\therefore$  Power output =  $13800 \times 43.48 = 600 \text{ KVA}$

4. A 3-phase delta-wye transformer has an induced emf of 6000 V on the delta-connected side. The secondary side is supplying full load current at a power factor 0.8 (lag). The line voltage at secondary is 415 V. The resistance and reactance of the winding is 1% and 5% respectively. Find the turns ratio of the transformer to the nearest integer.

Solution -

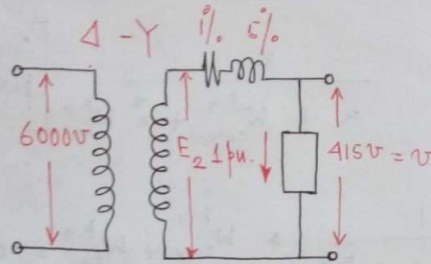

taking 415 V as 1 pu. voltage, the current will be  $1 \angle -\cos^{-1} 0.8$  p.u.

$$\begin{aligned} \text{induced emf} = E_2 &= V + I(R + jX) \\ &= 1 \angle 0^\circ + 1 \angle -36.87^\circ \times (0.01 + j0.05) \text{ p.u.} \\ &= 1.038 \angle 1.876^\circ \text{ p.u.} \end{aligned}$$

$$|E_2| = (1.038 \times 415) \text{ V} = 430.77 \text{ Volt}$$

Since, the secondary side is Y-connected,

$$|E_2|_{\text{ph}} = \frac{430.77}{\sqrt{3}} \text{ Volts} = 248.7 \text{ Volts}$$

$$\begin{aligned} \therefore \text{turns ratio} &= \frac{6000}{248.7} = 24.12 \\ &\approx 24 \text{ (Ans)} \end{aligned}$$