

**DEPARTMENT OF ELECTRICAL ENGINEERING  
INDIAN INSTITUTE OF TECHNOLOGY, KANPUR**

**EE 210**

**MINI-QUIZ #10B**

**28.4.21**

**Total Marks: 10**

**Total Time: 10 mins.**

The biasing circuits are omitted for simplicity. Use the technique of Miller Effect Approximation. Neglect body effect and CLM effect.

a) Choose  $R_2$  such that the pole frequency of the input circuit is 5 MHz.

b) Hence, find the pole frequency of the output circuit.

c) What is the gain-bandwidth product (GBP) of the circuit?

Data for M:  $g_m = 100 \mu\text{A/V}$ ,  $C_{gs} = 25 \text{ pF}$ ,  $C_{gd} = 1 \text{ pF}$ ,  $C_{sb} = 0.2 \text{ pF}$ ,  $C_{db} = 0.1 \text{ pF}$ .

