

Soln

1. If w; x; y; z are switches 1,2,3,4 respectively, you will get the function as $f = x \bar{y}z + wyz$.

2. Let
 A = Fair Weather
 B = Instrument Capability
 C = Air Controllers Strike
 D = Take Off

Rest states are don't care: $D = A \bar{C} + B \bar{C} = \bar{C}(A+B)$

AB C	00	01	11	10
	0	0	1	1
B \bar{C}	1	0	0	0

3. Implement using 3X8 decoder and 3 input OR gate


$$X = \bar{A}\bar{C} + B \bar{C} = A \bar{B}\bar{C} + B \bar{C}(A + \bar{A}) = A \bar{B}\bar{C} + AB \bar{C} + \bar{A}B \bar{C}$$

$$Y = \bar{B}\bar{C} + A \bar{C} = \bar{B}\bar{C}(A + \bar{A}) + A \bar{C}(B + \bar{B}) = A \bar{B}\bar{C} + \bar{A} \bar{B}\bar{C} + AB \bar{C} + A \bar{B} \bar{C}$$

$$Z = AB \bar{C} + \bar{A}B = AB \bar{C} + \bar{A}B(C + \bar{C}) = A \bar{B}\bar{C} + \bar{A}BC + \bar{A}B \bar{C}$$

Use 3-input OR for X and Z and Two 3-input OR gates for Y.

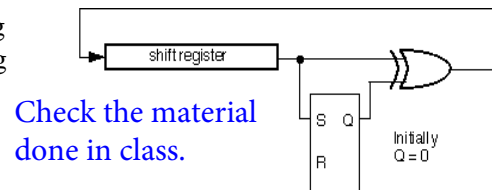4. The 2's complement of a binary number can be formed by leaving all least significant 0's and the first 1 unchanged and complementing all other higher significant bits. The circuit needs a shift register to store the binary number and an RS flip-flop to be set when the first least significant 1 occurs. An exclusive-OR gate can be used to transfer the unchanged bits or complement the bits.



5. (a) Use an XOR of S&R and AND it with Ck (i.e. same status as the 0,0 inputs) to send to the Ck input to the SR-latch.

5 (b) From the truth table shown of JK Flip-Flop, $Q_{n+1}=1$ for rows 3 ($J_n=1, K_n=0$) and row 4 (for $Q_n=0$) Or $Q_{n+1}=(\text{row3\&4}) Q_{n+1} = \bar{Q}_n J_n (\bar{K}_n + K_n)$. Again

$Q_{n+1} = Q_n \bar{K}_n (J_n + \bar{J}_n)$ from Row 1 (for $Q_n=1$) and 3.


Hence $Q_{n+1} = \bar{Q}_n J_n + Q_n \bar{K}_n$.

J_n	K_n	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n

6.

Characteristic table of J-k flip flop

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

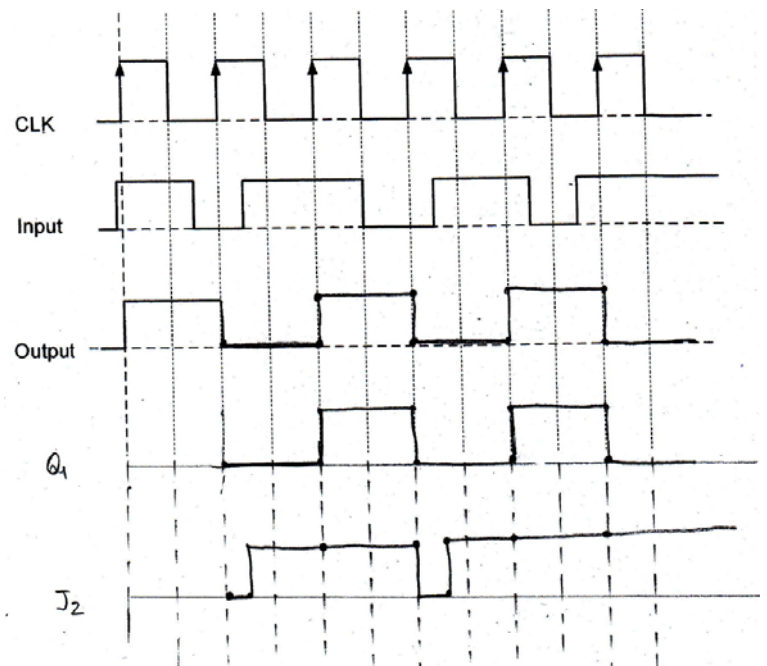

7.

Excitation Table for D F/F

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

State Transition Table

Present state $Q_A(t) \quad Q_B(t) \quad Q_C(t)$			Next state $Q_A(t+1) \quad Q_B(t+1) \quad Q_C(t+1)$			Inputs $D_A \quad D_B \quad D_C$		
0	1	0	1	1	0	1	1	0
1	1	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	1
0	1	1	0	1	0	0	1	0

D_A Q_A Q_B Q_C

Q_A	00	01	11	10
0	X	0	0	1
1	X	X	X	0

$$D_A = \bar{Q}_A \bar{Q}_C$$

D_B Q_A Q_B Q_C


Q_A	00	01	11	10
0	X	1	1	1
1	X	X	X	0

$$D_B = \bar{Q}_A$$



D_C Q_A Q_B Q_C

Q_A	00	01	11	10
0	X	1	0	0
1	X	X	X	1

$$D_C = Q_A + Q_B$$

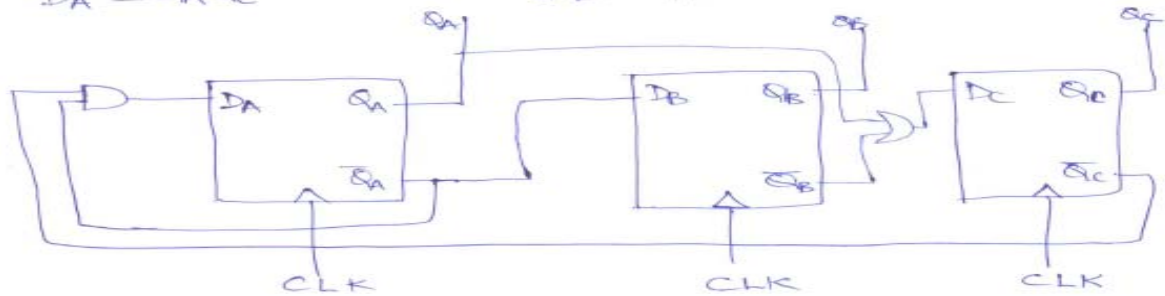

8.

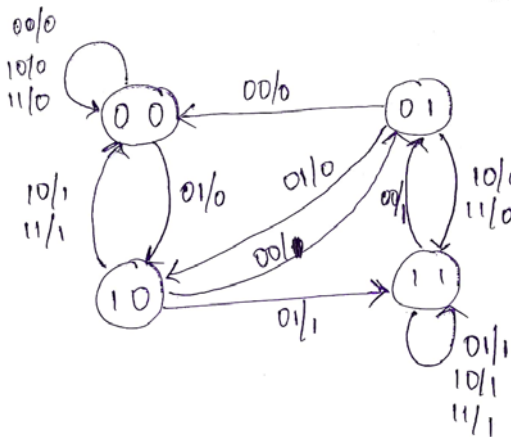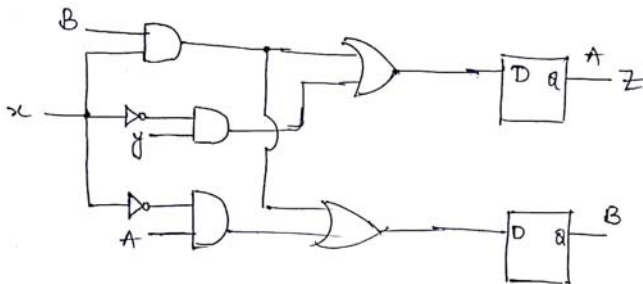

present state		output		Next state		
A	B	x	y	A	B	Z
0	0	0	0	0	0	0
0	0	0	1	1	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	0	1	1	0	0
0	1	1	0	1	1	0
0	1	1	1	1	1	0
1	0	0	0	0	1	1
1	0	0	1	1	1	1
1	0	1	0	0	0	1
1	0	1	1	0	0	1
1	1	0	0	0	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

9.


Required

X	Y	Q_{n+1}	J	K
1	0	Q_n	0	0
0	1	1	1	0
1	1	0	0	1
0	0	\bar{Q}_n	1	1


Express J & K in terms of X & Y

$J = \bar{X}$

$K = \bar{X}\bar{Y} + XY$

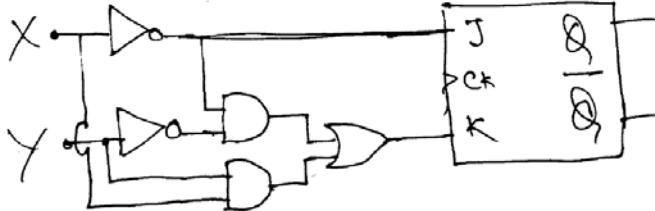

10.

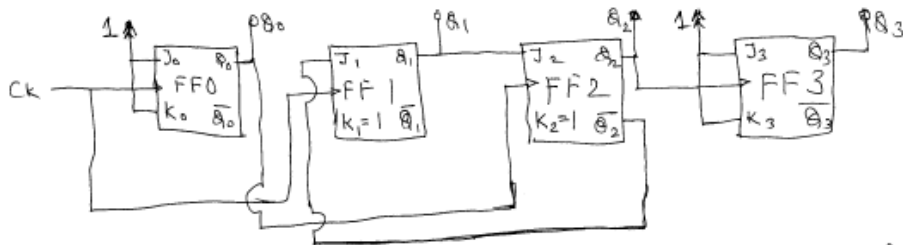

	Q_3	Q_2	Q_1	Q_0	J_0	K_0	Ck_0	$J_1 = \bar{Q}_0$	K_1	Ck_1	$J_2 = \bar{Q}_1$	$K_2 = 1$	$Ck_2 = Q_0$	$J_3 = 1$	$K_3 = 1$	$Ck_3 = Q_2$
Pulse 1	0	0	0	0	1	1	0	1	1	0	1	1	0	1	1	0
Pulse 2	0	0	1	1	1	1	1	0	1	1	0	1	0	1	1	0
Pulse 3	0	1	0	0	1	1	2	0	1	2	0	1	0	1	1	1
Pulse 4	1	1	0	1	1	1	3	0	1	3	0	1	1	1	1	1
	0	0	0	0	1	1	4	1	1	4	0	1	0	1	1	0
	0	0	1	1	1	1	5	1	1	5	1	1	1	1	1	0
	0	1	0	0	1	1	6	0	1	6	0	1	0	1	1	1
	1	1	0	1	1	1	7	0	1	7	0	1	1	1	1	1
	0	0	0	0												

Count of 4

11.

Present state			Next state					
A	B	C	A	B	C	T_A	T_B	T_C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	1	1	1	1	1	0	0
1	1	1	1	1	0	0	0	1
1	1	0	1	0	0	0	1	0
1	0	0	0	0	0	1	0	0

$T_A = \bar{A} \cdot B + A \cdot \bar{B}$

$T_B = \bar{B} \cdot C + B \cdot \bar{C}$

$T_C = \bar{A} \cdot \bar{C} + A \cdot C$

12.

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Time n			Time $n+1$			Required inputs					
Q_A	Q_B	Q_C	Q_A	Q_B	Q_C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	1	0	0	X	1	X	0	X
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	1	0	X	0	1	X	0	X
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	1	0	1	X	0	X	1	X	0
1	0	1	0	1	1	X	1	1	X	X	0
0	1	1	0	0	1	0	X	X	1	X	0
0	0	1	0	0	0	0	X	0	X	X	1
0	0	0									

$Q_A Q_B$		Q_C			
		00	01	11	10
0		0	1	X	X
1		0	0	X	X

$$J_A = Q_B \bar{Q}_C$$

$Q_A Q_B$		Q_C			
		00	01	11	10
0		X	X	0	0
1		X	X	0	1

$$K_A = \bar{Q}_B Q_C$$

$Q_A Q_B$		Q_C			
		00	01	11	10
0		1	X	X	1
1		0	X	X	1

$$J_B = Q_A + \bar{Q}_C$$

$Q_A Q_B$		Q_C			
		00	01	11	10
0		X	1	0	X
1		X	1	1	X

$$K_B = \bar{Q}_A + Q_C$$

$Q_A Q_B$		Q_C			
		00	01	11	10
0		0	0	1	0
1		X	X	X	X

$$J_C = Q_A Q_B$$


$Q_A Q_B$		Q_C			
		00	01	11	10
0		X	X	X	X
1		1	0	0	0

$$K_C = \bar{Q}_A \bar{Q}_B$$

13

The Reset button is an active high reset so it resets all flip flops to 0 when Reset = 1. The 6 stable states of the above counter are:
Note that the Master-slave J-K flip-flops will change state on the negative edge of the clock pulse. So when a preceding Q changes state from 0 to 1 no toggle of the flip-flop results but when the preceding Q changes state from 1 to 0 the flip-flop toggles its output state.

Q_{2n}	Q_{1n}	Q_{0n}	Q_{2n+1}	Q_{1n+1}	Q_{0n+1}
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	0	0	0

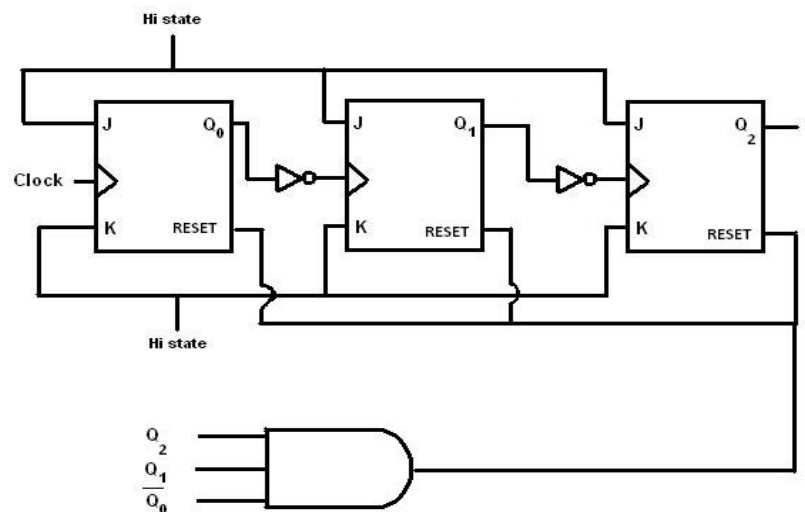

14.

Ans: We need a divide by 10 counter. So, 4 FFs are required. A possible state transition of the counter:

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1
1	0	0	0
1	0	0	1

Present state				Next state							
A	B	C	D	A	B	C	D	T _A	T _B	T _C	T _D
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	1	0	1	1	1	0	0	1
0	0	1	1	1	1	0	0	0	1	1	1
1	0	1	1	1	1	0	1	0	0	0	1
1	1	0	0	1	1	1	0	0	0	1	1
1	1	0	1	1	1	1	1	0	0	0	1
1	1	1	0	1	1	1	1	0	1	1	1
1	1	1	1	1	0	0	0	0	1	1	1
1	0	0	0	1	0	0	1	0	0	0	1
1	0	0	1	0	0	0	0	1	0	0	1

$T_D = 1$


FFA output will have the required waveform,

AB		CD				AB		CD				AB		CD			
		00	01	11	10			00	01	11	10			00	01	11	10
00	00	0	0	X	1	00	00	0	0	X	0	00	00	0	0	X	0
01	01	X	X	X	X	01	01	X	X	X	X	01	01	X	X	X	X
11	11	0	0	0	0	11	11	0	0	1	0	11	11	0	0	1	0
10	10	0	1	0	X	10	10	0	0	1	X	10	10	0	0	1	X

$$T_A = \bar{A}C + A\bar{B}\bar{C}D$$

$$T_B = CD$$

$$T_C = CD + BD + \bar{A}D$$

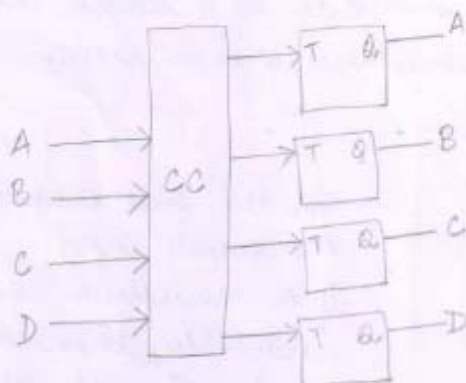

The combinational circuit can be synthesized using the derived expressions.