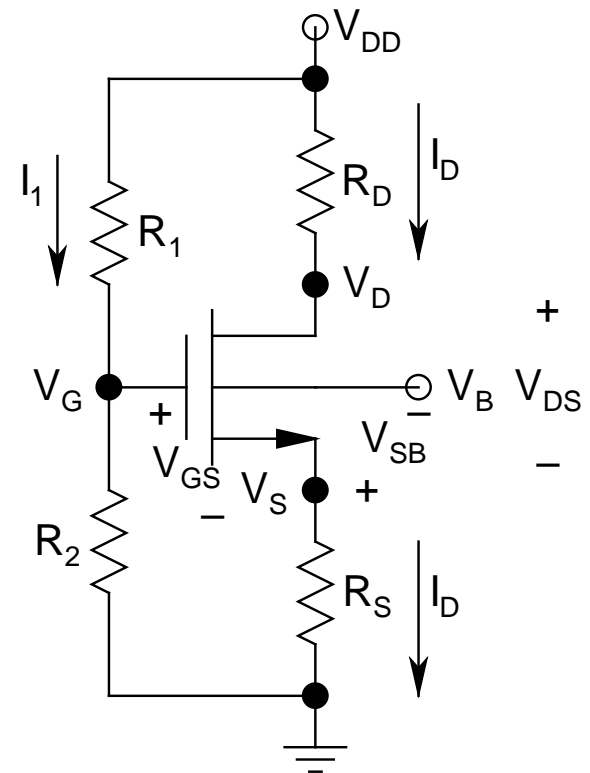


Discrete Stage Biasing: MOSFET

- *Almost universally biased using 4-Resistor Bias*
- *Significantly more complicated than BJT biasing, since there is no quick estimate*
- *Also, body effect and CLM complicate matters*



- **No I_G** \Rightarrow *R_1 - R_2 combination provides a perfect voltage division*

$$\Rightarrow V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

- $V_S = I_D R_S$ and $V_D = V_{DD} - I_D R_D$

$$\Rightarrow I_D = \frac{k_N}{2} (V_G - I_D R_S - V_{TN})^2 \times \\ \left(1 + \lambda [V_{DD} - I_D (R_S + R_D)] \right)$$

- Also:

$$V_{\text{TN}} = V_{\text{TN0}} + \gamma \left(\sqrt{2\phi_F + I_D R_S - V_B} - \sqrt{2\phi_F} \right)$$

- *Extremely intimidating!*
- *I_D equation becomes cubic!*
- *Thus, bias calculation including all higher order effects is pretty tedious, and almost impossible for hand analysis*
- *Need to make approximations!*

- Assume $\lambda V_{DS} < 0.1$:

$$\Rightarrow I_D = \frac{k_N}{2} (V_G - I_D R_S - V_{TN})^2$$

- *Even then it's quite complicated, since V_{TN} has a square root dependence on I_D*
- *Tie B and S together* $\Rightarrow V_{SB} = 0$ and $V_{TN} = V_{TN0}$

➤ *Note that it can't be done always!*

$$\Rightarrow I_D = \frac{k_N}{2} (V_G - I_D R_S - V_{TN0})^2$$

- *Even now, it's a quadratic equation in I_D*
- *However, much easier to solve than earlier cases*
- *No further simplification possible!*
- *Solving, we will get 2 values of I_D : one will be the correct one, while the other one will be unphysical*
- *2 values of I_D will give 2 different values of V_{GS} : one $> V_{TN0}$ and the other $< V_{TN0}$*

- *Obviously, I_D for $V_{GS} < V_{TN0}$ is completely meaningless, since the device is off under that condition*
- Compute $V_{DS} [= V_{DD} - I_D(R_S + R_D)]$
 - *Should be $> V_{GT}$ (saturation mode)*
 - *For BB, $V_{DS} = V_{DD}/3$*
- $P_D = V_{DD} \times (I_D + I_1) \quad [I_1 = V_{DD}/(R_1 + R_2)]$
- *Here, no constraints on R_1 and R_2 , and they can be made as large as physically possible to reduce I_1 , and thus P_D*

IC Stage Biasing

- *Avoids resistors as much as possible*
 - *Resistors take up very large area on IC chips, which is at a premium*
- *Uses transistors as biasing elements*
 - *Much more compact than resistors, and area consumption is almost negligible as compared to resistors*
- Also known as *active biasing*

- **Parameters:**

- **Output Current I_0**

- *As per specification*

- **Output Resistance R_0**

- $R_0 = \Delta V_0 / \Delta I_0 = dV_0 / dI_0 = v_0 / i_0$ (**ac**)
- *As large as possible - ideally infinite*

- **Minimum Allowed Output Voltage $V_{0,min}$**

- *As small as possible - ideally zero*
- **Dictated by:**
 - ❖ **For BJT:** $V_{CE(min)} = V_{CE(SS)} = 0.2 \text{ V}$
 - ❖ **For MOSFET:** $V_{DS(min)} = V_{GT(min)} = 80 \text{ mV}$