

OUTPUT STAGES

- *Main Purpose:*
 - *To drive load with sufficient current*
- Both *BJT* and *MOS* output stages available
- *BJT* output stages preferred due to their *large current handling capability*
- *BiMOS* circuits use *MOS* devices in the *core* of the circuit, while using *BJT* devices in the *output* stage
 - *Best of both worlds!*

- **Requirements:**
 - **Sufficient drive current/power transfer to load**
 - **Low output distortion**
 - **Ideal voltage source:**
 - **Thevenin equivalent: V_0 with $R_0 \rightarrow 0$**
 - **Voltage gain A_v independent of load**
 - **Ideally unity with no phase shift**
 - **Low Standby (or Idling) Power**
 - **While not driving any load**
 - **Should not degrade frequency response**

➤ *High power conversion efficiency η*

▪ $\eta = (\text{average power delivered to load}) / (\text{average power drawn from supply})$

• *Classification:*

➤ *Depends on the conduction angle (θ)*

▪ θ : Angle over the complete cycle (360°) for which either both or one of the output transistors are/is on

➤ *Class A:*

▪ $\theta = 360^\circ$ and $\eta_{max} = 25\%$ (*large standby power*)

➤ *Class B:*

▪ θ slightly less than 180° and $\eta_{max} = 78.5\%$ (*zero standby power*)

- **Class AB:**
 - $\theta = 180^\circ$ and $\eta_{max} \approx 78.5\%$ (*very small standby power*)
- **Class C:**
 - $\theta \ll 180^\circ$ (*used in RF applications*)
- There are *other classes* also, namely **D**, **E**, **F**, **G**, and **H**
 - Used only in *special cases*, e.g., *pulse width modulated input*, *lowering of distortion*, etc.
- In this course, we shall be discussing only about **Class B** and **Class AB** output stages

- ***Class B:***

- Uses ***complementary*** set of output transistors (***nnp and pnp, NMOS and PMOS***)
- One takes care of the ***positive half cycle***, while the other takes care of the ***negative half cycle***
- ***θ slightly less than 180° for each***
- ***Both output devices never ON simultaneously***
 - ***Zero standby power (significant advantage)***
- Also known as ***Push-Pull Stage***

- During *positive half cycle*, the stage *pushes current through load*
- During *negative half cycle*, the stage *pulls current away from load*
- *Very high η_{max} of 78.5%*
- However, there is a *very big limitation*, known as *Crossover Distortion*
 - Also known as *Deadband Distortion*
 - *Occurs during zero crossings of the signal*
 - *For BJT/MOS Class B stage*, the *input voltage must at least equal V_γ ($\sim 0.6\text{ V}$)/ $V_{TN}(|V_{TP}|)$ ($\sim 0.7\text{-}1\text{ V}$)* for the *output stage transistors to turn on*

- *Class AB:*
 - *Eliminates Crossover Distortion* by *prebiasing the output transistors*
 - *They remain at the verge of conduction in the standby stage*
 - *θ exactly equal to 180°*
 - *η_{max} slightly less than 78.5% due to a small amount of standby power*
 - *Extremely popular and most widely used*