

➤ Pole p_1 (p_2) is referred to as the pole of the *input* (*output*) circuit

➤ Also, $|p_1| \ll |p_2|$

$\Rightarrow p_1$ (p_2) is the *DP* (*NDP*) of the system

➤ *Matching coefficients:*

$$p_1 = -\frac{R_S + r_\pi}{R_S r_\pi} \frac{1}{C_T} = -\frac{1}{(R_S \parallel r_\pi) [C_\pi + (1 + g_m R_L) C_\mu]}$$

$$p_2 = -\frac{1}{R_L C'_M}$$

➤ Obviously, $|p_1| \ll |p_2|$

- Thus, *using DPA*: $f_H = |p_1|/(2\pi)$
- Applying *this technique* to the *previous example*, $f_H = 3.9 \text{ MHz}$ and *NDP frequency* = *156 MHz*
 - *Error of only 2.6% in f_H* , but the *ease of solution is much more*
- Thus, *this technique* is *quite popular* in getting a *quick estimate* of f_H , even though the *solution* may not be *exact*
- *Care*: *The gain in the multiplicative factor is that between the input and output terminals of the capacitor*

- *The Zero-Value Time Constant (ZVTC) Technique:*
 - *Gives information only about the DP of the system*
 - *Suppresses all information regarding other poles and zeros*
 - *The ease of application of this technique is mind-boggling*

- *Slightly less accurate*
- *The maximum error can be as high as 22%*
- *Underestimates f_H*
 - *Far better than overestimation and eventually not achieving it*
- *Applicable only for circuits that have a DP*
 - *Fortunately, almost all analog circuits of interest do have a DP*

- *The Algorithm:*
 - *Null all independent sources to the circuit*
 - *Short all independent voltage sources*
 - *Open all independent current sources*
 - *DO NOT TOUCH DEPENDENT SOURCES*
 - *Name the capacitors C_i ($i = 1-n$)*
 - *Consider C_1 and assign zero values to all other capacitors (thus the name!)*
 - Thus, *except C_1 , all other capacitors will open out*
 - *Determine the Thevenin Resistance (R_1^0) across the two terminals of C_1*

- *Find the time constant τ_1 associated with C_1*
 $(\tau_1 = R_1^0 C_1)$
- *Repeat for all other capacitors, taking one at a time, and find all the rest of the time constants $(\tau_2, \tau_3, \dots, \tau_n)$*
- Determine the *net time constant* τ_{net} by *summing up* all the *individual time constants*
$$\Rightarrow \tau_{\text{net}} = \sum_{i=1}^n \tau_i$$
- Then the *Upper Cutoff Frequency* f_H is simply given by: $f_H = 1/(2\pi\tau_{\text{net}})$

- ***Note:** The capacitor contributing the largest time constant, in effect, determines f_H*
- *The technique suppresses all information regarding other poles and zeros*
- Will present *several examples* to understand the *application* of this *technique*
- Some *topologies* will be appearing *frequently*, known as *Standard Forms*, which can be treated as *individual modules*, and the *results can be used freely*