

ESC201T: Introduction to Electronics


Users Online : 26

discussion quiz-2

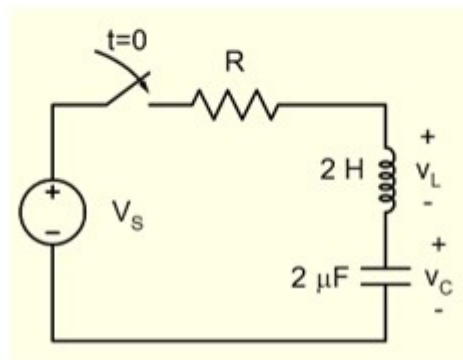Q.1

ESC201T : Introduction to Electronics
Discussion Quiz 2 (30/9/2020)

Q. Determine the value of resistance (in $k\Omega$) below which oscillations in capacitor voltage V_C in the circuit shown below will occur upon closing of the switch.
(Assume that switch is open for a long time and there is zero initial charge on capacitor. Give answer only as an integer)



Your answer:

2

Score: Will be uploaded after end date.