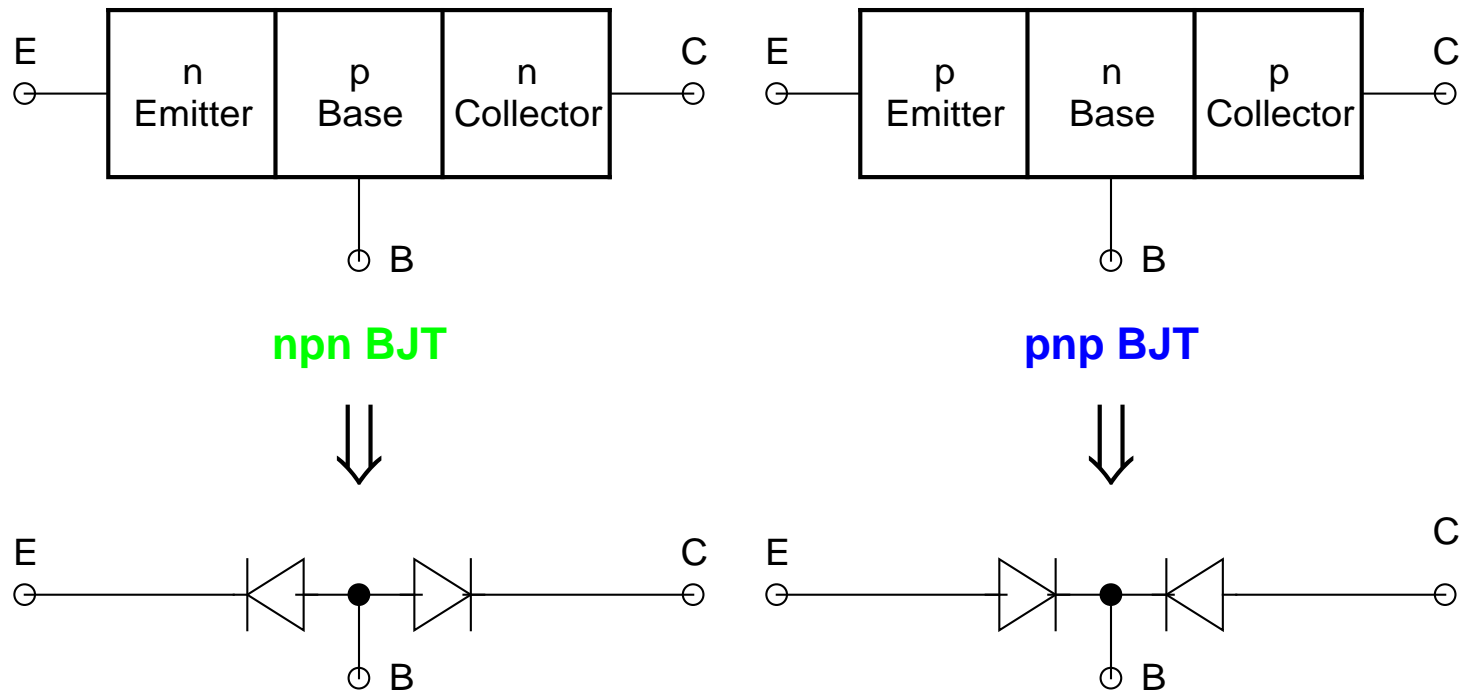


BIPOLAR JUNCTION TRANSISTOR (BJT)

- Basically two *back-to-back diodes*




- Name originates from *transfer of resistor*

- *Three-Layer/Terminal* [*Emitter* (E), *Base* (B), *Collector* (C)] *Two-Junction* [*Base-Emitter* (BE), *Base-Collector* (BC)] device
- Current through *two terminals* (E and C) can be *controlled* by the current through the *third terminal* (B)
 - *Current controlled device*
- *Bipolar device*
 - *Both electrons and holes* participate in *current conduction*

- *Active device*
 - Capable of producing *voltage/current/power gain*
- *Two basic usage:*
 - *Amplification (Analog Circuits)*
 - *Switching (Digital Circuits)*
- *Two Types:*
 - *npn*
 - *pnp*
- *Immensely important device*

Symbols and Current-Voltage Conventions

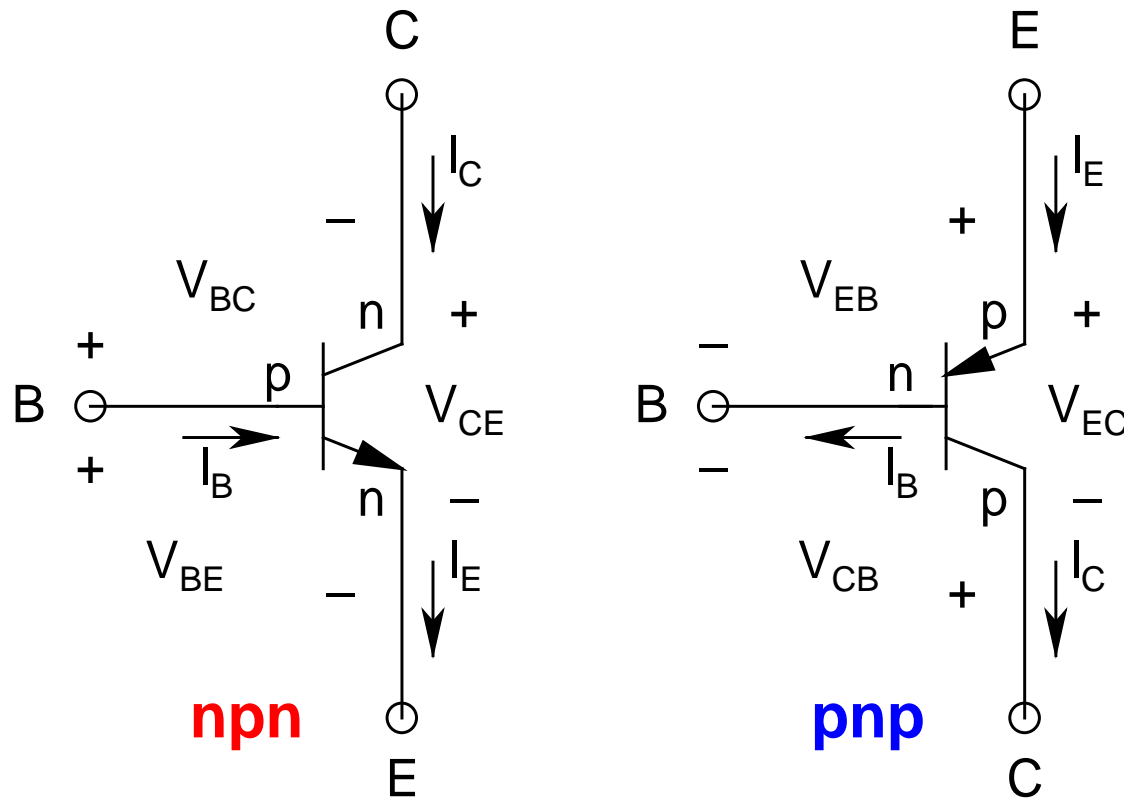

- ***Voltage Convention:***

- ***p-side first:***

- ***Sign of the voltage*** immediately lets us know the ***biasing state*** (***forward or reverse***)

- ***nnp***: V_{BE} (***base-emitter voltage***), V_{BC} (***base-collector voltage***), and V_{CE} (***collector-emitter voltage***)

- ***npn***: V_{EB} (***emitter-base voltage***), V_{CB} (***collector-base voltage***), and V_{EC} (***emitter-collector voltage***)

- ***Note***: ***Collector-Emitter is NOT a junction***

- *Current Convention:*

- *npn:*

- I_C and I_B flow in, I_E flows out

- *pnp:*


- I_E flows in, I_C and I_B flow out

- *Applying KCL*, treating the whole BJT as a *big node*, for *both npn and pnp*:

- $I_E = I_C + I_B$

- *Extremely important KCL for the BJT*

Modes of Operation

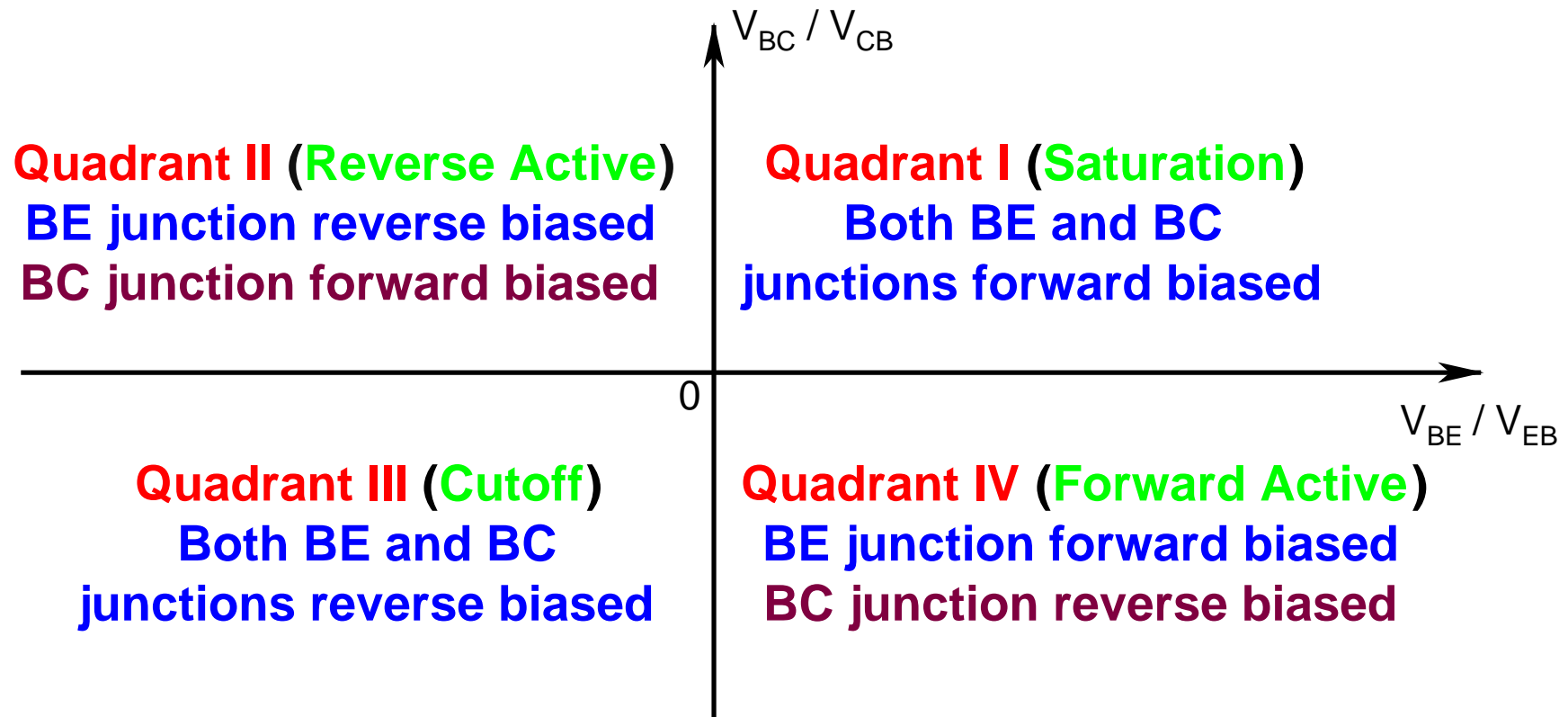


Quadrants III and IV: Analog Domain

Quadrants I and III: Digital Domain

Quadrant II: Finds use only in TTL circuits

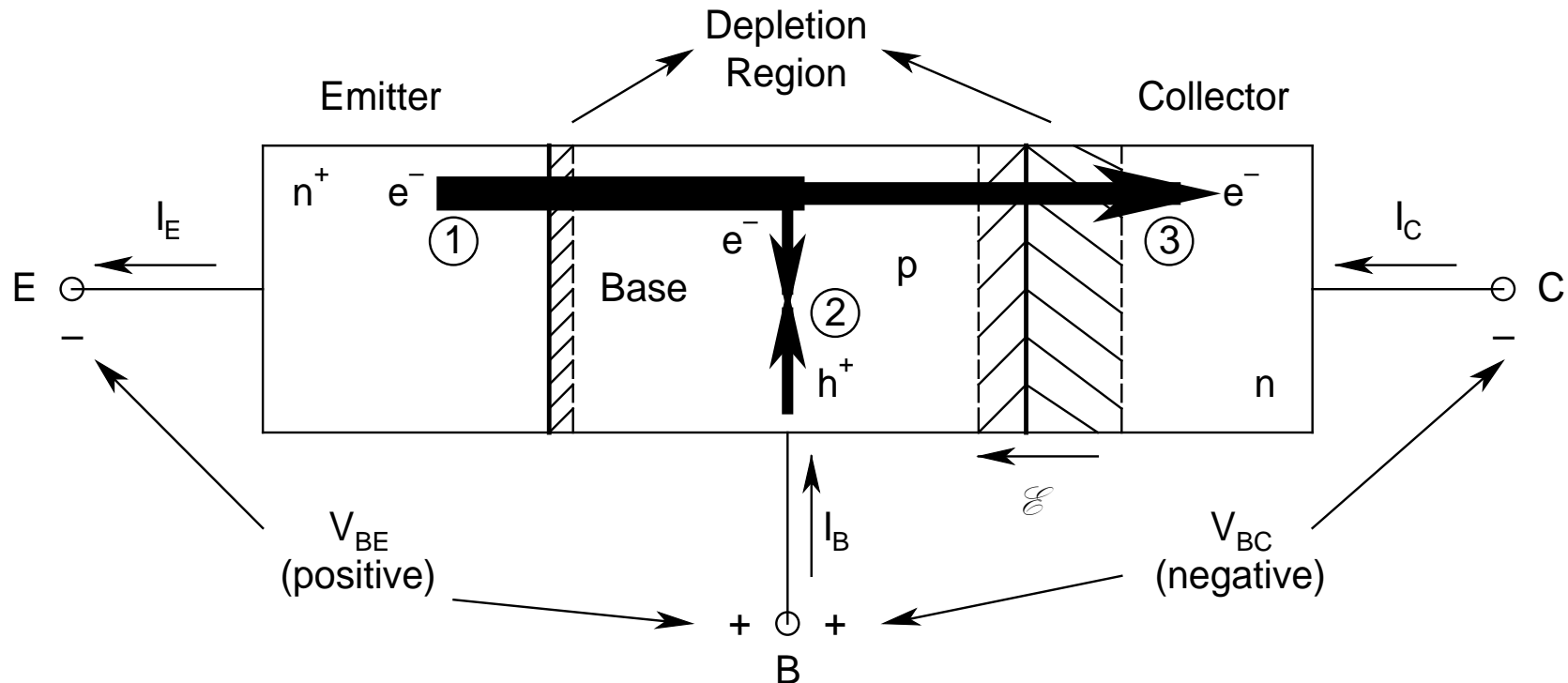Operation in the Forward Active (FA) Mode



① Injection Component, ② Recombination Component, ③ Collection Component

- *BE junction forward biased, BC junction reverse biased*
- *Emitter injects electrons to base*
 - *Supplied by the external terminal to maintain charge neutrality in emitter*
 - *Emitter current (I_E) flows out of the emitter terminal*
- *Base injects holes to emitter*
 - *This component is reduced as much as possible by doping emitter very heavily*

- Injected electrons *diffuse* through the base due to *concentration gradient*
 - At the same time, some of them *recombine* with the *holes* in the *base*
 - Supplied by the *external terminal* to maintain *charge neutrality* in *base*
 - *Base current* (I_B) *flows into the base terminal*
- Electrons that *survived recombination* will reach the *base edge* of the *BC depletion region*

- Note the *direction* of the *electric field* (E) present in the *BC depletion region*
- This *field* will *sweep* the *survived electrons* to the *collector*
 - These *electrons* will *flow out* of the *collector terminal*
 - *Collector current* (I_C) *flows into the collector terminal*
- *Base Control:*
 - A *small change* in I_B can cause a *large change* in $I_C \Rightarrow$ *Transistor action*

- For a *good transistor*, the *ratio* I_C/I_B should be *as large as possible*
- Can be *achieved* by *reducing* the *chances of recombination* in the *base*
- *Two ways*:
 - *Reduce base doping* \Rightarrow *Limits supply of holes*
 \Rightarrow *Reduces recombination*
 - *Reduce base width* \Rightarrow *Reduces amount of time electrons spend in base* \Rightarrow *Reduces recombination*


Current Gain

- **Common-Emitter (CE) Current Gain:**
 - $\beta = I_C/I_B$ (*Higher the better!*)
- **Common-Base (CB) Current Gain:**
 - $\alpha = I_C/I_E$ (≤ 1 : *closer to 1, better it is!*)
- Also, $I_E = I_C + I_B$
 - $\alpha = \beta/(\beta + 1)$ and $\beta = \alpha/(1 - \alpha)$
- **Note:** As $\alpha \rightarrow 1$, $\beta \rightarrow \infty$
- **Typical values:** $\beta \sim 100\text{-}5000$, $\alpha \sim 0.99\text{-}0.9998$

Current-Voltage Relation

- **BE junction** basically a **diode**
 - $I_E = I_{ES} \exp(V_{BE}/V_T)$ ($V_{BE} > 4V_T$)
 - I_{ES} : **Reverse Saturation Current of BE junction**
- A **fraction** α of I_E reaches **collector**
 - $I_C = \alpha I_E = I_S \exp(V_{BE}/V_T)$
 - $I_S (= \alpha I_{ES})$: **Saturation current of the BJT**
- The **difference** between I_E and I_C is I_B
 - $I_B = I_E - I_C$

Output Characteristic

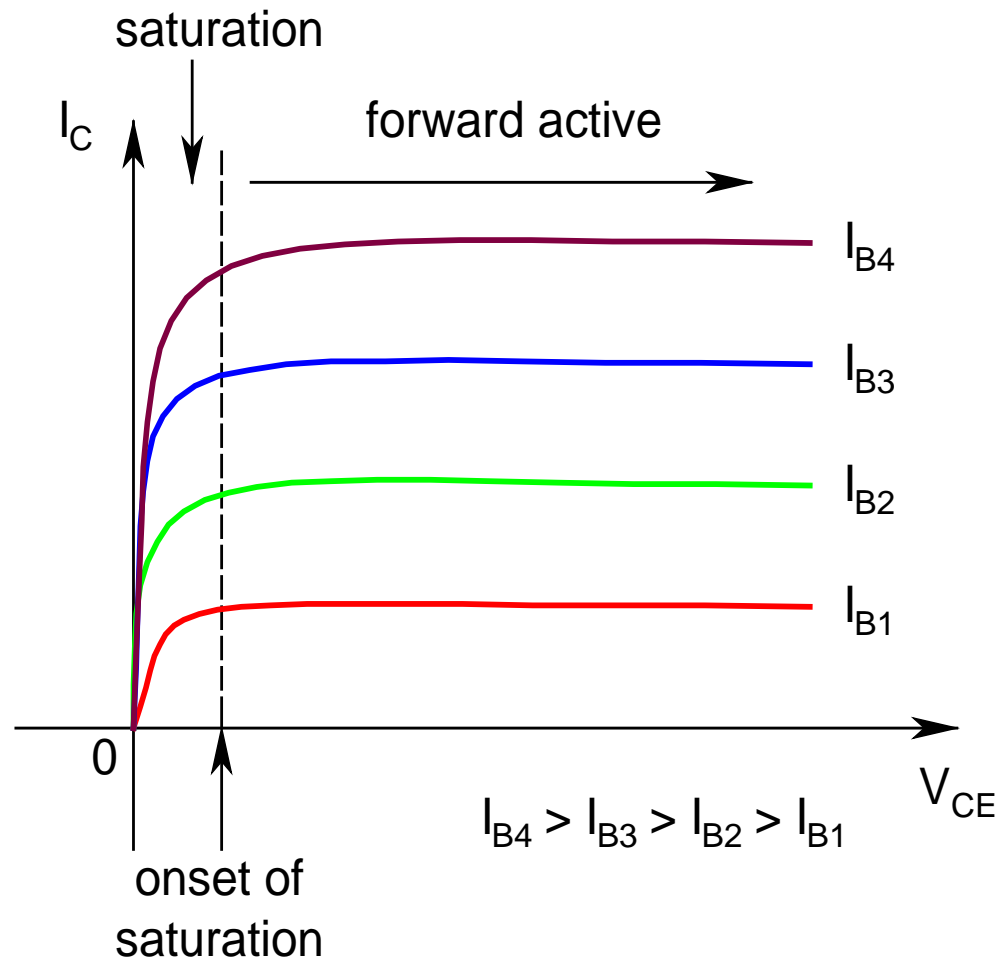

- *Quick Estimate:*
 - Under *forward bias*, $V_{BE} \sim 0.7 \text{ V}$
 - *Justification:*
 - $V_\gamma \sim 0.6 \text{ V}$
 - 0.7 V is 100 mV above $V_\gamma \Rightarrow$ *junction sufficiently forward biased*
 - I_C - V_{BE} relation *exponential* \Rightarrow A *little change* in V_{BE} can cause a *large change* in I_C
 - *Heuristic estimate: not accurate*, however, *extremely useful* for a *quick hand-calculation*
- $V_{CE} = V_{BE} - V_{BC}$ (*applying chain rule*)

- Thus, for $V_{CE} > 0.7 \text{ V}$, V_{BC} *negative*
 - BC junction *reverse biased* and FA operation is *maintained*
- As $V_{CE} \rightarrow 0.7 \text{ V}$, $V_{BC} \rightarrow 0$
 - BC junction *losing its reverse bias*
- At $V_{CE} = 0.7 \text{ V}$, $V_{BC} = 0$
 - BC junction *under zero bias*
- For $V_{CE} < 0.7 \text{ V}$, V_{BC} turns *positive*
 - Both BE and BC junctions become *forward biased* \Rightarrow *saturation*

- $V_{CE} = 0.7 \text{ V}$ is known as *onset of saturation* (OS)
- *Saturation*:
 - For $V_{CE} < 0.7 \text{ V}$
 - CB junction becomes *forward biased*
 - Collector also starts to *inject* electrons to base
 - *Two effects*:
 - *Net electrons reaching collector* $\downarrow \Rightarrow I_C \downarrow$
 - *Base gets flooded with electrons*
 \Rightarrow *Recombination increases manyfold* $\Rightarrow I_B \uparrow$
 - Thus, $\beta \downarrow \Rightarrow$ Defined as $\beta_{sat} (= I_{C,sat}/I_{B,sat})$

- Noting that $V_\gamma = 0.6 \text{ V}$, for $V_{BC} \leq 0.5 \text{ V}$, *injection* of electrons from *collector to base* will be *negligible*
 - It can be *assumed* that *FA operation* is *maintained* till this point, with β *retaining* its *nominal (FA) value*
 - $V_{CE} = 0.2 \text{ V}$ at this point, and is known as the *point of soft saturation* (SS)
- Beyond this point, BJT enters the *operating domain* known as *hard saturation* (HS)


- In *hard saturation*, $V_{BC} \approx 0.7 \text{ V}$, and collector *injects* electrons *vigorously* into the base
- To *counter* this effect, V_{BE} automatically *increases* to about 0.8 V
- At this point, $V_{CE} = 0.1 \text{ V}$, and is known as the *point of hard saturation* (HS)
- Note that all these numbers are for *quick estimates*, and *actual values* can be a *little different* from these

- ***Degree of Saturation*** (DoS):
 - $\text{DoS} = \beta/\beta_{\text{sat}} (\geq 1)$
 - Portrays how *deeply* the BJT is driven into *saturation*
- ***Commonly used values*** of *parameters* for *quick estimate*:
 - $V_{\text{BE}}(\text{FA}) = V_{\text{BE}}(\text{SS}) = 0.7 \text{ V}$
 - $V_{\text{BE}}(\text{HS}) = 0.8 \text{ V}$
 - $V_{\text{CE}}(\text{OS}) = 0.7 \text{ V}, V_{\text{CE}}(\text{SS}) = 0.2 \text{ V}$
 - $\text{DoS}(\text{FA}, \text{OS}, \text{SS}) = 1, \text{DoS}(\text{HS}) > 1$

- BJTs in *analog circuits* are used as *amplifiers*, and should *never* be pushed to *hard saturation* (β drops significantly)
 - *Lowest limit* of $V_{CE} = 0.2 \text{ V}$ (*soft saturation*)
- On the other hand, BJTs used in *digital circuits*, while *on*, are always pushed to *hard saturation*, since they act basically as *switches*
 - $V_{CE} = 0.1 \text{ V}$ (*hard saturation*)

Finding the Operating Point: Load Line Analysis

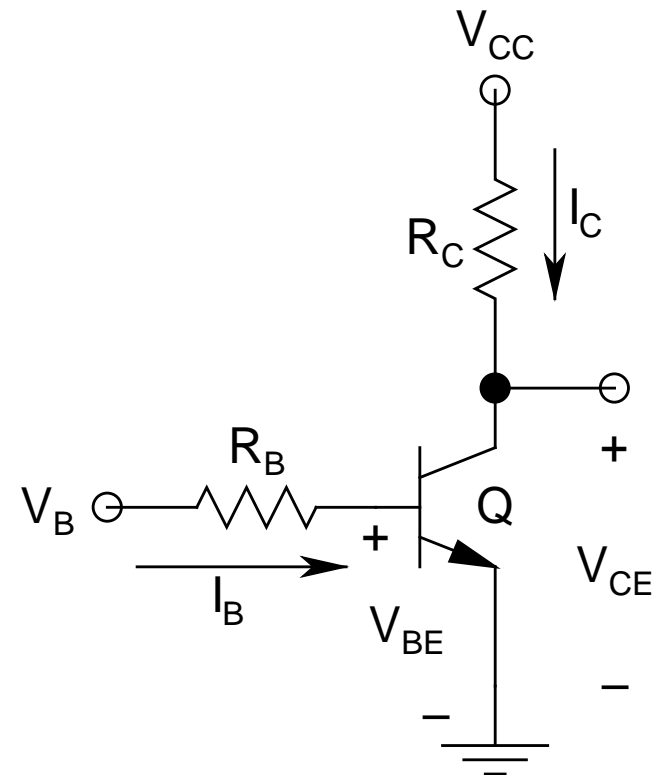
- *Quick estimate* in *FA mode*:
 - $I_B = (V_B - V_{BE})/R_B$
 - $V_{BE} = 0.7 \text{ V}$
 - $I_C = \beta I_B$
 - *Independent* of R_C , so long as *FA operation* is *maintained*




- For *continuous variation* of V_B , *continuous variation* of I_C and I_B
 - The *output characteristics* will *fill up* the *entire quadrant*
- The *operating point* (*Q-point*) can *lie anywhere* in this *quadrant*
- To find the *unique* Q-point, need to *draw* the *load line*
- *Load line equation*:
 - $I_C = (V_{CC} - V_{CE})/R_C$


- *2 boundary points:*
 - For $I_C = 0$, $V_{CE} = V_{CC}$
 - For $V_{CE} = 0$, $I_C = V_{CC}/R_C$
- *Joining* these *2 points* by a *straight line* gives the *load line*
- The *intersection point* of the *load line* with the *output characteristic* gives the *Q-point*
- Gives *infinite number* of *choices* for *possible Q-point*

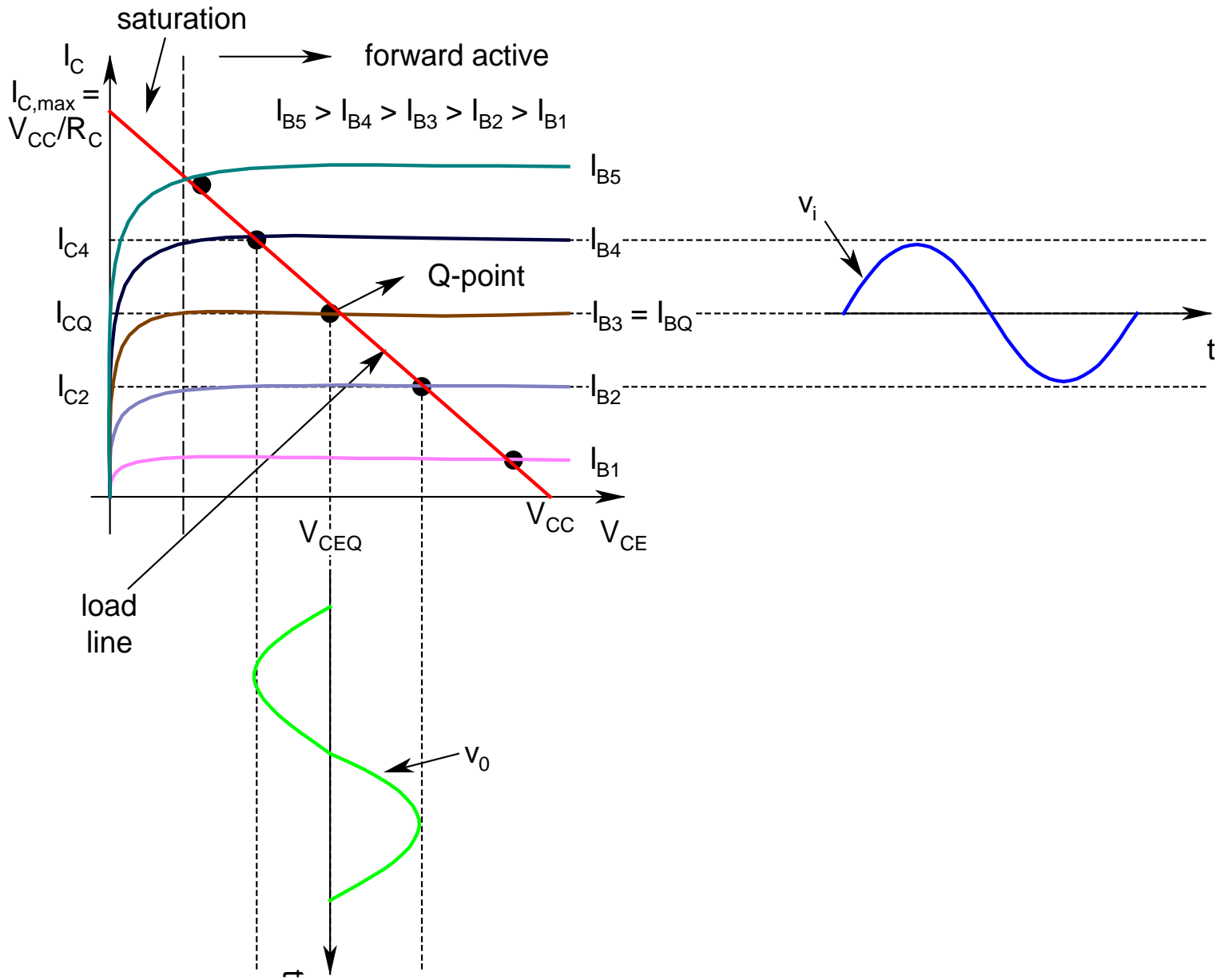- The *best choice* for the *Q-point* is *right at the center* of the *load line*
 - $V_{CEQ}(\text{best}) = V_{CC}/2$ and $I_{CQ}(\text{best}) = V_{CC}/(2R_C)$
- *Permits the maximum possible signal swing in both directions*
- If $V_{CEQ} > V_{CC}/2$, it's *biased more towards cutoff*
- If $V_{CEQ} < V_{CC}/2$, it's *biased more towards saturation*
- *Either way*, we will get a *distorted output*



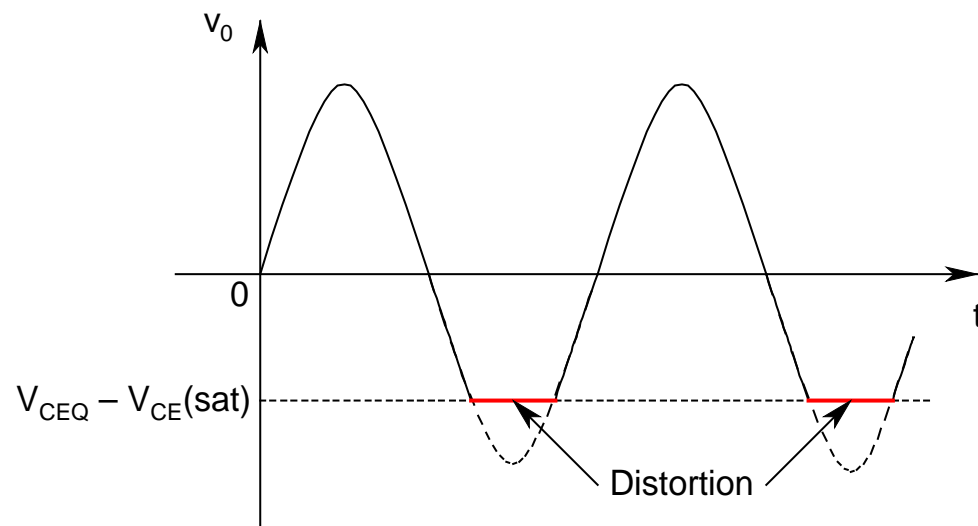

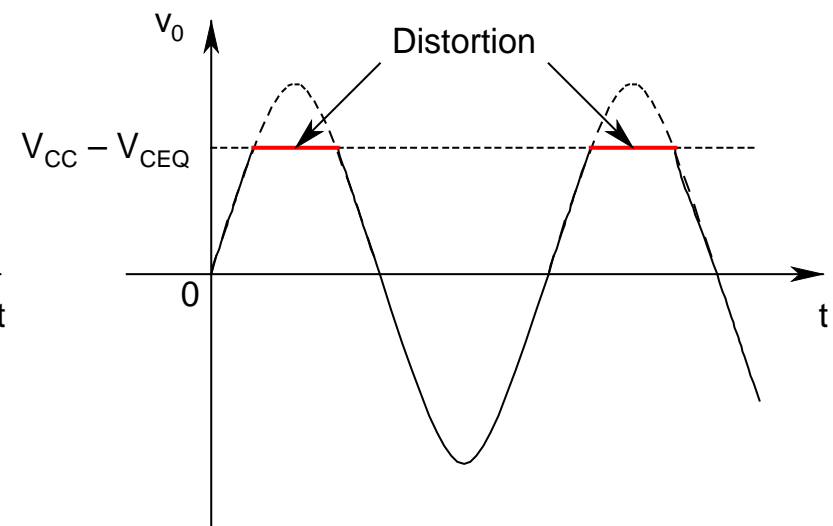(a) Negative Clipping:
Saturation Induced



(b) Positive Clipping:
Cutoff Induced

- Under *application* of an *ac signal* (v_i), the *dynamic operating point* (DOP) will *move along the load line*
- For *positive* v_i , the DOP *will move* Q *towards saturation* ($V_{CE} \rightarrow 0, I_C \rightarrow I_{C,max}$)
 - The *output signal* (v_o) will be in its *negative excursion*
 - If Q enters *saturation*, *negative peak* of v_o will get *clipped*
 - *Distorted output*

- For *negative* v_i , the DOP *will move* Q *towards cutoff* ($V_{CE} \rightarrow V_{CC}$, $I_C \rightarrow 0$)
 - The *output signal* (v_o) will be in its *positive excursion*
 - If Q *cuts off*, *positive peak* of v_o will get *clipped*
 - *Distorted output*
- *Golden rule of thumb for BJT biasing:*
 - *To get maximum undistorted peak-to-peak swing of v_o , Q-point must be chosen to be at the middle of the load line*

- **Role of R_C :**

- Under **FA mode**, R_C does not control I_C , however, it **changes V_{CE}** ($= V_{CC} - I_C R_C$)
- If $R_C \uparrow$, $V_{CE} \downarrow \Rightarrow Q$ moves **towards saturation**
- If $R_C \downarrow$, $V_{CE} \uparrow \Rightarrow Q$ moves **towards cutoff**
- Thus, **different values of R_C** can produce **different Q -points** (in terms of V_{CE})

- **DC Power Dissipation:**

- $P_D = V_{BEQ} \times I_{BQ} + V_{CEQ} \times I_{CQ}$
 $\approx V_{CEQ} \times I_{CQ}$ (**under FA mode**)

Some Observations

- Q should be *biased* such that it is in the *FA* mode of operation
 - Behaves like a *constant and ideal current source with infinite output resistance*, since I_C is *independent* of V_{CE}
 - *Ideal region to bias a BJT*
- For *very high* R_C , $I_{C,max}$ *very small*
 - *Load line may not have any intersection point in the FA region at all*

- *Q-point moves to saturation region*
- *Ceases to become a constant current source*, since in *saturation*, I_C becomes a *strong function* of V_{CE}
- *Disastrous way of biasing a BJT*
- *Similar situation* will arise if R_C is *very small*
 - $I_{C,max}$ will become *very large* and *Q-point will move towards cutoff*
 - *Another disastrous way of biasing a BJT*

- **Example:** Let $V_{CC} = V_B = 5\text{ V}$, $R_B = 430\text{ k}\Omega$, and $\beta = 100$
 - $I_B = (V_B - V_{BE})/R_B = (5 - 0.7)/(430\text{ k}\Omega) = 10\text{ }\mu\text{A}$ (assuming **FA** mode of operation with $V_{BE} = 0.7\text{ V}$)
 - $I_C = \beta I_B = 1\text{ mA}$
 - V_{CE} will **depend** on our **choice** of R_C
 - R_C for **best biasing** (BB) ($V_{CE}(\text{BB}) = V_{CC}/2$):
 - $R_C(\text{BB}) = V_{CC}/(2I_C) = 2.5\text{ k}\Omega$
 - R_C that puts Q at OS ($V_{CE}(\text{OS}) = 0.7\text{ V}$):
 - $R_C(\text{OS}) = [V_{CC} - V_{CE}(\text{OS})]/I_C = 4.3\text{ k}\Omega$

➤ *Any value of R_C higher than $4.3\text{ k}\Omega$ would push Q in saturation*

➤ Choose $R_C = 20\text{ k}\Omega$:

- Assuming *FA* operation is maintained, V_{CE} comes out to be -15 V !

- *Golden rule*:

- ❖ *Potential at any point in a circuit can never go beyond the positive and negative extremes of the power supply voltages, unless there is a power source within the circuit*

- Thus, $V_{CE} = -15\text{ V}$ is *absurd*!


- Hence, Q is *no more* in the *FA* mode of operation, rather it has been pushed into *saturation*

- Whether it is in *soft saturation* (SS) or *hard saturation* (HS), would *depend* on the *degree of saturation* (DoS)
- *For HS, DoS must be ≥ 2* ($\beta_{\text{sat}} \leq \beta/2$)
- Assume *HS*: $V_{\text{BE}}(\text{HS}) = 0.8 \text{ V}$, $V_{\text{CE}}(\text{HS}) = 0.1 \text{ V}$
 - ❖ $I_{\text{B,sat}} = [V_{\text{CC}} - V_{\text{BE}}(\text{HS})]/R_{\text{B}} = (5 - 0.8)/(430 \text{ k}\Omega) = 9.77 \text{ }\mu\text{A}$
 - ❖ $I_{\text{C,sat}} = [V_{\text{CC}} - V_{\text{CE}}(\text{HS})]/R_{\text{C}} = (5 - 0.1)/(20 \text{ k}\Omega) = 245 \text{ }\mu\text{A}$
 - ❖ $\beta_{\text{sat}} = I_{\text{C,sat}}/I_{\text{B,sat}} = 245/9.77 = 25$
 - ❖ $\text{DoS} = \beta/\beta_{\text{sat}} = 4 (> 2)$
 - ❖ *Assumption verified, and analysis is correct!*
- *Ex.*: Find the values of R_{C} that would put Q at the edge of: i) HS, and ii) SS

Base Width Modulation Effect

- In **FA** mode, as $|V_{BC}| \uparrow$, BC *depletion region width* $\uparrow \Rightarrow$ *neutral base width* \downarrow
 - *Electrons spend less time in base* \Rightarrow *chance of recombination* \downarrow
 - *More electrons make it to the collector* $\Rightarrow I_C \uparrow$
as $V_{CE} \uparrow$
 - Known as the **Base Width Modulation Effect**
(or *Early Effect*)

- The *current-voltage characteristic*, including *Early Effect*, is modeled as:
 - $I_C = I_S[\exp(V_{BE}/V_T)](1 + V_{CE}/V_A)$
 - V_A : *Early Voltage* (~ 130 V for *nnp*, and ~ 52 V for *pnnp*)
 - V_A is a *negative number*, but taken to be a *positive quantity*
- Imparts a *positive slope* in the *output characteristics* in the *FA region*
 - Introduces an *output resistance*, and makes the current source *non-ideal*!

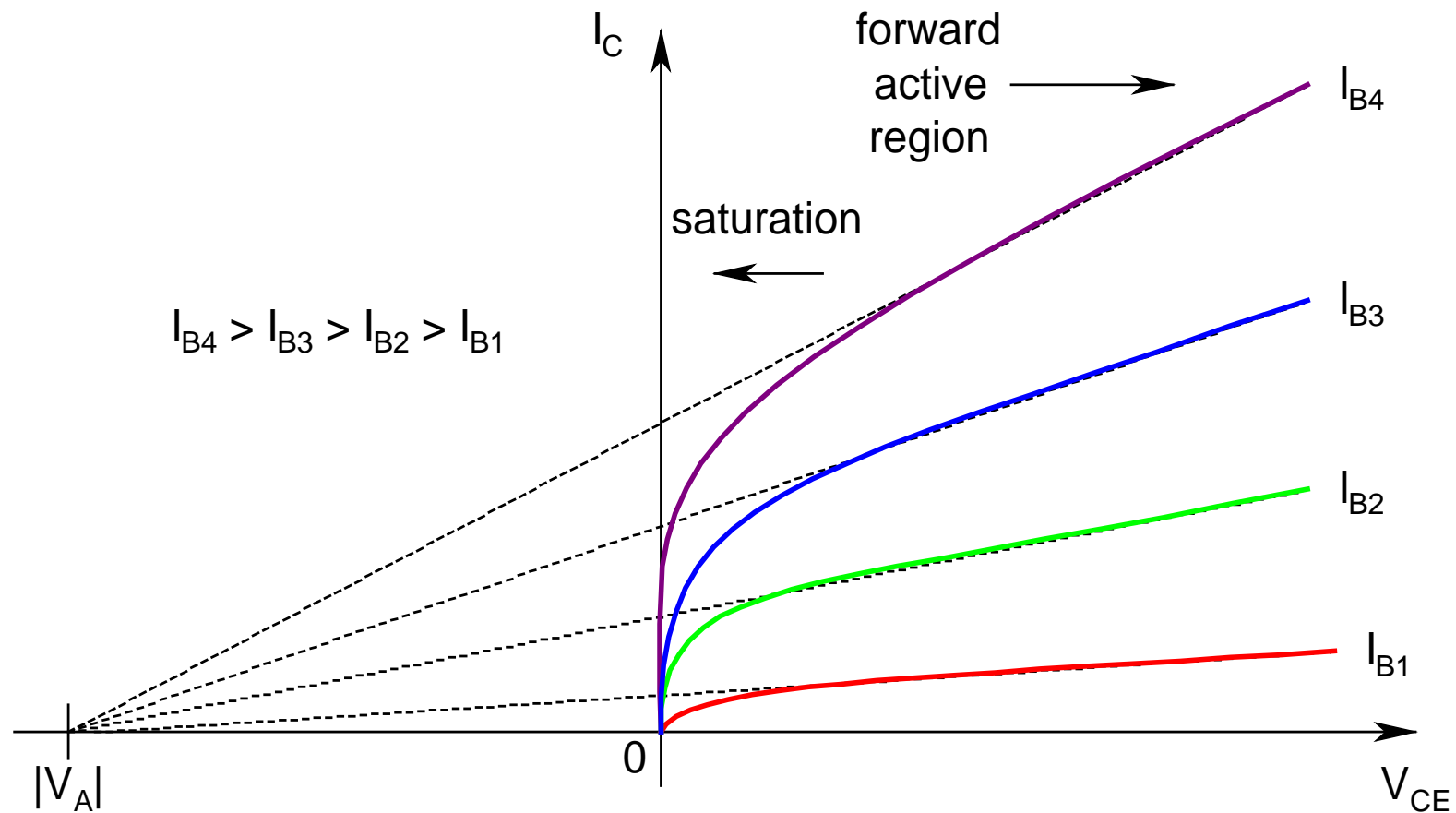

All characteristics merge at $|V_A|$ in the negative V_{CE} axis

Note: If $V_A \rightarrow \infty$, all characteristics become horizontal in the FA region

IEEE Notational Convention


- *Pure DC quantities:*
 - *Capital letter with capital subscript* (e.g., V_{BE})
- *Pure ac quantities:*
 - *Small-case letter with small-case subscript* (e.g., v_{be})
- *Instantaneous (DC + ac) quantities:*
 - Either *capital letter with small-case subscript* (e.g., V_{be}) or *small-case letter with capital subscript* (e.g., v_{BE})

Small-Signal Model

- The *electrical equivalent* of the BJT at the *DC bias point*
- Basically an *electrical network*, having *passive and active elements*
- To obtain this model, *DC analysis* is needed, since the *information* regarding the *Q-point* (I_C , V_{CE}) is necessary
- *This model for npn and pnp BJT is same*

Validity of the Small-Signal Model

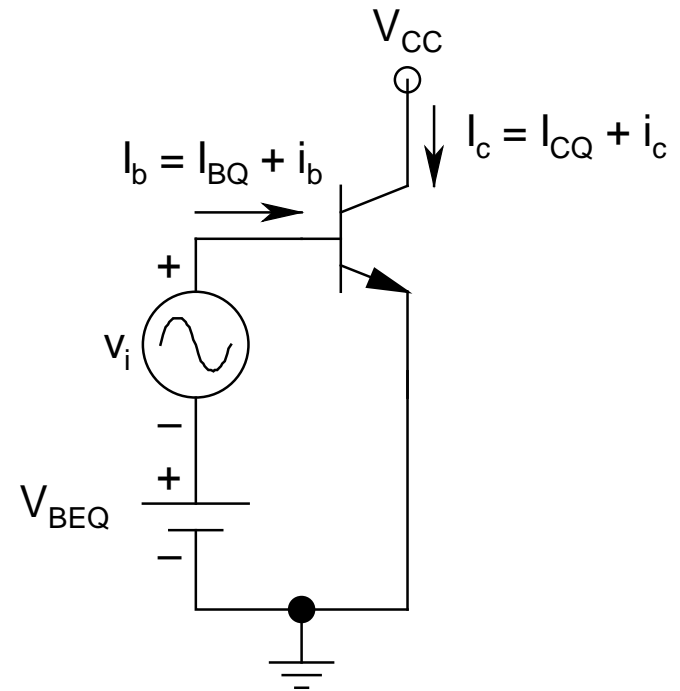- Basically *linearization* of the *operating region* around the *Q-point*
- *This linearization should not contain any higher-order terms*



- To start with, assume $V_A \rightarrow \infty$
 - $I_{CQ} = I_S \exp(V_{BEQ}/V_T)$
- Thus:

$$\begin{aligned} I_c &= I_S \exp\left(\frac{V_{be}}{V_T}\right) = I_S \exp\left(\frac{V_{BEQ} + v_i}{V_T}\right) \\ &= I_S \exp\left(\frac{V_{BEQ}}{V_T}\right) \exp\left(\frac{v_i}{V_T}\right) = I_{CQ} \exp\left(\frac{v_i}{V_T}\right) \end{aligned}$$

- Expand the *exponential term* in series:

$$\blacktriangleright I_c = I_{CQ} \left[1 + \frac{v_i}{V_T} + \frac{1}{2!} \left(\frac{v_i}{V_T} \right)^2 + \frac{1}{3!} \left(\frac{v_i}{V_T} \right)^3 + \dots \right]$$

- Thus:

$$\blacktriangleright i_c = I_c - I_{CQ} = I_{CQ} \left[\frac{v_i}{V_T} + \frac{1}{2!} \left(\frac{v_i}{V_T} \right)^2 + \frac{1}{3!} \left(\frac{v_i}{V_T} \right)^3 + \dots \right]$$

- *True linearization* of i_c - v_i relation *can be achieved* only if *all higher-order terms* can be *neglected* $\Rightarrow v_i$ should be $\ll V_T$

Small-Signal Model Parameters

- *Incremental Emitter Resistance* (r_E):

$$r_E = \frac{i_e}{v_i} = \frac{\Delta I_E}{\Delta V_{BE}} \equiv \left. \frac{dI_E}{dV_{BE}} \right|_{V_{CE} \text{ constant}} = \frac{V_T}{I_E}$$

- *Transconductance* (g_m):

$$g_m = \frac{i_c}{v_i} = \frac{\Delta I_C}{\Delta V_{BE}} \equiv \left. \frac{dI_C}{dV_{BE}} \right|_{V_{CE} \text{ constant}} = \frac{I_C}{V_T}$$

- Thus, $g_m r_E = I_C/I_E = \alpha \approx 1$
- *A frequently used approximation:*
 - $g_m = 1/r_E$
- For $I_C = 1 \text{ mA}$:
 - $r_E = 26 \Omega$ and $g_m = 1/26 \text{ A/V}$
- As $I_C \uparrow$:
 - $g_m \uparrow$ and $r_E \downarrow$
 - Also $P_D \uparrow$
- Gain = $f(g_m)$
 - \Rightarrow For *higher gain*, the circuit has to be fed *more power*

- **Base-Emitter Resistance** (r_π):

$$r_\pi = \frac{v_i}{i_b} = \frac{\Delta V_{BE}}{\Delta I_B} \equiv \left. \frac{dV_{BE}}{dI_C} \frac{dI_C}{dI_B} \right|_{V_{CE} \text{ constant}} = \frac{\beta}{g_m} \simeq \beta r_E$$

➤ For $I_C = 1 \text{ mA}$ and $\beta = 100$: $r_\pi = 2.6 \text{ k}\Omega$

- **Output Resistance** (r_o):

$$r_o = \frac{v_{ce}}{i_c} = \left[\frac{dI_C}{dV_{CE}} \right]^{-1} \bigg|_{V_{BE} \text{ constant}} = \frac{V_A}{I_C} = \frac{V_A}{V_T} \frac{V_T}{I_C} = \frac{1}{\eta g_m}$$

- For $I_C = 1 \text{ mA}$, $V_{AN} = 130 \text{ V}$, and $V_{AP} = 52 \text{ V}$:
 $r_0(\text{nnp}) = 130 \text{ k}\Omega$ and $r_0(\text{pnp}) = 52 \text{ k}\Omega$
- $\eta (= V_T/V_A)$: 2×10^{-4} (nnp) and 5×10^{-4} (pnp)
- $g_m r_0 = \eta^{-1}$

- **Collector-Base Resistance** (r_μ):

$$r_\mu = \frac{V_{ce}}{i_b} = \frac{\Delta V_{CE}}{\Delta I_B} \bigg|_{V_{BE} \text{ constant}} = \frac{dV_{CE}}{dI_C} \frac{dI_C}{dI_B} = \beta r_0$$

- **Oversimplification** – *actual value much higher* ($\sim 5\text{-}10\beta r_0$) $> 100\text{s of M}\Omega$

- ***Emitter-Base Capacitance*** (C_π):

$$C_\pi = C_{je} + C_b$$

- C_{je} : ***Emitter-base depletion capacitance***

$$\approx 2C_{je0}$$

- C_{je0} : ***Emitter-base depletion capacitance at zero bias***

- C_b : ***Emitter-base diffusion capacitance***
(known as ***base charging capacitance***)

$$= \tau_F g_m \quad (>> C_{je})$$

- τ_F : ***Base transit time***

- $C_\pi \uparrow$ as $g_m \uparrow$ (***Problem!***)


- **Collector-Base Capacitance** (C_μ):

$$C_\mu = \frac{C_{\mu 0}}{\left(1 - \frac{V_{BC}}{V_{0,BC}}\right)^m}$$

- $C_{\mu 0}$: **Collector-base depletion capacitance at zero bias**
- $V_{0,BC}$: **Built-in voltage of collector-base junction**
- m : **Grading coefficient** ($1/2$ for **abrupt step junction**, $1/3$ for **linearly graded junction**)

- *Quasi-Neutral Emitter, Base, and Collector Resistances* (r_e , r_b , and r_c):
 - In *IC BJT*, *emitter highest doped, followed by base*, with *collector being least doped*
 - Thus, $r_c > r_b > r_e$
 - *Typical values*:
 - $r_e \sim 5\text{-}10\ \Omega$
 - $r_b \sim 100\text{-}200\ \Omega$
 - $r_c \sim$ can be as high as $\text{k}\Omega$
 - *Become important only at very high frequencies*


The Hybrid- π Model

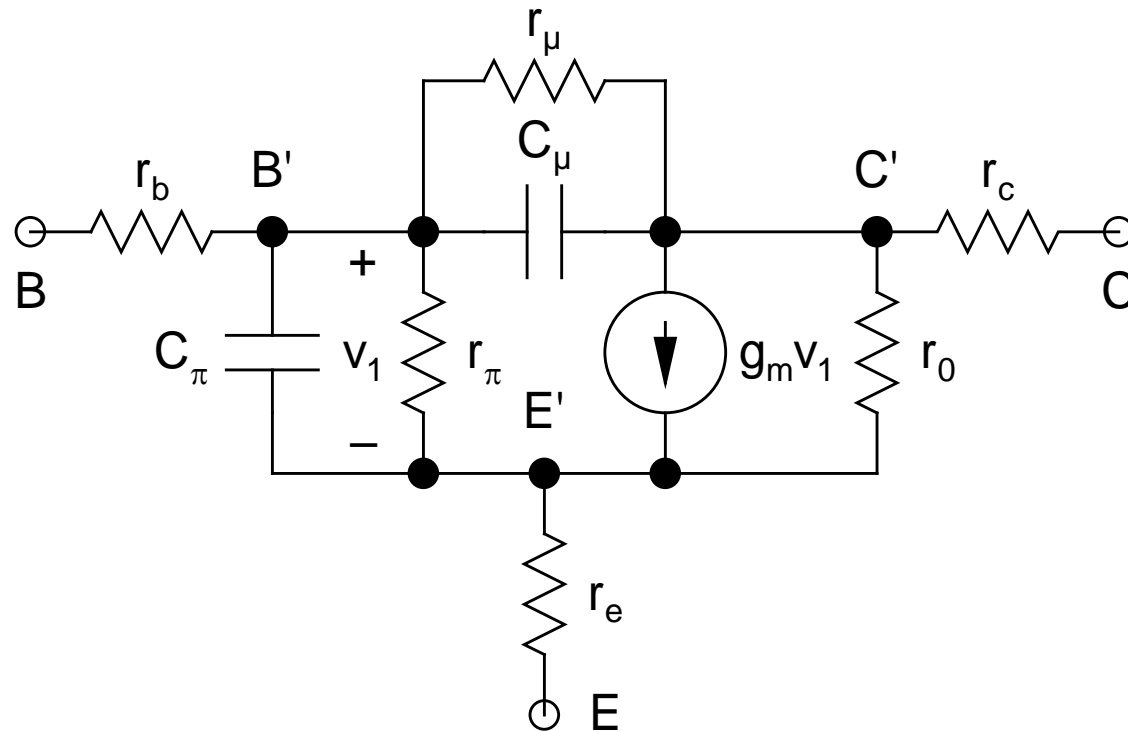

E,B,C: Extrinsic Terminals
E',B',C': Intrinsic Terminals

- ***Simplifications:***


- r_e, r_b, r_c can be *safely neglected* under *low to moderate frequencies* of operation
- r_μ can be *neglected*, since it's *extremely large*
- At *low to moderate frequencies*, the *capacitive reactances* of C_π and C_μ will be *extremely large* \Rightarrow can be *neglected*
- Leads to the ***Low-Frequency T-Model***, having only *three components*: r_π , $g_m v_1$, and r_0
- *Simplest possible equivalent results if r_0 is also neglected!*

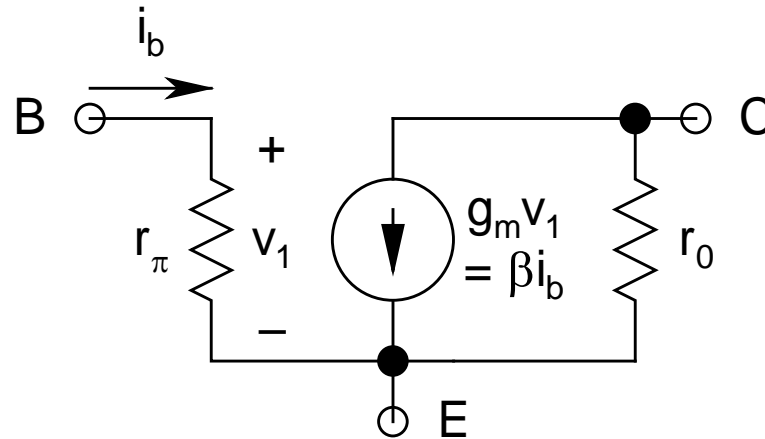

Low-Frequency T-Model


- **Note:** The *output circuit* resembles a **non-ideal current source** of *magnitude* $g_m v_1$ (or equivalently, βi_b) with *output resistance* r_o

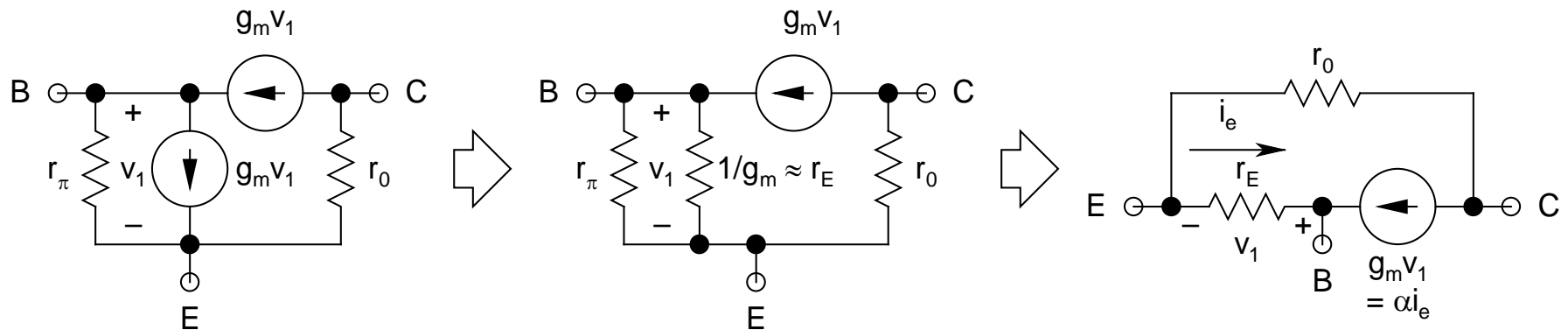- *This model is appropriate when the ac input is applied to base*
- *When the ac input is applied to the emitter, then need to draw this circuit in a slightly different way*



Frequency Specifications of BJTs

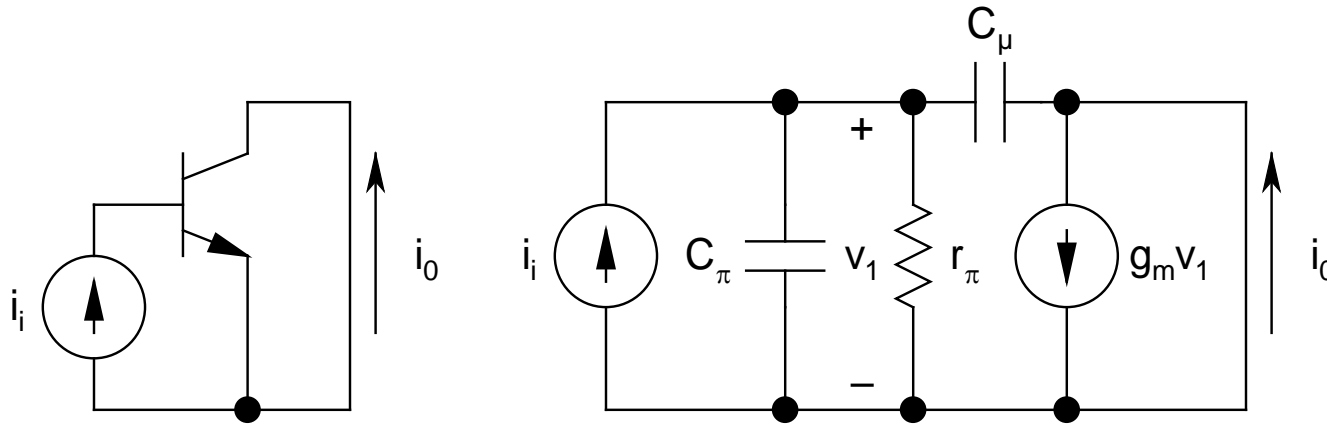- *Four important characteristic frequencies:*
 - *Beta Cutoff Frequency* (f_{β})
 - *Unity Gain Cutoff Frequency* (f_T)
 - *Alpha Cutoff Frequency* (f_{α})
 - *Maximum Operable Frequency* (f_{\max})



- $i_o \approx g_m v_1$ (*neglecting reverse transmission through C_μ*)
- $v_1 = i_i Z_{eq}$

$$Z_{eq} = \frac{r_\pi}{1 + s r_\pi (C_\pi + C_\mu)} \quad (s = j\omega)$$

- Thus:

$$\beta(j\omega) = \frac{i_o(j\omega)}{i_i(j\omega)} = \frac{\beta_0}{1 + j\omega/\omega_\beta}$$

$\beta_0 (= g_m r_\pi)$: *Low-frequency short-circuit common-emitter current gain*


$$\omega_\beta = \frac{g_m}{\beta_0 (C_\pi + C_\mu)}$$

- $f_\beta [= \omega_\beta/(2\pi)]$: *Beta Cutoff Frequency*
- At $f = f_\beta$, $\beta = \beta_0/\sqrt{2}$

- For $f \gg f_\beta$:

$$\beta(j\omega) \simeq \frac{g_m}{j\omega(C_\pi + C_\mu)}$$

- At $\omega = \omega_T = g_m/(C_\pi + C_\mu)$, $|\beta| = 1$
- $f_T [= \omega_T/(2\pi)]$: **Unity Gain Cutoff Frequency** (also known as **Unity Gain Bandwidth**)
- **Note**: $f_T = \beta_0 f_\beta$
- $f_T > f_\beta$, and their spacing depends on β_0

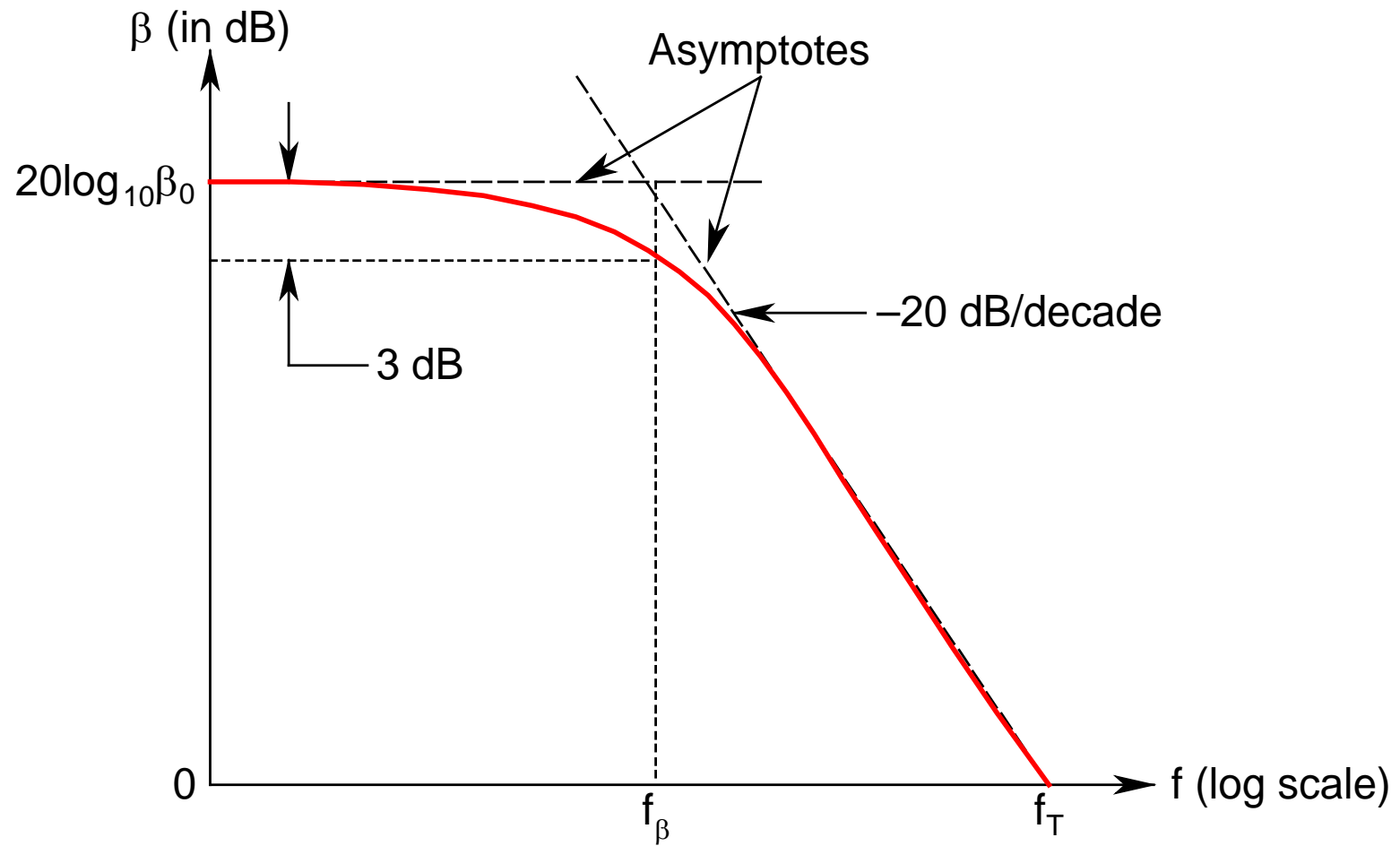

- *Actual measurement of f_T difficult - measured indirectly*
- *Measurement done at $f_x \gg f_\beta$, where β has dropped to about 5-10*
- Then, $f_T = \beta(f_x)f_x$
- Using $\alpha = \beta/(\beta + 1)$:

$$\alpha(j\omega) = \frac{\beta(j\omega)}{1 + \beta(j\omega)} = \frac{\alpha_0}{1 + j\omega/\omega_\alpha}$$

$$\alpha_0 [= \beta_0/(\beta_0 + 1)]: \text{ *Low-frequency short-circuit common-base current gain* }$$

$$\omega_{\alpha} = (\beta_0 + 1)\omega_{\beta}$$

- $f_{\alpha} [= \omega_{\alpha}/(2\pi)]$: *Alpha Cutoff Frequency*

- At $f = f_{\alpha}$, $\alpha = \alpha_0/\sqrt{2}$

- *Note: f_{α} and f_T extremely close to each other, with f_{α} marginally higher than f_T , with both being much larger than f_{β}*

- *Maximum Operable frequency:*

$$f_{\max} = f_T \Big|_{\max} = \frac{1}{2\pi\tau_F}$$

➤ Known as the *Transit Time Model*