


- ***Emitter Feedback Bias:***

- *While writing KVL, never take CE or BC loops, since V_{CE} and V_{BC} are not known*

- *Consider only BE loops with $V_{BE} = 0.7\text{ V}$*

- $V_{CC} = I_B R_B + V_{BE} + I_E R_E$
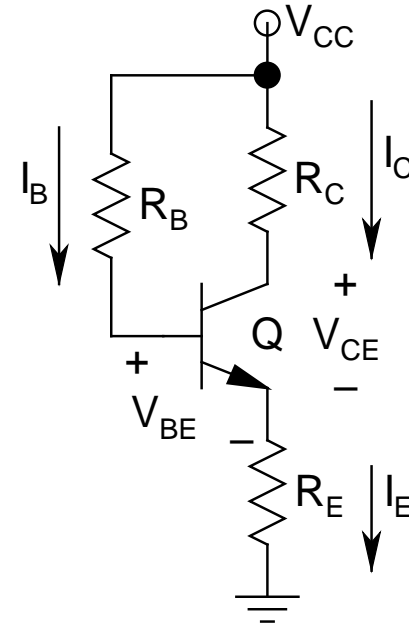
$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$



- $I_C = \beta I_B$
- $V_{CE} = V_{CC} - I_C R_C - I_E R_E \approx V_{CC} - I_C (R_C + R_E)$
- $P_D = V_{CC} \times I_E$
- This is a **3-element output branch**, with $V_{CE} = V_{CC}/3$ for **BB**
- **Rest $2V_{CC}/3$ drops across R_C and R_E , with the ratio typically chosen to be 2:1** (reason later!)
- Circuit is **very robust** since R_E provides **negative feedback**
- Also, has **better β insensitivity**

- ***Collector Feedback Bias:***

- $V_{CC} = I_E(R_C + R_E) + I_B R_B + V_{BE}$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)(R_C + R_E)}$$


- $I_C = \beta I_B$

- $V_{CE} = V_{CC} - I_E(R_C + R_E)$

- $P_D = V_{CC} \times I_E$

- This circuit also provides

better β insensitivity

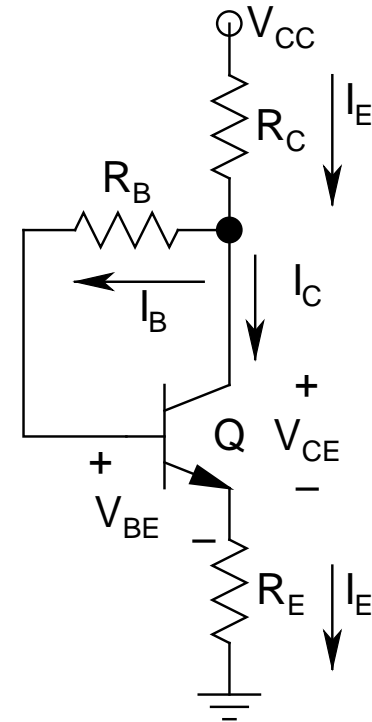

- ***Voltage Divider (or 4-Resistor) Bias:***

- *The best: Extremely robust and versatile*

- If properly designed, *almost β independent*

- If $I_1 \geq 10I_B$, $I_1 \approx I_2$

$$\Rightarrow V_B \approx \frac{R_2}{R_1 + R_2} V_{CC}$$

$$\Rightarrow V_E = V_B - V_{BE} \text{ and } I_C \approx I_E = V_E / R_E$$

