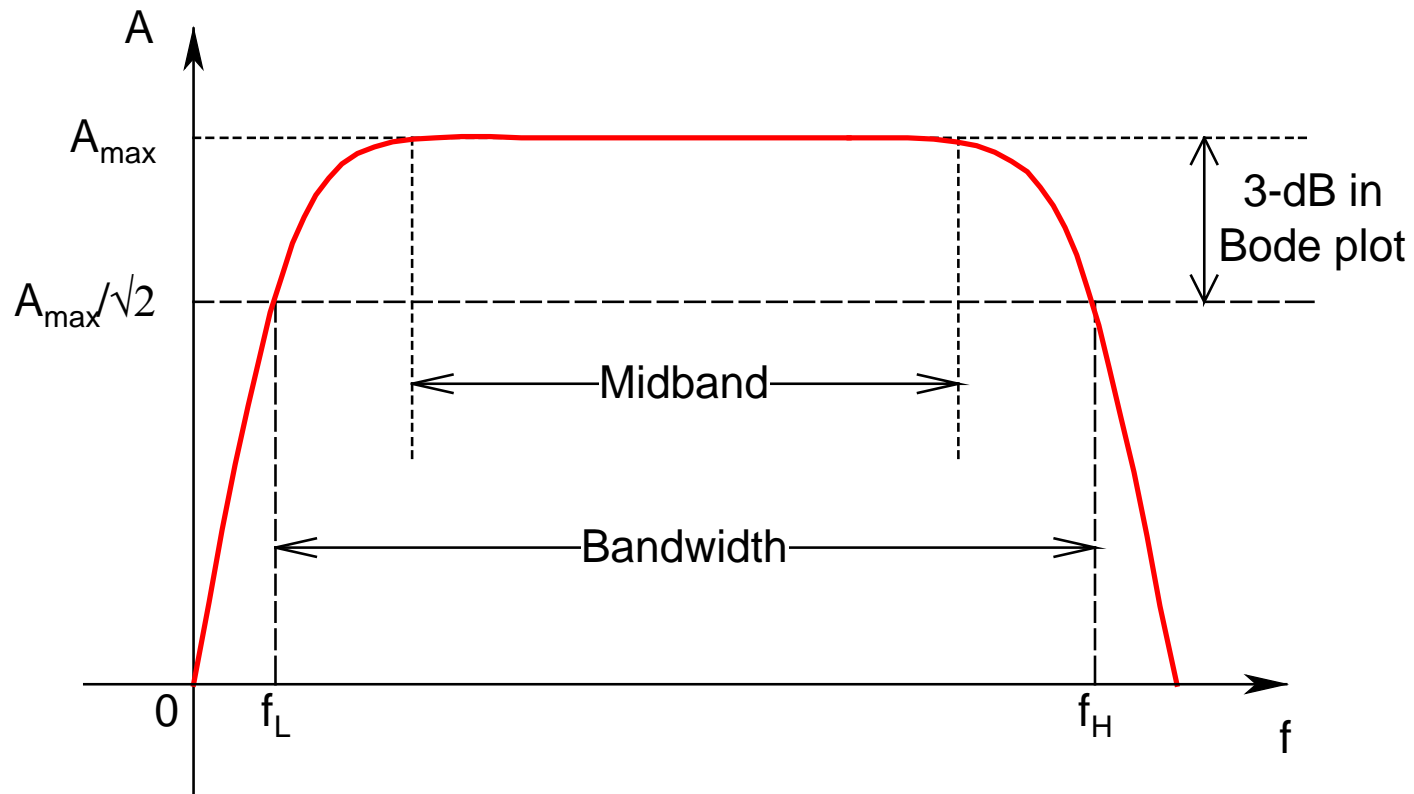


FREQUENCY RESPONSE

- So far, considered *midband analysis*, where *all capacitive effects were neglected*
 - *Voltage/current gain was independent of frequency*
- In *practical amplifier circuits*, however, the *gain would depend on frequency*
- *Characterized by:*
 - *Lower Cutoff Frequency* (f_L)
 - *Contributed by external capacitors* (C_E , C_B , C_C)

- *Upper Cutoff Frequency* (f_H)
 - *Contributed by device capacitances* (for BJT: C_π , C_μ ; *for MOSFETs*: C_{gs} , C_{gd} , C_{sb} , C_{db})
- These capacitors create *charge storage effects*, and *introduce time constants* into the circuit
- *Discrete circuits show both f_L and f_H*
- *IC stages show only f_H* , since most of them are *direct coupled* without the need for any *external capacitors*



f_L : Lower Cutoff Frequency

f_H : Upper Cutoff Frequency

$$\text{Bandwidth} = f_H - f_L$$

- *Exact analysis extremely complicated*
 - Most often, results in *very complicated expressions*, *completely hiding the physical feel of the phenomenon*
 - *Makes debugging extremely difficult*
 - For example, a circuit having *4 capacitors*, will have a *fourth-order transfer function*, which needs to be *solved* to get all the *poles and zeros* of the system
 - However, there are *techniques*, which make these *analyses* extremely *trivial*
 - *Not accurate*, but *extremely simple*, and makes *debugging easy*

- *Techniques:*
 - *Infinite-Value Time Constant (IVTC) Method*
 - *Used for obtaining f_L*
 - *Zero-Value Time Constant (ZVTC) Method*
 - *Used for obtaining f_H*
- These techniques are *extremely easy to apply*, and the results are *quite close to actuals*
- However, there is *one limitation* of these techniques

- They give information only regarding the *Dominant Pole* (DP) of the circuit
- *Completely hides information* about *other poles and zeros* of the circuit [known as *Non-Dominant Poles* (NDP) or *Zeros* (NDZ)]
- Anyway, information about *NDP and NDZ* are *not* that *critically important* from *practical point of view*

Low-Frequency Response

- *The Infinite-Value Time Constant (IVTC) Technique:*
 - Used for obtaining the *lower cutoff frequency* (f_L)
 - If a circuit has n number of *capacitors*, then it would have n number of *time constants*
 - *This technique derives the information regarding f_L from these time constants*

- *The Algorithm:*

- *Null all independent sources to the circuit*
 - *Short all independent voltage sources*
 - *Open all independent current sources*
 - *DO NOT TOUCH DEPENDENT SOURCES*
- *Name the capacitors C_i ($i = 1-n$)*
- *Consider C_1 and assign infinite values to all other capacitors (thus the name!)*
 - Thus, *except C_1 , all other capacitors will short out*
- *Determine the Thevenin Resistance (R_1^∞) across the two terminals of C_1*

- *Find the time constant τ_1 associated with C_1*
 $(\tau_1 = R_1^\infty C_1)$
- *Calculate the corresponding frequency $f_1 = 1/(2\pi\tau_1)$*
- *Repeat for all other capacitors, taking one at a time, and find all the rest of the frequencies*
 (f_2, f_3, \dots, f_n)
- Then the *Lower Cutoff Frequency* f_L can be expressed as:

$$f_L = \left[\sum_{i=1}^n f_i^2 \right]^{1/2}$$

- In *discrete circuits*, a *major component of total cost* is due to the *cost of the capacitors* (*directly proportional to the value*)
- Hence, an attempt is made to *minimize* the *total capacitor requirement of the circuit*
- For this, the *Dominant Pole* (DP) technique is used
 - *One of the frequencies among f_1 - f_n is made dominant*
 - *Others are made to lie at least 10 times away from it*

- For example, if f_d is chosen to be the DP, then all other poles are assumed to be at $f_d/10$

$$\Rightarrow f_L = \left[f_d^2 + \sum_{n=1} \left(\frac{f_d}{10} \right)^2 \right]^{1/2}$$


- C_d , which contributes f_d , is chosen to be that capacitor that sees the least Thevenin resistance across its terminals

- Reason is obvious:


- If any other capacitor were chosen to contribute f_d , then C_d would have been ten times higher

- This choice is based on heuristics

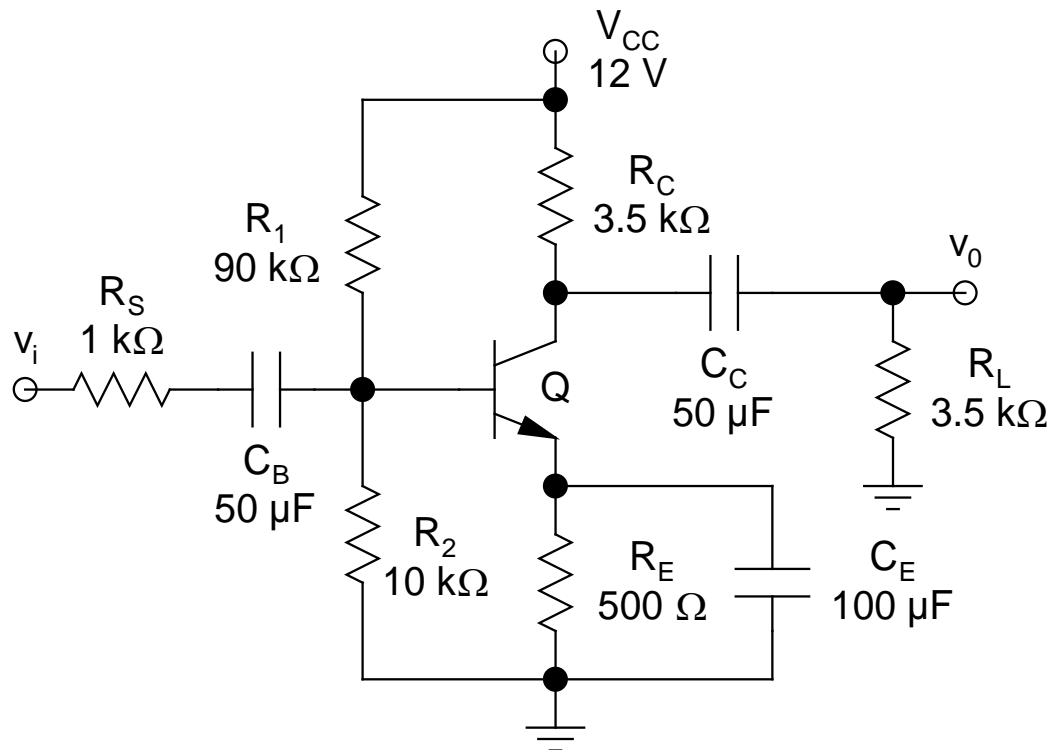- Low-Frequency Response of RC-Coupled Amplifier:***



Complete Circuit

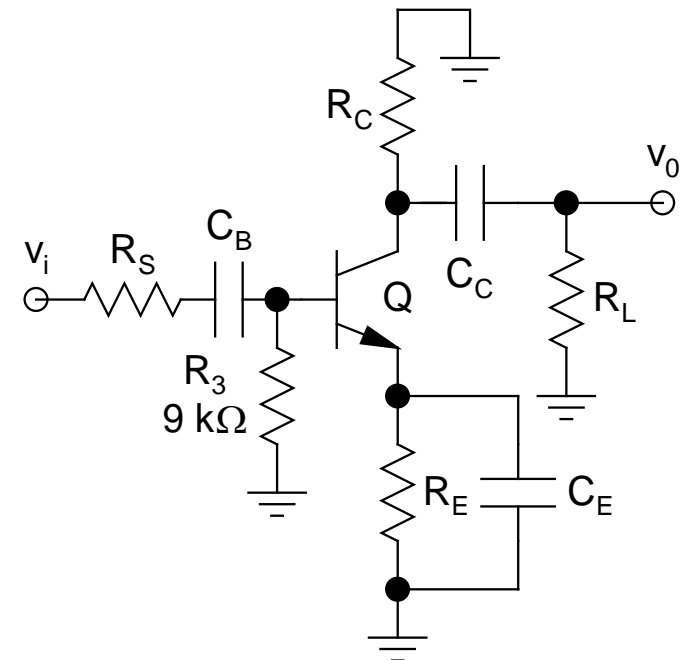

ac Schematic

- *DC analysis* gives $I_C = 1 \text{ mA}$ and $V_{CE} = 4 \text{ V}$
 $\Rightarrow r_E = 26 \Omega$ and $r_\pi = 2.6 \text{ k}\Omega$ (assuming $\beta = 100$)
- *Neglect Early effect*
 $\Rightarrow r_0 \rightarrow \infty$
- 3 *capacitors* (C_B, C_E, C_C) with *time constants* τ_1, τ_2, τ_3 , and corresponding *cutoff frequencies* f_1, f_2, f_3
- To apply the *IVTC technique*, we have to take *one capacitor at a time* and *treat other capacitors as short circuits*
- *The analysis can be done by inspection!*

➤ C_B :


- *Short C_C and C_E*
- $R_3 = R_1 \parallel R_2 = 9 \text{ k}\Omega$
- $R_4 = R_C \parallel R_L = 1.75 \text{ k}\Omega$
- $R_i = r_\pi = 2.6 \text{ k}\Omega$
- By inspection, the *Thevenin*

resistance seen by C_B :

$$R_B^\infty = R_S + (R_3 \parallel R_i) = 3 \text{ k}\Omega$$

$$\Rightarrow \tau_1 = R_B^\infty C_B = 150 \text{ ms}$$
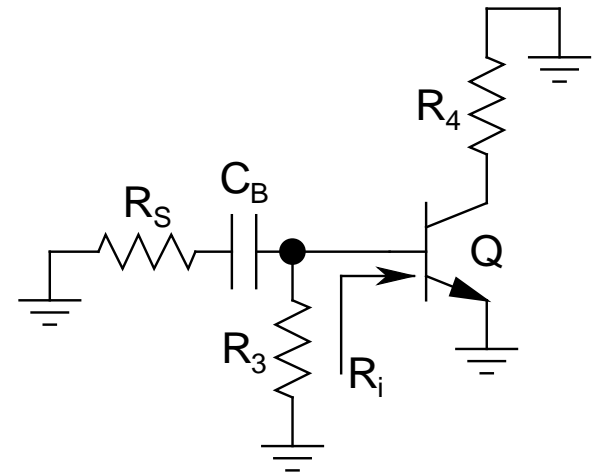
$$\Rightarrow f_1 = 1/(2\pi\tau_1) = 1.06 \text{ Hz}$$




➤ C_E :

- *Short C_C and C_B*
- $R_{01} = r_E + (R_S \parallel R_3)/(\beta + 1)$
 $= 34.9 \Omega$
- By inspection, the *Thevenin resistance* seen by C_E :

$$R_E^\infty = R_E \parallel R_{01} = 32.6 \Omega$$

$$\Rightarrow \tau_2 = R_E^\infty C_E = 3.26 \text{ ms}$$
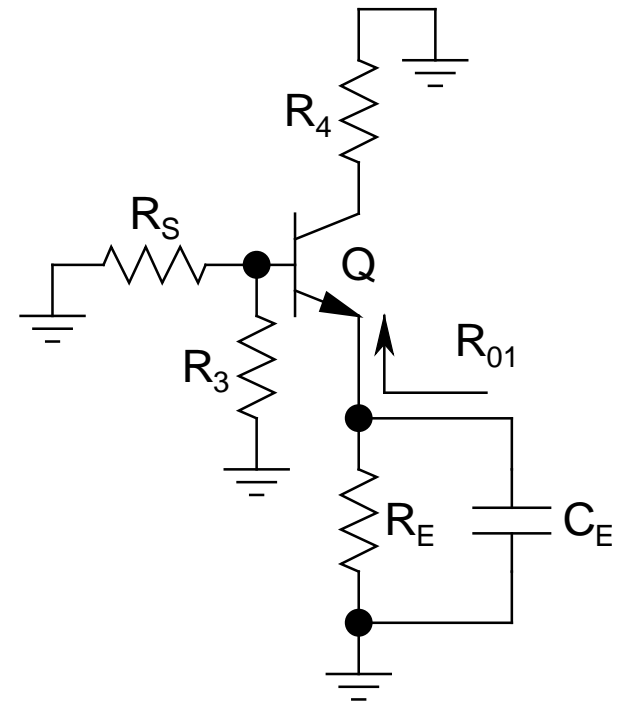
$$\Rightarrow f_2 = 1/(2\pi\tau_2) = 48.8 \text{ Hz}$$



➤ C_C :

- *Short C_E and C_B*

- By inspection, the *Thevenin resistance* seen by C_C :

$$R_C^\infty = R_C + R_L = 7 \text{ k}\Omega$$

$$\Rightarrow \tau_3 = R_C^\infty C_C = 350 \text{ ms}$$

$$\Rightarrow f_3 = 1/(2\pi\tau_3) = 0.45 \text{ Hz}$$

- Thus, the *lower cutoff frequency* of the circuit:

$$f_L = \left[f_1^2 + f_2^2 + f_3^2 \right]^{1/2} = 48.8 \text{ Hz}$$

➤ Note that f_L is equal to f_2 (contributed by C_E)

➤ Now let's attempt to *minimize* the *total capacitance requirement* of the circuit

➤ ***Minimization of the Total Capacitance:***

- From the previous analysis, we note that C_E *sees the least Thevenin resistance across its two terminals*

⇒ *Let's choose C_E to contribute the DP f_d , and let C_C and C_B each contribute poles at $f_d/10$*

$$\Rightarrow 48.8 = \sqrt{f_d^2 + 2(f_d/10)^2}$$

$$\Rightarrow f_d = 48.3 \text{ Hz and } f_d/10 = 4.83 \text{ Hz}$$

- Thus:

$$C_E = 1/(2\pi f_d R_E^\infty) = 101.1 \text{ } \mu\text{F}$$


$$C_B = 1/[2\pi(f_d/10)R_B^\infty] = 11 \text{ } \mu\text{F}$$

$$C_C = 1/[2\pi(f_d/10)R_C^\infty] = 4.7 \text{ } \mu\text{F}$$

- Thus, the *total capacitance* requirement comes out to be *116.8 μF* , for the *same f_L of 48.8 Hz*
- The *original circuit* had a *total capacitance* of *200 μF*
- Thus, this approach gave a *cost saving* of almost *42%* in terms of the *capacitors*
- As an *exercise*, you can pick *either C_C or C_B* to *contribute f_d* , and find the *total capacitance* requirement for each case
- Finally, after all, this is a *heuristic*
- To get the *absolute minimum value* of the *total capacitance*, we need to *formulate the problem*, and *find the minima of the function mathematically*

- **Tilt/Sag:**

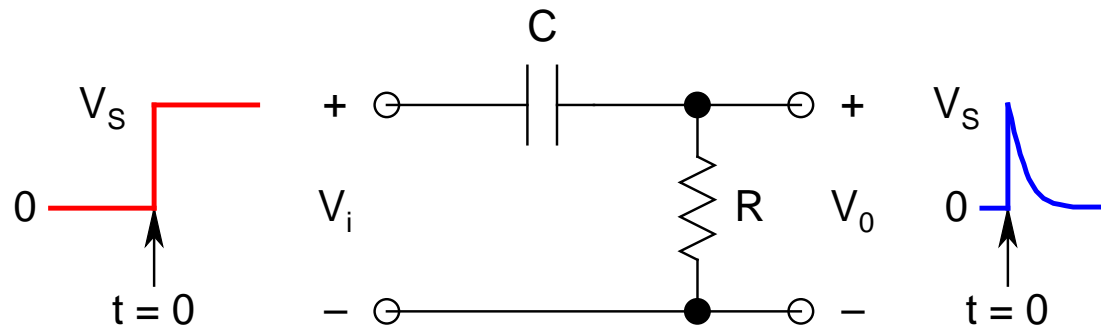- For **pulse/square wave excitation**, f_L dictates the amount of **tilt/sag** present in the **output**
- **Due to f_L** , the circuit effectively behaves like a **HPF**, represented by a simple **RC circuit**
- Under **step input**, the **output** would be a **spike**



➤ Thus:

$$V_0 = V_S \exp(-t/\tau_L)$$


$$\tau_L = RC = 1/\omega_L \quad (\omega_L = 2\pi f_L)$$

➤ For $t \ll \tau_L$:

$$\begin{aligned} V_0 &\approx V_S(1 - t/\tau_L) \\ &= V_S(1 - \omega_L t) \\ &= V_S(1 - 2\pi f_L t) \end{aligned}$$

➤ Thus, *V_0 drops linearly with time*

➤ *Quantified by percent tilt/sag (P)*

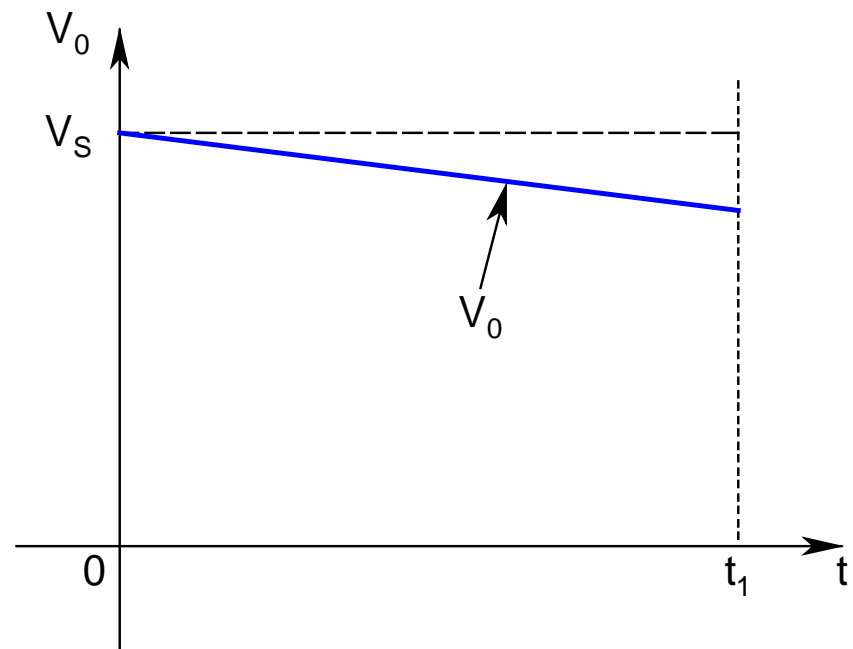

$$\begin{aligned} \text{➤ } P &= [(V_S - V_0)/V_S] \times 100\% \\ &= (t_1/\tau_L) \times 100\% \end{aligned}$$


t_1 = *Time at which the tilt is measured*

➤ For *square wave input*, $t_1 = T/2$ (T = *period* = $1/f$, f = *cycle frequency*)

$$\begin{aligned} \Rightarrow P &= [T/(2\tau_L)] \times 100\% = [\omega_L/(2f)] \times 100\% \\ &= (\pi f_L/f) \times 100\% \end{aligned}$$

➤ *Note: P is directly proportional to f_L and inversely proportional to f*

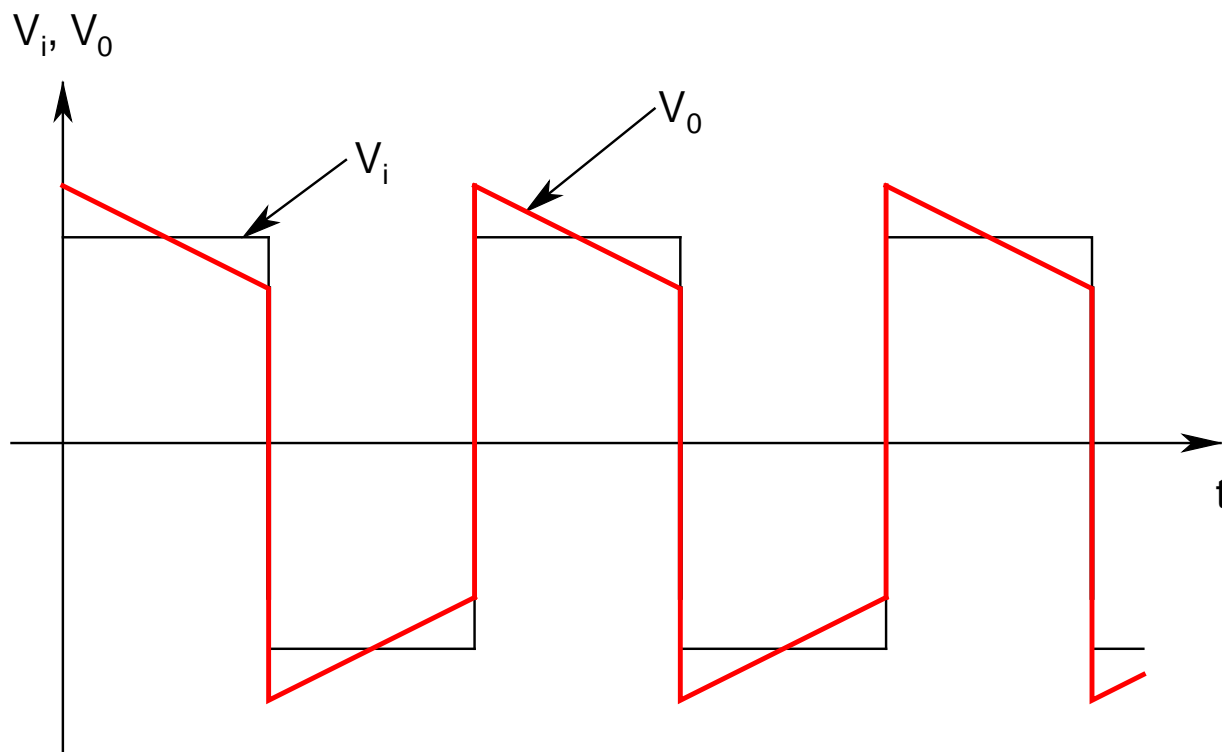\Rightarrow *Circuits having low f_L , will show significant amount of tilt/sag at low frequencies*



Tilt/Sag

High-Frequency Response


- Will consider *3 methods*:
 - *Exact Analysis*:
 - The *most accurate* and the *most rigorous*
 - *Gives information about all poles and zeros of the system*
 - *Miller Effect Approximation*:
 - *One level of approximation*
 - *Gives information about the Dominant Pole (DP) and one Non-Dominant Pole (NDP)*

➤ *Zero-Value Time Constant (ZVTC)*


Technique:

- *The easiest one*
- *Information regarding only the DP*
- *Suppresses information about all other poles and zeros of the system*
- *Reasonable accuracy*
- *Underestimates f_H slightly (better than overestimating and not achieving it!)*
- *Based on heuristic*
- *Similar to the IVTC technique, based on an algorithm*

- *Exact Analysis of a CE Stage:*

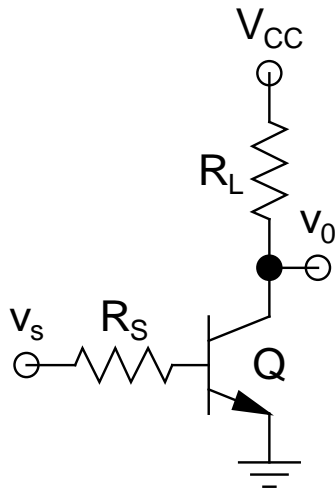

ac Schematic

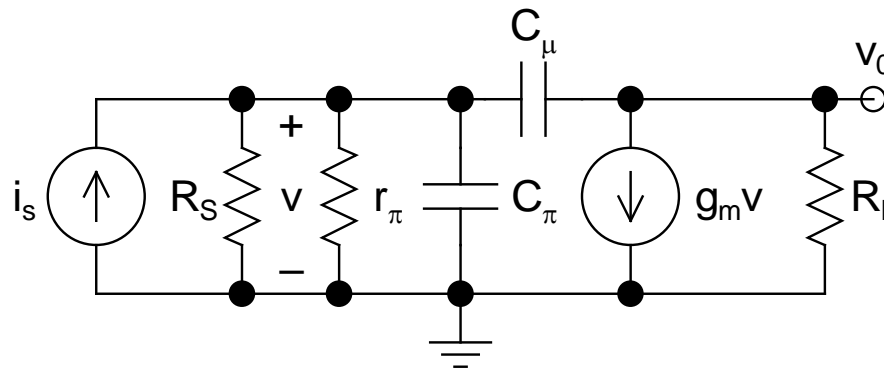

High-Frequency Equivalent

- *Biasing circuits omitted for simplicity*
- *Converted input v_s to its Norton equivalent*

➤ ***KCL at input node*** (using ***Laplace operator*** $s = j\omega$ and $R = R_S || r_\pi$):

$$\begin{aligned} i_s &= v/R + sC_\pi v + sC_\mu(v - v_0) \\ &= [1/R + s(C_\pi + C_\mu)]v - sC_\mu v_0 \end{aligned}$$

➤ ***KCL at output node***:

$$sC_\mu(v_0 - v) + g_m v + v_0/R_L = 0$$

$$\Rightarrow v = -\frac{1/R_L + sC_\mu}{g_m - sC_\mu} v_0$$

$$\Rightarrow \frac{v_0}{i_s}(s) = -\frac{R_L R (g_m - sC_\mu)}{1 + s(R_L C_\mu + RC_\mu + RC_\pi + g_m R_L RC_\mu) + s^2 R_L RC_\pi C_\mu}$$

➤ Thus, the *voltage gain*:

$$A_v(s) = \frac{V_0}{V_s} = -\frac{g_m R_L R}{R_s} \frac{(1 - sC_\mu / g_m)}{1 + sa + s^2 R_L R C_\pi C_\mu} \quad (1)$$

$$a = R_L C_\mu + R(C_\pi + C_\mu) + g_m R_L R C_\mu$$

➤ Hence, the circuit has *one zero* and *two poles*

$$\Rightarrow A_v(s) = A_{v0} \frac{(1 - s/z_1)}{(1 - s/p_1)(1 - s/p_2)} \quad (2)$$

$$\begin{aligned} A_{v0} &= \textit{midband gain} = -g_m R_L R / R_s \\ &= -g_m R_L r_\pi / (r_\pi + R_s) \end{aligned}$$

- $z_1 (= g_m/C_\mu)$: *positive real zero*
- The *frequency* corresponding to z_1 occurs at $z_1/(2\pi)$, which is *extremely high*, and generally, is *not of much consequence*
- *Computation of the two poles p_1 and p_2 is slightly more tricky*
- From Eqs.(1) and (2), it is obvious that *both p_1 and p_2 are real and negative*

- To find these, *write the denominator* of Eq.(1) as:

$$\begin{aligned} D(s) &= (1 - s/p_1)(1 - s/p_2) \\ &= 1 - s(1/p_1 + 1/p_2) + s^2/(p_1 p_2) \end{aligned} \quad (3)$$

- *Matching coefficients* with Eq.(2), we can get p_1 and p_2 , however, the *resulting algebra* will become *extremely tedious*
- Hence, we invoke the *Dominant Pole Approximation* (DPA)


➤ **DPA:**

- The *smallest pole* [*Dominant Pole* (DP)] is *at least 10 times away from its nearest pole*
- This is an *excellent approximation for practical analog circuits*

➤ *Apply this approximation* and *assume p_1 to be the DP* and *at least 10 times away from p_2* [*Non-Dominant Pole* (NDP)]

➤ The *pole frequencies* are $|p_1|/(2\pi)$ and $|p_2|/(2\pi)$

➤ *Note:* $|p_1|/(2\pi)$ is the *Upper Cutoff Frequency* (f_H)

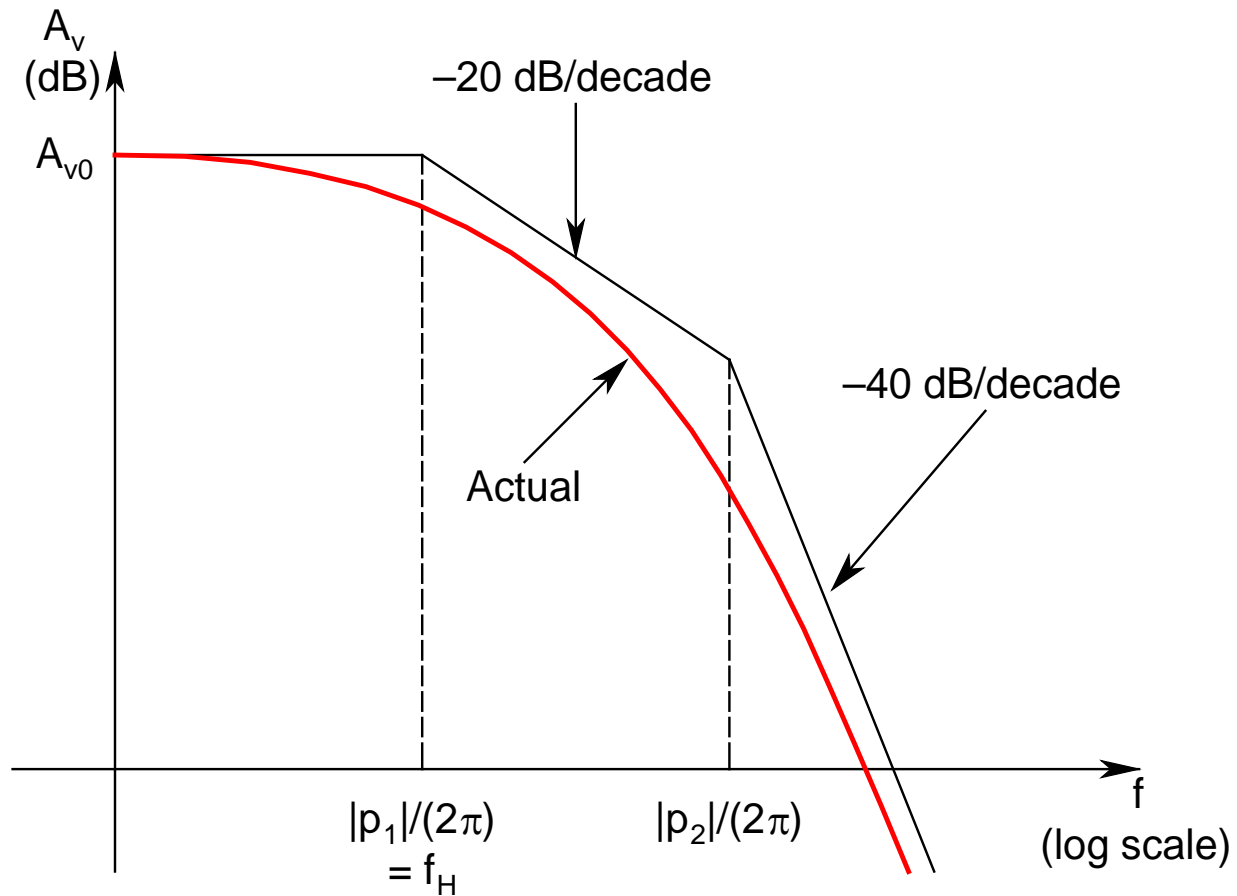

Bode Plot of the Frequency Response of a 2-Pole System

- **2-pole system**
- **For frequencies till the first pole p_1 , gain remains constant at its midband value of $20\log_{10}A_{v0}$**
- **Beyond this**, the **gain rolls off at -20 dB/decade till the second pole p_2 is encountered**
- **After this**, the **gain rolls off at -40 dB/decade**, and **eventually crosses zero**
- **Beyond this**, the circuit actually **attenuates the input signal instead of amplifying it (gain magnitude drops below unity)**

- *It's assumed that z_1 is $\gg |p_2|$*
- *Task remains to find p_1 and p_2*
- *Under DPA*, Eq.(2) can be simplified as:


$$D(s) \approx 1 - s/p_1 + s^2/p_1 p_2 \quad (4)$$
- *Comparing* Eq.(4) with the *denominator* of Eq.(1):

$$p_1 = -\frac{1}{(R_S \parallel r_\pi)C_\pi + [(R_S \parallel r_\pi) + R_L + g_m (R_S \parallel r_\pi)R_L]C_\mu}$$


$$p_2 = -\left(\frac{1}{R_L C_\mu} + \frac{1}{(R_S \parallel r_\pi)C_\pi} + \frac{1}{R_L C_\pi} + \frac{g_m}{C_\pi} \right)$$

- In general, $|p_2| \gg |p_1|$
- **Ex.**: $I_C = 1 \text{ mA}$, $\beta = 200$, $R_S = 1 \text{ k}\Omega$, $R_L = 2 \text{ k}\Omega$, $C_\pi = 10 \text{ pF}$, $C_\mu = 0.5 \text{ pF}$
 $\Rightarrow DPF = 3.8 \text{ MHz}$, $NDPF = 798.8 \text{ MHz}$, $ZF = 12.3 \text{ GHz}$, and $f_H = DPF = 3.8 \text{ MHz}$
- **Note**: Even for a *simple CE circuit*, the *analysis is so cumbersome*, and the *results are so complicated*
- *Definitely not acceptable for routine application, particularly for circuits having more than one active device*

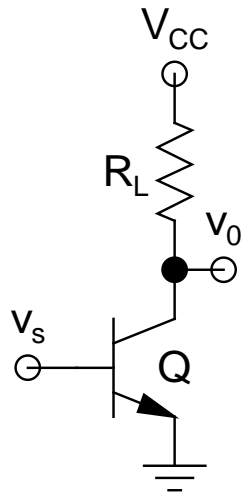- *Miller Effect Approximation:*
 - *Technique by which an input-output coupled circuit can be decoupled by removing the coupling element*
 - This *removal* is done by *splitting* it into *two components* - putting *one in the input circuit*, and the *other in the output circuit*
 - We take the *same example* as the *CE circuit* discussed earlier, but now *without R_S*



ac Schematic

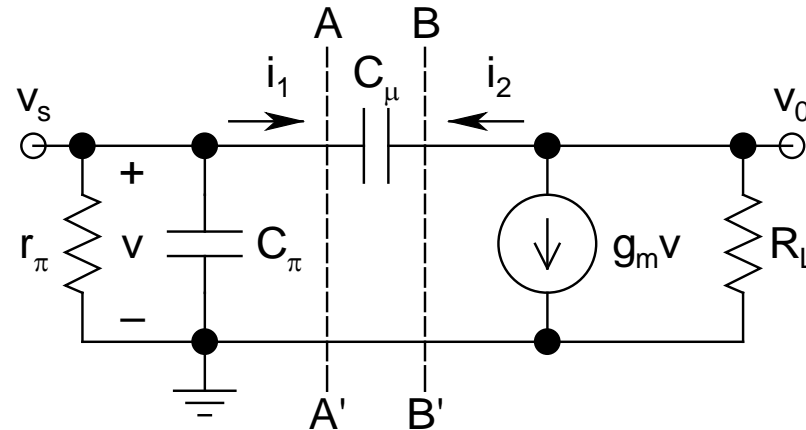

High-Frequency Equivalent

- *Identify C_μ as the input-output coupling element*
- After *application* of the *technique*, this *coupling element* will be *removed* by *splitting* it into *two parts* - *one at input*, *other at output*

➤ These *two parts* can be found by *evaluating* the *impedances* looking into the *planes* AA' and BB'

➤ *KCL at output node:*

$$g_m v + v_0/R_L + sC_\mu(v_0 - v) = 0$$

➤ Noting that $v = v_s$, the *voltage gain*:

$$A_v(s) = v_0/v_s = -g_m R_L (1 - sC_\mu/g_m) / (1 + sR_L C_\mu)$$

⇒ *Midband or low-frequency gain*:

$$A_v(0) = -g_m R_L$$

This result can also be written from inspection

- *Current entering plane AA' :*

$$i_1 = sC_\mu(v - v_0) = sC_\mu[1 - A_v(s)]v$$

- Hence, the *admittance* looking into the *plane* AA':

$$y|_{AA'} = i_1/v = sC_\mu[1 - A_v(s)]$$

- This *admittance* is *capacitive* in nature, and is known as the *Miller Capacitance* C_M :

$$C_M = C_\mu[1 - A_v(s)]$$

- Now, since $A_v(s)$ is a function of frequency, *so would* $C_M \Rightarrow$ *Problem!*

- Here, we invoke the *Miller Effect Approximation* (MEA)
 - $A_v(s)$ is replaced by $A_v(0)$, i.e., by its *midband value*, which is a *constant*
 - Thus, C_M becomes a constant with a value of

$$C_M = [1 - A_v(0)]C_\mu = (1 + g_m R_L)C_\mu$$
- Thus, $C_M \gg C_\mu$, since, in general, $g_m R_L \gg 1$
- This effect is known as the *Miller Effect Multiplication*
- *Care: The gain that multiplies C_μ is across its two ends*

- Similarly, *current entering plane BB'*:

$$i_2 = sC_\mu(v_0 - v) = sC_\mu[1 - 1/A_v(s)]v_0$$

- Hence, the *admittance* looking into the *plane BB'*:


$$y'|_{BB'} = i_2/v_0 = sC_\mu[1 - 1/A_v(s)]$$

- Again *replacing* $A_v(s)$ by $A_v(0)$, we get:

$$C'_M = [1 - 1/A_v(0)]C_\mu = [1 + 1/(g_m R_L)]C_\mu$$

- In general, $g_m R_L \gg 1 \Rightarrow C'_M \simeq C_\mu$

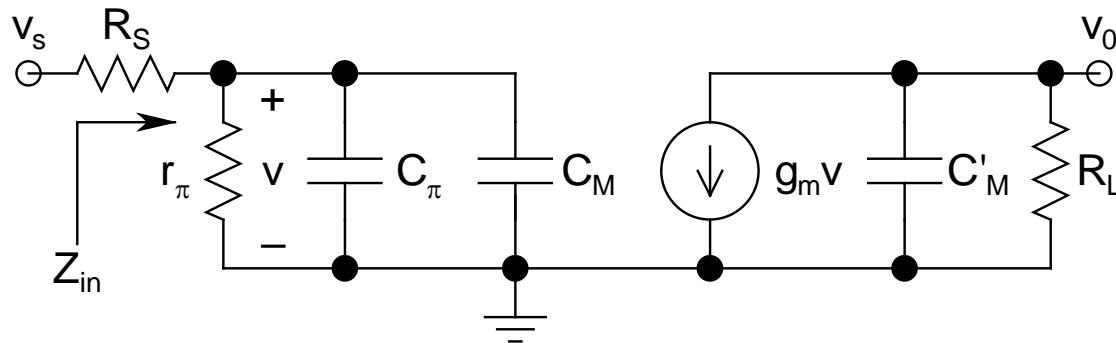- C_μ can now be **removed** as the **coupling element**, **split into 2 parts** C_M and C'_M , with C_M appearing in the **input circuit** and C'_M appearing in the **output circuit**
- Now, **include R_S** - note that the circuit is **completely decoupled** now



Complete Circuit Including R_S

$$\triangleright Z_{\text{in}} = r_{\pi} \parallel [1/(sC_T) = r_{\pi}/(1 + sr_{\pi}C_T)]$$

$$C_T = C_{\pi} + C_M$$

$$\Rightarrow v = \frac{Z_{\text{in}}}{Z_{\text{in}} + R_S} v_s$$

$$= \frac{r_{\pi}}{(R_S + r_{\pi}) \left[1 + sr_{\pi}R_S C_T / (R_S + r_{\pi}) \right]} v_s$$

$$v_0 = -g_m \left(R_L \parallel \frac{1}{sC'_M} \right) v = -\frac{g_m R_L}{1 + sR_L C'_M} v$$

➤ Thus:

$$A_v(s) = \frac{V_0}{V_s}$$
$$= -g_m R_L \frac{r_\pi}{R_S + r_\pi} \frac{1}{\left[1 + sR_S r_\pi C_T / (R_S + r_\pi)\right] (1 + sR_L C'_M)}$$

➤ *Comparing* this expression with

$$A_v(s) = \frac{A_{v0}}{(1 - s/p_1)(1 - s/p_2)}$$

we note that the *denominator* is already in a *factorized form*

- $A_{v0} = \text{midband gain} = -g_m R_L r_\pi / (R_S + r_\pi)$
- The *transfer function* shows that the system has *two negative real poles* and *no zero*
 \Rightarrow *Information regarding the zero is suppressed by this technique*
- Also, the *two poles* obtained by *this technique* are *not identical* to those obtained from the *exact analysis*

➤ Pole p_1 (p_2) is referred to as the pole of the *input* (*output*) circuit

➤ Also, $|p_1| \ll |p_2|$

$\Rightarrow p_1$ (p_2) is the *DP* (*NDP*) of the system

➤ *Matching coefficients:*

$$p_1 = -\frac{R_S + r_\pi}{R_S r_\pi} \frac{1}{C_T} = -\frac{1}{(R_S \parallel r_\pi) [C_\pi + (1 + g_m R_L) C_\mu]}$$

$$p_2 = -\frac{1}{R_L C'_M}$$

➤ Obviously, $|p_1| \ll |p_2|$

- Thus, *using DPA*: $f_H = |p_1|/(2\pi)$
- Applying *this technique* to the *previous example*, $f_H = 3.9 \text{ MHz}$ and *NDP frequency* = *156 MHz*
 - *Error of only 2.6% in f_H* , but the *ease of solution is much more*
- Thus, *this technique* is *quite popular* in getting a *quick estimate* of f_H , even though the *solution* may not be *exact*
- *Care*: *The gain in the multiplicative factor is that between the input and output terminals of the capacitor*

- *The Zero-Value Time Constant (ZVTC) Technique:*
 - *Gives information only about the DP of the system*
 - *Suppresses all information regarding other poles and zeros*
 - *The ease of application of this technique is mind-boggling*

- *Slightly less accurate*
- *The maximum error can be as high as 22%*
- *Underestimates f_H*
 - *Far better than overestimation and eventually not achieving it*
- *Applicable only for circuits that have a DP*
 - *Fortunately, almost all analog circuits of interest do have a DP*

- *The Algorithm:*

- *Null all independent sources to the circuit*
 - *Short all independent voltage sources*
 - *Open all independent current sources*
 - *DO NOT TOUCH DEPENDENT SOURCES*
- *Name the capacitors C_i ($i = 1-n$)*
- *Consider C_1 and assign zero values to all other capacitors (thus the name!)*
 - Thus, *except C_1 , all other capacitors will open out*
- *Determine the Thevenin Resistance (R_1^0) across the two terminals of C_1*

- *Find the time constant τ_1 associated with C_1*
 $(\tau_1 = R_1^0 C_1)$
- *Repeat for all other capacitors, taking one at a time, and find all the rest of the time constants $(\tau_2, \tau_3, \dots, \tau_n)$*
- Determine the *net time constant* τ_{net} by *summing up* all the *individual time constants*

$$\Rightarrow \tau_{\text{net}} = \sum_{i=1}^n \tau_i$$
- Then the *Upper Cutoff Frequency* f_H is simply given by: $f_H = 1/(2\pi\tau_{\text{net}})$

- *Note: The capacitor contributing the largest time constant, in effect, determines f_H*
- *The technique suppresses all information regarding other poles and zeros*
- Will present *several examples* to understand the *application* of this *technique*
- Some *topologies* will be appearing *frequently*, known as *Standard Forms*, which can be treated as *individual modules*, and the *results can be used freely*

- **CE:**

- Refer to the *high-frequency equivalent* given in the *exact analysis*

- **2 capacitors:** C_π and C_μ

- \Rightarrow *2 time constants:* τ_1 and τ_2

- C_π :

- **C_μ opens up**

- *By inspection:*

$$R_\pi^0 = R_S \parallel r_\pi$$

$$\Rightarrow \tau_1 = R_\pi^0 C_\pi$$


➤ C_μ :

- C_π opens up
- This is one *Standard Form*, known as the *Three-Legged Creature*
- Show that:

$$R_\mu^0 = R + R_L + g_m R_L R \quad (R = R_S \parallel r_\pi)$$

$$\Rightarrow \tau_2 = R_\mu^0 C_\mu$$

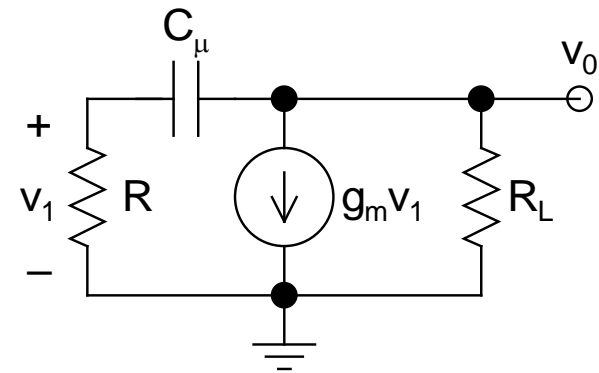- Thus, $\tau_{\text{net}} = \tau_1 + \tau_2$, and $f_H = 1/(2\pi\tau_{\text{net}})$
- Note the *amazing simplicity* of the analysis



➤ Putting *values* of our previous *example*:

$$R_{\pi}^0 = 838.7 \, \Omega, \, \tau_1 = 8.4 \, \text{ns}$$


$$R_{\mu}^0 = 67.4 \, \text{k}\Omega, \, \tau_2 = 33.7 \, \text{ns}$$

$$\Rightarrow \tau_{\text{net}} = 42.1 \, \text{ns} \quad \text{and} \quad f_H = 3.8 \, \text{MHz}$$


➤ This is *identical* to the *result* obtained from the *exact analysis*, however, at a *fraction* of the *effort*!

➤ Also, *τ_2 is the dominant time constant*
 $\Rightarrow f_H$ *is primarily dictated by C_{μ}*

- ***CS:***

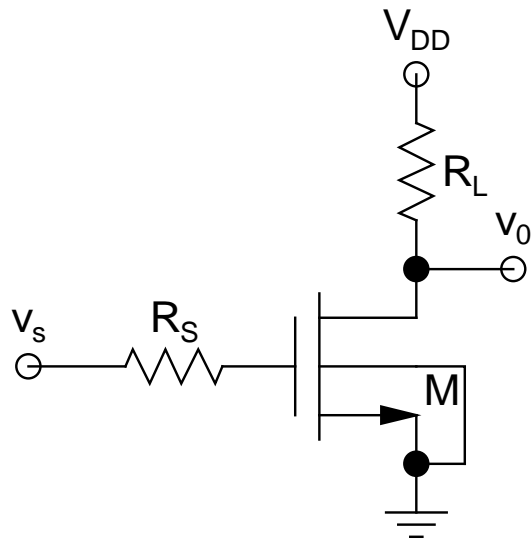

ac Schematic

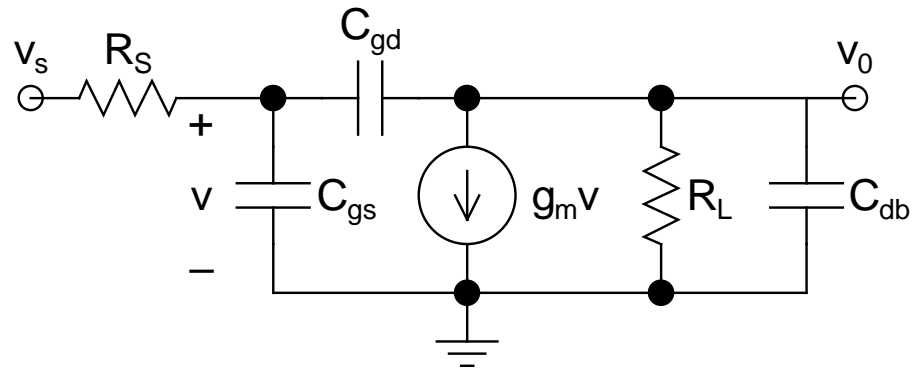

High-Frequency Equivalent

➤ ***C_{sb} absent (Why?)***

➤ **3 capacitors**: C_{gs} , C_{gd} , and C_{db}

⇒ **3 time constants**: τ_1 , τ_2 , and τ_3

➤ C_{gs} :

- **C_{gd} and C_{db} open up**

- **By inspection**:

$$R_{gs}^0 = R_S$$

$$\Rightarrow \tau_1 = R_{gs}^0 C_{gs}$$

➤ C_{gd} :

- **C_{gs} and C_{db} open up**

- **By inspection**, it can be *identified* as a **Three-Legged Creature**

- Thus:

$$R_{gd}^0 = R_S + R_L + g_m R_S R_L$$

$$\Rightarrow \tau_2 = R_{gd}^0 C_{gd}$$

➤ ***C_{db}***:

- *C_{gs} and C_{gd} open up*

- *By inspection:*

$$R_{db}^0 = R_L$$


$$\Rightarrow \tau_3 = R_{db}^0 C_{db}$$

➤ Thus:


$$\tau_{net} = \tau_1 + \tau_2 + \tau_3, \text{ and } f_H = 1/(2\pi\tau_{net})$$

➤ ***Mind-bogglingly simple*** - isn't it?

- **CB:**

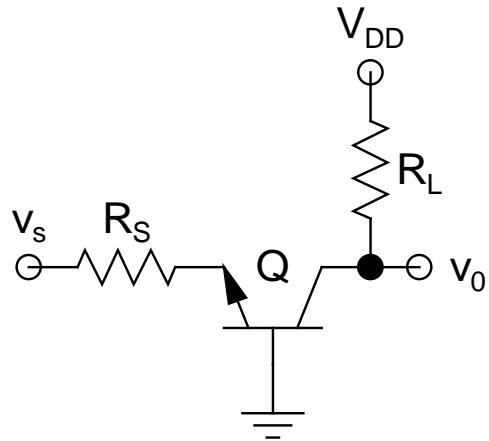

ac Schematic

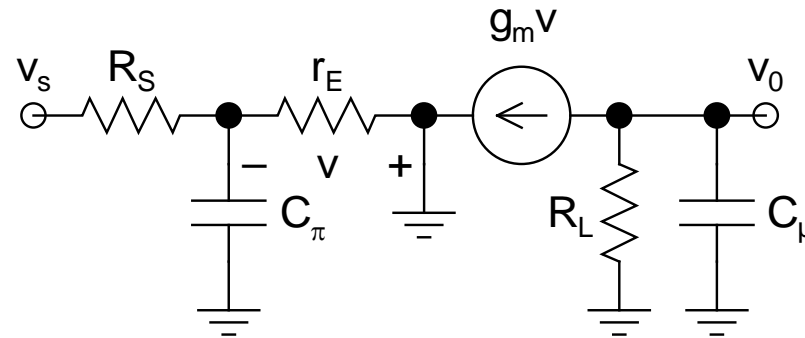

High-Frequency Equivalent

➤ *Note that there is no input-output coupling capacitor present in this circuit*

⇒ *Miller effect will be absent*, and the *circuit will have very high f_H*

➤ C_π :

$$R_\pi^0 = R_S \parallel r_E \quad \text{and} \quad \tau_1 = R_\pi^0 C_\pi$$

➤ C_μ :

$$R_\mu^0 = R_L \quad \text{and} \quad \tau_2 = R_\mu^0 C_\mu$$

➤ Taking the *values* of our previous *example*:


$$R_\pi^0 = 25.34 \, \Omega, \quad \tau_1 = 0.253 \, \text{ns}$$

$$R_\mu^0 = 2 \, \text{k}\Omega, \quad \tau_2 = 1 \, \text{ns}$$


$$\Rightarrow \tau_{\text{net}} = 1.25 \, \text{ns} \quad \text{and} \quad f_H = 127.3 \, \text{MHz}$$

➤ *Note the enormous increase of f_H from about 4 MHz for a CE amplifier*

- **CG:**

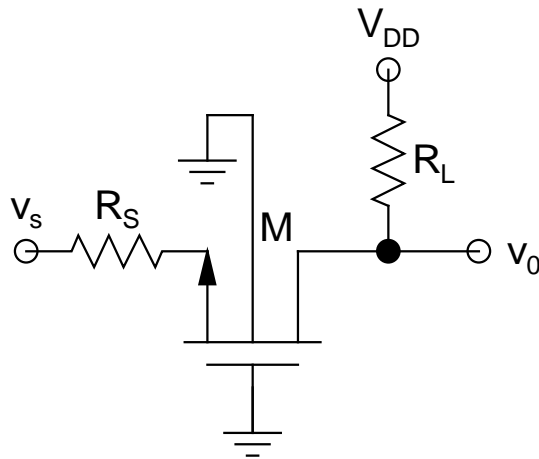

ac Schematic

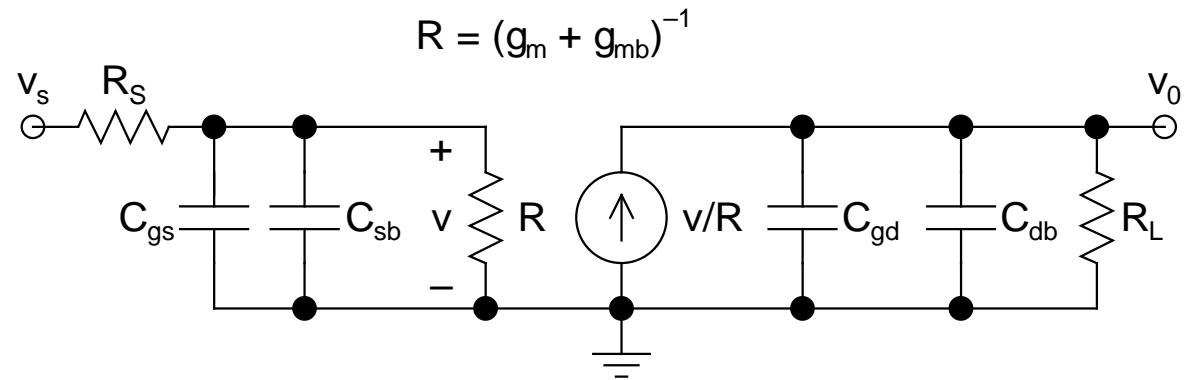


High-Frequency Equivalent


➤ *Note that all 4 capacitors would be present and none could be eliminated*

- *C_{gs} and C_{sb} are in parallel*
 - ⇒ *Can be clubbed to a single capacitor $C_1 = C_{gs} + C_{sb}$, with time constant τ_1*
- Also, *C_{gd} and C_{db} can be clubbed to another single capacitor $C_2 = C_{gd} + C_{db}$, with time constant τ_2*
- *Again note the absence of any input-output coupling capacitor*
 - ⇒ *This circuit should also have very high f_H*
- *C_1 : $R_1^0 = R_s \parallel R$ and $\tau_1 = R_1^0 C_1$*
- *C_2 : $R_2^0 = R_L$ and $\tau_2 = R_2^0 C_2$*

- **CC:**

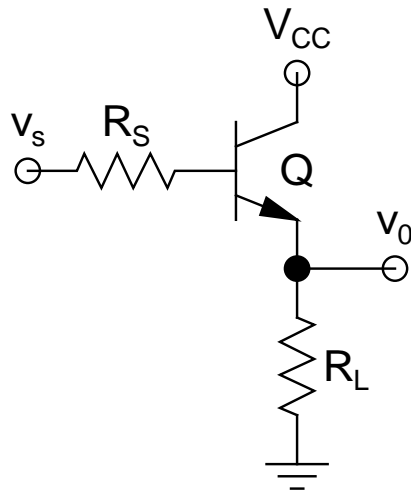

ac Schematic

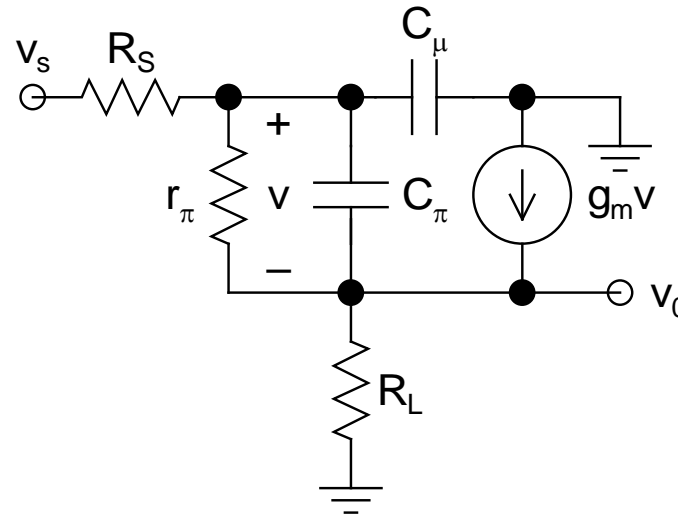

High-Frequency Equivalent

- *This circuit is slightly more involved - can't be done by inspection*
- *But we will have some other Standard Forms*

➤ This circuit has a *peculiar frequency response*

- *At midband:*

$$A_v = v_o/v_s = [R_L/(R_L + r_E)] \times [R_i/(R_i + R_S)]$$

$$R_i = r_\pi + (\beta + 1)R_L$$

- *Beyond f_H , as $f \uparrow$, reactance of $C_\pi \downarrow$ earlier than that of C_μ (since, in general, $C_\pi \gg C_\mu$)*
- *Eventually, reactance of C_π would approach zero, thus shorting out r_π*
- *Under this condition, circuit behaves like a simple voltage divider with a gain of $R_L/(R_L + R_S)$*
- *If $f \uparrow$ further, then eventually C_μ also will short out, and v_o would go to zero*

- Thus, the *frequency response* of this circuit looks like a *staircase*, having *two steps*


➤ C_π :

- R_π^0 *can't be obtained by inspection*
- *Analyze the circuit and show that:*

$$R_\pi^0 = r_\pi \parallel \left(\frac{R_S + R_L}{1 + g_m R_L} \right)$$

$$\Rightarrow \tau_1 = R_\pi^0 C_\pi$$

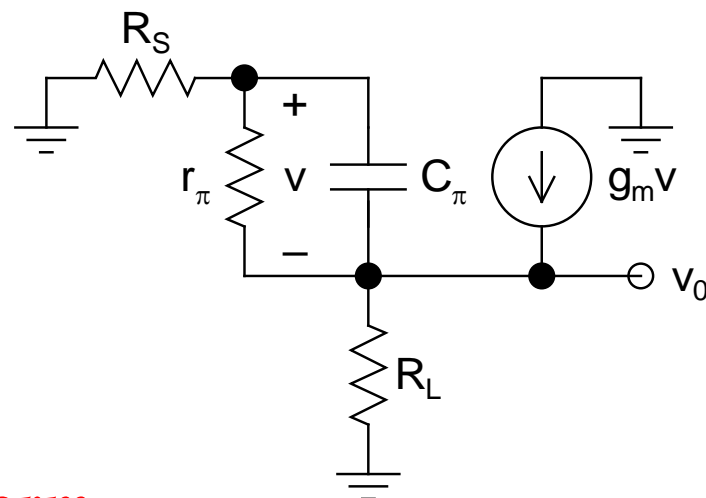- This is another *Standard Form* and the *topology should be carefully noted*



➤ C_μ :


- This is *relatively straightforward*
- *By inspection*:

$$R_{eq} = r_\pi + (\beta + 1)R_L$$


$$R_\mu^0 = R_S \parallel R_{eq}$$

$$\Rightarrow \tau_2 = R_\mu^0 C_\mu$$

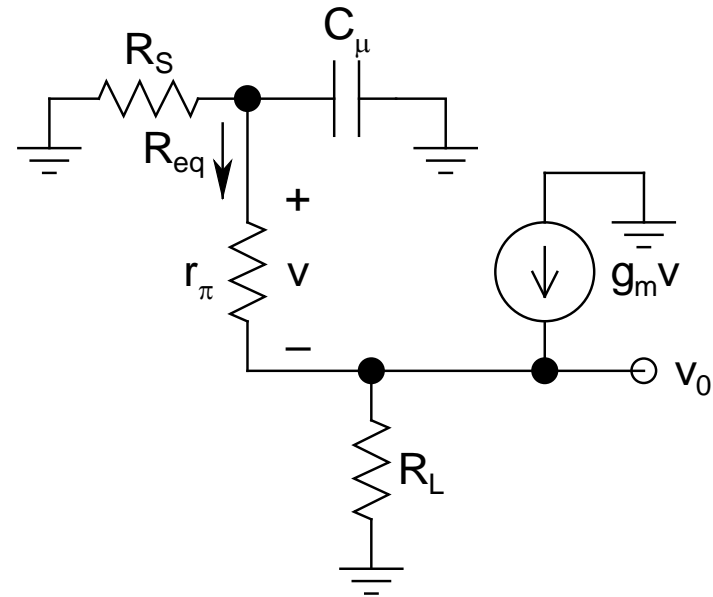
➤ *This circuit also has reasonably good frequency response*



- ***CD***:

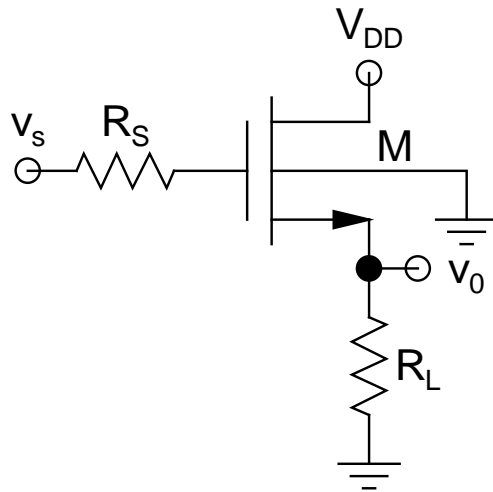

ac Schematic

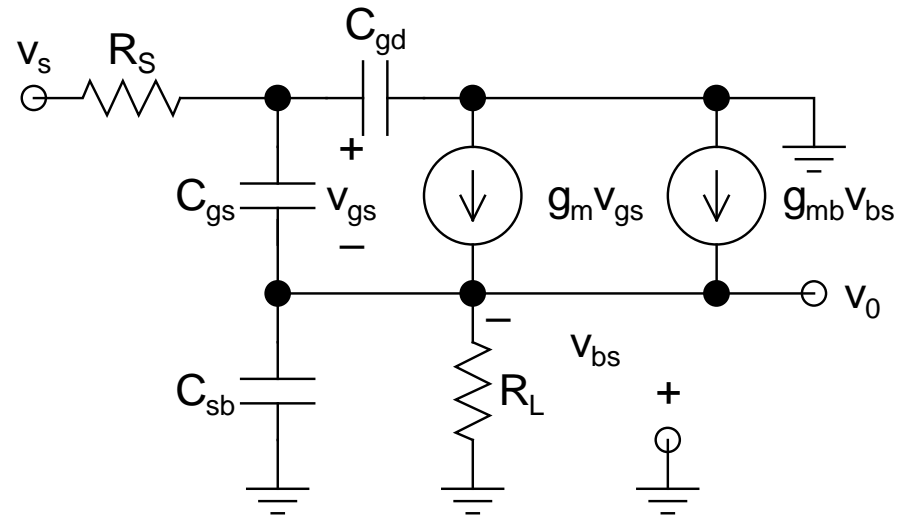

High-Frequency Equivalent

➤ ***C_{db} absent due to obvious reason***

➤ $V_{bs} = -V_0$

$\Rightarrow g_{mb}v_{bs}$ is simple a conductance g_{mb} , in parallel with R_L

\Rightarrow Club them to R [$= R_L || (1/g_{mb})$]

➤ C_{gs} :

▪ Standard Form sans r_π (CC)

$$\Rightarrow R_{gs}^0 = \frac{R_s + R}{1 + g_m R}$$

$$\Rightarrow \tau_1 = R_{gs}^0 C_{gs}$$

➤ C_{gd} :

▪ *By inspection:*

$$R_{gd}^0 = R_S$$

$$\Rightarrow \tau_2 = R_{gd}^0 C_{gd}$$

➤ C_{sb} :


▪ *By inspection:*

$$R_{sb}^0 = R \parallel (1/g_m)$$


$$\Rightarrow \tau_3 = R_{sb}^0 C_{sb}$$

➤ *Loving it? :)*

- ***CE(D)***:

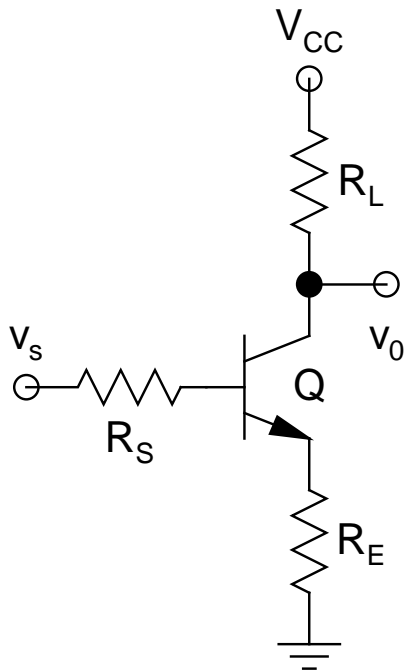

ac Schematic

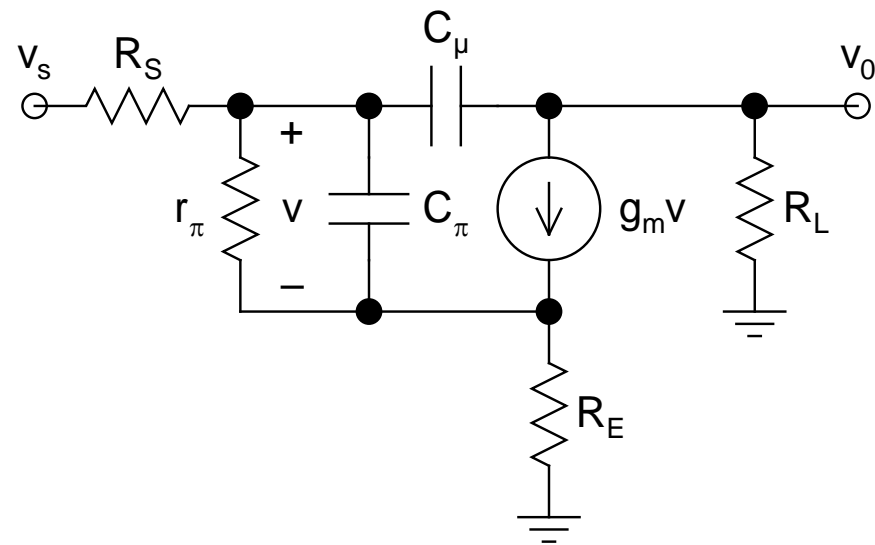

High-Frequency Equivalent

➤ C_π :

- *Standard Form* (similar to *CC*, with R_L replaced by R_E)

$$\Rightarrow R_\pi^0 = r_\pi \parallel \left(\frac{R_S + R_E}{1 + g_m R_E} \right)$$

$$\Rightarrow \tau_1 = R_\pi^0 C_\pi$$

➤ C_μ :

- *Slightly more complicated*
- *Remove C_π and look across 2 terminals of C_μ*
- *Can be represented by a 2-port network*

- *Show that:*

$$R_{eq} = R_S || R_{\pi}$$


$$\text{with } R_{\pi} = r_{\pi}(1 + g_m R_E)$$

$$G_m = g_m / (1 + g_m R_E)$$

- This can be *easily identified* as a *Three-Legged Creature*


$$\Rightarrow R_{\mu}^0 = R_{eq} + R_L + G_m R_{eq} R_L$$
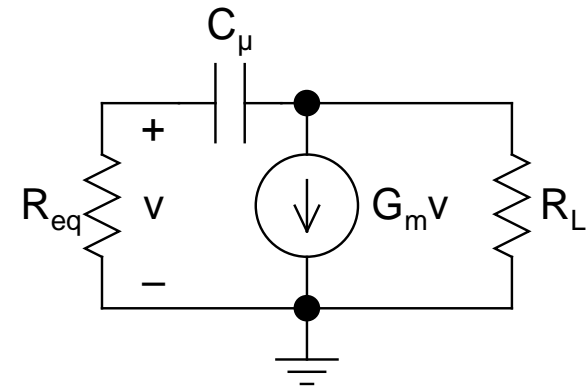
$$\Rightarrow \tau_2 = R_{\mu}^0 C_{\mu}$$




**2-Port Representation
of a CE(D) Stage**

- ***CS(D)***:

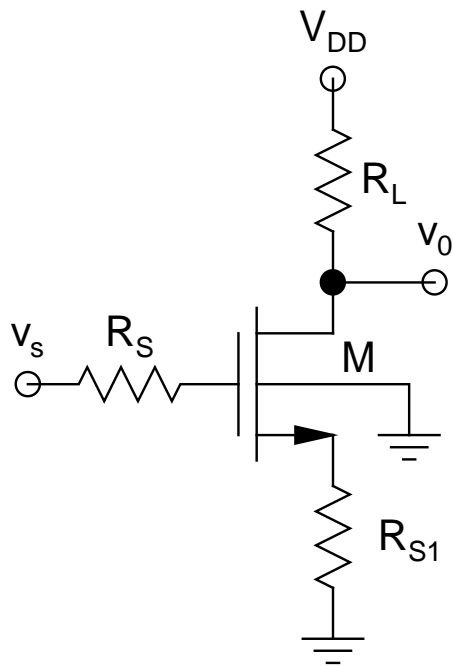


ac Schematic

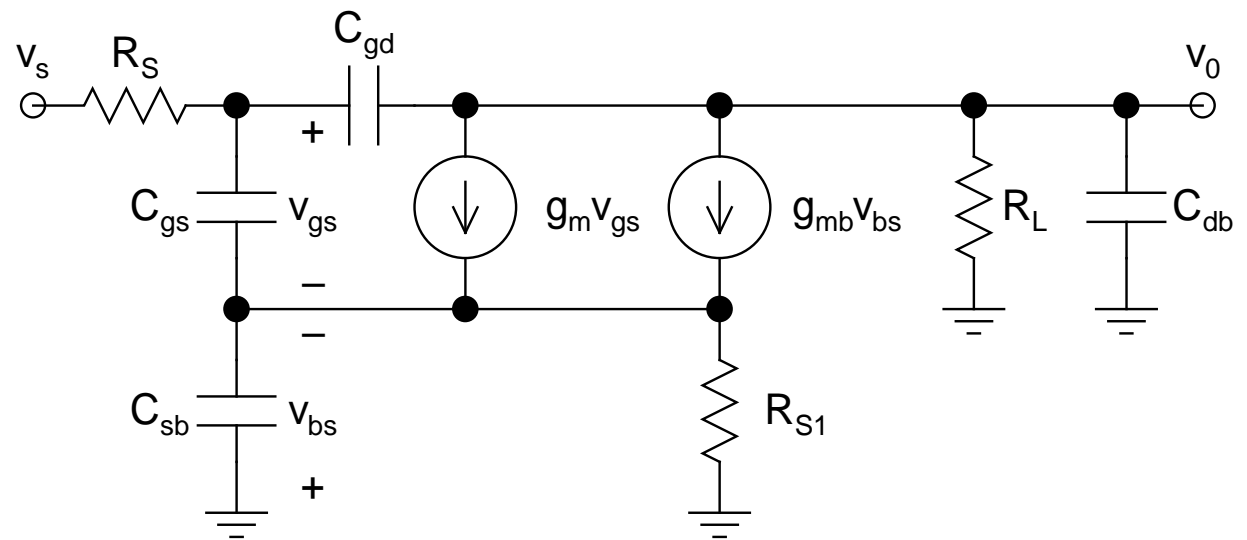

High-Frequency Equivalent

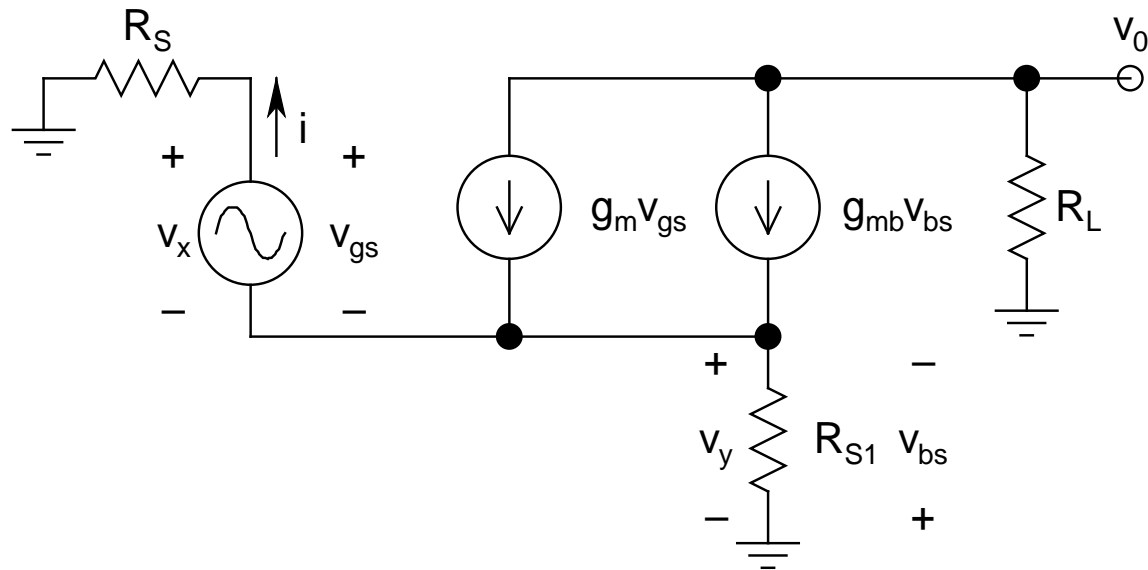- *Inarguably, the most complex module*
 - *All the capacitors will be present*
 - *None will have **Standard Form***
 - *Detailed analysis needed for each of them*
- C_{gs} :



- *Open all other capacitors*
- *Replace C_{gs} by a voltage source v_x*
- $v_{gs} = v_x$ and $v_{bs} = -v_y$
- $i = (v_x + v_y)/R_S$

$$= g_m v_{gs} + g_{mb} v_{bs} - v_y/R_{S1}$$


$$= g_m v_x - g_{mb} v_y - v_y/R_{S1}$$

$$\Rightarrow v_y = [R_{S1}(g_m R_S - 1)]v_x / (R_{S1} + R_S + g_{mb} R_S R_{S1})$$

$$\Rightarrow R_{gs}^0 = \frac{v_x}{i} = \frac{R_S + R_{S1} + g_{mb} R_S R_{S1}}{1 + (g_m + g_{mb}) R_{S1}}$$

$$\Rightarrow \tau_1 = R_{gs}^0 C_{gs}$$
- Note that *if body effect is neglected* (g_{mb} *ignored*), then it becomes *identical to that of a CD stage*

➤ C_{gd} :

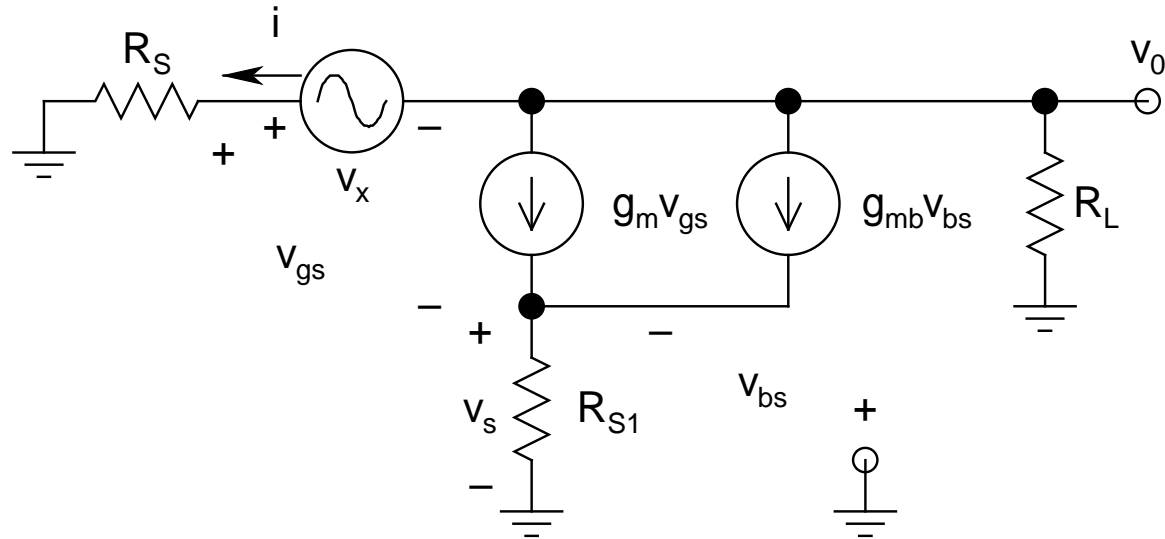

- *Open all other capacitors*
- *Replace C_{gd} by v_x*
- $v_{gs} = (v_0 + v_x - v_s)$ and $v_{bs} = -v_s$

- $i = (v_0 + v_x)/R_S$
- $v_s = (g_m v_{gs} + g_{mb} v_{bs})R_{S1}$
 $\Rightarrow v_s = g_m R_{S1}(v_0 + v_x)/[1 + (g_m + g_{mb})R_{S1}]$
- ***KCL at output node:***
 $i + g_m v_{gs} + g_{mb} v_{bs} + v_0/R_L = 0$
- ***The rest of the process involves huge amount of algebra!***
- ***Finally, if done right (check!)***

$$R_{gd}^0 = \frac{v_x}{i} = R_L \left[1 + g_m R_S + \frac{R_S}{R_L} - \frac{(g_m + g_{mb})g_m R_S R_{S1}}{1 + (g_m + g_{mb})R_{S1}} \right]$$

$$\Rightarrow \tau_2 = R_{gd}^0 C_{gd}$$

- *This is by far the most complicated calculation/expression*
- However, an *exact analysis* would have yielded a *4th-order transfer function* in ω , which had to be *solved* to get the *individual poles*
- *This is still simpler than that :)*


➤ *C_{db}*:

- *The easiest of the lot*
- *By inspection:*

$$R_{db}^0 = R_L$$

$$\Rightarrow \tau_3 = R_{db}^0 C_{db}$$


➤ C_{sb} :

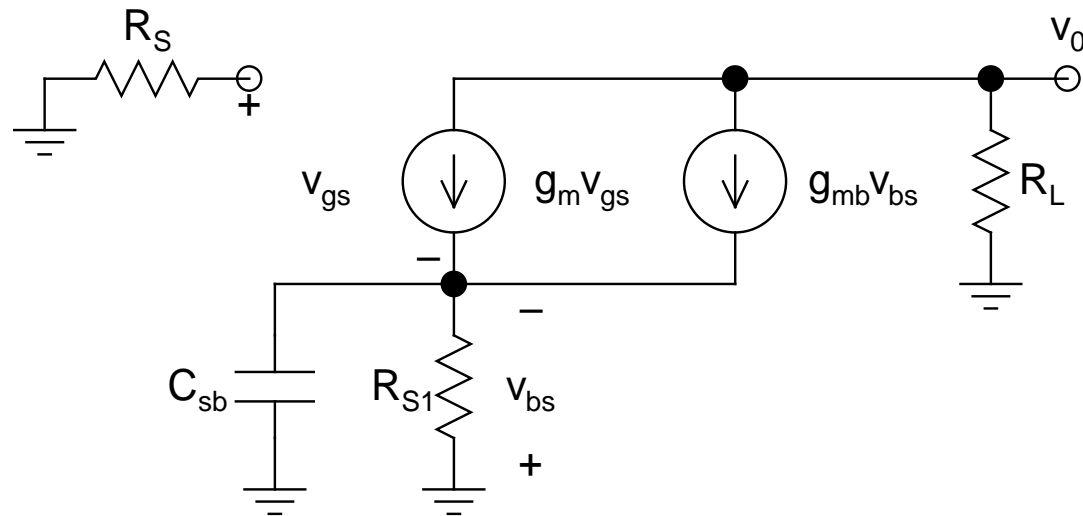

- *Analysis of this circuit is pretty straightforward*

$$R_{sb}^0 = \frac{R_{S1}}{1 + (g_m + g_{mb}) R_{S1}} \Rightarrow \tau_4 = R_{sb}^0 C_{sb}$$

- *npn Cascode:*

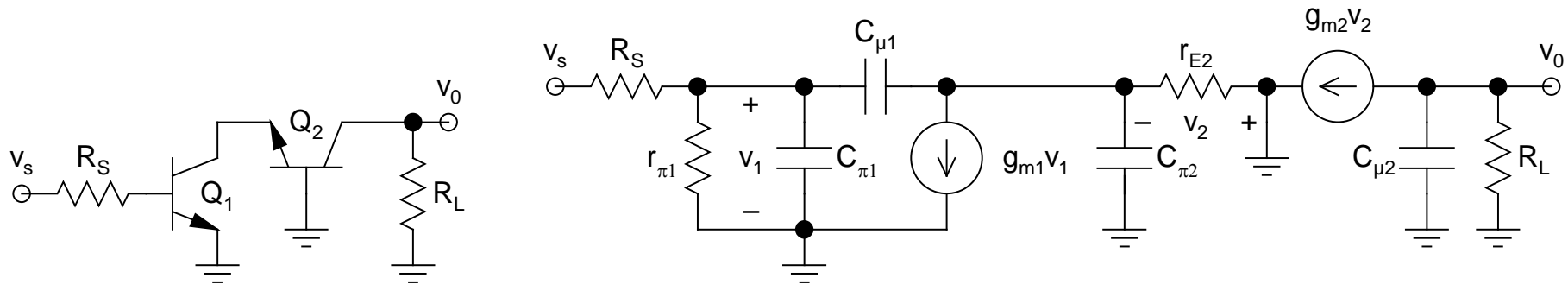

ac Schematic

High-Frequency Equivalent

- *Looks intimidating*, but *extremely easy to solve* (*just by inspection*)
- Also known as *Wideband* (or *Broadband*) *Amplifier* due to its *superb frequency response*

➤ **Reason:**

- *The circuit does have an input-output coupling capacitor ($C_{\mu 1}$)*
- *Miller Effect Multiplication Factor (MEMF) of $C_{\mu 1} = (1 - A_{v1})$*
 $A_{v1} = \text{voltage gain of } Q_1 = -r_{E2}/r_{E1} = -1$
(since Q_1 and Q_2 are biased with the same I_C)
 \Rightarrow Thus, the *MEMF of $C_{\mu 1}$ is only 2*
- For *NMOS Cascode* stage, the *MEMF of C_{gd1}* of M_1 (*CS stage*) will be $[1 + 1/(1 + \chi_2)]$ (*verify this expression*), which is *even less than 2*

➤ $C_{\pi 1}$:

▪ *By inspection:*

$$R_{\pi 1}^0 = R_S \parallel r_{\pi 1} \Rightarrow \tau_1 = R_{\pi 1}^0 C_{\pi 1}$$

➤ $C_{\mu 1}$:

▪ Can be easily identified as the *Three-Legged Creature*

$$\Rightarrow R_{\mu 1}^0 = R_{\pi 1}^0 + r_{E2} + g_{m1} R_{\pi 1}^0 r_{E2}$$

$$\Rightarrow \tau_2 = R_{\mu 1}^0 C_{\mu 1}$$

➤ $C_{\pi 2}$:

▪ *By inspection:*

$$R_{\pi 2}^0 = r_{E2} \Rightarrow \tau_3 = R_{\pi 2}^0 C_{\pi 2}$$

➤ $C_{\mu 2}$:

▪ *By inspection:*

$$R_{\mu 2}^0 = R_L \Rightarrow \tau_4 = R_{\mu 2}^0 C_{\mu 2}$$

➤ Generally, for this circuit, $C_{\pi 1}$ is the *dominant capacitor* that determines f_H , since it sees the *largest resistance*

➤ The *resistance seen by $C_{\mu 1}$* , which is the *largest for CE stage*, *becomes quite small here, due to the low gain of Q_1*


➤ Note how *simple* it is to use this *technique* even for *multi-stage amplifiers*!

- ***NMOS 2-Stage Cascaded CS:***


- *Except C_{sb} , all other capacitors will be present for both devices*

- *6 capacitors*

⇒ ***6 time constants***

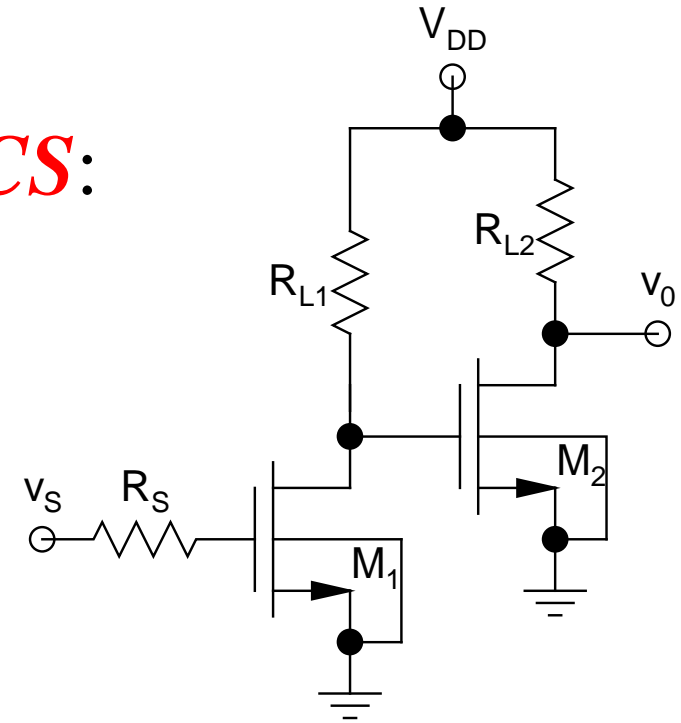

ac Schematic

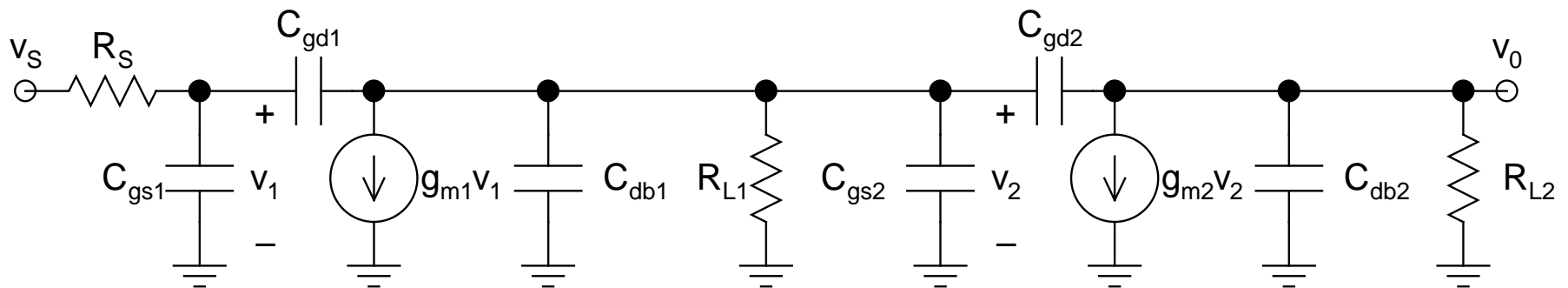

High-Frequency Equivalent

- **Note:** An *exact analysis* would have required *solving* a *6th-order equation in ω* !
- Let's perform a *quantitative analysis* of this circuit
- **Data:** $g_{m1} = 3 \text{ mA/V}$, $g_{m2} = 6 \text{ mA/V}$, $C_{gs1} = 5 \text{ pF}$, $C_{gs2} = 10 \text{ pF}$, $C_{gd1} = C_{gd2} = 1 \text{ pF}$, $C_{db1} = C_{db2} = 2 \text{ pF}$, $R_S = 10 \text{ k}\Omega$, $R_{L1} = 10 \text{ k}\Omega$, and $R_{L2} = 5 \text{ k}\Omega$.
 - **C_{gs1} :**

$$R_{gs1}^0 = R_S = 10 \text{ k}\Omega \quad \Rightarrow \quad \tau_1 = R_{gs1}^0 C_{gs1} = 50 \text{ ns}$$

■ C_{gd1} :

$$R_{gd1}^0 = R_S + R_{L1} + g_{m1} R_S R_{L1} = 320 \text{ k}\Omega$$

$$\Rightarrow \tau_2 = R_{gd1}^0 C_{gd1} = 320 \text{ ns}$$

■ C_{db1} and C_{gs2} in parallel

$$\Rightarrow \text{Club them to a single capacitor } C_3 = C_{db1} + C_{gs2} \\ = 12 \text{ pF}$$

$$R_3^0 = R_{L1} = 10 \text{ k}\Omega$$

$$\Rightarrow \tau_3 = R_3^0 C_3 = 120 \text{ ns}$$

- C_{gd2} :

$$R_{gd2}^0 = R_{L1} + R_{L2} + g_{m2} R_{L1} R_{L2} = 315 \text{ k}\Omega$$

$$\Rightarrow \tau_4 = R_{gd2}^0 C_{gd2} = 315 \text{ ns}$$

- C_{db2} :

$$R_{db2}^0 = R_{L2} = 5 \text{ k}\Omega$$

$$\Rightarrow \tau_5 = R_{db2}^0 C_{db2} = 10 \text{ ns}$$

- Thus:

$$\tau_{\text{net}} = 815 \text{ ns and } f_H = 195.3 \text{ kHz}$$

- Such a *low value* of f_H is the *result* of the *presence* of a *large number of capacitors* in the circuit

- *Limitations of the ZVTC Technique:*
 - *One obvious limitation is the suppression of information of all other poles and zeros of the system except the DP*
 - *This limitation is not that acute since we are actually interested in only the DP, which gives the information about f_H*
 - *The other limitation is the error, which can reach as high as 22%*
 - However, *this error is negative*, i.e., *underestimation* (far better than *overestimation*)

- The *maximum error* of 22% occurs if the *actual circuit* has *two overlapping poles*
- In *real situations*, this is *highly unlikely*, due to the effect of *pole splitting* caused by *compensation* (*to be discussed in the next chapter*)
- *The resulting circuit after compensation would have a single DP*

➤ *Proof that the maximum error is 22%*

- Consider a circuit having *2 negative real poles* at the *same angular frequency* ω_x

- The *Transfer Function*:

$$A(j\omega) = A_0/(1 + j\omega/\omega_x)^2$$

A_0 : *Midband gain*

$$\Rightarrow |A(j\omega)| = A_0/[1 + (\omega/\omega_x)^2]$$

- At the *upper cutoff frequency* ω_H , the *gain would drop to $1/\sqrt{2}$ of its maximum value*

$$\Rightarrow 1 + (\omega_H/\omega_x)^2 = \sqrt{2}$$

$$\Rightarrow \omega_H = [\sqrt{(\sqrt{2} - 1)}]\omega_x = 0.64\omega_x$$

- Now, using the *ZVTC technique*, the *net time constant*

$$\tau_{\text{net}} = \sum_{i=1}^n (-1/p_i)$$

i = *number of poles*

p_i = *individual poles*

- For the *given problem*, $i = 2$ and $p_i = -\omega_x$ (*for both*)
- Thus:

$$\tau_{\text{net}} = 2/\omega_x \text{ and } \omega_H = 1/\tau_{\text{net}} = 0.5\omega_x$$

- Therefore, the *maximum error is about -22%*
- This being an *underestimation*, is *not that dangerous* :)

- ***Rise/Fall Time:***

- ***Recall:*** f_L caused tilt/sag in the output for square-wave input
- ***On the other side of the frequency spectrum,*** f_H causes rise/fall time of the output for square-wave input
- ***These two phenomena can be thought of as an interlinking between the analog and digital domains***
- Assume that a circuit has some ω_H , with the ***corresponding pole*** at $p_1 (= -\omega_H)$

- The **Transfer Function** is **single-pole**:

$$v_0(s)/v_i(s) = A_0/(1 - s/p_1)$$

A_0 : **Midband gain**

- Now, consider v_i to be **step input** of **amplitude**

$$V_A \quad (\Rightarrow v_i = V_A/s)$$

$$\begin{aligned}\Rightarrow v_0(s) &= (A_0 V_A/s)/(1 - s/p_1) \\ &= A_0 V_A [1/s - 1/(s - p_1)]\end{aligned}$$


- Taking **inverse Laplace Transform**:

$$v_0(t) = A_0 V_A [1 - \exp(p_1 t)]$$

\Rightarrow **Output approaches its maximum value of $A_0 V_A$ with a time constant $1/|p_1|$ (p_1 negative)**

➤ ***Calculation of Rise/Fall Time:***

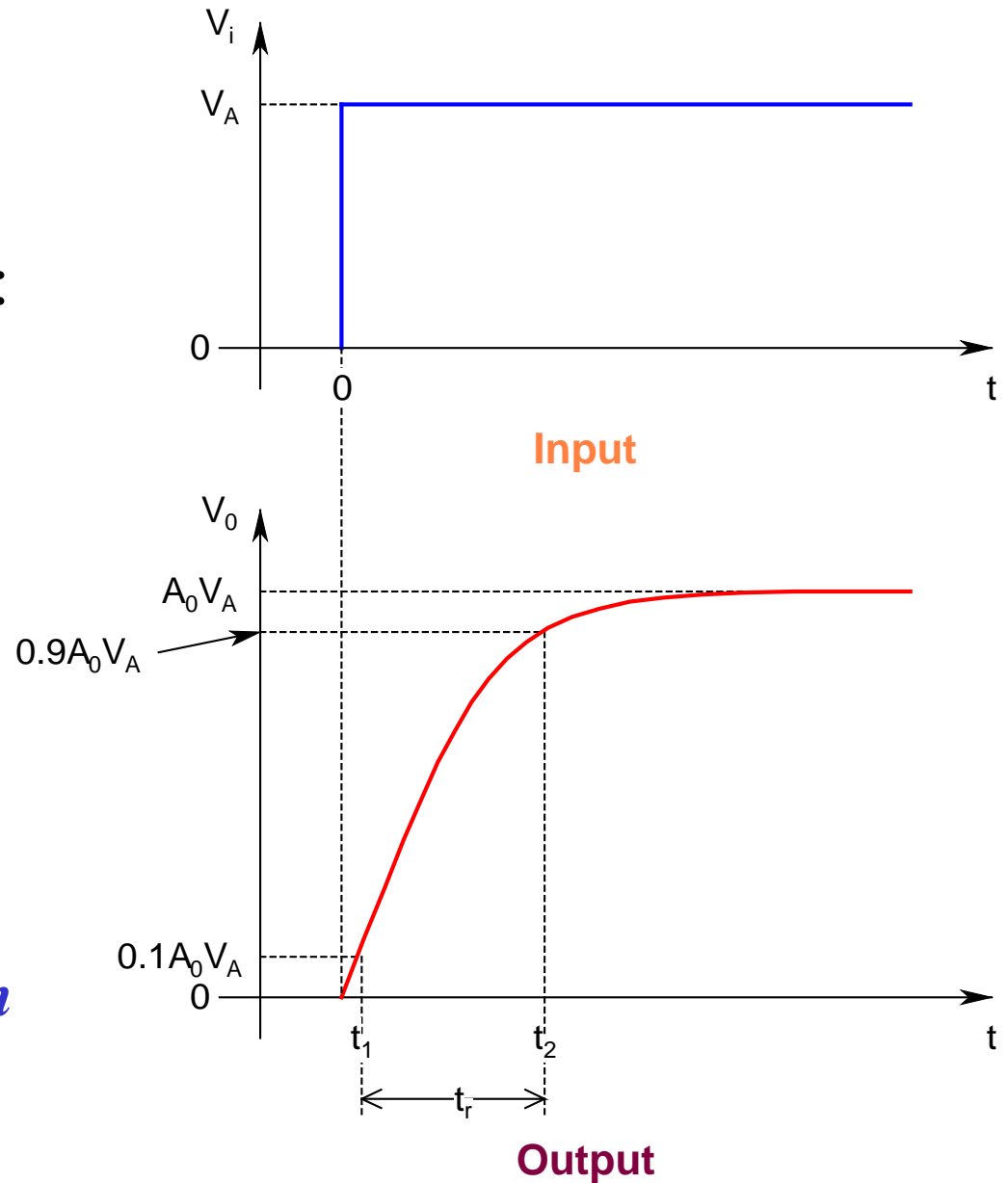- ***Time taken for the output to rise (fall) from 10% (90%) to 90% (10%)***
- ***Can be calculated from the figure***



- *At $t = t_1$:*

$$0.1A_0V_A = A_0V_A[1 - \exp(p_1t_1)]$$

$$\Rightarrow t_1 = \ln(0.9)/p_1$$

- *At $t = t_2$:*

$$0.9A_0V_A = A_0V_A[1 - \exp(p_1t_2)]$$

$$\Rightarrow t_2 = \ln(0.1)/p_1$$


- Thus, the *rise time*:

$$t_r = t_2 - t_1 = -2.2/p_1 = 2.2/\omega_H = 0.35/f_H$$

- Hence, *higher the f_H , smaller the t_r*
- *The same expression holds for the fall time (t_f) as well*

- Thus, circuits having *high bandwidth* under *sinusoidal excitation* (*analog domain*), will also have *superb switching characteristics* under *square-wave excitation* (*digital domain*)
- Under *square-wave excitation*, *due to t_r/t_f* , *enough time should be provided for the transient in the output to get completed*
- *Rule of Thumb*:
 - *At least 5 time constants should be allowed for each rising and falling transient*
 - This determines the *maximum allowable frequency* of the *input pulse train*:

$$f_{\max} = 1/T_{\min} \approx 1/(10\tau) = \omega_H/10 = |p_1|/10$$

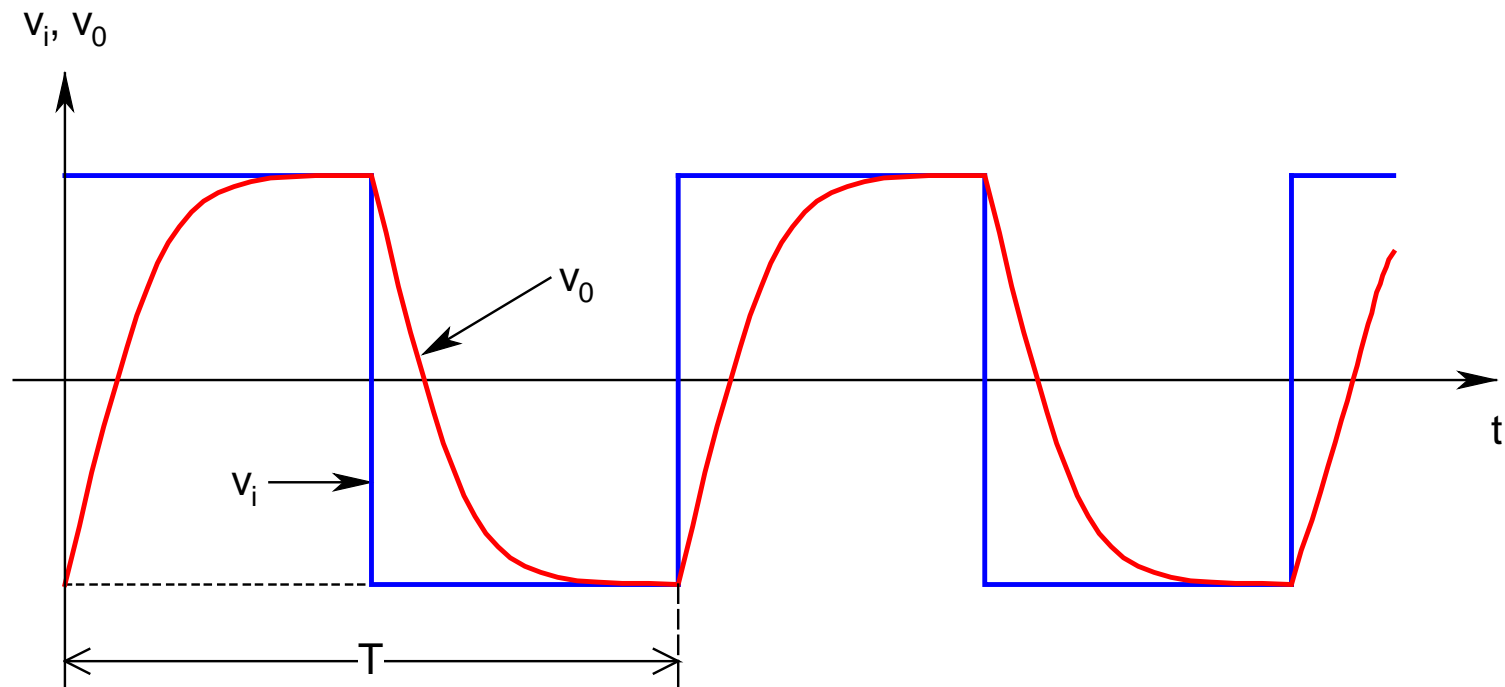

Effect of t_r/t_f on the Output for Square-Wave Excitation

- *As $f \uparrow$, $T \downarrow$, V_0 first starts to become triangular (incomplete transient), then the amplitude starts to drop, and eventually drops to zero (no output at all!)*