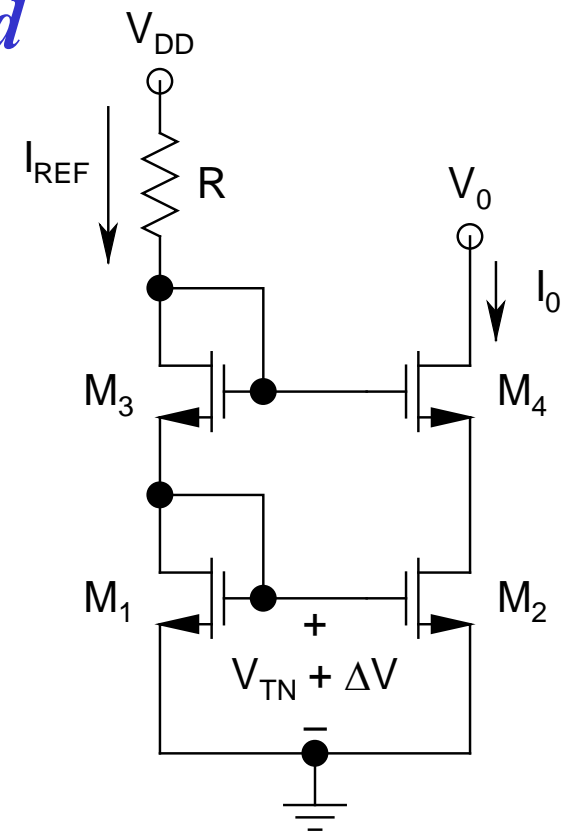


- **NMOS Cascode:**

- *All Ms perfectly matched*
- *All bodies connected to ground*
  - *$M_1$ - $M_2$  does not have body effect, but  $M_3$ - $M_4$  does!*
  - *Makes hand analysis quite tedious*
    - ⇒ *Neglect body effect*
- *All Ms operate with same  $V_{GS}$*
- Define  $\Delta V = V_{GS} - V_{TN} = V_{GT}$ 
  - $\Delta V =$  *Gate Overdrive*



➤ *The reference current:*

$$I_{\text{REF}} = \frac{V_{\text{DD}} - 2V_{\text{GS}}}{R} = \frac{k_{\text{N}}}{2} V_{\text{GT}}^2 \quad (\text{neglecting } \lambda)$$

➤  *$V_{\text{GS}}$  and  $I_{\text{REF}}$  can be found  $\Rightarrow I_0 = I_{\text{REF}}$*

➤  $V_{\text{G1}} = V_{\text{G2}} = V_{\text{GS}} = V_{\text{TN}} + \Delta V$

➤  $V_{\text{G3}} = V_{\text{G4}} = 2V_{\text{GS}} = 2(V_{\text{TN}} + \Delta V)$


➤  $V_{\text{S4}} = V_{\text{D2}} = V_{\text{TN}} + \Delta V$

$$\Rightarrow V_{\text{GS2}} = V_{\text{DS2}}$$


$\Rightarrow M_2$  *can never enter linear region*

$$\Rightarrow V_{0,\text{min}} = V_{\text{DS2}} + V_{\text{DS4}} = V_{\text{TN}} + 2\Delta V$$

- *This can be quite significant, since  $V_{TN}$  is added to  $\Delta V$* 
  - *Assuming  $\Delta V \sim 0.1\text{ V}$  and  $V_{TN} \sim 0.7\text{ V}$ ,  $V_{0,min} \sim 0.8\text{ V}$ , which is very large*
  - *This is one of the drawbacks of this simple cascode circuit (modified cascode doesn't have this problem)*
- *If  $V_0$  drops below  $(V_{TN} + 2\Delta V)$ , first  $M_4$  enters linear region, and circuit performance starts to get affected*
- *For further drop in  $V_0$ ,  $M_2$  also enters linear region, and the current mirror collapses!*

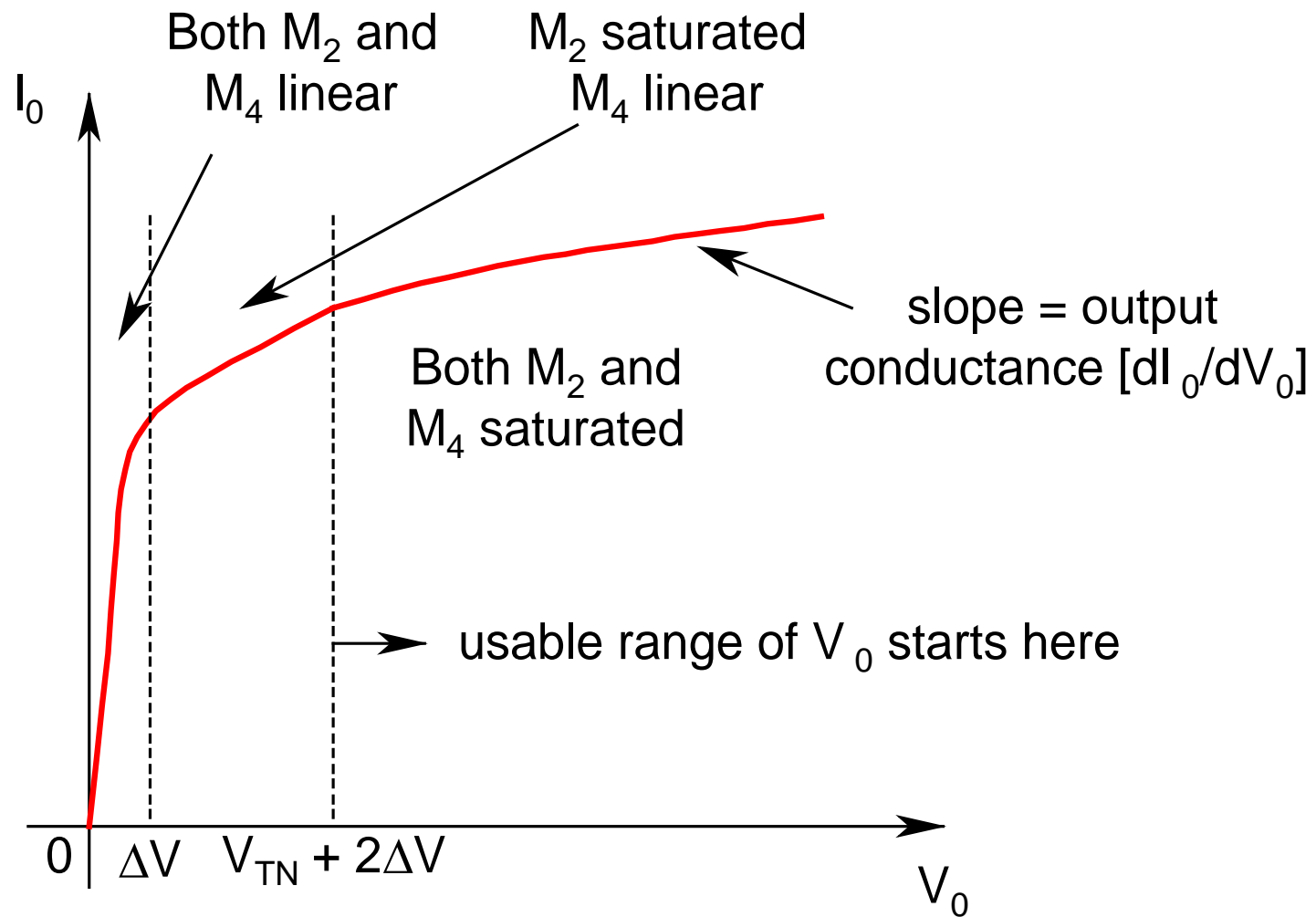

➤ *Calculation of  $R_o$ :*

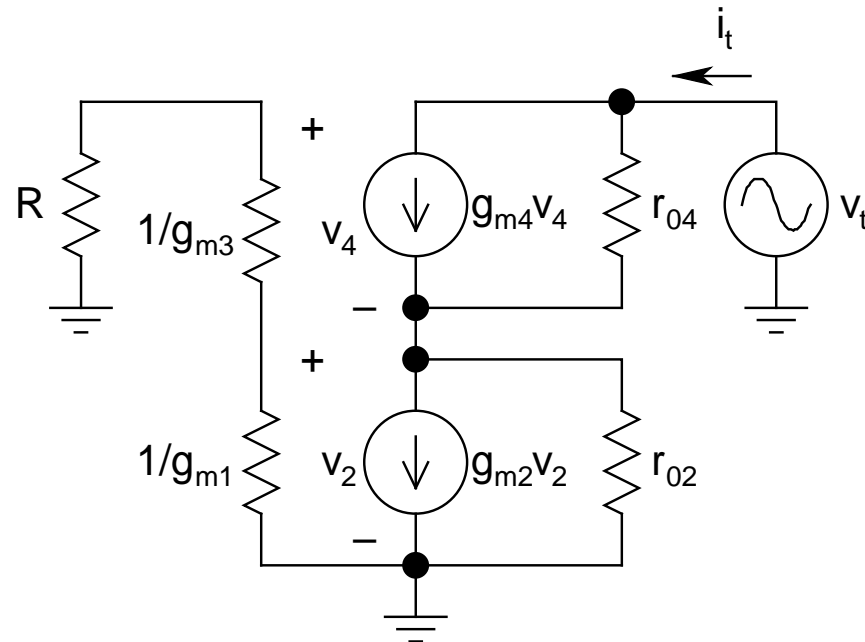

**Exact Equivalent**

- *$M_1$  and  $M_3$  diode-connected*  $\Rightarrow 1/g_{m1}$  and  $1/g_{m3}$

- *The left part of the circuit has no source*

$$\Rightarrow v_2 = 0 \Rightarrow g_{m2}v_2 = 0$$


$\Rightarrow$  *Leads to the simplified equivalent* (now should look very familiar!)

- *By inspection:*

$$R_0 \approx r_{o4}(1 + g_{m4}r_{o2})$$

$$\approx g_{m4}r_{o2}r_{o4}$$

- *Can be huge!*

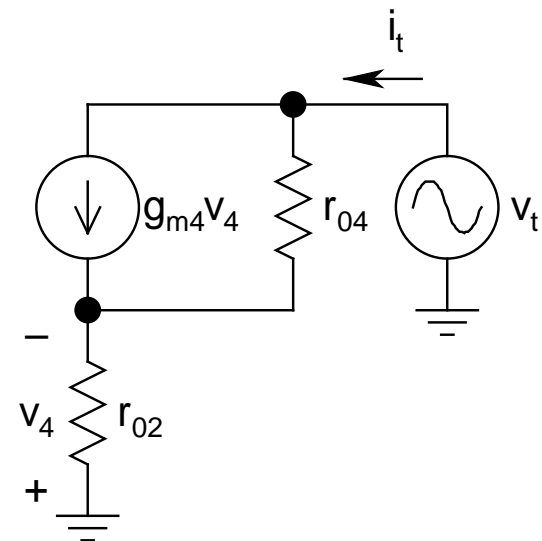

Simplified Equivalent

- **Double Cascode:**

- *Can be implemented in both BJT & MOS*
- *In npn Double Cascode, another pair  $Q_5$ - $Q_6$  stacked upon  $Q_3$ - $Q_4$* 
  - *Find  $V_{0,min}$  and  $R_0$*
- *In NMOS Double Cascode, another pair  $M_5$ - $M_6$  stacked upon  $M_3$ - $M_4$* 
  - *Find  $V_{0,min}$*
  - $R_0 \approx g_{m6}r_{o6}R_0$  ( $R_0 \approx g_{m4}r_{o2}r_{o4}$ )
- *Hence, show that double cascode in BJT offers absolutely no advantage in terms of  $R_0$*

- *Low Value Current Source:*
  - *Current thrust: Low-power circuits*  
⇒ *Increase in battery life*
  - *If bias current can be reduced from mA to  $\mu A$ , for the same power supply voltage, power drawn reduces by three orders of magnitude!*
  - *Normal CMs can also produce bias current in  $\mu A$  range, however, the required resistance will be huge ⇒ uneconomical for ICs*
  - *Most common: Widlar Current Source*
    - *After its inventor Bob Widlar (father of op-amp)*