

Neglect base current, Early effect, body effect, CLM effect.

Data: For Q_1 : $r_{E1} = 26 \, \Omega$, $\beta_1 = 100$; for M_2 : $g_{m2} = 2 \, \text{mA/V}$.

- a) Determine the ac small-signal midband voltage gain (v_0/v_s). **2.5**
- b) Using IVTC method, and the technique of total capacitance minimization, choose the values of C_1 , C_2 , and C_3 , such that the tilt in the output v_0 for pulse excitation of frequency $1.57 \, \text{kHz}$, does not exceed 2%. **9.5**

