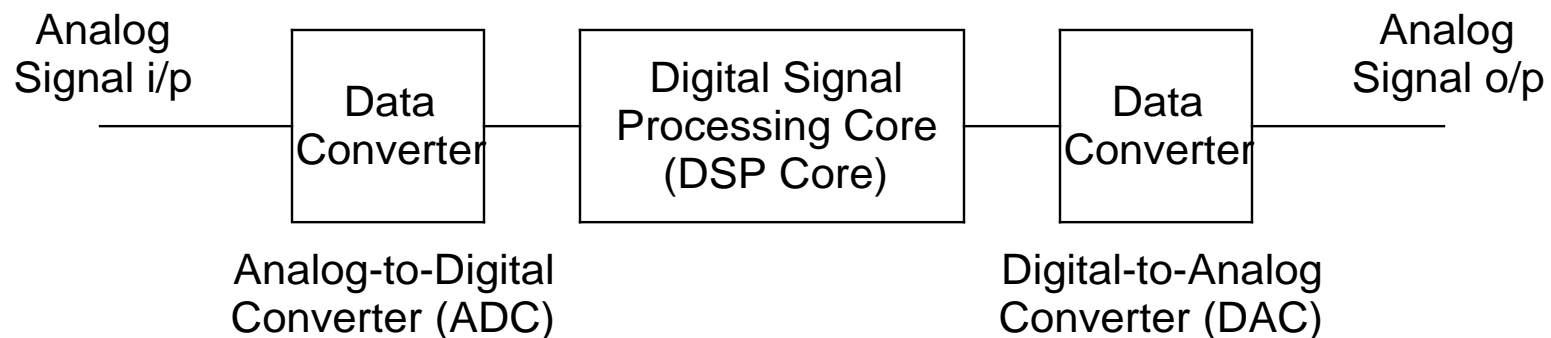


Data Converters

- Signals are of two types: *Analog & Digital*
- *Digital Signal Processing (DSP)* is much easier, since we have to keep track of only *1s and 0s*
- *Analog signal processing* is pretty tedious (Remember BJT Amplifiers?)
- Particularly, in *communication systems*, **digital data transmission** produces almost *error-free* and *noise-free* operation

- * There is very little chance that digital signals would get *corrupted by noise* (Remember Noise Margins?)
- * Also, much less chance of *signal interference* in **digital transmissions**
- * However, after the digital signal is *processed*, we may still need the o/p in **analog form**, e.g., *speech*
- * Thus, the **basic signal processing architecture**:



Sampling of Analog Signals:

- * Known as **Sample-and-Hold Circuit**

- * V_C : *Switch Control Signal*:

- Makes the switch *close periodically*

- * **Produces pulses of width Δt and period T**


- * Δt : *Sampling Interval*


- * $f_{\text{sampling}} = \text{Sampling Frequency} = 1/T$

- * $(T - \Delta t)$: *Hold Interval*

- **During this time, V_0 is fed to an ADC, and converted to corresponding digital signal**

- * *O/p is in N -bit binary form*

 

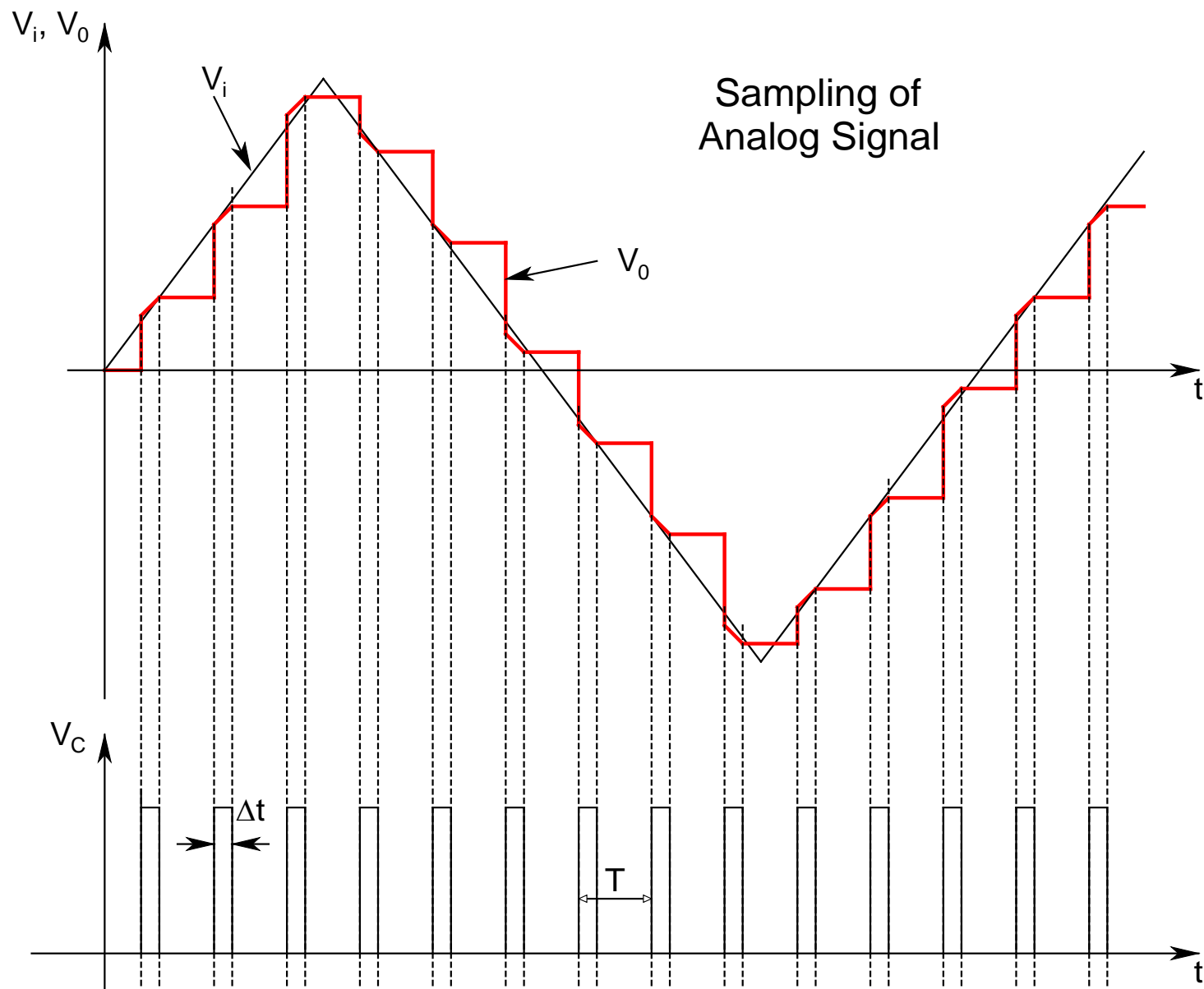

Signal Quantization:

- * Let an analog signal range from **0 to 10 V**, which needs to be converted to a **4-bit digital signal**
- * **Recall:** A **4-bit digital signal** can represent **16 equispaced values (*from 0 to 15*)**
- * Thus, each value is *spaced apart* by $(10 \text{ V})/15 = \mathbf{0.67 \text{ V}}$, which corresponds to **1 LSB**
- * This is known as **Resolution of Conversion**
- * **Chart:** 0000 \rightarrow 0.00 V; 0001 \rightarrow 0.67 V; 0010 \rightarrow 1.34 V; 0100 \rightarrow 2.68 V; 1000 \rightarrow 5.36 V; 1010 \rightarrow 6.7 V; 1100 \rightarrow 8.04 V; 1110 \rightarrow 9.38 V; 1111 \rightarrow 10 V

- * **Note:** For **each bit increment**, analog i/p range is **0.67 V**
- * What happens if the analog signal lies **within a range**, e.g., let's say **7 V**?
- * Now, **1010 is 6.7 V** and **1011 is 7.37 V**
 - ⇒ The o/p can be either of **1010 or 1011**
 - ⇒ Either way, there is an **error**, known as
Quantization Error (QE)
- * **$QE = (\text{Analog Full Scale}) / (2^N - 1)$** ,
where **$N = \text{Number of bits}$**

** Obviously, this error can be reduced by increasing N*

** Example:*

- For $N = 16$, $QE = (10 \text{ V}) / (2^{16} - 1) = 0.15 \text{ mV}$

- For $N = 32$, $QE = (10 \text{ V}) / (2^{32} - 1) = 2.33 \text{ nV}$

(vanishingly small)

** Another way to express QE : $\pm \text{LSB}/2$*

** Example: $N = 4$, $QE = \pm 0.335 \text{ V}$*

$$N = 16, QE = \pm 0.075 \text{ mV}$$


$$N = 32, QE = \pm 1.165 \text{ nV}$$

DAC:

* *Two types:*

- **Binary Weighted**
- **R-2R Ladder**

Binary Weighted DAC:

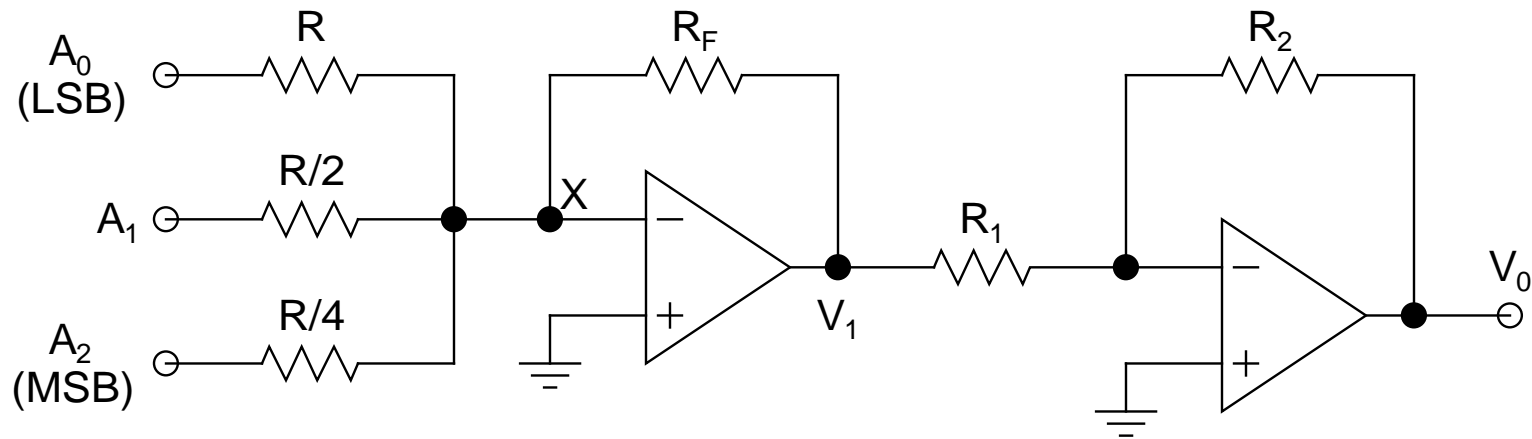

* $A_2 A_1 A_0$ are *digital i/p bits*, which can be either **0 or 1 (logically)**, equivalent to **0 V** or some V_{REF} (*Reference Voltage*)

* *KCL at node X:*

$$\frac{V_{\text{REF}} \times A_0}{R} + \frac{V_{\text{REF}} \times A_1}{R/2} + \frac{V_{\text{REF}} \times A_2}{R/4} = -\frac{V_1}{R_F}$$

$$\Rightarrow V_1 = -\frac{R_F}{R} \times (4A_2 + 2A_1 + A_0) \times V_{\text{REF}}$$

* Thus, the *output voltage*:

$$V_0 = -\frac{R_2}{R_1} \times V_1 = \frac{R_2 R_F}{R_1 R} \times (4A_2 + 2A_1 + A_0) \times V_{\text{REF}}$$

\Rightarrow **Binary Weighting**

- * **Note:** Maximum weight is assigned to A_2 , which has the **least resistance** ($R/4$) attached to it, so that it draws the **maximum current** from the reference voltage \rightarrow **MSB**
- * Similarly, **minimum weight** is assigned to A_0 , which has the **highest resistance** (R) attached to it, so that it draws the **minimum current** from the reference voltage \rightarrow **LSB**
- * **Note:** If $R_1 = R_F$ and $R_2 = R$, then
$$V_0 = (4A_2 + 2A_1 + A_0) \times V_{REF}$$

Design Example:

* Let $V_0(\text{max}) = 5 \text{ V}$

$\Rightarrow A_2 A_1 A_0 = 111$ should correspond to 5 V

$\Rightarrow V_{\text{REF}} = (5 \text{ V}) / (4 + 2 + 1) = 0.714 \text{ V}$

* For $A_2 A_1 A_0 = 000$, $V_0 = 0$, while for $A_2 A_1 A_0$

$= 001$, $V_0 = 0.714 \text{ V} = (5 \text{ V}) / (2^3 - 1)$

\Rightarrow For each bit increment, V_0 jumps by 0.714 V

\Rightarrow Resolution of the DAC $= 0.714 \text{ V}$

* **Note:** For $A_2 A_1 A_0 = 100$, $V_0 = 2.856 \text{ V} \neq V_0(\text{max})/2$


R-2R Ladder DAC:

* For additional i/p bits, the resistors scale as

$R/8$, $R/16$, $R/32$, and so on

\Rightarrow Becomes a very *clumsy* design

* ***Remedy: R-2R Ladder DAC***

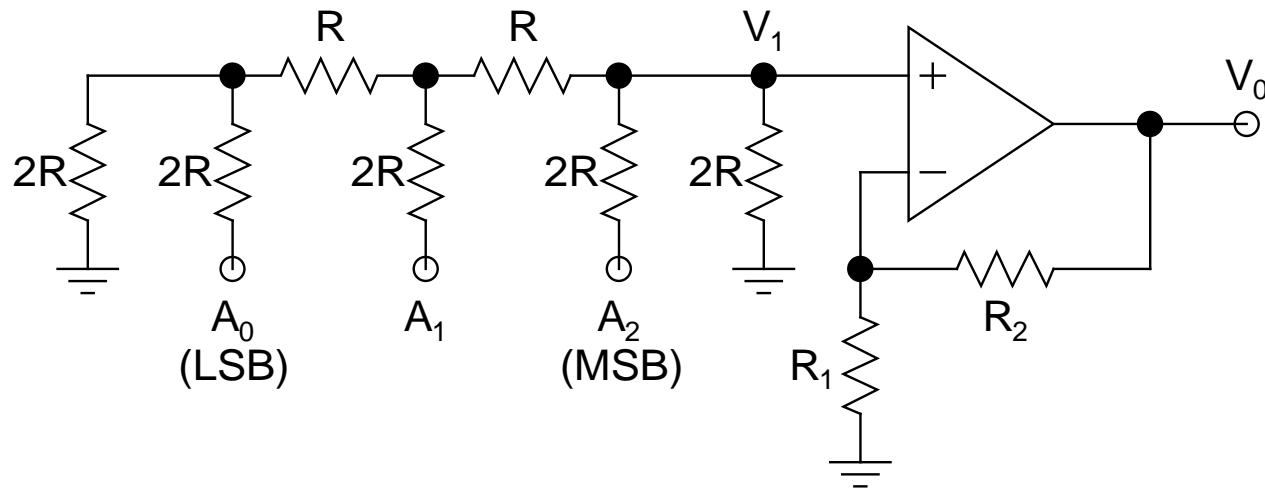

- * Uses resistors of values ***R and 2R only***, and a ***single op-amp*** (OA)
- * **MSB** (A_2) is ***closest*** to the OA, while **LSB** (A_0) is ***furthest*** from it
- * A_0 A_1 A_2 connected to **either 0 or V_{REF}** (***logic 0 or 1***)
- * ***Show that:***

- $V_1 \big|_{A_2=1 \text{ and } A_1=A_0=0} = (A_2/3) \times V_{REF}$
- $V_1 \big|_{A_1=1 \text{ and } A_2=A_0=0} = (A_1/6) \times V_{REF}$
- $V_1 \big|_{A_0=1 \text{ and } A_2=A_1=0} = (A_0/12) \times V_{REF}$

* Thus, by *superposition*:

$$\bullet V_1 = (1/12)(4A_2 + 2A_1 + A_0) \times V_{\text{REF}}$$

* The OA is *non-inverting*, with gain:

$$V_0/V_1 = 1 + R_2/R_1$$

* Choose $R_2/R_1 = 11$

$$\Rightarrow V_0 = (4A_2 + 2A_1 + A_0) \times V_{\text{REF}}$$

* The result is exactly same as that obtained in the previous case, but using resistors of *only 2 values* (**R and 2R**)


* *Extremely popular DAC and heavily used*

ADC:

* Various options available, out of which, we will be discussing two of them:

- **Counting Type**
- **Flash (or *Parallel Comparator*)**

Counting Type:

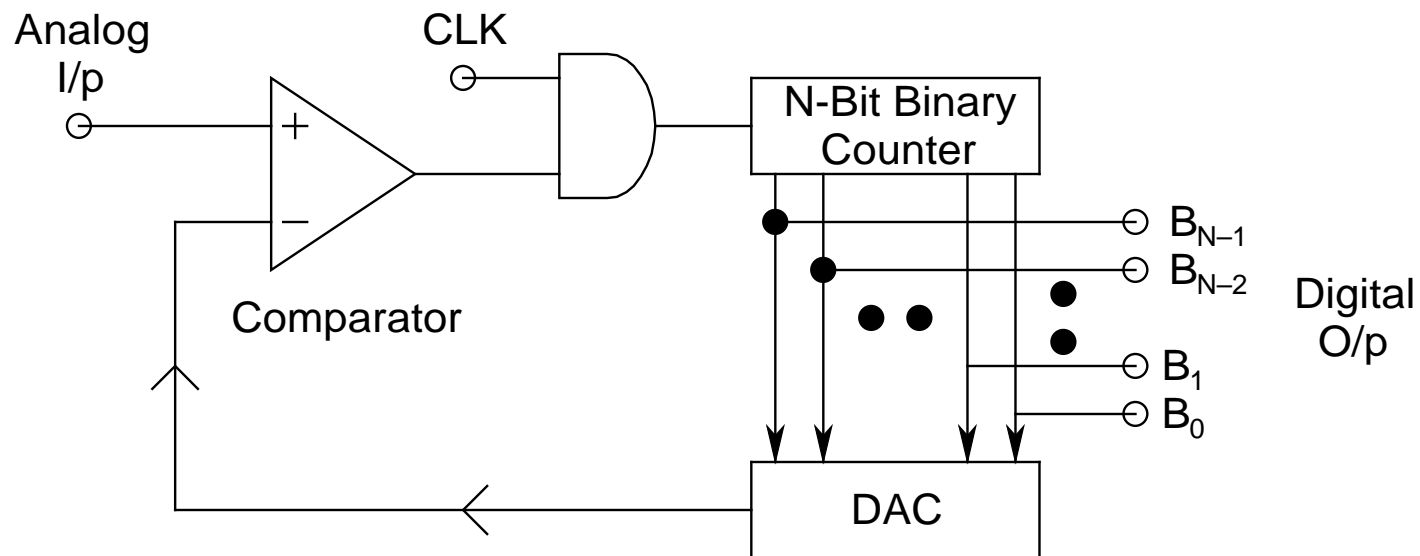

* **Note:** It employs a **DAC** within it

Operating Principle:


- * Initially, the Binary Counter is **reset** (*all o/ps zero*)
- * Thus, **DAC o/p = 0**, fed back to the comparator
- * **Comparator o/p high** \Rightarrow CLK is allowed to pass to the counter through the AND gate
- * The counter *starts counting* and *increments by 1* at *each CLK pulse*
- * DAC *converts* this digital o/p to its *analog equivalent* and feeds it back to the comparator, which *compares* it with the analog i/p signal

- * So long as the analog i/p signal is ***greater*** than the DAC o/p, the o/p of the comparator remains ***high***, and the counter keeps on ***counting***
- * As soon as the DAC o/p becomes ***greater*** than the analog i/p signal, the comparator o/p goes ***low***, and the CLK signal is ***prevented*** from reaching the i/p of the counter \Rightarrow the count ***stops***
- * At that instant of time, the ***binary o/p is taken out***, and immediately thereafter the ***counter is reset***, which ***starts the counting process again***

- * **Note:** During the entire conversion period, the analog i/p *should not change*, i.e., it must be held **constant**
- * Implemented using a **Sample-and-Hold (S/H) circuit**, with its *hold time at least equal to or greater than the conversion time of the ADC*
- * **Note:** The conversion time itself is a function of the analog i/p (**smaller value leads to quicker conversion** and vice-versa)

- * As soon as the count *stops*, the **Hold** of the S/H circuit is *released*, and it samples and holds the *next* analog data for conversion
- * Needs a maximum of $(2^N - 1)$ *CLK cycles for N -bit data*
- * *Quite slow*, if the analog i/p voltage is large, since the **count has to always start from zero**
- * *Advantage: Very simple design and needs very limited hardware \Rightarrow costs less*

Flash (Parallel Comparator):

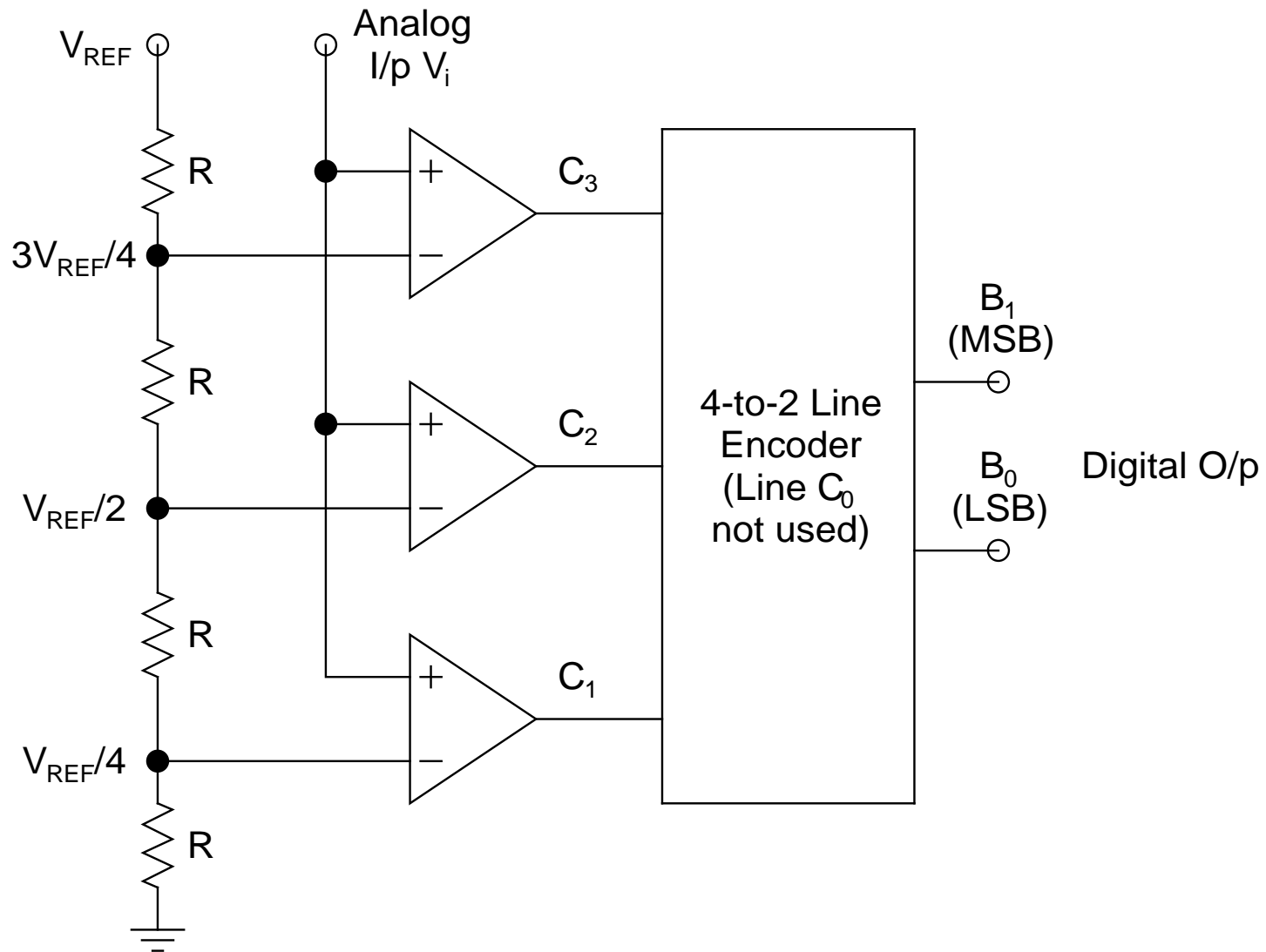

** Fastest ADC available to date*

** Note:*

- For $0 < V_i < V_{\text{REF}}/4$:

$$C_1 = C_2 = C_3 = 0$$

- For $V_{\text{REF}}/4 < V_i < V_{\text{REF}}/2$:

$$C_1 = 1, C_2 = C_3 = 0$$

- For $V_{\text{REF}}/2 < V_i < 3V_{\text{REF}}/4$:

$$C_1 = C_2 = 1, C_3 = 0$$

- For $V_i > 3V_{\text{REF}}/4$:

$$C_1 = C_2 = C_3 = 1$$

* The ***4-to-2 Line Encoder*** takes these as i/ps and produces **2-bit binary output**

* ***Encoding Scheme:***

			MSB	LSB
C_3	C_2	C_1	B_1	B_0
0	0	0	0	0
0	0	1	0	1
0	1	1	1	0
1	1	1	1	1

* The entire operation is done **parallely** (*in a flash*)
 \Rightarrow Known as a **Parallel Comparator** (or *Flash*) ADC

* **Note:** **QE** (or **Resolution**) = $\pm V_{\text{REF}}/8$

* Number of comparators needed = $(2^N - 1)$ for

N-bit digital o/p

⇒ For **8-bit** digital o/p, need **255** comparators!!!

⇒ One of the major ***drawbacks*** of flash ADC, i.e.,
hardware requirement (and thus, the **cost**) is
huge

⇒ ***Use limited to 8-bit o/p***

* **Note:** Needs only **one** clock cycle for data conversion

⇒ ***Extremely fast***