


➤ **DPA:**

- The *smallest pole* [*Dominant Pole* (DP)] is *at least 10 times away from its nearest pole*
- This is an *excellent approximation for practical analog circuits*

➤ *Apply this approximation* and *assume p_1 to be the DP* and *at least 10 times away from p_2* [*Non-Dominant Pole* (NDP)]

➤ The *pole frequencies* are $|p_1|/(2\pi)$ and $|p_2|/(2\pi)$

➤ *Note:* $|p_1|/(2\pi)$ is the *Upper Cutoff Frequency* (f_H)

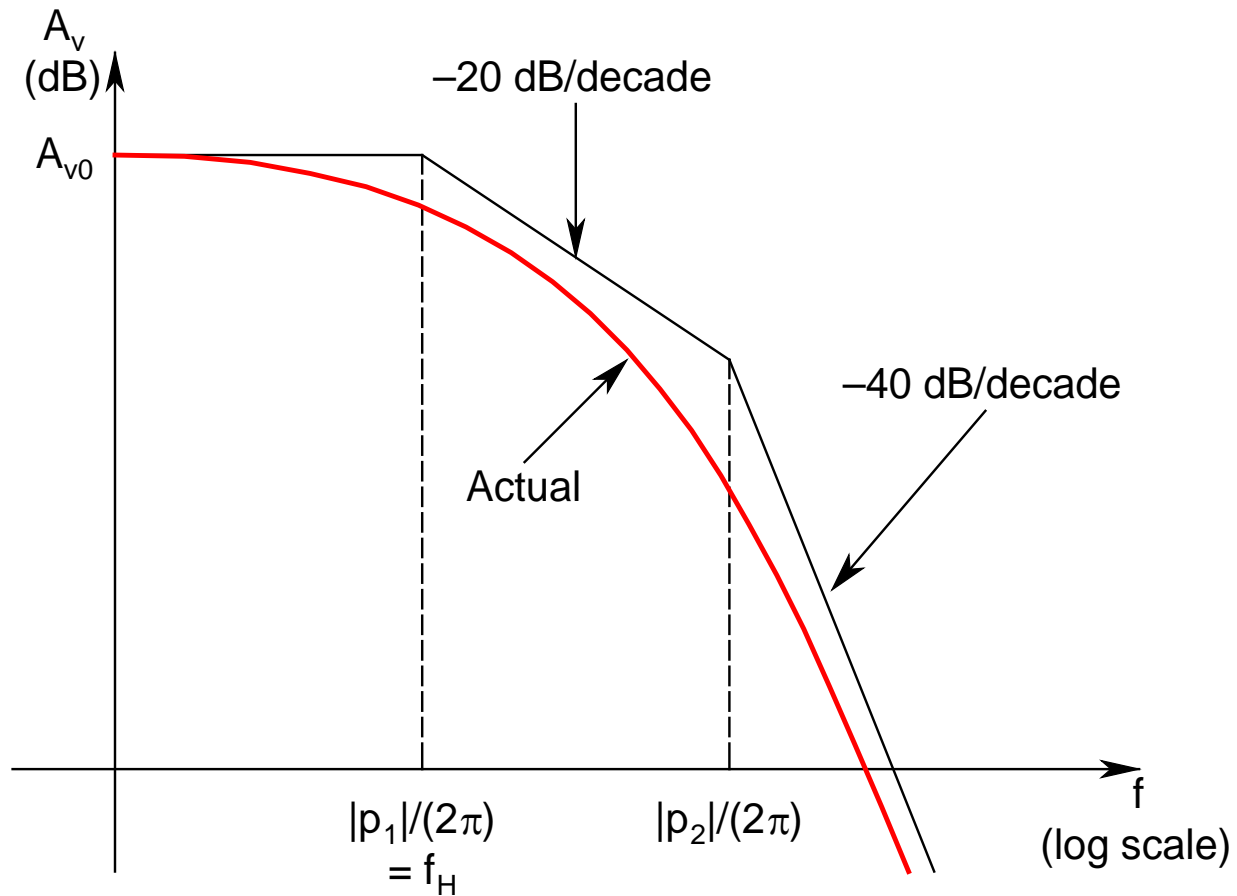

Bode Plot of the Frequency Response of a 2-Pole System

- *2-pole system*
- *For frequencies till the first pole p_1 , gain remains constant at its midband value of $20\log_{10}A_{v0}$*
- *Beyond this*, the *gain rolls off at -20 dB/decade till the second pole p_2 is encountered*
- *After this*, the *gain rolls off at -40 dB/decade*, and *eventually crosses zero*
- *Beyond this*, the circuit actually *attenuates the input signal instead of amplifying it* (gain magnitude drops below unity)

- *It's assumed that z_1 is $\gg |p_2|$*
- *Task remains to find p_1 and p_2*
- *Under DPA*, Eq.(2) can be simplified as:


$$D(s) \approx 1 - s/p_1 + s^2/p_1 p_2 \quad (4)$$
- *Comparing* Eq.(4) with the *denominator* of Eq.(1):

$$p_1 = -\frac{1}{(R_S \parallel r_\pi)C_\pi + [(R_S \parallel r_\pi) + R_L + g_m (R_S \parallel r_\pi)R_L]C_\mu}$$


$$p_2 = -\left(\frac{1}{R_L C_\mu} + \frac{1}{(R_S \parallel r_\pi)C_\pi} + \frac{1}{R_L C_\pi} + \frac{g_m}{C_\pi} \right)$$

- In general, $|p_2| \gg |p_1|$
- **Ex.**: $I_C = 1 \text{ mA}$, $\beta = 200$, $R_S = 1 \text{ k}\Omega$, $R_L = 2 \text{ k}\Omega$, $C_\pi = 10 \text{ pF}$, $C_\mu = 0.5 \text{ pF}$
 $\Rightarrow DPF = 3.8 \text{ MHz}$, $NDPF = 798.8 \text{ MHz}$, $ZF = 12.3 \text{ GHz}$, and $f_H = DPF = 3.8 \text{ MHz}$
- **Note**: Even for a *simple CE circuit*, the *analysis is so cumbersome*, and the *results are so complicated*
- *Definitely not acceptable for routine application, particularly for circuits having more than one active device*

- ***Miller Effect Approximation:***
 - *Technique by which an input-output coupled circuit can be decoupled by removing the coupling element*
 - This ***removal*** is done by ***splitting*** it into ***two components*** - putting ***one in the input circuit***, and the ***other in the output circuit***
 - We take the ***same example*** as the ***CE circuit*** discussed earlier, but now ***without R_S***

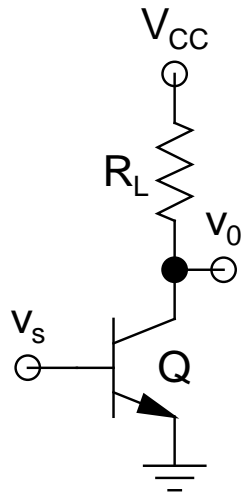

ac Schematic

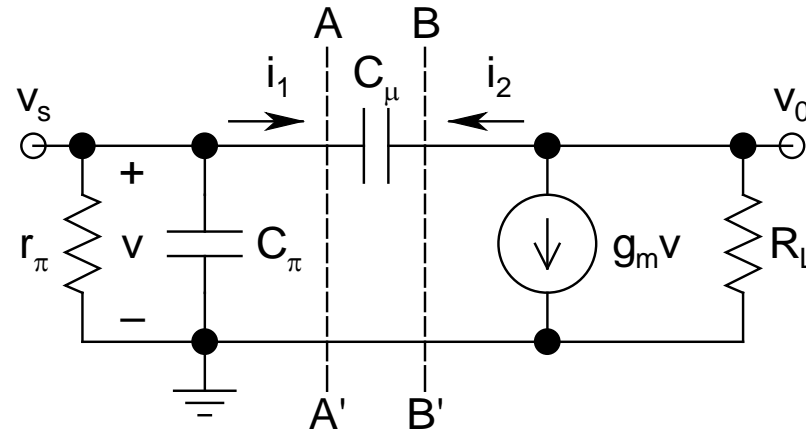

High-Frequency Equivalent

- *Identify C_μ as the input-output coupling element*
- After *application* of the *technique*, this *coupling element* will be *removed* by *splitting* it into *two parts* - *one at input*, *other at output*