 


- *What if the output is taken from emitter?*
- Redraw the *ac schematic*:



**ac Midband Schematic for
Output Taken from Emitter**

- *First, short v_i to ground*
 - \Rightarrow *R_3 comes in parallel with R_S (call this combination R_5)*
 - $\Rightarrow R_5 = R_3 || R_S = 900 \Omega$
- *R_5 comes in series with r_π (call this combination R_6)*
 - $\Rightarrow R_6 = R_5 + r_\pi = 2.2 \text{ k}\Omega$
- *Transform R_6 to emitter by dividing it by $(\beta + 1)$*
 - $\Rightarrow R_{01} = R_6 / (\beta + 1) = 21.8 \Omega$

- Thus, $R_0 = 20 \, \Omega$ (*Easy?*)
- *Summary:*
 - $A_v = 0.827$
 - $R_i = 6.72 \, \text{k}\Omega$
 - Resistance *seen* by $v_i = 7.72 \, \text{k}\Omega$
 - $R_0 = 20 \, \Omega$
- Thus, this circuit has *voltage gain close to unity*, *ok input resistance*, and *very small output resistance*
 - *Ideal characteristics* needed for a *Buffer/Isolator/Impedance Matcher*

- **Loading Effect:**

- **Neglecting r_o :**


$$A_v = -g_m(R_C || R_L)$$

- R_L has no role in DC biasing, but comes into picture in ac calculations

- As $R_L \downarrow \Rightarrow |A_v| \downarrow$

- Known as **Loading Effect**

 - Similar situation happens when a **high output resistance driver** drives a **low input resistance load** (e.g., **CE stage driving a CB stage**)




- The *gain of the CE stage* will be *severely compromised* due to *low input resistance* of the *CB stage*
 - Known as *Impedance Mismatch* between *Driver and Load*
- Under such a situation, need an *Isolator/Buffer/Impedance Matcher* between the two stages
- A *CC stage perfectly fits the bill* due to its *high input resistance* and *low output resistance*, and *can be used to couple the CE stage to CB stage*
- *MOS circuits generally don't have this problem*

Compound Connections


- *Multi-Stage*
- Have some *special properties*
- *Popular Topologies:*
 - *Darlington*
 - *Cascode*
 - *DP* (or *DA*)
- *Modules by themselves*

- *Darlington:*

 
- Cascade of a *CC* stage, followed by either a *CE* or a *CC* stage
 - *Two biggest advantages:*
 - *Extremely large R_i*
 - *Extremely large A_i*
 - *These two advantages are automatic for MOS stages*
- ⇒ *MOS Darlington has no special use*




Generic Circuit

 

CC-CE Stage

 

CC-CC Stage

 

Compact Representation

➤ For ***DC biasing***:

$$I_{C2} = \beta_2 I_{B2} = \beta_2 I_{E1} \approx \beta_2 I_{C1}$$

$$\Rightarrow r_{\pi 2} = \beta_2 r_{E2} = \beta_2 V_T / I_{C2} = V_T / I_{C1} = r_{E1}$$