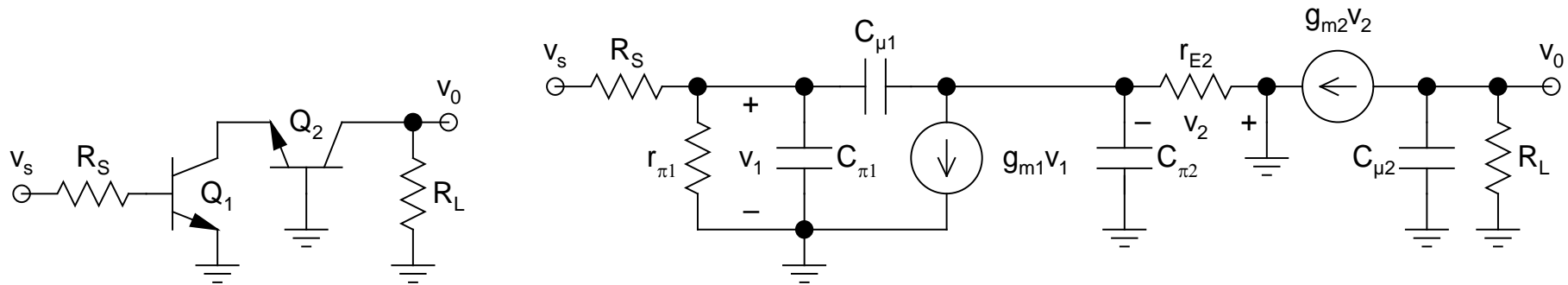


- *npn Cascode:*



ac Schematic

High-Frequency Equivalent

- *Looks intimidating*, but *extremely easy to solve* (*just by inspection*)
- Also known as *Wideband* (or *Broadband*) *Amplifier* due to its *superb frequency response*

➤ **Reason:**

- *The circuit does have an input-output coupling capacitor ($C_{\mu 1}$)*
- *Miller Effect Multiplication Factor (MEMF) of $C_{\mu 1} = (1 - A_{v1})$*
 $A_{v1} = \text{voltage gain of } Q_1 = -r_{E2}/r_{E1} = -1$
(since Q_1 and Q_2 are biased with the same I_C)
 \Rightarrow Thus, the *MEMF of $C_{\mu 1}$ is only 2*
- For *NMOS Cascode* stage, the *MEMF of C_{gd1}* of M_1 (*CS stage*) will be $[1 + 1/(1 + \chi_2)]$ (*verify this expression*), which is *even less than 2*

➤ $C_{\pi 1}$:

▪ *By inspection:*

$$R_{\pi 1}^0 = R_S \parallel r_{\pi 1} \Rightarrow \tau_1 = R_{\pi 1}^0 C_{\pi 1}$$

➤ $C_{\mu 1}$:

▪ Can be easily identified as the *Three-Legged Creature*

$$\Rightarrow R_{\mu 1}^0 = R_{\pi 1}^0 + r_{E2} + g_{m1} R_{\pi 1}^0 r_{E2}$$

$$\Rightarrow \tau_2 = R_{\mu 1}^0 C_{\mu 1}$$

➤ $C_{\pi 2}$:

▪ *By inspection:*

$$R_{\pi 2}^0 = r_{E2} \Rightarrow \tau_3 = R_{\pi 2}^0 C_{\pi 2}$$

➤ $C_{\mu 2}$:

▪ *By inspection:*

$$R_{\mu 2}^0 = R_L \Rightarrow \tau_4 = R_{\mu 2}^0 C_{\mu 2}$$

➤ Generally, for this circuit, $C_{\pi 1}$ is the *dominant capacitor* that determines f_H , since it sees the *largest resistance*

➤ The *resistance seen by $C_{\mu 1}$* , which is the *largest for CE stage*, *becomes quite small here, due to the low gain of Q_1*


➤ Note how *simple* it is to use this *technique* even for *multi-stage amplifiers*!

- ***NMOS 2-Stage Cascaded CS:***


- *Except C_{sb} , all other capacitors will be present for both devices*

- *6 capacitors*

⇒ ***6 time constants***

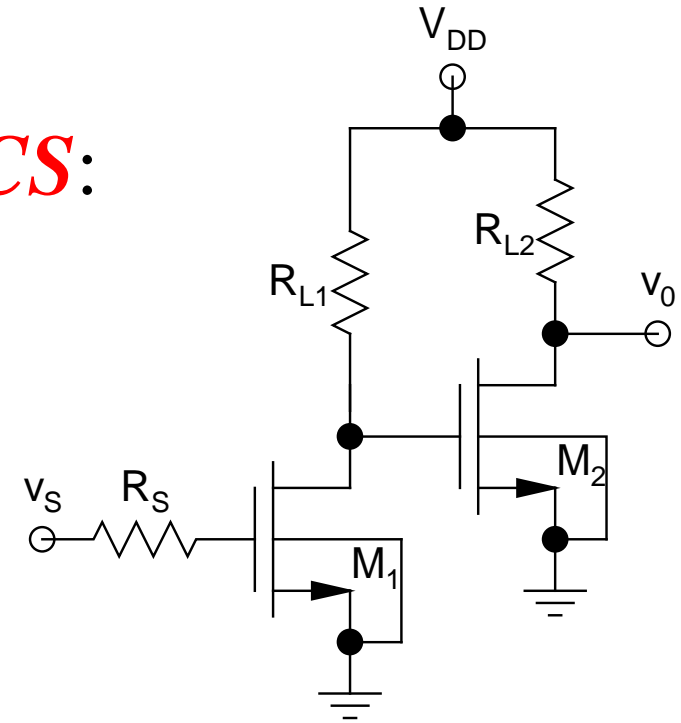

ac Schematic

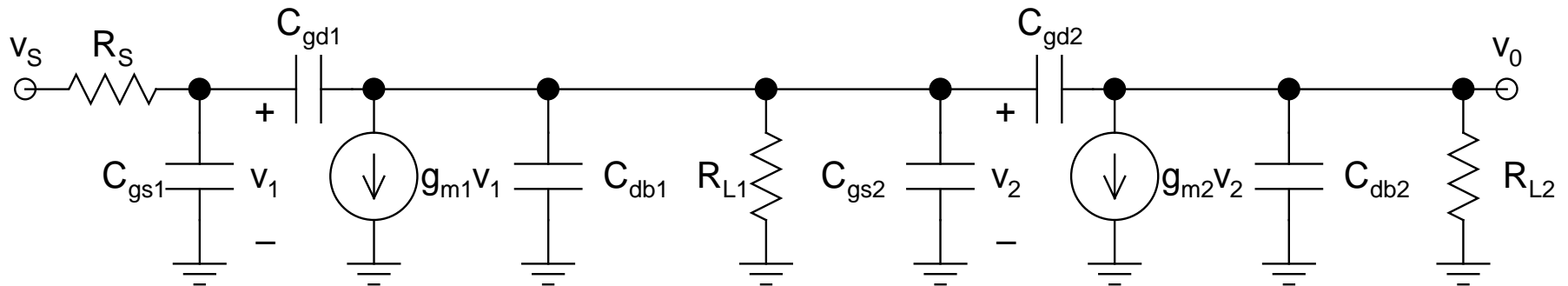

High-Frequency Equivalent

- **Note:** An *exact analysis* would have required *solving* a *6th-order equation in ω* !
- Let's perform a *quantitative analysis* of this circuit
- **Data:** $g_{m1} = 3 \text{ mA/V}$, $g_{m2} = 6 \text{ mA/V}$, $C_{gs1} = 5 \text{ pF}$, $C_{gs2} = 10 \text{ pF}$, $C_{gd1} = C_{gd2} = 1 \text{ pF}$, $C_{db1} = C_{db2} = 2 \text{ pF}$, $R_S = 10 \text{ k}\Omega$, $R_{L1} = 10 \text{ k}\Omega$, and $R_{L2} = 5 \text{ k}\Omega$.
 - **C_{gs1} :**

$$R_{gs1}^0 = R_S = 10 \text{ k}\Omega \quad \Rightarrow \quad \tau_1 = R_{gs1}^0 C_{gs1} = 50 \text{ ns}$$