

i.e., at $V_{CE1} = \underline{\underline{\quad\quad\quad}}$

1 $V_{OM} = V_{CC} - V_{CE(sat)} = \underline{\underline{11.8V}}$

$I_{supply} = \frac{V_{OM}}{\pi R_L} = \frac{11.8}{\pi \times 10^3} = \underline{\underline{3.756mA}}$

$P_{supply} = 2V_{CC} I_{supply} = 2 \times 12 \times 3.756 = \underline{\underline{90.15mW}}$


$P_L = \frac{V_{OM}^2}{2R_L} = \frac{11.8^2}{2 \times 10^3} = \underline{\underline{69.62mW}}$

$\Rightarrow \eta = \frac{P_L}{P_{supply}} = \frac{69.62}{90.15} = \underline{\underline{77.23\%}}$

Max. Q_1/Q_2 dissipation occurs at middle

$\&$ load line, i.e., at $V_{CE1} = \frac{V_{CC}}{2} = \underline{\underline{6V}}$ & $I_{C1} = \frac{V_{CC}}{2R_L} = \underline{\underline{6mA}}$, \therefore each of Q_1 &

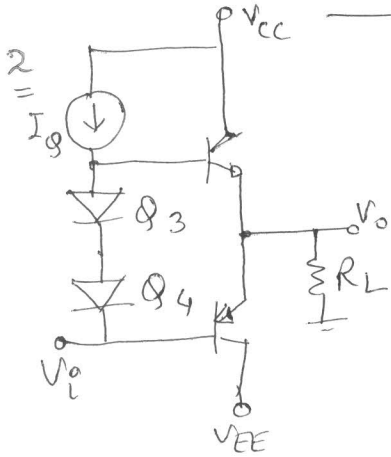Q_2 conducts for only $\frac{1}{2}$ cycle $\Rightarrow P_{C1max} = P_{C2max} = \underline{\underline{36mW}}$.




a) $V_o^- = V_{EE} + V_{EC2}(\text{sat}) = -14.8\text{V}$, & would remain independent of R_L . On the other hand, V_o^+ would depend on R_L , \therefore with I_g fixed at $200\mu\text{A}$, the max. current that Q_1 can deliver $= I_{C1, \text{max}} = (\beta_{npn} + 1)I_g = 201 \times 200\mu\text{A} = 40.2\text{mA}$. Thus, $V_o^+ = I_{C1, \text{max}} R_L$, provided that it is less than or equal to $[V_{CC} - V_{CE1}(\text{sat})] = 14.8\text{V}$. For $R_L = 10\text{k}\Omega$, $I_{C1, \text{max}} R_L = 402\text{V}$, which is way higher than $14.8\text{V} \Rightarrow V_o^+ = 14.8\text{V}$ & the o/p would be symmetric. Similarly, for $R_L = 1\text{k}\Omega$, $I_{C1, \text{max}} R_L = 40.2\text{V} \Rightarrow V_o^+ = 14.8\text{V}$, & again the o/p would be symmetric. However, for $R_L = 200\Omega$, $I_{C1, \text{max}} R_L = 8.04\text{V}$, which is less than $14.8\text{V} \Rightarrow$ for this case, $V_o^+ = 8.04\text{V}$, & the o/p is asymmetric & highly distorted.

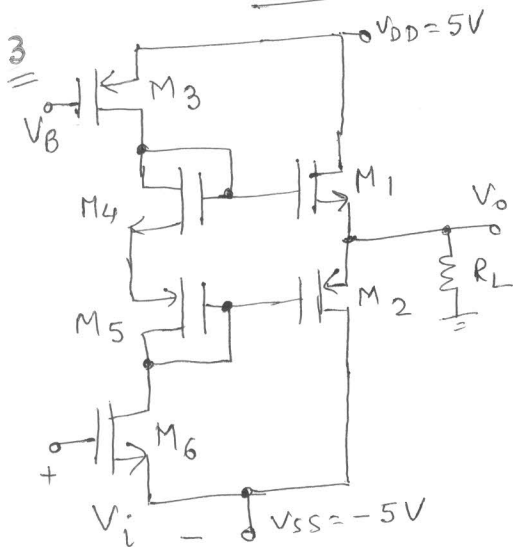b) With $R_L = 1\text{k}\Omega$, $V_{om} = 14.8\text{V} \Rightarrow P_{L, \text{max}} = \frac{1}{2} \frac{V_{om}^2}{R_L} = 109.52\text{mW}$. Supply power $P_{\text{supply}} = \frac{2V_{CC} V_{om}}{\pi R_L} = 141.33\text{mW} \Rightarrow \eta = \frac{P_{L, \text{max}}}{P_{\text{supply}}} = 0.775 (= 77.5\%)$.

The mid-pt. of load line $V_{ce} = \frac{V_{CC}}{2} = 7.5\text{V}$, & $I_c = \frac{V_{ce}}{R_L} = 7.5\text{mA} \Rightarrow$

$$P_{C1, \text{max}} = P_{C2, \text{max}} = V_{ce} I_c = 56.25\text{mW}$$



$$I_{D6} = I_{D3} = I_{D4} = I_{D5} = 10\mu\text{A}, \text{ \& } \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_6 = 100.$$

$$I_{D3} = 10\mu\text{A} = \frac{k_p'}{2} \left(\frac{W}{L}\right)_3 (|V_{GS3}| - |V_{TP3}|)^2 = \frac{30 \times 10^{-6}}{2} \times 100 \times (|V_{GS3}| - 1)^2 \Rightarrow |V_{GS3}| = 1.082\text{V}$$

$$\Rightarrow V_{GS3} = -1.082\text{V} = V_B - V_{DD} \Rightarrow V_B = 3.918\text{V}$$

$$\text{Also, } I_{D6} = 10\mu\text{A} = \frac{k_n'}{2} \left(\frac{W}{L}\right)_6 (V_{GS6} - V_{TN6})^2 = \frac{60 \times 10^{-6}}{2} \times 100 \times (V_{GS6} - 0.7)^2 \Rightarrow V_{GS6} = V_i = 0.758\text{V}$$

Now, with $V_o = 3\text{V}$ & $R_L = 1\text{k}\Omega$, M_1 should be able to deliver $\frac{V_o}{R_L} = 3\text{mA}$ to the load, & under this

Condⁿ, M_3 should remain saturated. Min. reqd. $|V_{DS3}| = |V_{GS3}| - |V_{TP3}| = 82\text{mV}$. Note that it is slightly greater than the min allowed saturation voltage of $3V_T$, which is $78\text{mV} \Rightarrow$ should be okay. $\Rightarrow V_{G1} = V_{DD} - |V_{DS3}| = 4.918\text{V}$, & $V_{S1} = V_o = 3\text{V} \Rightarrow V_{GS1} = 1.918\text{V} \Rightarrow \left(\frac{W}{L}\right)_1 = \frac{2I_{D1}}{k_n' (V_{GS1} - V_{TN1})^2} = \frac{2 \times 3 \times 10^{-3}}{60 \times 10^{-6} \times (1.918 - 0.7)^2} = 67.41$. Similarly, when $V_o = -3\text{V}$, M_2 should be able to sink 3mA . Under this condⁿ, M_6 should remain saturated. Min. reqd. $V_{DS6} = V_{GS6} - V_{TN6} = 58\text{mV}$, which is lower than the smallest permissible value of 78mV . \therefore We should not let V_{DS6} fall below $78\text{mV} \Rightarrow V_{G2} = V_{SS} + V_{DS6} = -4.922\text{V}$

Also, with $V_{S2} = V_0 = -3V$, $V_{GS2} = -1.922V$. $\therefore \left(\frac{W}{L}\right)_2 = \frac{2I_{D2}}{K_P'(|V_{GS2}| - |V_{TP2}|)^2}$ (2)

$$= \frac{2 \times 3 \times 10^{-3}}{30 \times 10^{-6} \times (1.922 - 1)^2} = \underline{235.27}$$

for the calculation of aspect ratios of M_4 & M_5 , consider idling condⁿ, with $V_0 = 0$, & idling current of $100\mu A$ flowing thru $M_1 - M_2$. Thus, $I_{D1} = 100\mu A = \frac{K_n'}{2} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN1})^2 = \frac{60 \times 10^{-6}}{2} \times 67.41 \times$

$$(V_{GS1} - 0.7)^2 \Rightarrow V_{GS1} = 0.922V \Rightarrow V_{G1} = V_{G4} = \underline{0.922V} \quad (\because V_{S1} = V_0 = 0).$$

Now, from the symmetry of the ckt, $V_{S4} = V_{S5} = 0$, which gives $V_{GS4} = V_{GS5} =$

$\underline{0.922V}$. Also, the idling current flowing thru M_1 should equal $10\mu A$. \therefore

$$\left(\frac{W}{L}\right)_4 = \frac{2I_{D4}}{K_n' (V_{GS4} - V_{TN4})^2} = \frac{2 \times 10 \times 10^{-6}}{60 \times 10^{-6} \times (0.922 - 0.7)^2} = \underline{6.76} \quad (\text{note how small})$$

this is as compared to $(W/L)_1$. Similarly, for M_2 , we get $I_{D2} = 100\mu A =$

$$\frac{K_P'}{2} \left(\frac{W}{L}\right)_2 (|V_{GS2}| - |V_{TP2}|)^2 = \frac{30 \times 10^{-6}}{2} \times 235.27 \times (|V_{GS2}| - 1)^2 \Rightarrow |V_{GS2}| = \underline{1.168V}$$

$$\Rightarrow V_{G2} = V_{G5} = -\underline{1.168V} \quad (\because V_{S2} = V_0 = 0) \Rightarrow \text{Also, } \because V_{S5} = 0, \therefore V_{GS5} = -\underline{1.168V}$$

$$\therefore \left(\frac{W}{L}\right)_5 = \frac{2I_{D5}}{K_P' (|V_{GS5}| - |V_{TP5}|)^2} = \frac{2 \times 10 \times 10^{-6}}{30 \times 10^{-6} \times (1.168 - 1)^2} = \underline{23.62} \quad (\text{note how small})$$


it is as compared to $(W/L)_2$. This completes the design.

* The ratio of the aspect ratio of the o/p transistor & pre-bias transistor is equal to the ratio of the idling current. * $\because M_1 - M_2$ branch carries an idle current of $100\mu A$, & $M_4 - M_5$ branch carries an idling current of $10\mu A$, \therefore the aspect ratio of M_1 (M_2) should be ~ 10 times that of M_4 (M_5), which we have rigorously proved in this problem, i.e., $\frac{(W/L)_1}{(W/L)_4} = \frac{67.41}{6.76} = \underline{9.97}$, &

$$\frac{(W/L)_2}{(W/L)_5} = \frac{235.27}{23.62} = \underline{9.96} \quad [\text{Note how close these values are to } 10]$$

$$\times \frac{1}{\beta \beta} I_{D1} R_1 = 150 \times 150 \times 150\mu A \times 1k\Omega =$$

4 The eqv. ckt.

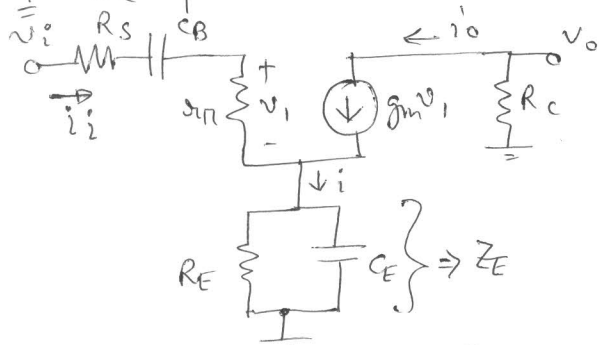

$$Z_E = R_E \parallel \frac{1}{sC_E} = \frac{R_E}{1 + sR_EC_E}, \quad v_o = -i_o R_C =$$

$$-g_m R_C v_1, \quad v_1 = i_i r_{\pi}, \quad i = i_o + i_i = (1 + g_m r_{\pi}) i_i,$$

$$\text{and } i_i = \frac{v_i - i Z_E}{R_S + \frac{1}{sC_B} + r_{\pi}}$$

$$\Rightarrow v_i = i_i \left[\frac{s(R_S + r_{\pi})C_B + 1}{sC_B} \right] + i \frac{R_E}{1 + sR_EC_E}$$

$$\Rightarrow v_i = i_i \left[\frac{(1 + sR_EC_E) [s(R_S + r_{\pi})C_B + 1] + s(1 + \beta)R_EC_B}{sC_B(1 + sR_EC_E)} \right] \quad (\because g_m r_{\pi} = \beta)$$

$$\text{Now, } v_1 = i_i r_{\pi} = v_i \frac{s r_{\pi} C_B (1 + sR_EC_E)}{s(R_S + r_{\pi})C_B + 1 + s^2 R_E (R_S + r_{\pi})C_B C_E + sR_EC_E + s(1 + \beta)R_EC_B}$$

$$\Rightarrow v_o = -g_m R_C v_1 = -g_m R_C \frac{s r_{\pi} C_B (1 + sR_EC_E)}{1 + s[R_EC_E + \{R_S + r_{\pi} + (1 + \beta)R_E\}C_B] + s^2 R_E (R_S + r_{\pi})C_B C_E} v_i$$

$$\Rightarrow A_v(s) = \frac{v_o}{v_i}(s) = A_{vo} \frac{(s/\omega_B)(1 + s/Z_1)}{1 + a_1 s + a_2 s^2} \quad (\text{Look at the complexity of soln.})$$

$$\text{where } A_{vo} = -g_m R_C, \quad \omega_B = \frac{1}{r_{\pi} C_B}, \quad Z_1 = \frac{1}{R_EC_E}, \quad a_1 = [R_EC_E + \{R_S + r_{\pi} + (1 + \beta)R_E\}C_B],$$

and $a_2 = R_E (R_S + r_{\pi}) C_B C_E$. Thus, the low freq. response has a zero at zero freq., another -ve real zero at Z_1 , & 2 -ve real poles, which can be evaluated by solving the quadratic expression in the denominator. Thus, the actual freq. resp. characteristic is pretty complicated. Now, $I_C = 1 \text{ mA} \Rightarrow r_{\pi} = 26 \Omega$, & $r_{\pi} = 5.2 \text{ k}\Omega$ ($\beta = 200$). $\omega_B = \frac{1}{r_{\pi} C_B} = 19.23 \text{ rad/sec} \Rightarrow f_B = \omega_B / (2\pi) = \boxed{3.06 \text{ Hz}}$

$$Z_1 = \frac{1}{R_EC_E} = 20 \text{ rad/sec} \Rightarrow f_{Z_1} = \boxed{3.18 \text{ Hz}}, \quad \text{The coeffs. } a_1 = R_EC_E + [R_S + r_{\pi} + (\beta + 1)R_E]C_B = 1.117, \quad \& \quad a_2 = R_EC_E(R_S + r_{\pi})C_B = 3.1 \times 10^{-3} \Rightarrow D(s) = 1 + 1.117s + 3.1 \times 10^{-3}s^2, \text{ with soln. } s \text{ 2 -ve real roots at } -0.898 \text{ \& } -359.42 \Rightarrow \omega_{P_1} = 0.898 \text{ rad/sec \& } \omega_{P_2} = 359.42 \text{ rad/sec} \Rightarrow f_{P_1} = \boxed{0.14 \text{ Hz}} \text{ \& } f_{P_2} = \boxed{57.2 \text{ Hz}}$$

Thus, the actual lower cutoff freq. is at 57.2 Hz (the highest of all poles & zeros). Now, using the IVTC technique, $R_B^{\infty} = R_S + r_{\pi} = 6.2 \text{ k}\Omega \Rightarrow \tau_1 = R_B^{\infty} C_B = 62 \text{ ms} \Rightarrow f_1 = \frac{1}{2\pi \tau_1} = 2.57 \text{ Hz}$, and $R_E^{\infty} = R_E \parallel [r_{\pi} + \frac{R_S}{\beta + 1}] = 29.17 \Omega \Rightarrow \tau_2 = R_E^{\infty} C_E = 2.917 \text{ ms} \Rightarrow f_2 = \frac{1}{2\pi \tau_2} = 54.56 \text{ Hz} \Rightarrow f_L = \sqrt{f_1^2 + f_2^2} = 54.62 \text{ Hz}$ (compare with 57.2 Hz obtd. from the exact analysis, & appreciate the simplicity of IVTC.

5 Refer to P8 (HA#8). The bias pt. has already been calculated, & $r_{E1} = 4$
 $= r_{E2} = r_E = 24.76 \Omega$, $r_{\pi} = 2.48 k\Omega$, & $R = R_1 || R_2 = 31.97 k\Omega$. \therefore There are

5 caps. in the ckt., we will have five time consts., & five cutoff freqs.

for C_1 , $R_1^{\infty} = R_S + R || r_{\pi} = 7.3 k\Omega \Rightarrow \tau_1 = R_1^{\infty} C_1 = 73 ms \Rightarrow f_1 = \frac{1}{2\pi\tau_1} = 2.18 Hz$

for C_2 , $R_2^{\infty} = R_{E1} || [r_E + \frac{R_S || R}{\beta+1}] = 66.42 \Omega \Rightarrow \tau_2 = R_2^{\infty} C_2 = 6.64 ms \Rightarrow f_2 = 23.96 Hz$

for C_3 , $R_3^{\infty} = R_{C1} + R || r_{\pi} = 9.1 k\Omega \Rightarrow \tau_3 = R_3^{\infty} C_3 = 91 ms \Rightarrow f_3 = 1.75 Hz$


for C_4 , $R_4^{\infty} = R_{E2} || [r_E + \frac{R_{C1} || R}{\beta+1}] = 78.66 \Omega \Rightarrow \tau_4 = 7.87 ms \Rightarrow f_4 = 20.23 Hz$

for C_5 , $R_5^{\infty} = R_{C2} + R_L = 8.8 k\Omega \Rightarrow \tau_5 = 176 ms \Rightarrow f_5 = 0.9 Hz$

$\therefore f_L = [\sum_{i=1}^5 f_i^2]^{1/2} = 31.5 Hz \rightarrow$ Overall lower cutoff freq. of the amplifier.


$P \leq 10\%$ ($= \frac{\pi f_L}{f} \times 100\%$) $\Rightarrow f = \frac{\pi f_L}{P} \times 100 = 989.6 Hz \rightarrow$ min freq. for 10% tilt

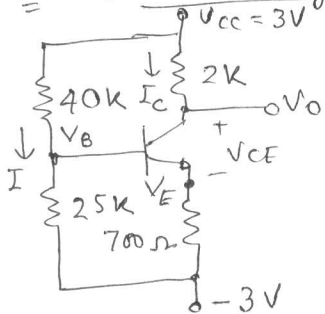6 a) DC Analysis: All capacitors open up. Neglecting base current, $I = \frac{6}{40+25}$



$= 92.31 \mu A \Rightarrow V_B = -3 + 92.31 \mu A \times 25k = -0.692V$
 $\Rightarrow V_E = V_B - V_{BE} = -1.392V \Rightarrow I_C \approx I_E = \frac{-1.392 + 3}{700} = 2.3 mA$
 & $V_O = V_{CC} - I_C \times 2k = 3 - 2.3 mA \times 2k = -1.6V$

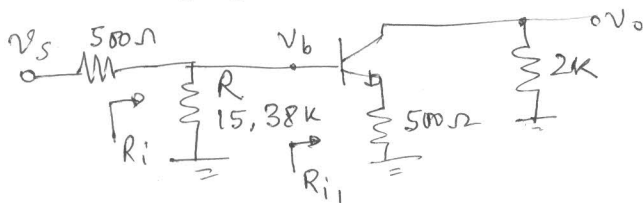b) for ac analysis, at midband, all caps. short out, thus shunting 200Ω resistor at the emitter lead.



$R = 40k || 25k = 15.38k$

$r_E = \frac{V_T}{I_C} = 11.3 \Omega$, $r_{\pi} = \beta r_E = 2.26k$

$R_{i1} = r_{\pi} + (\beta+1) \times 500 = 102.76k$

$R_i = R || R_{i1} = 13.38k$

$\frac{v_o}{v_b} = -\frac{2k}{11.3 + 500} = -3.9$, $\frac{v_b}{v_s} = \frac{R_i}{R_i + 500} = 0.96 \Rightarrow \frac{v_o}{v_s} = \frac{v_o}{v_b} \times \frac{v_b}{v_s} = -3.76$

c) C_E made arbitrarily large $\Rightarrow 200 \Omega$ resistor remains shorted out.

$R_B^{\infty} = 500 + R_i = 13.88k$, $\therefore f_L$ is $20 Hz$, $\therefore C_B = \frac{1}{2\pi f_L R_B^{\infty}} = 0.57 \mu F$

d) C_B is made arbitrarily large. for this case, $R_E^{\infty} = 200 \Omega || R^*$, where

$R^* = 500 + r_E + \frac{15.38k || 500k}{201} = 513.7 \Omega \Rightarrow R_E^{\infty} = 143.95 \Omega$. \therefore for $f_L = 20 Hz$,

$C_E = \frac{1}{2\pi f_L R_E^{\infty}} = 55.28 \mu F$


e) $\therefore C_E$ "sees" much lower resistance than C_B , \therefore we choose C_E to contribute the dominant pole, f_d . \therefore The pole contributed by C_B will be at $f_d/10$.

such that $\sqrt{f_d^2 + (f_d/10)^2} = 20 = f_L \Rightarrow f_d = 19.9 Hz$ & $f_d/10 = 1.99 Hz$

$\Rightarrow C_B = \frac{1}{2\pi (f_d/10) R_B^{\infty}} = 5.76 \mu F$, & $C_E = \frac{1}{2\pi f_d R_E^{\infty}} = 55.56 \mu F$

$\Rightarrow \Sigma C = 61.32 \mu F \Rightarrow$ which is the minimum possible, given the design paradigm.

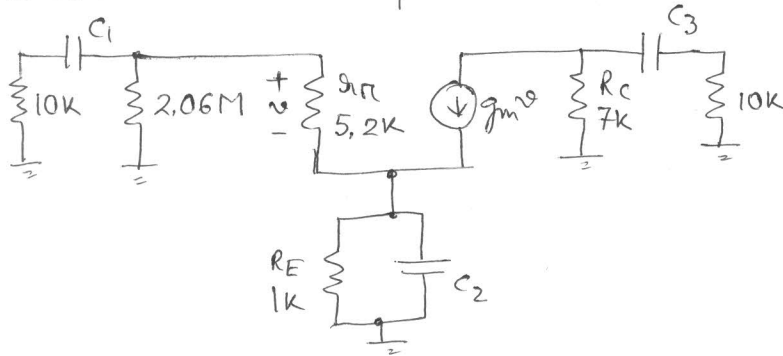7 From Prob. 5 (HA # 8), $R_C = 7\text{K}\Omega$ & $R_B = 2.06\text{M}\Omega$. The i/p is being a (5) current source, we open it. The small-signal eqv. can be drawn as:



for C_1 , $R_1^\infty = 10\text{K} + 2.06\text{M} \parallel 5.2\text{K} = \underline{15.2\text{K}}$

for C_2 , $R_2^\infty = 1\text{K} \parallel \left(\frac{5.2\text{K} + 2.06\text{M} \parallel 10\text{K}}{201} \right)$
 $= \underline{70.1\Omega}$

for C_3 , $R_3^\infty = 10\text{K} + 7\text{K} = \underline{17\text{K}}$

R_2^∞ is least \Rightarrow pick C_2 to contribute

the dominant pole f_d . C_1 & C_3 contribute poles at $f_d/10$ each.

$\Rightarrow \sqrt{f_d^2 + 2(f_d/10)^2} = f_L = 20\text{Hz} \Rightarrow f_d = \underline{19.8\text{Hz}}$ $f_d/10 = \underline{1.98\text{Hz}}$

$\Rightarrow C_2 = \frac{1}{2\pi f_d R_2^\infty} = \underline{114.7\mu\text{F}}$, $C_1 = \frac{1}{2\pi (f_d/10) R_1^\infty} = \underline{5.3\mu\text{F}}$, &

$C_3 = \frac{1}{2\pi (f_d/10) R_3^\infty} = \underline{4.73\mu\text{F}} \Rightarrow \Sigma C = \underline{124.73\mu\text{F}}$

b) $P = \frac{\pi f_L}{f} \times 100\% = \frac{\pi \times 20}{200} \times 100 = \underline{31.4\%}$

c) $P = 2\% \Rightarrow f = \frac{\pi f_L}{P} \times 100 = \frac{\pi \times 20}{2} \times 100 = \underline{3.14\text{KHz}}$