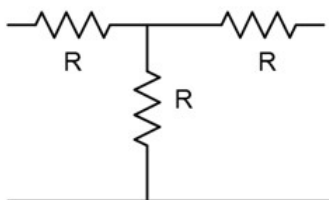


Q.1

ESC201T : Introduction to Electronics
Discussion Quiz 4 (28/10/2020)

Q.1 Determine the Z parameters for the circuit shown. Enter integer values normalized by R and separated by commas as $\frac{z_{11}}{R}, \frac{z_{12}}{R}, \frac{z_{21}}{R}, \frac{z_{22}}{R}$

(if you determine answer as $z_{11} = 5R$, $z_{12} = 6R$, $z_{21} = 7R$ and $z_{22} = 8R$ then enter 5,6,7,8 as the answer)




Your answer:

2,1,1,2

Q.2

ESC201T : Introduction to Electronics
DQ4 (28/10/2020)

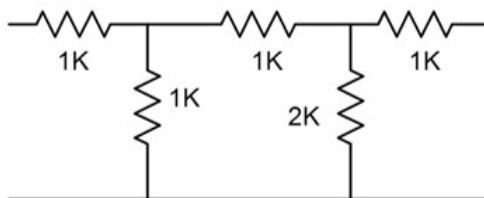Q.2 Determine h_{12} parameter for the circuit shown. (Enter value as y.yy as an example 0.89)



Your answer:

0.25

