

1. Consider an NMOS common-source stage, as shown in Fig.1, with $I_D = 0.5$ mA. Using the ZVTC method, estimate the upper cutoff frequency of the circuit. Data: $W = 100$ μm , $L = 2$ μm , $k'_N = 60$ $\mu\text{A}/\text{V}^2$, $C_{sb} = C_{db} = 20$ fF, $C'_{ox} = 0.7$ fF/ μm^2 , and $C_{gd} = 14$ fF. Also, calculate the rise time for pulse response. Neglect the body effect and the CLM effect.
2. Show that, neglecting R_S , Fig.2(a) is the 2-port representation of a CE(D) circuit, shown in Fig.2(b) with $R_\pi = r_\pi(1 + g_m R_E)$, and $G_m = g_m/(1 + g_m R_E)$. Hence, using the ZVTC technique, evaluate its upper cutoff frequency. Data: $R_S = 10$ k Ω , $R_L = 5$ k Ω , $R_E = 300$ Ω , $\beta = 200$, $f_T = 600$ MHz (at $I_C = 1$ mA), $C_\mu = 0.2$ pF, and $I_C = 1$ mA. Also, calculate the rise time for pulse response.
3. The ac schematics of a common-source-common gate (cascode) stage is shown in Fig.3. Using the ZVTC technique, estimate its upper cutoff frequency. Use the data given in Prob.1, and assume that $\chi_2 = 0.2$. Also, calculate the rise time for pulse response.
4. A wideband monolithic current amplifier is shown in Fig.4. The dc collector bias current of Q_1 is equal to 1 mA, and the emitter area of Q_2 is four times that of Q_1 . Calculate the ac small-signal midband current gain i_o/i_i , and use the ZVTC method to estimate the upper cutoff frequency. Also, calculate the rise time for pulse response. Data: for both Q_1 and Q_2 : $\beta = 200$, and $\tau_F = 0.2$ nsec; for Q_1 : $C_\mu = 0.2$ pF, and $C_{je} = 1$ pF; and for Q_2 : $C_\mu = 0.8$ pF, and $C_{je} = 4$ pF.



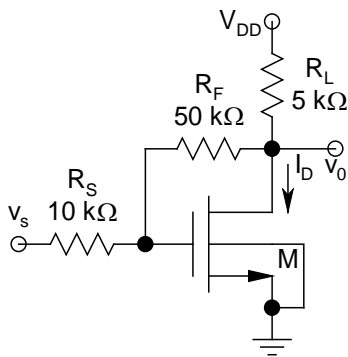


Fig.1

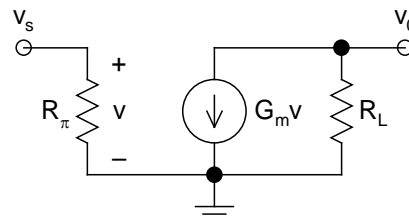

(a)

Fig.2

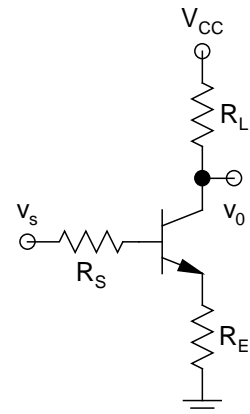

(b)

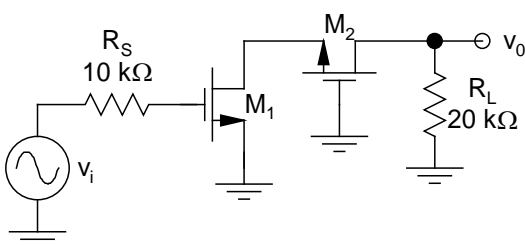


Fig.3

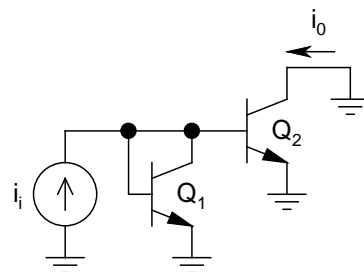


Fig.4