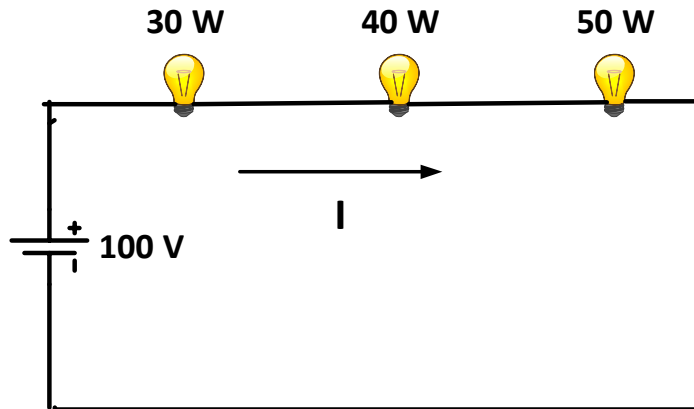


Quiz 1

1. Three light bulbs are connected to a 100 V battery in series. The bulbs are consuming 30 W, 40 W, and 50 W power as shown below. Find the current 'I' through it.



Solution –

Solution :


Resistance of Bulb $B_1 \rightarrow 'R_1'$
" " " $B_2 \rightarrow 'R_2'$
" " " $B_3 \rightarrow 'R_3'$

$$\therefore R_1 = \frac{P_1}{I^2} = \frac{30}{I^2} \Omega$$
$$\sim R_2 = \frac{P_2}{I^2} = \frac{40}{I^2} \Omega$$
$$\sim R_3 = \frac{P_3}{I^2} = \frac{50}{I^2} \Omega$$

§ As, $V = IR$

$$\therefore 100 = I \left(R_1 + R_2 + R_3 \right) = I \left(\frac{30}{I^2} + \frac{40}{I^2} + \frac{50}{I^2} \right)$$
$$\Rightarrow 100 = I \left(\frac{120}{I^2} \right) \Rightarrow 100I = 120$$
$$\boxed{I = 1.2 \text{ A}}$$

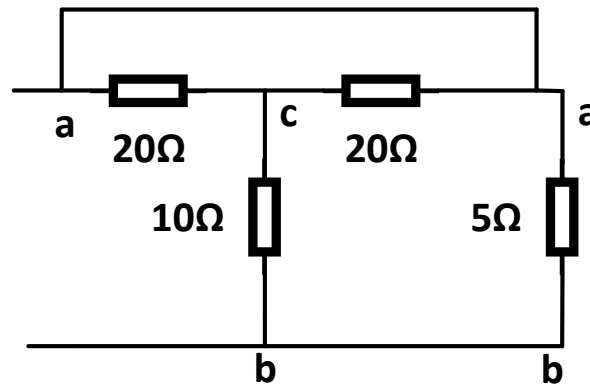2. For the circuit shown below, find the equivalent resistance across a-b.



Solution –


Solution:

In the circuit, 'ac' and 'ca' are in parallel.
So,

$$R_{eq} = \frac{5 \times 20}{25}$$

$$R_{eq} = 4\Omega$$

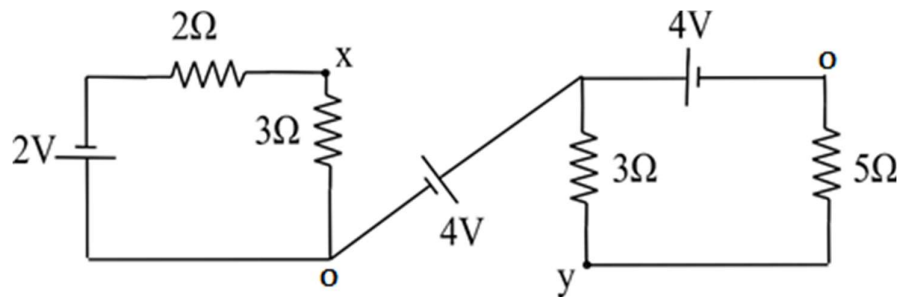3. What is the potential difference between the points x and y in the circuit given below (O are the grounded nodes) -



Solution –

2.

Current in Loop-1 (L-1) = $\frac{2}{5} \text{ A} = 0.4 \text{ A}$

Corresponding potential of x w.r.t ground = -1.2 V

Similarly, Current in Loop-2 (L-2) = $\frac{4}{8} = 0.5 \text{ A}$

Corresponding potential of y w.r.t o = $+2.5 \text{ V}$

\therefore y is at- 3.7 V higher potential w.r.t. x

So, $V_{xy} = 3.7 \text{ V}$

4. The current through a 0.2 Henry inductor is $i(t) = 2te^{-t}$ A. Find the voltage across it and the energy stored in the inductor?

Solution -

Given that 0.2 H inductor.

$$i(t) = 2te^{-t} \text{ Amp.}$$

⇒ voltage across inductor:

$$\begin{aligned} v(t) &= L \frac{di}{dt} = 0.2 \frac{d}{dt} (2te^{-t}) \\ &= 0.2 \left[2t(-1)e^{-t} + e^{-t} \cdot 2 \right] \\ &= 0.4 e^{-t} (1-t) \text{ V} \end{aligned}$$

⇒ Energy stored :

$$\begin{aligned} W(t) &= \frac{1}{2} L i^2 \\ &= \frac{1}{2} \cdot 0.2 \times 2^2 t^2 e^{-2t} \\ &= 0.4 t^2 e^{-2t} \text{ J} \end{aligned}$$

5. Calculate the phase angle between $v_1 = -5 \cos(50t+20)$ and $v_2 = 20 \sin(50t+240)$? Also find which voltage is leading?

Solution -

$$\begin{aligned} \text{Given } v_1 &= -5 \cos(50t+20) \\ &= 5 \cos(50t+20+180) \\ &= 5 \cos(50t+200) \end{aligned}$$

$$\begin{aligned} v_2 &= 20 \sin(50t+240) \\ &= 20 \cos(50t+240-90) \\ &= 20 \cos(50t+150) \end{aligned}$$


$$\Rightarrow \text{Phase angle difference} = 200^\circ - 150^\circ = 50^\circ$$

$$\Rightarrow v_1 \text{ leads } v_2 \text{ by } 50^\circ.$$


\Rightarrow Phasor form:

$$v_1 = 5 \angle 200^\circ$$

$$v_2 = 20 \angle 150^\circ$$

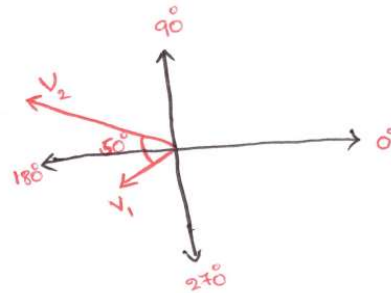

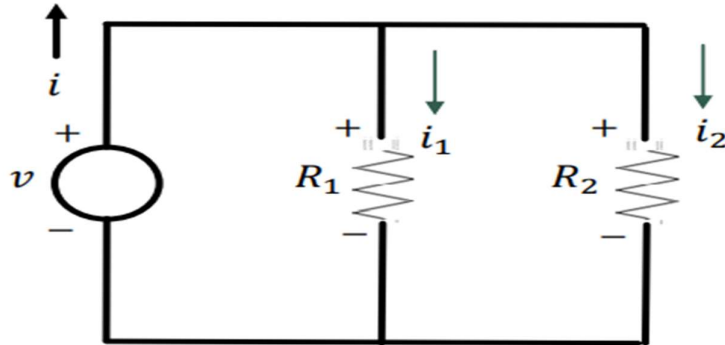6. In Figure below, Let $R_1 : R_2 = 1 : 2$, and total current $i = 15$ A. Find the branch currents i_1 and i_2 ? Let v is the supply voltage; v_1, v_2 are the voltage across R_1 and R_2 respectively. If $v : v_1 : v_2 = a : b : c$, then, find a, b , and c ?



Given $R_1 : R_2 = 1 : 2$; total current $i = 15$ A.

⇒ Branch Currents :

$$\begin{aligned} i_1 &= i \frac{R_2}{R_1 + R_2} \\ &= i \frac{1}{\left(\frac{R_1}{R_2}\right) + 1} \\ &= i \frac{1}{1.5} \\ &= \frac{15}{1.5} = 10 \text{ A} \end{aligned}$$

$$\begin{aligned} i_2 &= i \frac{R_1}{R_1 + R_2} \\ &= i \frac{1}{1 + \frac{R_2}{R_1}} \\ &= i \frac{1}{1 + 2} \\ &= \frac{15}{3} = 5 \text{ A} \end{aligned}$$

⇒ voltage across all the parallel branches is same

So $v = v_1 = v_2$.

So, $a = b = c = 1$.