

**DEPARTMENT OF ELECTRICAL ENGINEERING
INDIAN INSTITUTE OF TECHNOLOGY, KANPUR**

EE 210

MINI-QUIZ #8B

31.3.21

Total Marks: 10

Total Time: 10 mins.

V_i, V_o have both DC (V_I, V_O) and ac (v_i, v_o) components. Data: For M_n : $V_{TN0} = 0.6 \text{ V}$, $k'_N = 50 \mu\text{A}/\text{V}^2$, $\lambda_n = 0.15 \text{ V}^{-1}$; for M_p : $V_{TP0} = -0.6 \text{ V}$, $k'_P = 20 \mu\text{A}/\text{V}^2$, $\lambda_p = 0.1 \text{ V}^{-1}$.

- If $(W/L)_p = 50$, choose $(W/L)_n$, such that the stage is *unmatched by nature, but matched by performance*.
- Hence, evaluate the ac midband voltage gain v_o/v_i .
- If $V_{TN0} \neq |V_{TP0}|$, how will the result of part a) change? Discuss.

