

Consider all voltage and current sources to be ideal.

1. In the circuit shown in fig. 2.1, R_L is an adjustable resistive load. What is the value of this load (R_L) for which maximum power is dissipated at the load? What is this maximum power dissipation at R_L ?

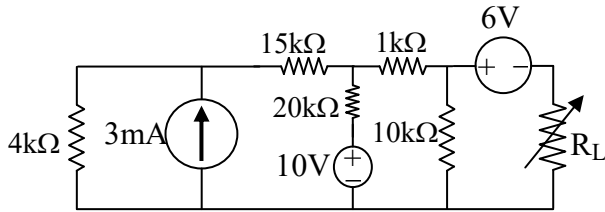


Figure 2.1

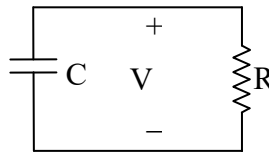


Figure 2.2

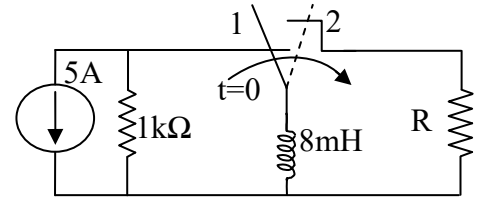


Figure 2.3

2. In the R-C circuit shown in fig. 2.2 the voltage and the current expressions are: $v(t) = 72e^{-500t}$ V, $t \geq 0$, and $i(t) = 9e^{-500t}$ mA for $t \geq 0^+$. Find (i) R, (ii) C, (iii) τ [ms], (d) the initial energy stored in the capacitor, and (e) how many ms it takes to dissipate 75% of the initial energy stored in the capacitor?
3. The switch in the circuit seen in fig. 2.3 has been in position 1 for a long time. At $t = 0$ the switch moves instantaneously to position 2. Find the value of R so that half of the initial energy stored in the 8-mH inductor is dissipated in R in $10\mu\text{s}$.
4. The capacitor in the circuit shown in fig. 2.4 has been charged to 300V. At $t=0$, switch S1 closes and the switch S2 closes $200\mu\text{s}$ after switch S1 has closed. Find the current through the switch S2 at a time $t=300\mu\text{s}$.

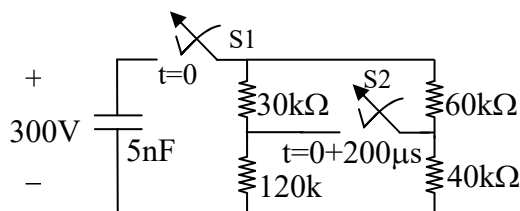


Figure 2.4

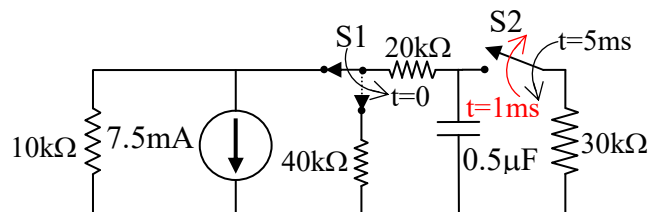


Figure 2.5

5. In the circuit of fig. 2.5, switch S1 disconnects from the $10k\Omega$ resistance and instantaneously connects to the $40k\Omega$ resistor at time $t = 0$, with the switch S2 closed (connected to the $20k\Omega$ resistor). At $t = 1\text{ms}$, switch S2 opens out. Again at $t = 5\text{ms}$, switch S2 closes.
 - (a) Find the voltage across the capacitor (v_C) at all times.
 - (b) What percentage of the total energy stored on the capacitor is dissipated in the $30k\Omega$ resistor till 15ms ?
6. The switch in the circuit of fig. 2.6 has been closed for a long time. The switch opens at time $t = 0$. Find the inductor voltage $v_L(t)$ for all $t \geq 0^+$.

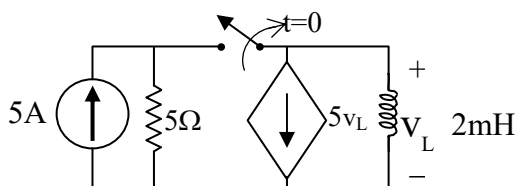


Figure 2.6

7. The switch in fig. 2.7 has been open for a long time. At $t = 0$ the switch closes. Find the inductor voltage $v_L(t)$ for all $t \geq 0^+$.

8. For the $2\mu\text{F}$ capacitor circuit, shown in fig. 2.8, the switch has been closed for a long time. The capacitor is rated for a maximum voltage of 1.5kV , after which the dielectric breaks down and shorts it. If the switch opens at time $t = 0$, then at what time does the capacitor reach the dielectric breakdown voltage?

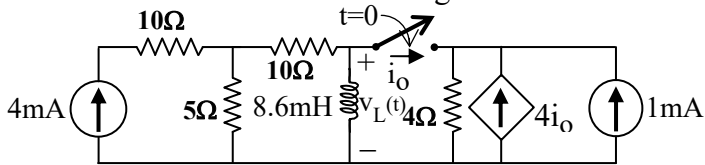


Figure 2.7

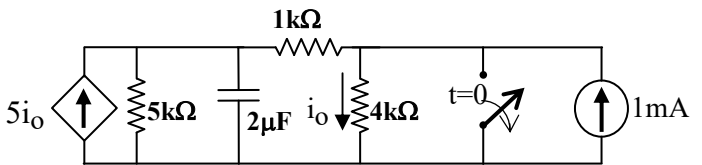


Figure 2.8

9. The voltage waveform in Fig. 9(a) is applied to the circuit in Fig. 9(b). If the initial voltage on the capacitor is zero, (a) Calculate $v_o(t)$, and (b) Sketch $v_o(t)$ versus t .

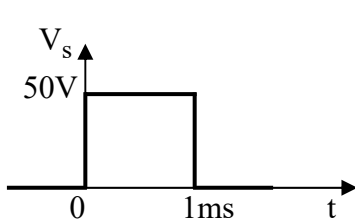


Figure 2.9(a)
2.10(b)

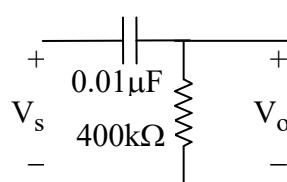


Figure 2.9(b)


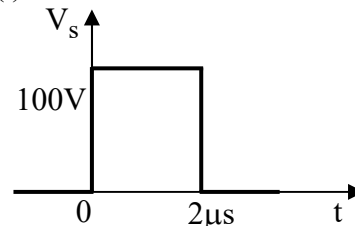






Figure 2.10(a)

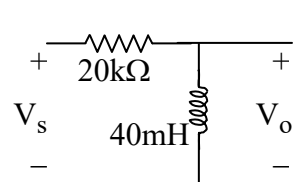

Figure

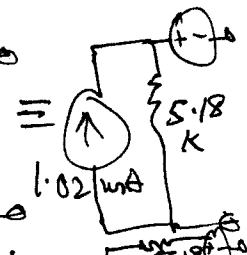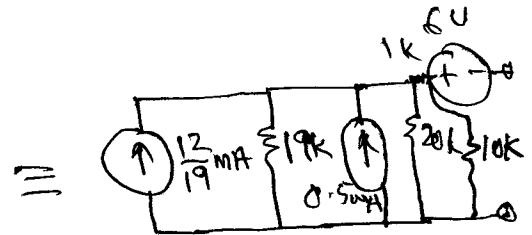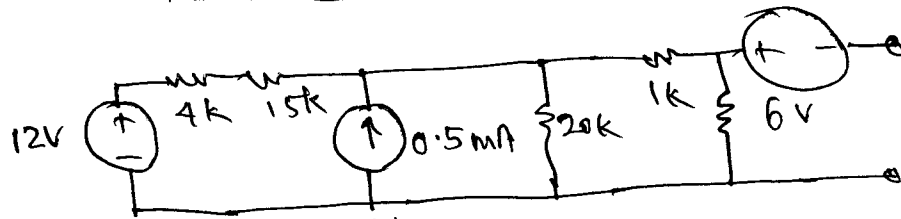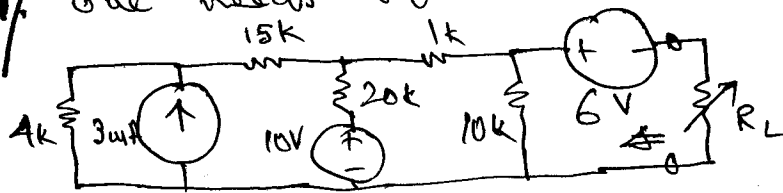10. The voltage waveform shown in Fig. 10(a) is applied to the circuit of Fig. 10(b). If the initial current in the inductor is zero, then (i) calculate $v_o(t)$ and (ii) sketch $v_o(t)$ versus t .

one needs to find the Thevenin Equivalent across R_L .



$$\therefore V_{oc} = 5.28 - 6 = -0.72V$$

$$R_{Th} = 9.74k + 3.18k = 12.92k$$

$$\therefore \text{Maximum power transfer when } R_L = R_{Th} = 12.92k$$

$$P_{max} = \frac{(V_{oc})^2}{4R_{Th}} = \frac{(-0.72)^2}{4 \times 12.92k} = 99.5 \mu W$$

2/ $v(t) = 72e^{-500t} V$, $i(t) = 9e^{-500t} mA$

$$\frac{1}{\tau} = 500 \text{ or } RC = \frac{1}{500} = 2 \times 10^{-3} = 2ms$$

$$R = \frac{v(t)}{i(t)} = \frac{72}{9 \times 10^{-3}} = 8k\Omega \therefore C = \frac{2 \times 10^{-3}}{8 \times 10^3} = 0.25 \mu F$$

$$v_c(\infty) = 0, \therefore v_c(0^+) = 72V \therefore W_{c,initial}(0^+) = \frac{1}{2} C v_c(0^+)^2$$

$$= 0.5 \times 0.25 \mu \times 72^2 = 648 \mu J$$

$$W_c(t) = v(t) \cdot i(t)$$

$$= 72 \times 9 \times e^{-1000t}$$

$$= 0.75 \times 648 \times 10^{-6}$$

$$\ln\left(\frac{0.75 \times 648 \times 10^{-6}}{72 \times 9}\right) = -1000t \text{ or } t = \frac{14.1}{1000} = 14.1 ms$$

At time "t" energy stored in the capacitor is

$$W_c(t) = \frac{1}{2} C v_c(t)^2 = 0.5 \times 0.25 \mu \times 72^2 e^{-1000t} = 0.25 \times 648 \mu J$$

$$\text{or } 1000t = -\ln(0.25) = 1.39$$

$$\therefore t = 1.39 ms$$

3/ $i_L(0^-) = -5A$ as the 100Ω resistor is shorted.

$$\therefore i_L(0^+) = -5A. \quad \therefore W_L(0^+) = \frac{1}{2} L i_L^2(0^+) = 0.5 \times 8 \times 10^{-3} \times 25 = 100 \text{ mJ}.$$


$$i_L(\infty) = 0 \quad \therefore i_L(t) = 0 + [5 - 0] e^{-t/\tau_{LR}}$$

$$\text{where } \tau_{LR} = \frac{L}{R} \Rightarrow \text{or } \frac{1}{2} L \times 25 e^{-2t/(L/R)} = 50 \text{ mJ}, \quad \text{and } t = 10 \mu s.$$

$$\therefore \frac{50 \times 2}{8 \times 25} = e^{-2 \times 10^{-5} / (L/R)} \quad \text{or } \ln(0.5) = - \frac{2 \times 10^{-5}}{L/R}$$

$$\text{or } 0.693 = \frac{2 \times 10^{-5}}{8 \times 10^{-3}} R \quad \text{or } R = 277.2 \Omega$$

4/ $0 \leq t \leq 200 \mu s$

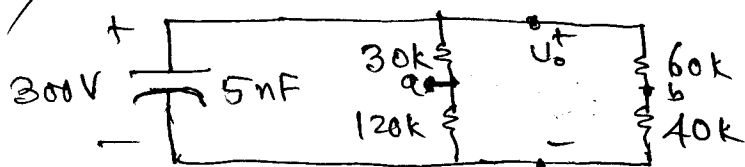

$$U_o(0^-) = 300V$$

$$R_{eq} = (30 + 120) \parallel (60 + 40) \text{ k}\Omega$$

$\therefore U_o(\infty) = 0V$ discharging by R_{eq} .

$$R_{eq} = 60 \text{ k}\Omega \quad \& \quad \tau_{RC} = 60 \times 10^3 \times 5 \times 10^{-9} = 0.3 \text{ ms}.$$

$$\therefore U_o(t) = 300 e^{-t/0.3 \times 10^{-3}} \quad \text{for } 0 \leq t \leq 200 \mu s.$$

$$\text{at } t = 200 \mu s \quad U_o(200 \mu s) = 300 e^{-200/300} = 154V.$$

$t \geq 200 \mu s$ $U_o(\infty) = 0$, $U_o(0^-) = 154V$. and point a & b are shorted.

$$\text{Now } R_{eq} = (30 \parallel 60) + (120 \parallel 40) \text{ k}\Omega = 50 \text{ k}\Omega$$

$$\tau_{RC} = 5 \times 10^{-9} \times 50 \times 10^3 = 250 \times 10^{-6} \text{ s}, \quad \frac{1}{\tau} = 4000$$

$$U_o(t \geq 200 \mu s) = 154 e^{-4000(t - 200 \times 10^{-6})}$$

$$\text{a \& b are shorted} \quad \therefore U_a = U_b = \frac{154}{50} \times (120 \parallel 40) e^{-4000(t - 200 \times 10^{-6})}$$

$$= 92.4 e^{-4000(t - 200 \times 10^{-6})}$$

$$i_{30k} = \frac{U_o(t \geq 200 \mu s) - U_a(t \geq 200 \mu s)}{30k} = \frac{(154 - 92.4)}{30} e^{-4000(t - 200 \times 10^{-6})} \text{ mA}$$

$$\therefore i_{30k}(300 \mu s) = 2.05 e^{-4000 \times 100 \times 10^{-6}} = 2.05 \times 0.67 = 1.374 \text{ mA}$$

Similarly

$$i_{60k}(300 \mu s) = \frac{154 - 92.4}{60} \times 0.67 = 0.688 \text{ mA}$$

$$i_{120k}(300 \mu s) = \frac{92.4 \times 0.67}{120k} = 0.516 \text{ mA}$$

$$i_{40k}(300 \mu s) = \frac{92.4}{40} \times 0.67 = 1.55 \text{ mA}$$

$$\therefore i_{a \rightarrow b} = \frac{1.374 - 0.516}{0.858} = \frac{1.55 - 0.688}{0.862} = 0.86 \text{ mA}$$

In the left branch


current reduces from 1.374 mA to 0.96 mA

& in the right branch

current increases from 0.688 mA to 2.31 mA .

5/

$t < 0$

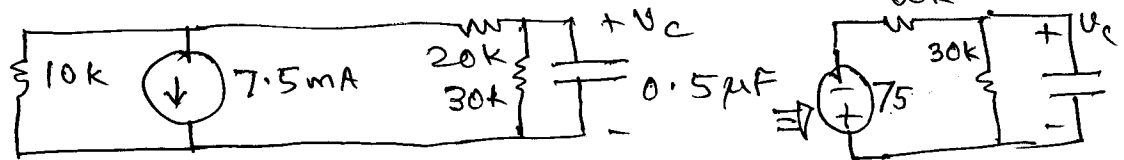

$V_c(0^-) = -37.5V = V_c(0^+)$

$0 \leq t \leq 1ms$




$R_{Th} = 30k || 60k = 20k\Omega$

$\tau = 0.5\mu \times 20k = 10ms$

$V_c(0 \leq t \leq 1ms) = -37.5 e^{-100t}$, $V_c(\infty) = 0$

$V_c(t=1ms) = -37.5 e^{-0.1} = -33.9V$

$1ms \leq t \leq 5ms$

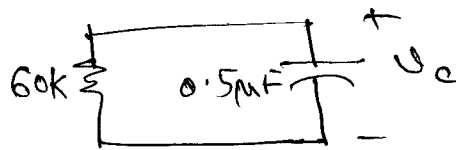


$\tau_{1-5ms} = 60k \times 0.5\mu = 30ms$

$V_c(1ms) = -33.9$, $V_c(\infty) = 0$

$\therefore V_c(1ms \leq t \leq 5ms) = -33.9 e^{-\frac{(t-1ms)}{30ms}}$

At $t=5ms$, $V_c(5ms) = -33.9 e^{-4/30} = -29.7V$

$5ms \leq t < \infty$

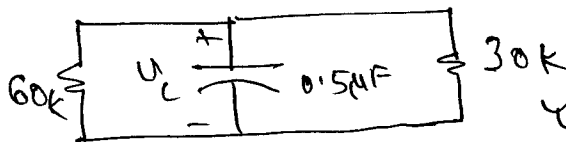

$R_{Th} = \frac{60 \times 30}{90} = 20k$

$\tau(t \geq 5ms) = 0.5 \times 10^{-6} \times 20 \times 10^3 = 10ms$

Again $V_c(\infty) = 0$

$\therefore V_c(t \geq 5ms) = -29.7 e^{-(t-5ms)/10ms}$

$V_c(t=15ms) = -29.7 e^{-1} = -1.1V$

Energy stored at $t=0^+ \rightarrow W_c = \frac{1}{2} C V_c^2(0^+) = 0.5 \times 0.5 \times 10^{-6} \times 37.5^2 = 352 \mu J$

Dissipation:

$P_{30k} = \frac{V_c^2(t \leq 1ms)}{30k} = \frac{37.5^2 e^{-200t}}{30k}$

$\therefore W_{30k}(0 \leq t \leq 1ms) = -\frac{0.47 \times 10^{-3}}{200} [e^{-200t}]_0^{1ms} = -235 \mu \times [e^{-0.2} - 1] \mu J = 42.6 \mu J$

$P_{30k}(1ms \leq t \leq 5ms) = 0$

$P_{30k}(5ms \leq t \leq 15ms) = \frac{29.7^2 e^{-2(t-5ms)/10ms}}{30k} = \frac{29.7^2}{30k} e^{-2(t-5ms)/10ms}$

$W_{30k} = +29.4 m \times \int_{5ms}^{15ms} e^{-200(t-5ms)} dt = -\frac{29.4}{200} m [e^{-200(t-5ms)}]_5^{15}$


$= -1.47 \mu \times [e^{-200 \times 10 \times 10^{-3}} - 1] = -1.47 \mu \times [e^{-2} - 1] = 127 \mu J$

$\sum W_{30k} = (42.6 + 0 + 127) \mu J = 170 \mu J$

$\% = \frac{170}{352} \times 100 = 48.3\%$

6/ At $t < 0$ The inductor acts as a short \therefore
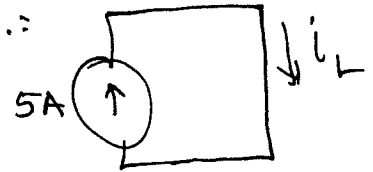
$$i_L(0^-) = 5A \text{ and } v_L(0^-) = 0.$$




$t > 0$ v_L should decrease with time as there are no independent sources connected

$$\therefore i_L(\infty) = 0 \quad v_L \rightarrow 0, \text{ so } v_L \rightarrow 0.$$

$$\therefore i_L(t) = i_L(\infty) + [i_L(0^+) - i_L(\infty)] e^{-t/\tau} = 5e^{-t/\tau}$$

To find τ for $t > 0$

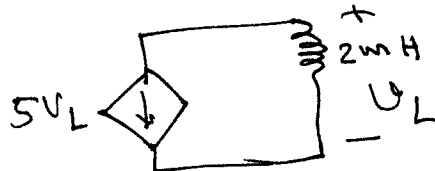

$$\therefore v_{oc} = v_L(t)$$



$$R_{Th} = \frac{v_t}{i_t} = \frac{v_L(t)}{5v_L(t)} = 0.2\Omega$$

$$\therefore \tau = \frac{2mH}{0.2\Omega} = 10ms.$$

$$\therefore i_L(t) \Big|_{t>0} = 5e^{-t/10ms} = 5e^{-100t} \text{ A}$$

$$\text{Again } v_L(t) \Big|_{t>0} = -i_L(t) \Big|_{t>0} \times R_{Th} = -5 \times 0.2 e^{-100t} = -e^{-100t}$$

$$\begin{aligned} \text{Alternatively } v_L(t) \Big|_{t>0} &= L \frac{di_L(t)}{dt} \Big|_{t>0} = 2 \times 10^{-3} \times (-100) \times 5e^{-100t} \\ &= -e^{-100t} \end{aligned}$$

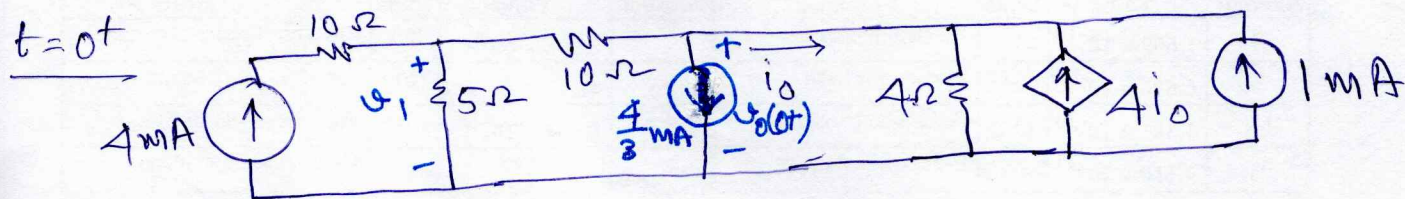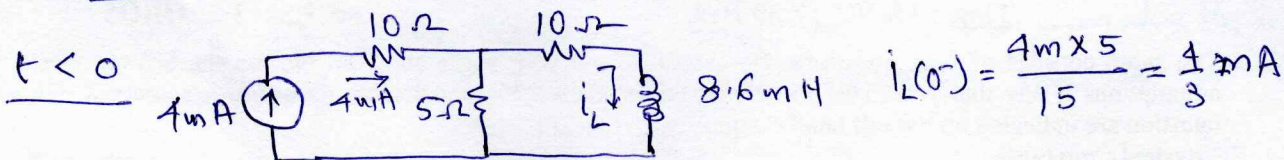

$v_o(0^+)$ node KCL

$$\frac{4mA}{3} + \frac{v_o(0^+) - v_1}{10} + \frac{v_o(0^+)}{4} - 4i_o - 1mA = 0.$$

$$\text{or } v_o(0^+) \times \frac{14}{40} = 4i_o + \frac{v_1}{10} - \frac{1}{3}m \Rightarrow 14v_o(0^+) = 160i_o + 4v_1 - \frac{40}{3}m \quad \dots (1)$$

At node for v_1 KCL: $\frac{v_1}{5} + \frac{v_1 - v_o(0^+)}{10} - 4mA = 0.$

$$\text{or } \frac{v_o(0^+)}{10} = \frac{3v_1}{10} - 4m \Rightarrow v_o(0^+) = 3v_1 - 40m.$$

$$\text{or } v_1 = \frac{v_o(0^+)}{3} - \frac{40}{3}m \quad \dots (2)$$

KCL at right node


$$i_o = \frac{v_o(0^+)}{30} - \frac{v_o(0^+)}{10} - \frac{4}{3}m - \frac{4}{3}m = -\frac{1}{15}v_o(0^+) - \frac{8}{3}m \quad \dots (3)$$

\therefore using (2) & (3) in (1)

$$14v_o(0^+) = -160\left(\frac{v_o(0^+)}{15} + \frac{8}{3}m\right) + \frac{4}{3}(v_o(0^+) - 40m) - \frac{40}{3}m$$

$$\text{or } -1.33v_o(0^+) = -193.33m \Rightarrow v_o(0^+) = 371mV.$$

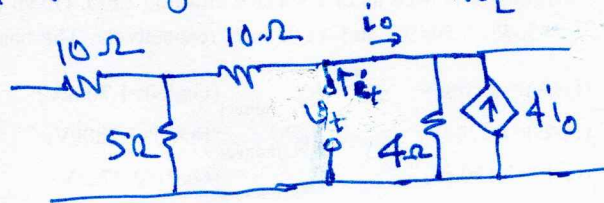$v(\infty)$ has to be $v(\infty) = 0$ as parallel resistances are dissipative.
Next is to find the R_{Th} whose equivalent circuit is:



$$\therefore i_t = \frac{v_t}{15} + \frac{v_t}{4} - 4i_o$$

$$\& i_o = \frac{v_t}{4} - 4i_o \text{ or } i_o = \frac{v_t}{20}$$

$$\therefore i_t = \frac{v_t}{15} + \frac{v_t}{4} - \frac{v_t}{5} = 0.1167v_t \text{ and } R_{Th} = \frac{v_t}{i_t} = 8.57 \approx 8.6\Omega$$

$$\therefore \tau_L = \frac{L}{R_{Th}} = \frac{8.6m}{8.6} = 1ms.$$

At $t = \infty$

$$i = \frac{4m \times 5}{15}, i_o = -4i_o - 1mA \rightarrow i_o = -0.2mA$$


$$i(\infty) - i_o(\infty) = i_L(\infty) = 1.533mA$$

$$\therefore i_L(t \geq 0) = 1.533 + [1.333 - 1.533]e^{-1000t}$$

$$= 1.533 - 0.2e^{-1000t}$$

$$v_L(t \geq 0) = L \frac{di_L}{dt} = 1.72e^{-1000t}$$

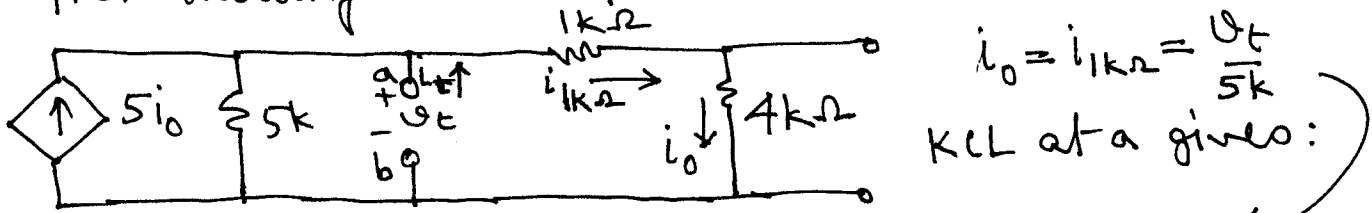
8/ For $t > 0$ find the Thevenin eqv. at the terminals a, b, after nulling the independent sources. The eqv. circuit is



$$i_t = \frac{V_t}{5k} - 5i_o + \frac{V_t}{5k} = \frac{2V_t}{5k} - 5i_o = \frac{2V_t}{5k} - V_t$$

$$= -\frac{3V_t}{5k} \quad \text{or} \quad R_{Th} = -\frac{5k}{3} = -1.67k\Omega$$

To find V_{oc}

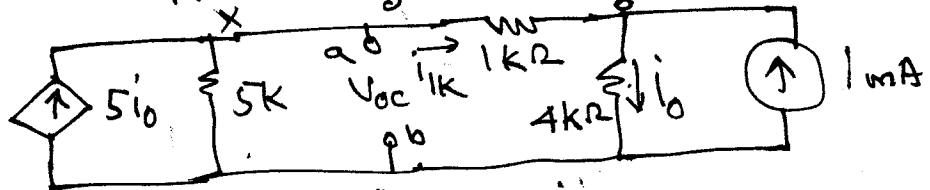

At node y, $i_{1k} = i_o - 1m$ or $i_{1k} + 1m = i_o$


$$V_{oc} = 1k \times i_{1k} + i_o \times 4k = 5k i_{1k} + 4$$

At node x, $i_{1k} - 5i_o + \frac{V_{oc}}{5k} = 0$ or $\frac{i_{1k}}{5} + \frac{V_{oc}}{25k} = i_o = i_{1k} + 1m$

$$\therefore \frac{4}{5} i_{1k} = \frac{V_{oc}}{25k} - 1m \quad \text{or} \quad i_{1k} = \frac{1}{20k} V_{oc} - \frac{5}{4} m$$

$$\therefore V_{oc} = 5k \times \left(\frac{V_{oc}}{20k} \right) - 5k \times \frac{5}{4} m + 4 = \frac{5}{20} V_{oc} - \frac{25}{4} + 4$$
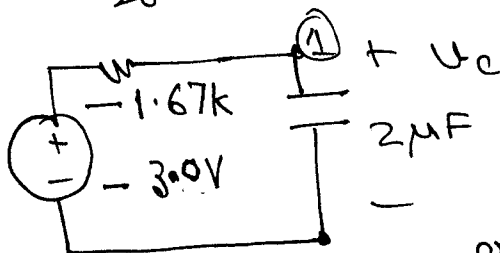
$$\text{or} \quad \frac{15}{20} V_{oc} = -\frac{9}{4} \quad \text{or} \quad V_{oc} = -\frac{3}{4} \times \frac{20}{15} = -3.0 \text{ V}$$



KCL gives at ①

$$C \frac{dV_c}{dt} + \frac{V_c - (-3.0)}{-1.67k} = 0$$

$$\text{or} \quad 2 \times 10^{-6} \frac{dV_c}{dt} - \frac{V_c + 3.0}{1.67k} = 0$$

$$\text{or} \quad \frac{dV_c}{dt} = 299.4 (V_c + 3.0)$$

$$\text{let } x = V_c + 3.0$$

$$\therefore \frac{dx}{dt} = \frac{dV_c}{dt}$$

$$\text{or} \quad \frac{dx}{dt} = 299.4 x$$


$$\therefore \int \frac{dx}{x} = \int 299.4 dt \quad \text{or} \quad \ln x = \frac{299.4 t}{299.4}$$

$$\therefore x = e$$

$$\therefore V_c = -3.0 + e^{299.4 t} = 1500 \text{ V for capacitor breakdown.}$$

$$\text{or} \quad 299.4 t_B = \ln(1503.0)$$


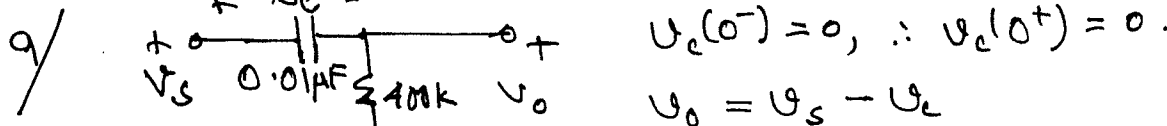
$$\text{and } t_B = \frac{\ln(1503.0)}{299.4} = 0.0244 \text{ s} \approx 24.4 \text{ ms.}$$



$0 \leq t \leq 1 \text{ ms}$ $V_c(0^+) = 0, V_c(\infty) = 50 \text{ V}, \tau = 0.01 \times 10^{-6} \times 400 \times 10^3 = 4 \text{ ms}.$
 $\therefore V_c(0 \leq t \leq 1 \text{ ms}) = 50 - 50 e^{-t/4 \text{ ms}} = 50(1 - e^{-250t}), \therefore V_o = 50 e^{-250t}$ --- (1)

$1 \text{ ms} \leq t \leq \infty$ $V_s = 0 \text{ V}.$
 $V_c(1 \text{ ms}) = 50(1 - e^{-250 \times 10^{-3}}) = 11.06 \text{ V}$ and $V_c(\infty) = 0.$
 $V_c(1 \text{ ms} \leq t \leq \infty) = 0 + (11.06 - 0)e^{-250(t - 0.001)}$
 $= 11.06 e^{-250(t - 0.001)} = 14.2 e^{-250t}$ --- (2)
 $V_o(t = 1 \text{ ms}) = 50 - 11.06 = 38.94 \text{ V}.$

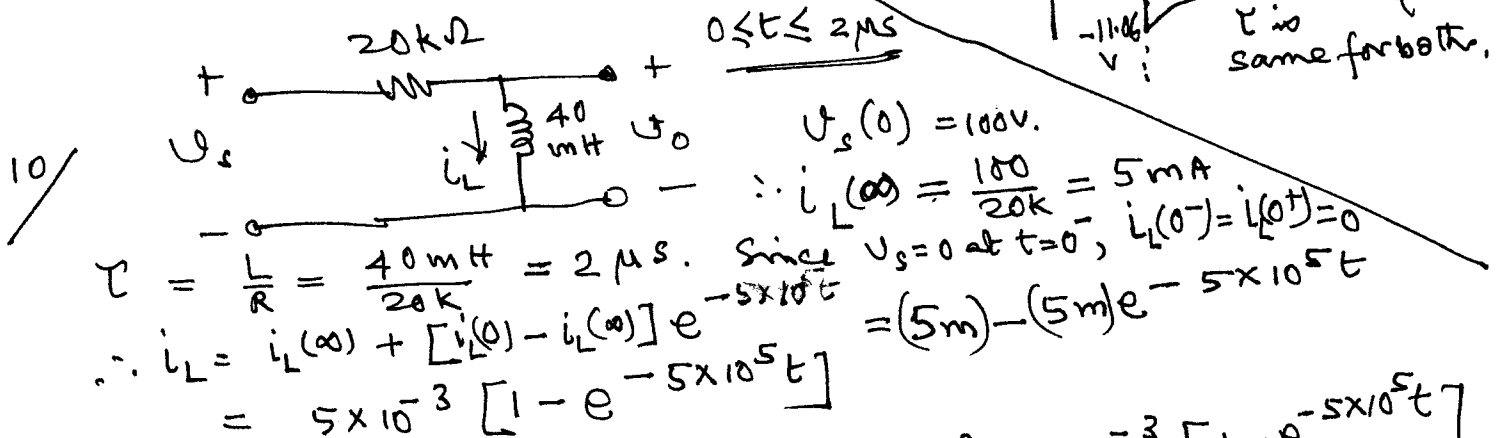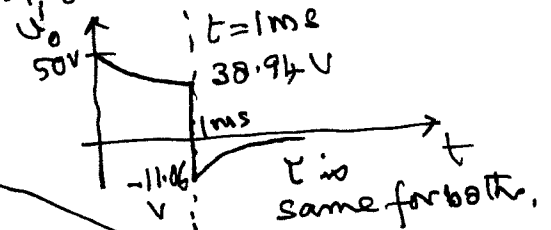$V_o(t = 1 \text{ ms})$ from (2) $= 0 - 14.2 e^{-0.25} = -11.06 = 38.94 - 50$
 This calculation need not be done as when V_s goes from 50 to 0 the voltage across the capacitor (38.94V) cannot change.
 \therefore the change must occur across the 400 kΩ resistance, which is $38.94 - 50 = -11.06 \text{ V}.$




$\therefore V_o = V_s - 20k \times i_L = 100 - 20 \times 10^3 \times 5 \times 10^{-3} [1 - e^{-5 \times 10^5 t}]$ --- (1)
 $V_o(t = 2 \mu \text{ s}) = 100 e^{-5 \times 10^5 \times 2 \times 10^{-6}} = 36.79 \text{ V}$

$2 \mu \text{ s} \leq t \leq \infty$ $i_L(2 \mu \text{ s}) = 5 \text{ m} [1 - e^{-1}] = 3.16 \text{ mA}$
 again $i_L(\infty) = 0$ & $i_L(t \geq 2 \mu \text{ s}) = 0 + (3.16 \text{ m} - 0) e^{-5 \times 10^5 (t - 2 \times 10^{-6})}$
 $= 3.16 e^{-5 \times 10^5 (t - 2 \mu \text{ s})} \text{ mA} = 8.59 e^{-5 \times 10^5 (t - 2 \mu \text{ s})}$

At $t = 2 \mu \text{ s}$ $V_o = L \frac{di_L}{dt} = 40 \text{ m} \times 3.16 \text{ m} \times (-5 \times 10^5) e^{-5 \times 10^5 (t - 2 \mu \text{ s})}$

$\therefore V_o(t = 2 \mu \text{ s}) = -63.2 \text{ V}$

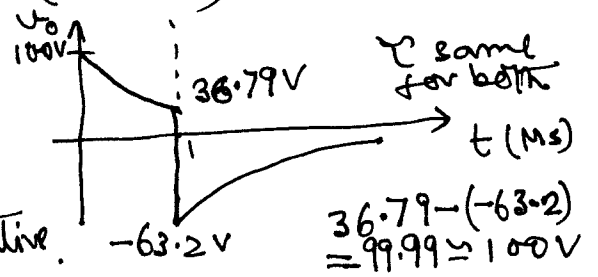Again the argument here is that since the current cannot change instantaneously in the inductor at $t = 2 \mu \text{ s}$ is dropped across R and when $V_s \rightarrow 0$ at $2 \mu \text{ s}$, the voltage across the inductor is negative.



$36.79 - (-63.2) = 99.99 \approx 100 \text{ V}$