

- Thus, the *frequency response* of this circuit looks like a *staircase*, having *two steps*


➤ C_π :

- R_π^0 *can't be obtained by inspection*
- *Analyze the circuit and show that:*

$$R_\pi^0 = r_\pi \parallel \left(\frac{R_S + R_L}{1 + g_m R_L} \right)$$

$$\Rightarrow \tau_1 = R_\pi^0 C_\pi$$

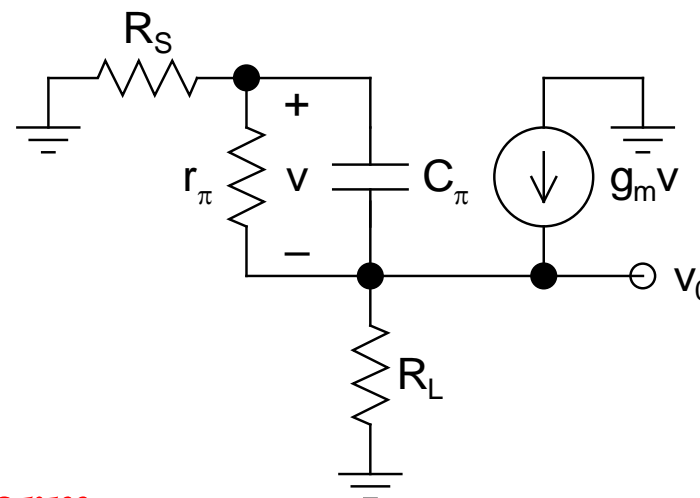- This is another *Standard Form* and the *topology should be carefully noted*



➤ C_μ :


- This is *relatively straightforward*
- *By inspection*:

$$R_{eq} = r_\pi + (\beta + 1)R_L$$


$$R_\mu^0 = R_S \parallel R_{eq}$$

$$\Rightarrow \tau_2 = R_\mu^0 C_\mu$$

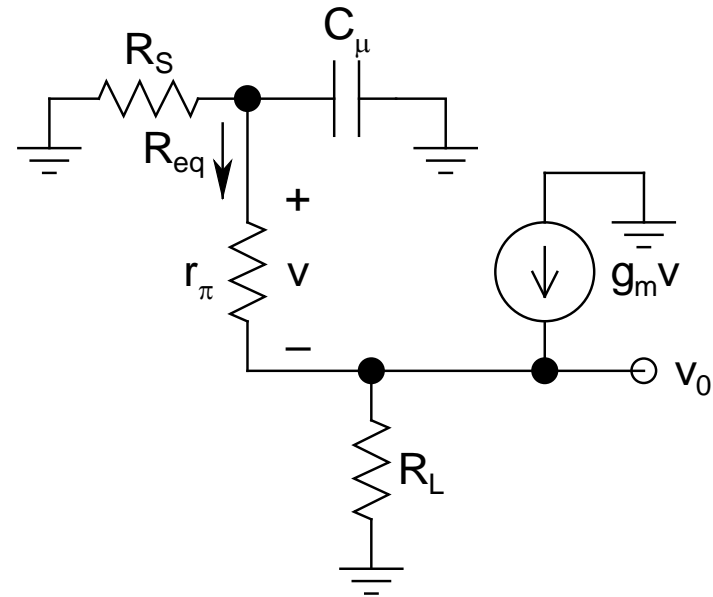
➤ *This circuit also has reasonably good frequency response*



- ***CD***:

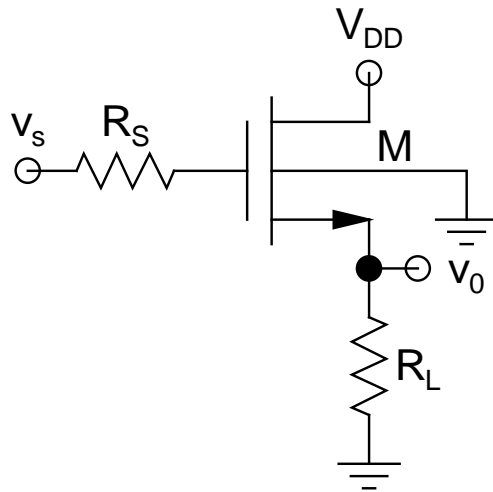

ac Schematic

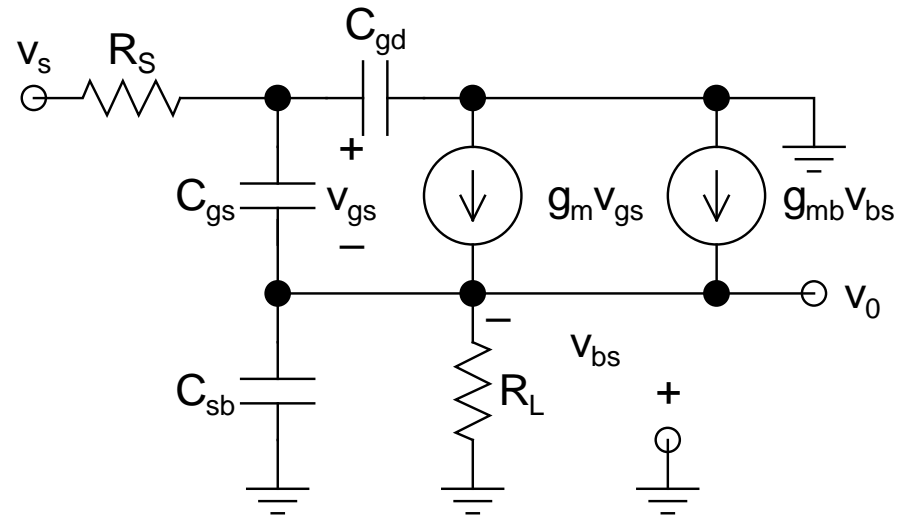

High-Frequency Equivalent

➤ ***C_{db} absent due to obvious reason***

➤ $V_{bs} = -V_0$

$\Rightarrow g_{mb}v_{bs}$ is simple a conductance g_{mb} , in parallel with R_L

\Rightarrow Club them to R [$= R_L || (1/g_{mb})$]

➤ C_{gs} :

▪ Standard Form sans r_π (CC)

$$\Rightarrow R_{gs}^0 = \frac{R_s + R}{1 + g_m R}$$

$$\Rightarrow \tau_1 = R_{gs}^0 C_{gs}$$

➤ C_{gd} :

▪ *By inspection:*

$$R_{gd}^0 = R_S$$

$$\Rightarrow \tau_2 = R_{gd}^0 C_{gd}$$

➤ C_{sb} :


▪ *By inspection:*

$$R_{sb}^0 = R \parallel (1/g_m)$$


$$\Rightarrow \tau_3 = R_{sb}^0 C_{sb}$$

➤ *Loving it? :)*

- ***CE(D)***:

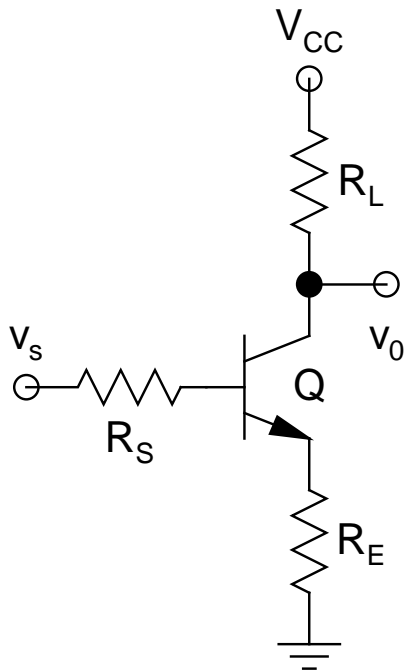

ac Schematic

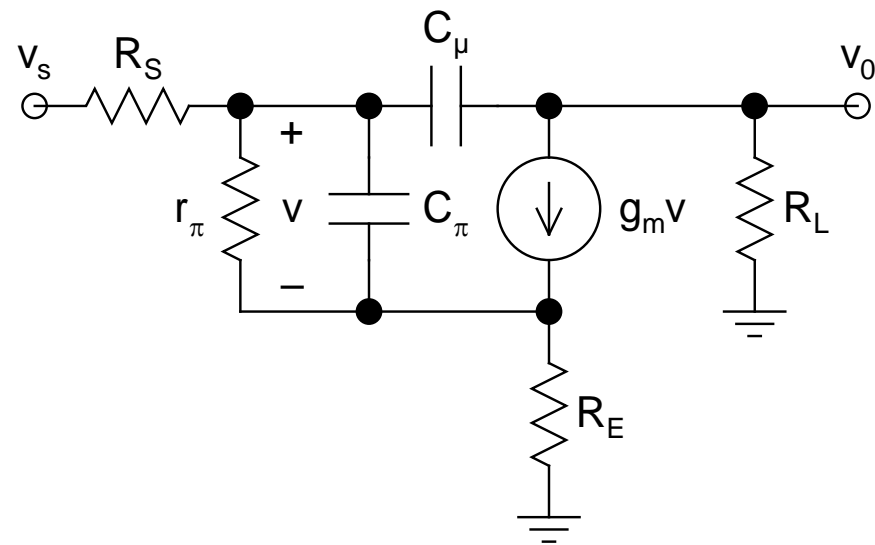

High-Frequency Equivalent

➤ C_π :

- *Standard Form* (similar to CC, with R_L replaced by R_E)

$$\Rightarrow R_\pi^0 = r_\pi \parallel \left(\frac{R_S + R_E}{1 + g_m R_E} \right)$$

$$\Rightarrow \tau_1 = R_\pi^0 C_\pi$$

➤ C_μ :

- *Slightly more complicated*
- *Remove C_π and look across 2 terminals of C_μ*
- *Can be represented by a 2-port network*

- *Show that:*

$$R_{eq} = R_S || R_{\pi}$$


$$\text{with } R_{\pi} = r_{\pi}(1 + g_m R_E)$$

$$G_m = g_m / (1 + g_m R_E)$$

- This can be *easily identified* as a *Three-Legged Creature*


$$\Rightarrow R_{\mu}^0 = R_{eq} + R_L + G_m R_{eq} R_L$$
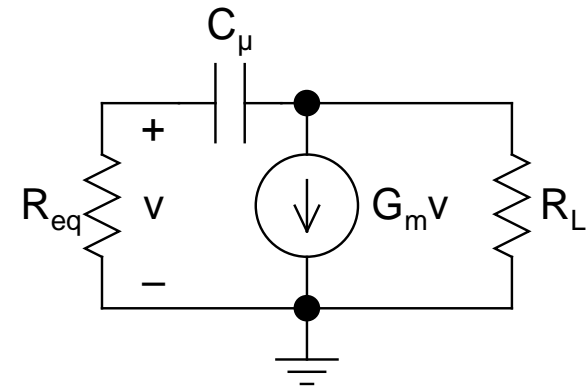
$$\Rightarrow \tau_2 = R_{\mu}^0 C_{\mu}$$




**2-Port Representation
of a CE(D) Stage**

- $CS(D)$:**

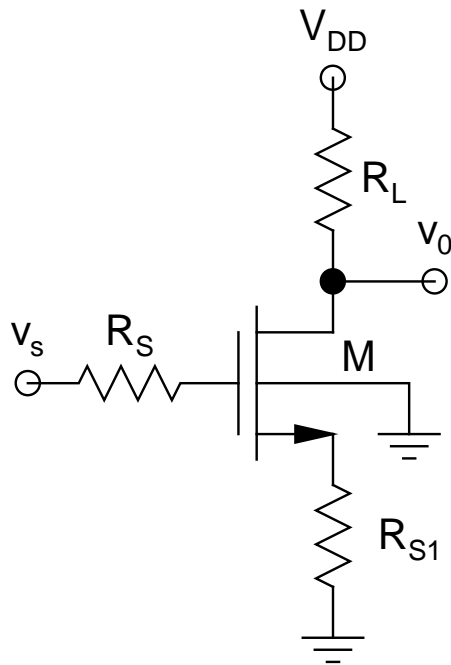

ac Schematic

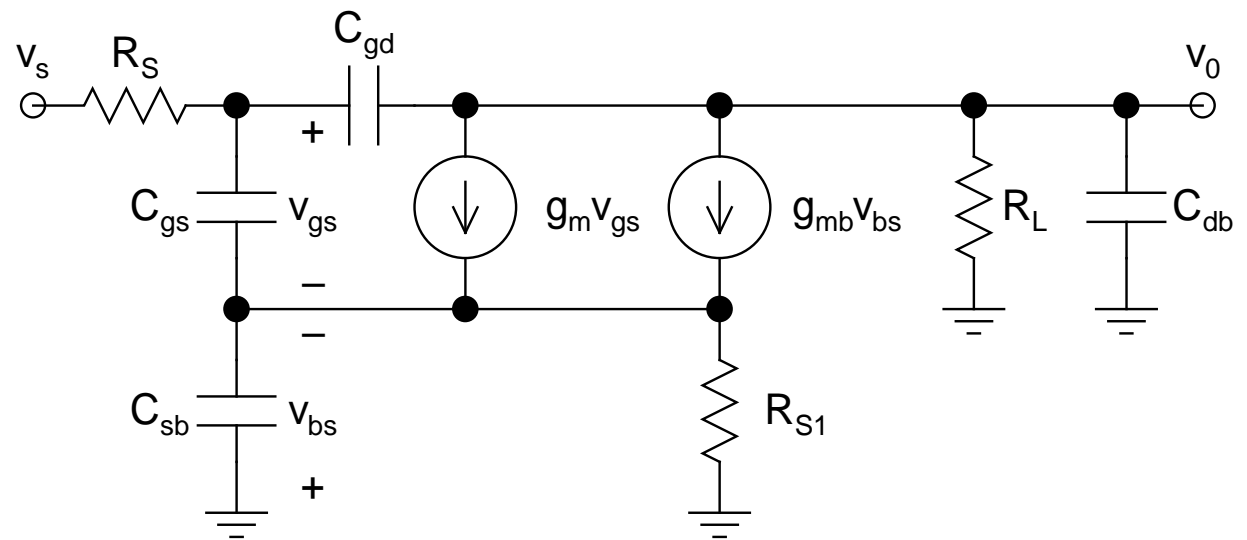

High-Frequency Equivalent