

- **Parameters:**

- **Output Current  $I_0$**

- *As per specification*

- **Output Resistance  $R_0$**

- $R_0 = \Delta V_0 / \Delta I_0 = dV_0 / dI_0 = v_0 / i_0$  (**ac**)
- *As large as possible - ideally infinite*

- **Minimum Allowed Output Voltage  $V_{0,min}$**

- *As small as possible - ideally zero*
- **Dictated by:**
  - ❖ **For BJT:**  $V_{CE(min)} = V_{CE(SS)} = 0.2 \text{ V}$
  - ❖ **For MOSFET:**  $V_{DS(min)} = V_{GT(min)} = 80 \text{ mV}$

- *$I_0$  should be independent of power supply and temperature*
  - *Temperature and Supply Independent Biasing*
- *Should use minimum number of circuit elements*
  - *Economization of space*
- *Should not affect frequency response*
- It is *almost impossible to satisfy all these constraints simultaneously*
  - *Look for optimization*

# Current Sources/Sinks

- Also known as *Current Mirrors* (CM)
- Can be used for *biasing* as well as *load elements* (known as *active load*)
- Designed based on *required specifications*
- *Two sources of errors:*
  - *Systematic: Even when devices are matched*
  - *Random: When there is a random mismatch between devices*

- **Simple npn CM:**

- $Q_1$  has its  **$B$  and  $C$  shorted**

- **Can never saturate** ( $V_{BC} = 0$ )
- Known as **diode-connected BJT**


- $Q_1$  and  $Q_2$  have **same  $V_{BE}$**

- $I_{REF} = \text{Reference Current}$   
 $= (V_{CC} - V_{BE})/R$

- $I_0 = \text{Output Current} = I_{C2}$

- $V_0 = \text{Output Voltage}$

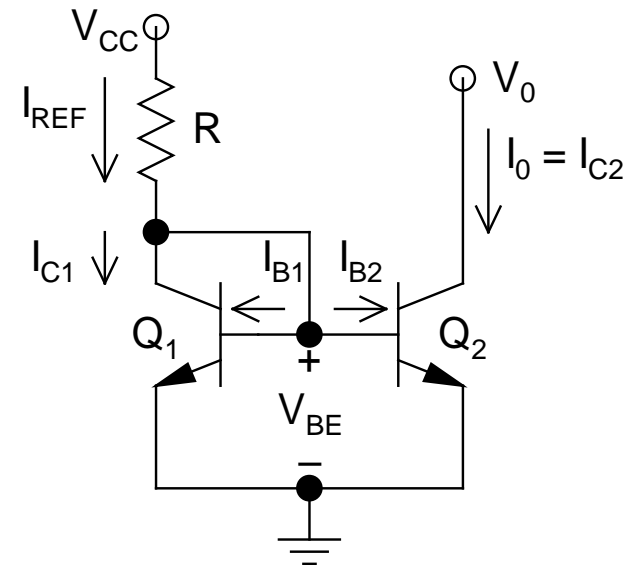- **Variable, depends on the load connected to it**



➤ *General Analysis:*

$$I_{\text{REF}} = I_{\text{C1}} + I_{\text{B1}} + I_{\text{B2}} = I_{\text{C1}} \left( 1 + \frac{1}{\beta_1} \right) + \frac{I_{\text{C2}}}{\beta_2}$$

➤ Now:

$$V_{\text{BE}} = V_{\text{T}} \ln \left( \frac{I_{\text{C2}}}{I_{\text{S2}}} \right) = V_{\text{T}} \ln \left( \frac{I_{\text{C1}}}{I_{\text{S1}}} \right)$$

$$\Rightarrow I_{\text{C2}} = K I_{\text{C1}} \quad (K = I_{\text{S2}}/I_{\text{S1}})$$

➤ Thus:

$$I_{\text{REF}} = I_{\text{C2}} \left[ \frac{1}{\beta_2} + \frac{1}{K} \left( 1 + \frac{1}{\beta_1} \right) \right]$$