

$$1 \quad I_{D1} + I_{D2} = I_{SS}, \text{ \& } I_{D1} - I_{D2} = \Delta I_D \Rightarrow I_{D1} = \frac{I_{SS} + \Delta I_D}{2} \text{ \& } I_{D2} = \frac{I_{SS} - \Delta I_D}{2}$$

Define $a = \frac{K_n'}{2} \left(\frac{W}{L} \right)$. Then, $V_{id} = \frac{\sqrt{I_{D1}} - \sqrt{I_{D2}}}{\sqrt{a}} \Rightarrow V_{id}^2 = \frac{1}{a} (I_{D1} + I_{D2} - 2\sqrt{I_{D1}I_{D2}})$

$$= \frac{1}{a} \left[I_{SS} - 2\sqrt{\frac{(I_{SS} + \Delta I_D)(I_{SS} - \Delta I_D)}{4}} \right] = \frac{1}{a} \left[I_{SS} - \sqrt{I_{SS}^2 - \Delta I_D^2} \right]$$

$$\Rightarrow \sqrt{I_{SS}^2 - \Delta I_D^2} = I_{SS} - a V_{id}^2$$

Squaring both sides & solving for ΔI_D , we get

$$\Delta I_D = a V_{id}^2 \left[\sqrt{\frac{2I_{SS}}{a} - V_{id}^2} \right]$$

Substituting the expression for a , & putting the result back in the expressions for I_{D1} & I_{D2} , we get the desired relations.

Now, range of V_{id} over which the devices stay in saturation can be found by putting either I_{D1} or I_{D2} in the expression for V_{id} , equal to I_{SS} .

$$\text{Thus, } V_{id} = \pm \sqrt{\frac{2I_{SS}}{K_n' (W/L)}} = \pm \sqrt{2} \left[\sqrt{\frac{2I_{D1}}{K_n' (W/L)}} \right]_{V_{id}=0}, \text{ as desired.}$$

$$2 \quad I_{SS} = 2I_D \Rightarrow g_m = \sqrt{2K_n' \left(\frac{W}{L} \right) I_D} = \sqrt{K_n' \left(\frac{W}{L} \right) I_{SS}} = 1 \text{ mS} \Rightarrow K_n' \left(\frac{W}{L} \right) = \frac{10^{-6}}{I_{SS}}$$

$$\text{Also, } \Delta I_D = \frac{K_n'}{2} \left(\frac{W}{L} \right) V_{id} \sqrt{\frac{4I_{SS}}{K_n' (W/L)} - V_{id}^2} = 0.85 I_{SS} \text{ for } V_{id} = 0.2 \text{ V.}$$

Substituting $K_n' \left(\frac{W}{L} \right) (= 10^{-6}/I_{SS})$ in the expression for ΔI_D , we get a quadratic in terms of I_{SS} :

$$7.225 \times 10^{13} I_{SS}^4 - 4 \times 10^6 I_{SS}^2 + 0.04 = 0 \Rightarrow I_{SS}^2 = 4.226 \times 10^{-8} \text{ A}^2$$

or $1.31 \times 10^{-8} \text{ A}^2 \Rightarrow I_{SS} = \underline{205.6 \mu\text{A}}$ or $\underline{114.5 \mu\text{A}}$. Now, both these values are possible, but may not be practical.

Consider $I_{SS} = 205.6 \mu\text{A} \Rightarrow \left(\frac{W}{L} \right) = 25.07$

$\Rightarrow \Delta V = 0.206 \text{ V}$. The linear range of $V_{id} = \sqrt{2} \times \Delta V = 0.291 \text{ V}$, & the applied V_{id} of 0.2 V lies well within this range. $\therefore I_{SS} = \underline{205.6 \mu\text{A}}$ is a physically correct value.

Now, consider $I_{SS} = 114.5 \mu\text{A} \Rightarrow \left(\frac{W}{L} \right) = 45.02 \Rightarrow \Delta V = 0.115 \Rightarrow$ linear range of $V_{id} = 0.162 \text{ V}$, which is less than the applied V_{id} of 0.2 V . \Rightarrow One of the transistor would leave their saturation mode of operation, & the pair will act like a switch. $\therefore I_{SS} = \underline{114.5 \mu\text{A}}$ is NOT a physically correct value.

Final answers: $I_{SS} = 205.6 \mu\text{A}$, $W/L = 25.07$, & with $L = 1 \mu\text{m}$, $W = 25.07 \mu\text{m}$.

3 DC Analysis: $I_{C1} = I_{REF} = I_{S1} \left[\exp \left(\frac{V_{BE1}}{V_T} \right) \right] (1 + V_{CE1}/V_{AN})$ with $V_{BE1} = V_I$, $V_{CE1} = V_O$, & $I_{REF} = 1 \text{ mA}$, for best biasing, $V_O = V_{CC}/2 = \underline{2.5 \text{ V}}$. Thus,

$$V_I = V_T \ln \left[\frac{I_{REF}}{I_{S1} (1 + V_O/V_{AN})} \right] = \underline{0.78 \text{ V}}$$

Now, $I_{C2} = I_{C1} = I_{REF} = I_{S2} e^{V_{BE2}/V_T} \left(1 + \frac{V_{CE2}}{V_{AP}} \right)$

with $|V_{CE2}| = V_{CC}/2 = \underline{2.5 \text{ V}} \Rightarrow |V_{BE2}| = 0.74 \text{ V} \Rightarrow V_{EB2} = \underline{0.74 \text{ V}}$ (EB voltage is +ve for pnp)

AC Analysis: $A_v = -g_{m1} R_o$, $g_{m1} = \frac{I_{C1}}{V_T} = \frac{1}{26} 25$, $R_o = R_{o1} \parallel R_{o2}$, (2)

$R_{o1} = \frac{V_{AN}}{I_{C1}} = 130 \text{ k}\Omega$, $R_{o2} = \frac{V_{AP}}{I_{C2}} = 52 \text{ k}\Omega \Rightarrow R_o = 37.14 \text{ k}\Omega \Rightarrow A_v = -1428.57$ (large!)

4 $5 - V_{o,max} = 0.6 + 0.2 (\sqrt{0.6 + V_{o,max}} - \sqrt{0.6}) \Rightarrow V_{o,max}^2 - 9.15 V_{o,max} + 20.724 = 0$

$\Rightarrow V_{o,max} = 5.03 \text{ V}$ or 4.12 V , 5.03 V is unphysical (does not satisfy the eqn., as well as is greater than V_{DD} of 5 V) $\Rightarrow V_{o,max} = 4.12 \text{ V}$. $V_{TN2} = 0.77 \text{ V}$. (at best

biasing $V_o = \frac{V_{o,max}}{2} = 2.06 \text{ V} \Rightarrow I_{D2} = \frac{K_n'}{2} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{TN2})^2 \times (1 + \lambda V_{DS2})$

$= \frac{40}{2} \times 1 \times (5 - 2.06 - 0.77)^2 \times (1 + 0.2 \times 2.94) = 149.55 \mu\text{A}$ ($V_{GS} = V_{DD} - V_{oq}$, $V_{DS} = V_{DD} - V_{oq}$)

Also, $I_{D2} = I_{D1} = 149.55 \mu\text{A} = \frac{K_n'}{2} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN1})^2 \times (1 + \lambda V_{DS1})$

$\Rightarrow \frac{40}{2} \times 25 \times (V_I - 0.6)^2 \times (1 + 0.2 \times 2.06) = 149.55 \Rightarrow V_I = 1.06 \text{ V}$

$\chi_2 = \frac{\gamma}{2\sqrt{2\phi_F + V_{oq}}} = \frac{0.2}{2\sqrt{0.6 + 2.06}} = 0.06$ $g_{m1} = \sqrt{2K_n' \left(\frac{W}{L}\right)_1 I_{D1} (1 + \lambda V_{DS1})}$

$= \sqrt{2 \times 40 \times 10^{-6} \times 25 \times 149.55 \times 10^{-6} \times (1 + 0.2 \times 2.06)} = 649.87 \mu\text{A/V}$

$g_{m2} = \sqrt{2 \times 40 \times 10^{-6} \times 1 \times 149.55 \times 10^{-6} \times (1 + 0.2 \times 2.94)} = 137.84 \mu\text{A/V}$

$\Rightarrow g_{mb2} = \chi_2 g_{m2} = 8.27 \mu\text{A/V}$. $g_{o1} = \frac{\lambda I_{D1}}{1 + \lambda V_{DS1}} = \frac{0.2 \times 149.55}{1 + 0.2 \times 2.06} = 21.18 \mu\text{A/V}$

$g_{o2} = \frac{\lambda I_{D2}}{1 + \lambda V_{DS2}} = \frac{0.2 \times 149.55}{1 + 0.2 \times 2.94} = 18.84 \mu\text{A/V} \Rightarrow R_o = (g_{m2} + g_{mb2} + g_{o1} + g_{o2})^{-1}$

$= (137.84 + 8.27 + 21.18 + 18.84)^{-1} \text{ M}\Omega = 5.37 \text{ k}\Omega$ (Note how low it is!)

& $A_v = -g_{m1} R_o = -649.87 \times 10^{-6} \times 5.37 \times 10^3 = -3.49$ (Note: Ideal max. gain = -5)

5 As V_o swings from 0 to V_{DD} ($= 5 \text{ V}$), the max. change in V_{TN} for M_2

$= 0.2(\sqrt{0.6 + 5} - \sqrt{0.6}) = 0.318 \text{ V}$. To keep a cushion of 78 mV in V_{TN2} , its threshold

voltage V_{T00} should be $-0.318 - 0.078 = -0.396 \text{ V}$. For best biasing,

$V_{oq} = \frac{V_{DD}}{2} = 2.5 \text{ V}$, corresponding $V_{TD} = -0.396 + 0.2(\sqrt{0.6 + 2.5} - \sqrt{0.6}) = -0.2 \text{ V}$

$\Rightarrow I_{D2} = \frac{K_n'}{2} \left(\frac{W}{L}\right)_2 (-V_{TD})^2 (1 + \lambda V_{DS2}) = \frac{40}{2} \times 1 \times (0.2)^2 \times (1 + 0.2 \times 2.5) = 1.2 \mu\text{A}$

$\Rightarrow I_{D1} = I_{D2} = 1.2 \mu\text{A} = \frac{40}{2} \times 25 \times (V_I - 0.6)^2 \times (1 + 0.2 \times 2.5) \Rightarrow V_I = 0.64 \text{ V}$

$g_{m1} = \sqrt{2 \times 40 \times 25 \times 1.2 \times 10^{-12} \times (1 + 0.2 \times 2.5)} = 60 \mu\text{A/V}$ $\chi_2 = \frac{\gamma}{2\sqrt{2\phi_F + V_o}} = 0.057$

$g_{m2} = \frac{g_{m1}}{5} = 12 \mu\text{A/V} \Rightarrow g_{mb2} = \chi_2 g_{m2} = 684 \text{ nA/V}$ $g_{o1} = g_{o2} = \frac{\lambda I_D}{1 + \lambda V_{DS}}$

$= \frac{0.2 \times 1.2}{1 + 0.2 \times 2.5} = 160 \text{ nA/V} \Rightarrow R_o = \frac{1}{g_{mb2} + g_{o1} + g_{o2}} = (684 \times 10^{-9} + 2 \times 160 \times 10^{-9})^{-1}$

$= 1 \text{ M}\Omega$ (note the vast improvement over Prob. 4) & $A_v = -g_{m1} R_o = -59.76$

(again remarkable improvement). If M_2 is in its well, $R_o = 3.125 \text{ M}\Omega$ & $A_v = -187.5$

$$6 \quad I_{D1} = \frac{k_n'}{2} \left(\frac{W}{L}\right)_n (V_{GSN} - V_{TN0})^2 (1 + \lambda_n V_{DSn}) \quad \text{No body effect. } V_{GSN} = V_I \quad (3)$$

$$\Rightarrow I_{D1} = I_{REF} = 100 \mu A = \frac{40}{2} \times 10 \times (V_I - 0.6)^2 \times (1 + 0.2 \times 2.5) \quad V_O = 2.5V \text{ for best biasing}$$

$$\Rightarrow V_I = \underline{1.177V}. \text{ Also, } I_{D2} = 100 \mu A = \frac{20}{2} \times 20 \times (|V_{GSP}| - |V_{TP0}|)^2 (1 + \lambda_p |V_{DSP}|)$$

$$\Rightarrow 100 = 200 (|V_{GSP}| - 0.7)^2 \times (1 + 0.15 \times 2.5) \Rightarrow |V_{GSP}| = \underline{1.3V} \quad \boxed{V_{GSP} = -1.3V, V_{SGP} = +1.3V}$$


$$g_{m1} = \sqrt{2k_n' \left(\frac{W}{L}\right)_n I_{D1} (1 + \lambda_n V_{DS1})} = \sqrt{2 \times 40 \times 10^{-6} \times 10 \times 100 \times 10^{-6} \times (1 + 0.2 \times 2.5)} = \underline{346.4 \mu A/V}$$

$$g_{o1} = \frac{\lambda_n I_{D1}}{1 + \lambda_n V_{DS1}} = \frac{0.2 \times 100 \times 10^{-6}}{1 + 0.2 \times 2.5} = \underline{13.33 \mu A/V} \quad g_{o2} = \frac{0.15 \times 100 \times 10^{-6}}{1 + 0.15 \times 2.5} = \underline{10.91 \mu A/V}$$

$$\Rightarrow R_o = (g_{o1} + g_{o2})^{-1} = (13.33 \times 10^{-6} + 10.91 \times 10^{-6})^{-1} = \underline{41.25 k\Omega}$$

$$\Rightarrow R_o = (g_{o1} + g_{o2})^{-1} = (13.33 \times 10^{-6} + 10.91 \times 10^{-6})^{-1} = \underline{41.25 k\Omega} \quad (\text{not that high})$$
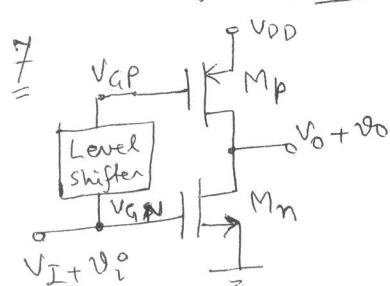
$$\& A_v = -g_{m1} R_o = -346.4 \times 10^{-6} \times 41.25 \times 10^3 = \underline{-14.29}$$



$$I_{DN} = \frac{k_n'}{2} \left(\frac{W}{L}\right)_n (V_{GSN} - V_{TN})^2 (1 + \lambda_n V_{DSn})$$

$$V_{GSN} = V_I = 2V \quad V_{TN} = V_{TN0} = 0.6V \quad V_{DSn} = 2.5V$$

$$\therefore I_{DN} = \frac{40}{2} \times 10 \times (2 - 0.6)^2 (1 + 0.2 \times 2.5) = \underline{588 \mu A}$$

$$\text{Also, } |I_{DP}| = I_{DN} = \frac{20}{2} \times 20 \times (|V_{GSP}| - 0.7)^2 (1 + 0.15 \times 2.5) = 588$$

$$\Rightarrow |V_{GSP}| = \underline{2.16V} \Rightarrow V_{GSP} = -2.16V \Rightarrow V_{GP} - V_{SP} = -2.16V \Rightarrow V_{GP} - V_{DD} = -2.16$$

$$\Rightarrow V_{GP} = -2.16 + 5 = \underline{2.84V} \Rightarrow \text{Amount of level shift} = V_{GP} - V_{GM} = \underline{+0.84V}$$

$$g_{mn} = \sqrt{2k_n' \left(\frac{W}{L}\right)_n I_{DN} (1 + \lambda_n V_{DSn})} = \sqrt{2 \times 40 \times 10^{-6} \times 10 \times 588 \times 10^{-6} \times (1 + 0.2 \times 2.5)} = \underline{840 \mu A/V}$$

$$g_{mp} = \sqrt{2 \times 20 \times 10^{-6} \times 20 \times 588 \times 10^{-6} \times (1 + 0.15 \times 2.5)} = \underline{804.24 \mu A/V}$$

$$g_{on} = \frac{\lambda_n I_{DN}}{1 + \lambda_n V_{DSn}} = \frac{0.2 \times 588}{1 + 0.2 \times 2.5} = \underline{78.4 \mu A/V} \quad g_{op} = \frac{0.15 \times 588}{1 + 0.15 \times 2.5} = \underline{64.15 \mu A/V}$$

$$\Rightarrow R_o = (g_{on} + g_{op})^{-1} = (78.4 + 64.15)^{-1} = \underline{7 k\Omega} \quad (\text{really low!})$$

$$\& A_v = -(g_{mn} + g_{mp}) R_o = -(840 + 804.24) \times 10^{-6} \times 7 \times 10^3 = \underline{-11.53}$$

Getting high gain from CMOS Amplifier stages is not an easy task!