

- ***npn Current Repeater:***


- *Uses multi-emitter BJTs*

- *Maximum number of emitters = 4*

- *All emitters tied together*

- *All  $Q$ s have same  $V_{BE}$*

- $I_{REF} = (V_{CC} - V_{BE})/R$

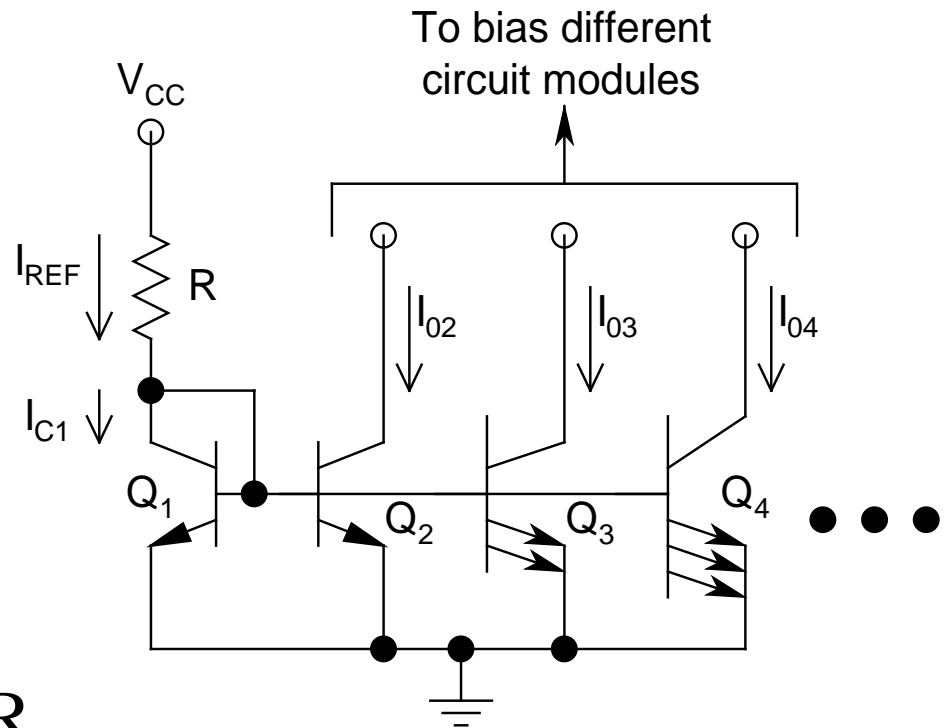


➤ *Neglecting  $I_B$ :*

$$I_{02} = I_{REF}, I_{03} = 2I_{REF}, I_{04} = 3I_{REF}, \dots$$

➤ *Limitations:*

- *Output current can never be a non-integer ratio of  $I_{REF} \Rightarrow$  no arbitrary scaling possible*
- *Loading Problem:*
  - ❖  *$I_{REF}$  not only supplies  $I_{C1}$ , but  $I_B$ s of all the  $Q$ s*
  - ❖ *As more  $Q$ s are added,  $I_B$ s will keep on increasing*
  - ❖  *$I_{C1}$  starts to depart significantly from  $I_{REF}$*
  - ❖ *It's not  $I_{REF}$  that's mirrored, it's  $I_{C1}$*
  - ❖ *A reduction in  $I_{C1}$  will affect all output currents*
  - ❖ *Hence, this circuit is not very popular*

- *NMOS Current Repeater:*

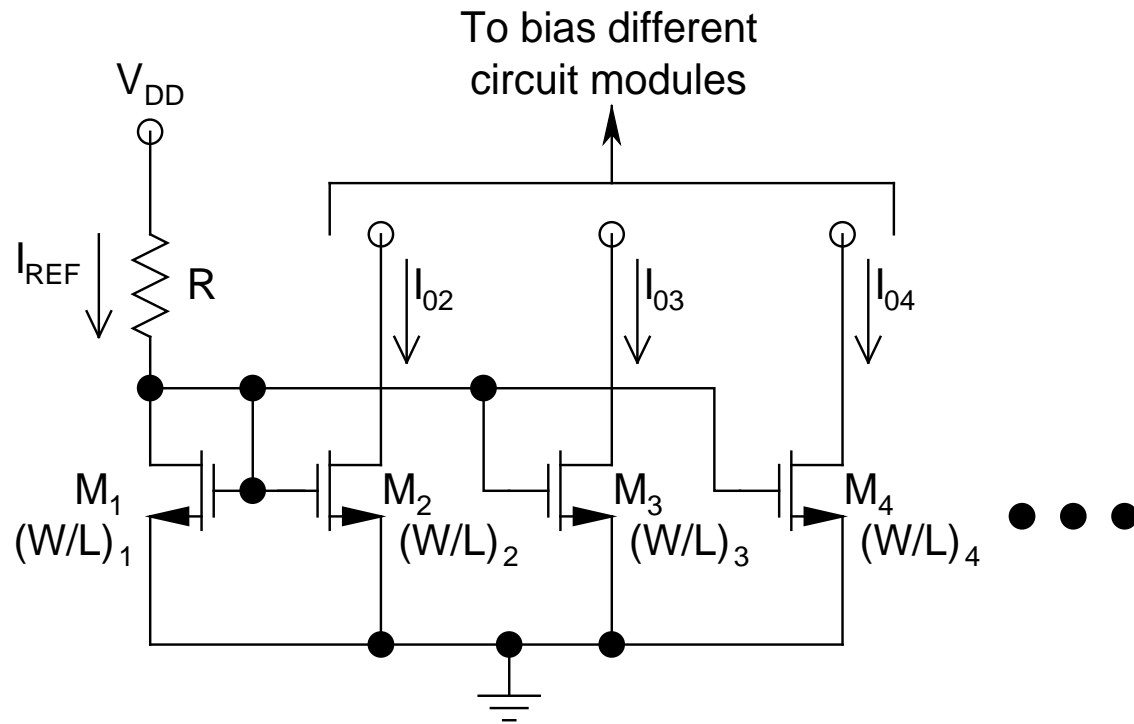

➤  $I_{\text{REF}} = I_{\text{D1}} = (V_{\text{DD}} - V_{\text{GS}})/R$

$$I_{\text{D1}} = \frac{k'_N}{2} \left( \frac{W}{L} \right)_1 V_{\text{GT}}^2 \quad (\text{assuming } \lambda V_{\text{DS}} < 0.1)$$

➤ *All Ms have same  $V_{\text{GS}}$  and are matched*

$$\Rightarrow I_{\text{oi}} = \frac{(W/L)_i}{(W/L)_1} I_{\text{REF}} \quad (i = 2, 3, 4, \dots)$$

➤ *Tremendous flexibility*

❖ *Any arbitrary current ratio can be obtained*

❖ *No loading effect*

❖ *Highly popular and universal choice*

- ***More on W/L Ratio:***

- ***Generally, in technology, W/L is kept between 0.01 and 100***

- ***The ideal ratio is between 0.02 and 50***

- ***Minimum Feature Size*** (MFS):

- ***Minimum dimension that can be resolved in an IC chip***

- ❖ ***Has gone down from 10s of  $\mu\text{m}$  in 80s to a few nm now!***

- ***For  $W/L > 1$  (or  $< 1$ ), L (or W) is chosen equal to MFS***

- ***Yields minimum possible device area ( $W \times L$ )***

- *npn CM With Better  $\beta$  Insensitivity:*

- $I_{REF} = (V_{CC} - 2V_{BE})/R$

- Neglecting  $I_{B3}$ :

$$I_{C1} = I_{REF}$$

- *If  $Q_1$  and  $Q_2$  are matched:*

$$I_0 = I_{C2} = I_{C1} = I_{REF}$$

$\Rightarrow$  *Simple CM*

- *The actual advantage of the circuit lies elsewhere!*

