

- **CE:**

- Refer to the *high-frequency equivalent* given in the *exact analysis*

- **2 capacitors:** C_π and C_μ

- \Rightarrow *2 time constants:* τ_1 and τ_2

- C_π :

- **C_μ opens up**

- *By inspection:*

$$R_\pi^0 = R_S \parallel r_\pi$$

$$\Rightarrow \tau_1 = R_\pi^0 C_\pi$$


➤ C_μ :

- C_π opens up
- This is one *Standard Form*, known as the *Three-Legged Creature*
- Show that:

$$R_\mu^0 = R + R_L + g_m R_L R \quad (R = R_S \parallel r_\pi)$$

$$\Rightarrow \tau_2 = R_\mu^0 C_\mu$$

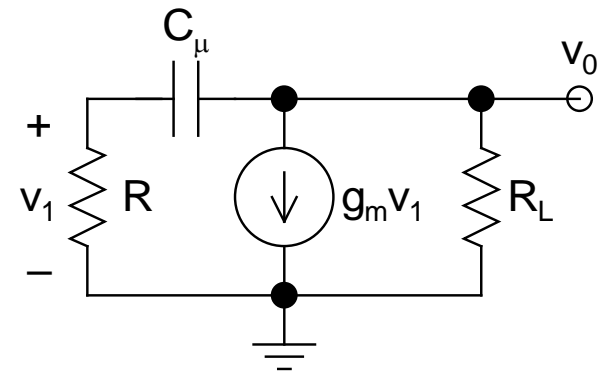- Thus, $\tau_{\text{net}} = \tau_1 + \tau_2$, and $f_H = 1/(2\pi\tau_{\text{net}})$
- Note the *amazing simplicity* of the analysis



➤ Putting *values* of our previous *example*:

$$R_{\pi}^0 = 838.7 \, \Omega, \, \tau_1 = 8.4 \, \text{ns}$$


$$R_{\mu}^0 = 67.4 \, \text{k}\Omega, \, \tau_2 = 33.7 \, \text{ns}$$

$$\Rightarrow \tau_{\text{net}} = 42.1 \, \text{ns} \quad \text{and} \quad f_H = 3.8 \, \text{MHz}$$


➤ This is *identical* to the *result* obtained from the *exact analysis*, however, at a *fraction* of the *effort*!

➤ Also, *τ_2 is the dominant time constant*
 $\Rightarrow f_H$ *is primarily dictated by C_{μ}*

- ***CS:***

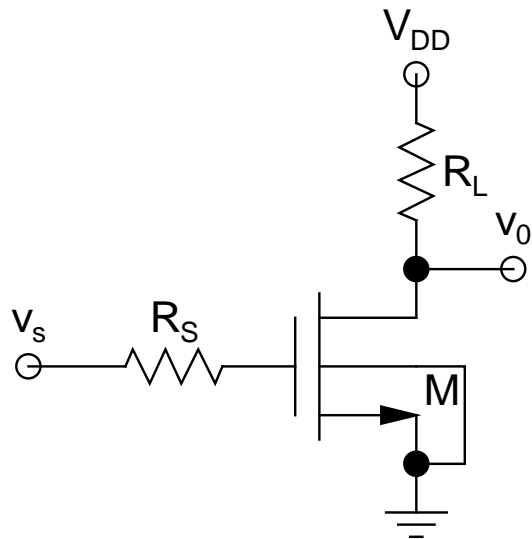

ac Schematic

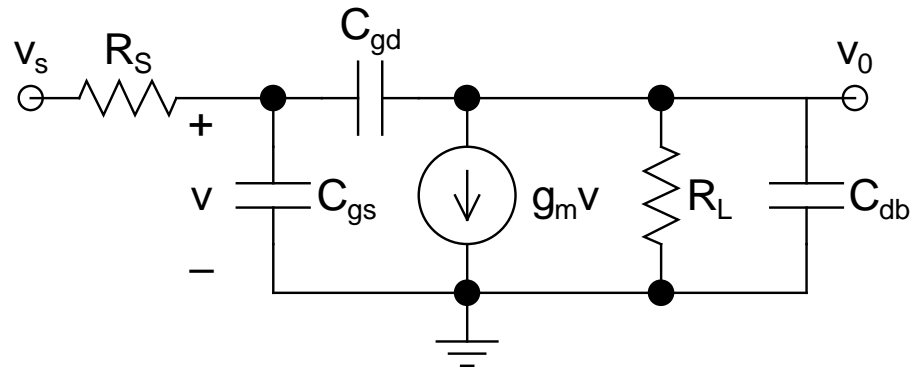

High-Frequency Equivalent

➤ ***C_{sb} absent (Why?)***

➤ *3 capacitors*: C_{gs} , C_{gd} , and C_{db}

⇒ *3 time constants*: τ_1 , τ_2 , and τ_3

➤ C_{gs} :

- *C_{gd} and C_{db} open up*

- *By inspection*:

$$R_{gs}^0 = R_S$$

$$\Rightarrow \tau_1 = R_{gs}^0 C_{gs}$$

➤ C_{gd} :

- *C_{gs} and C_{db} open up*

- *By inspection*, it can be *identified* as a *Three-Legged Creature*

- Thus:

$$R_{gd}^0 = R_S + R_L + g_m R_S R_L$$

$$\Rightarrow \tau_2 = R_{gd}^0 C_{gd}$$

➤ ***C_{db}***:

- *C_{gs} and C_{gd} open up*

- *By inspection:*

$$R_{db}^0 = R_L$$


$$\Rightarrow \tau_3 = R_{db}^0 C_{db}$$

➤ Thus:


$$\tau_{net} = \tau_1 + \tau_2 + \tau_3, \text{ and } f_H = 1/(2\pi\tau_{net})$$

➤ ***Mind-bogglingly simple*** - isn't it?

- **CB:**

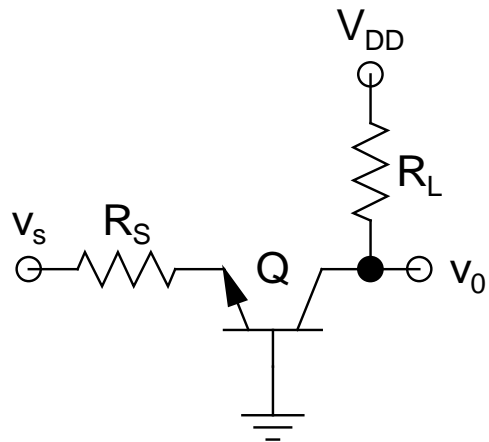

ac Schematic

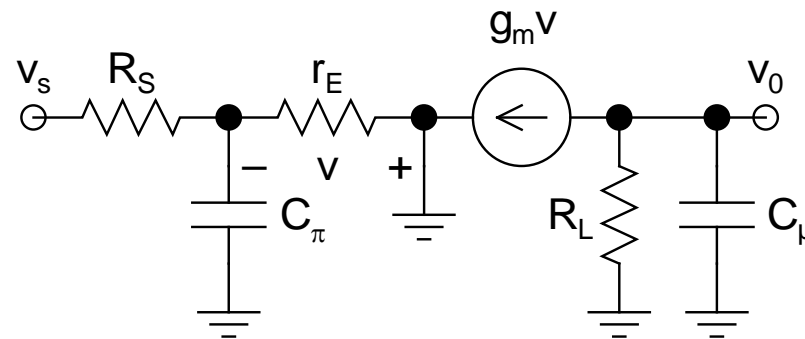

High-Frequency Equivalent

➤ *Note that there is no input-output coupling capacitor present in this circuit*

⇒ *Miller effect will be absent*, and the *circuit will have very high f_H*